

EECE 4121612

Midterm I Solutions

Problem 1

(a) 0.9V

(d) 0.9V

(g) 0V

(b) 1.2V

(e) 0.9V

(h) 0.6V

(c) 1.2V

(f) 1.2V

(i) 0.3V

Problem 2

$$(a) V_{TO} = \phi_{GC} - 2\psi_f - \frac{Q_{B0}}{C_{ox}} - \frac{Q_{ox}}{C_{ox}}$$

$$\phi_f = \frac{kT}{q} \ln \frac{n_i}{N_A} = 0.026 \ln \frac{1.45 \times 10^{10}}{2 \times 10^{15}} = -0.308V$$

$$C_{ox} = \frac{\epsilon_{ox}}{t_{ox}} = 1.758 \times 10^{-7} F/cm^2$$

$$Q_{B0} = -\sqrt{2q N_A \epsilon_s |1 - 2\psi_f|}$$

$$= -\sqrt{2 \times 1.6 \times 10^{19} \times 2 \times 10^{15} \times 11.7 \times 8.854 \times 10^{-17} \times |1 - 2 \times 0.308|} \\ = -2.01 \times 10^{-8}$$

$$V_{TO} = -0.85 + 0.615 + \frac{2 \times 10^{-8}}{1.758 \times 10^{-7}} - \frac{1.6 \times 10^{-19} \times 2 \times 10^{15}}{1.758 \times 10^{-7}} = -0.303$$

(b) p-type implanted needed in the amount ΔV :

$$\Delta V = 0.8 - V_{TO} = 1.303 = \frac{qN_I}{C_{ox}}$$

$$\Rightarrow N_I = 1.21 \times 10^{12} cm^{-2}$$

Problem 3: Use $C_j(N) = A \times \sqrt{\frac{E_{\text{Si}} q}{2} \left(\frac{N_{\text{ND}}}{N_A + N_D} \right)} \times \frac{1}{\sqrt{\varphi_0 - V}}$

, Do not use the formula for k_{eff}

$$-\varphi_0 = \frac{kT}{q} \ln \frac{N_{\text{ND}}}{N_A^2} = 0,939 \text{ V}$$

, for area use four sides and bottom plate:

$$A = [5 \times 10 + 2(5 \times 0.5) + 2(10 \times 0.5)] = 85 \times 10^{-8} \text{ m}^2$$

$$\Rightarrow C_j(N) = 85 \times 10^{-8} \sqrt{\frac{1107 \times 8,854 \times 10^{14} \pi \times 1,6 \times 10^{-19}}{2} \left(\frac{1 \times 10^{36}}{1 \times 10^{20} + 1 \times 10^{16}} \right)}$$

$$\times \frac{1}{\sqrt{0,939 + 5}}$$

$$= 7,678 \times 10^{-15} \text{ F}$$

Problem 4:

$$(a) N_{TO}: \text{ take row 1 \& row 2 } \quad I_{D(SAT)} = \frac{k_n}{2} (V_{ds} - V_{TO})^2$$

$$\frac{I_{D1}}{I_{D2}} = \frac{(4 - V_{TO})^2}{(5 - V_{TO})^2} = \frac{256}{441} \Rightarrow \frac{4 - V_{TO}}{5 - V_{TO}} = \pm \frac{16}{21}$$

$$\rightarrow V_{TO} = 0.8V$$

$$(b) mobility: C_{ox} = \frac{\epsilon_{ox}}{t_{ox}} = 1.0 \times 10^{-7} F/cm$$

$$256 \times 10^{-6} = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (4 - V_{TO})^2 \Rightarrow$$

$$\mu_n = \frac{2 \times 256 \times 10^{-6}}{1.0 \times 10^{-7} \times 1.0 \times 3.2} = 500 \text{ cm}^2/V.s$$

Use

$$(c) r: \text{ now 3 or now 4} \Rightarrow 144 \times 10^{-6} = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (4 - V_T)$$

$$\text{find } V_T \Rightarrow V_T = 1.6V$$

$$\Rightarrow \gamma = \frac{V_T(V_{SB}) - V_{TO}}{\sqrt{|124f| + V_{SB}} - \sqrt{|124f|}} = 0.8 \text{ V}^{-1}$$

Problem 5:

$$V_{OH}: \text{load is in SAT} \Rightarrow k \frac{k_{load}}{2} (V_{DD} - V_{OH} - V_T)^2 = 0$$

$$\Rightarrow V_{OH} = V_{DD} - V_T = 4.2V$$

V_{OL} : load in SAT, driver is linear, input is V_{OH} , output is V_{OL}

$$\Rightarrow k \frac{k_{load}}{2} (V_{DD} - V_{OL} - V_{TO})^2 = k_{driver} \frac{(2(V_{OH} - V_{TO})N_L - V_{OL})}{2}$$

$$\Rightarrow 11V_{OL}^2 - 76.4V_{OL} + 17.64 = 0 \Rightarrow \boxed{V_{OL} = 0.239V}$$

V_{IL} : load in sat

driver in sat

$$\frac{k_{load}}{2} (V_{DD} - V_{IL} - V_{TO})^2 = k_{driver} \frac{(V_{in} - V_{IL})}{2}$$

$$\Rightarrow (5 - V_{IL} - 0.8)^2 = 10(V_{in} - 0.8)^2$$

take derivative wrt V_{in} , set $\frac{dV_{IL}}{dV_{in}} = -1 \Rightarrow$

$$\boxed{V_{out} = 12.2 - 10V_{IL}}$$

when $V_{in} = V_{IL}$

replace $\Rightarrow (4.2 - 12.2 + 10V_{IL})^2 = 10(V_{IL} - 0.8)^2$

$$\Rightarrow \boxed{V_{IL} = 0.8V}$$

$$\Rightarrow NM_L = V_{IL} - V_{OL} = 0.8 - 0.239 = 0.561V$$

Problem 6 :

$$(a) V_{out}(t=0) = V_{DD} - V_{Th} = 2.5 - 0.43 = 2.07 \text{ V}$$

$$(b) V_m = \frac{V_{out}(t=\infty)}{2} = 1.04 \text{ V}$$

low to high when $V_{out} \Rightarrow I_1 = \frac{k_n W}{L} \left[(V_{AS} - V_{Th}) V_{DSAT} - \frac{V_{DSAT}}{2} \right]$

$$= 1.91 \times 10^{-4} \text{ A}$$

$$\Rightarrow R_1 = \frac{2.5}{1.91 \times 10^{-4}} = 13.1 \text{ k}\Omega$$

When $V_{out} = V_m \Rightarrow I_2 = \frac{k_n W}{L} \left((V_{AS} - V_m) V_{DSAT} - \frac{V_{DSAT}}{2} \right)$

$$= 7.78 \times 10^{-5} \text{ A}$$

$$\Rightarrow R_2 = \frac{2.5 - 1.04}{7.78 \times 10^{-5}} = 18.8 \text{ k}\Omega$$

$$\Rightarrow R_{eq} = \frac{R_1 + R_2}{2} = 15.95 \text{ k}\Omega$$

$$\Rightarrow t_{PLH} = 0.69 R_{eq} C_{L2} = 110 \text{ ns}$$

(c) Repeat for t_{PHL} , we get

$$\left. \begin{array}{l} I_1 = 1.91 \times 10^{-4} \text{ A} \\ V_{out} = 2.07 \text{ V} \end{array} \right\} \Rightarrow R_1 = \frac{2.07}{1.91 \times 10^{-4}} = 10.8 \text{ k}\Omega \quad \left. \begin{array}{l} \\ \end{array} \right\} \Rightarrow R_{eq} = 8 \text{ k}\Omega$$


$$\left. \begin{array}{l} I_2 = I_1 = 1.91 \times 10^{-4} \text{ A} \\ V_{out} = 1.04 \text{ V} \end{array} \right\} \Rightarrow R_2 = \frac{1.04}{1.91 \times 10^{-4}} = 5.4 \text{ k}\Omega$$

$$\Rightarrow t_{PHL} = 0.69 R_{eq} C_{L2} = 36 \text{ ns}$$



Problem 7 $\bar{F} = UV + (V + W)X$


(a)

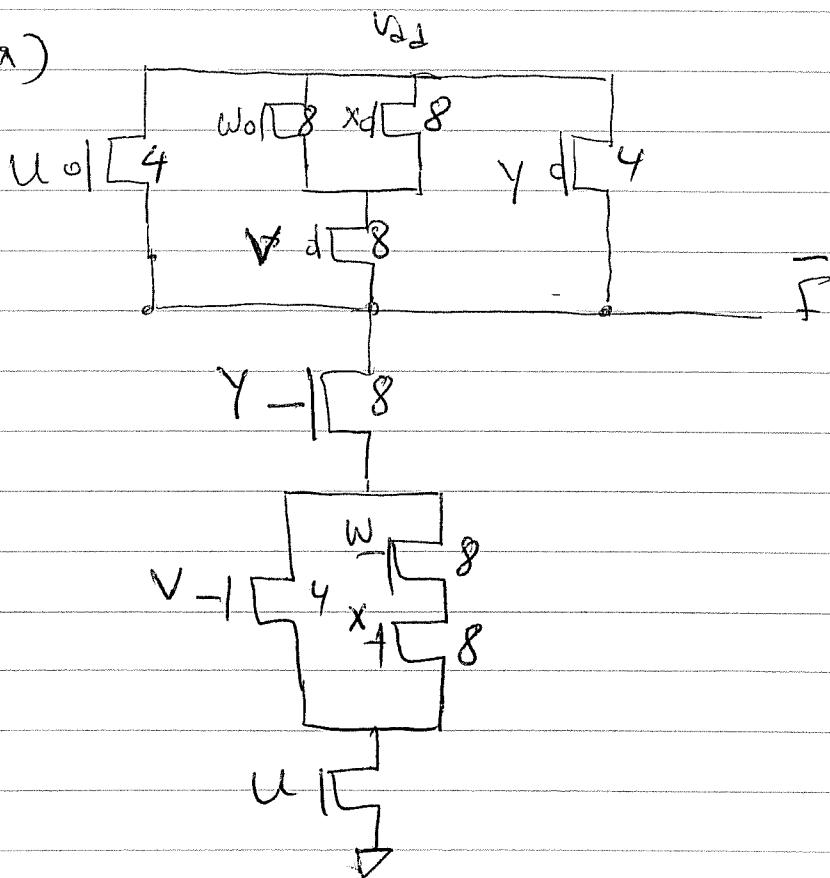


(b) Redraw (a), putting U closest to input

(c) Put X closest to input

PDN:

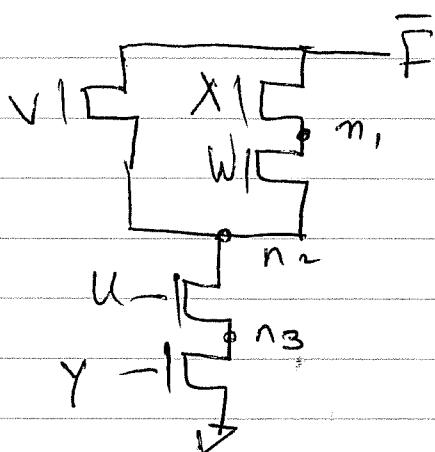

PUN:

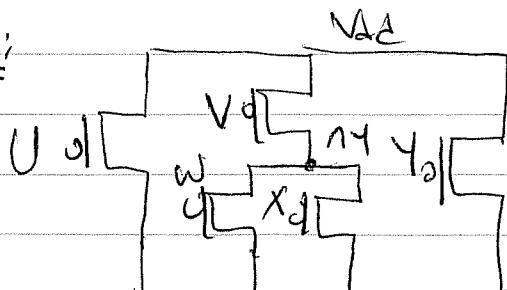

Path: $Y \rightarrow U \rightarrow V \rightarrow X \rightarrow W$

