
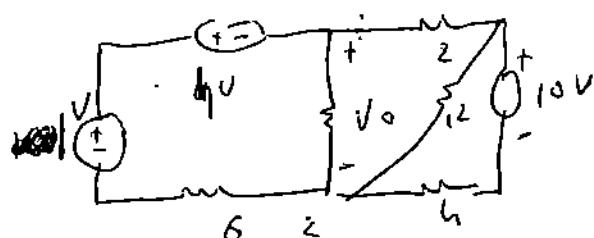
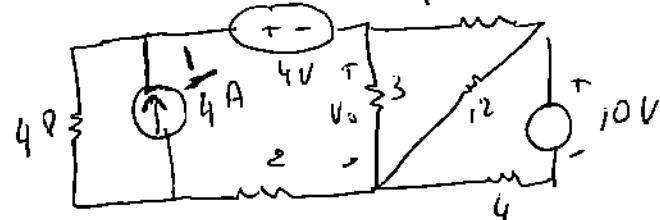
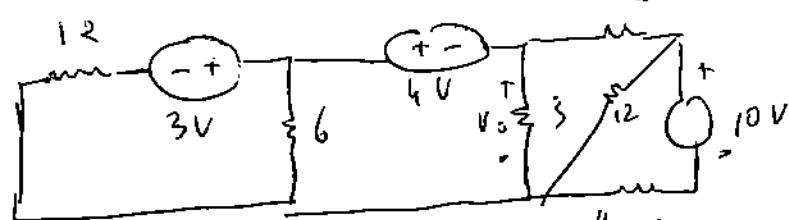
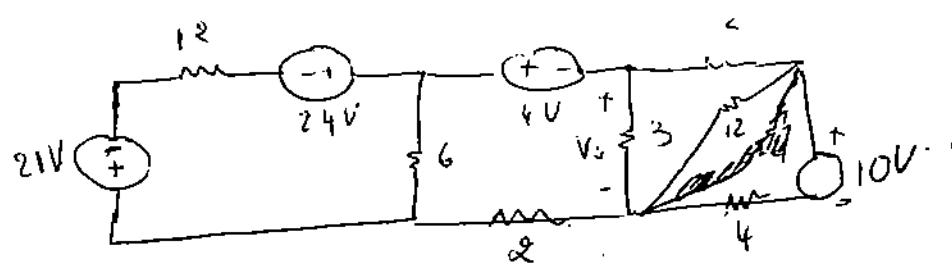


NAME: Amande Abi Nader

NOTE1: OPEN BOOK, OPEN NOTES, CLOSED OLD TESTS AND SOLUTIONS.  
NOTE2: SHOW ALL WORK IN ORDER TO RECEIVE FULL CREDIT.

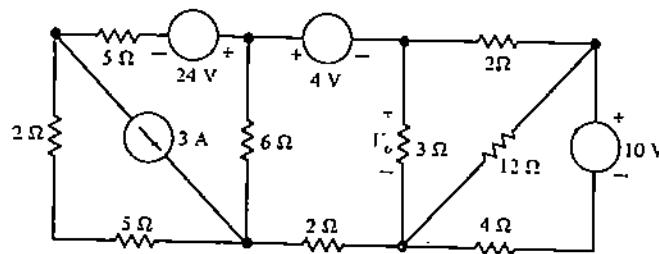1. 25 Pts. Use source transformation to find  $V_o$  in the network in Fig. P5.20.




$\Leftrightarrow 3V \xrightarrow{3A} 3V \xrightarrow{4A} 4V \xrightarrow{10A} 10V$


$\Leftrightarrow 3V \xrightarrow{3A} 3V \xrightarrow{4A} 4V \xrightarrow{10A} 10V$

$\Leftrightarrow \text{Next page}$

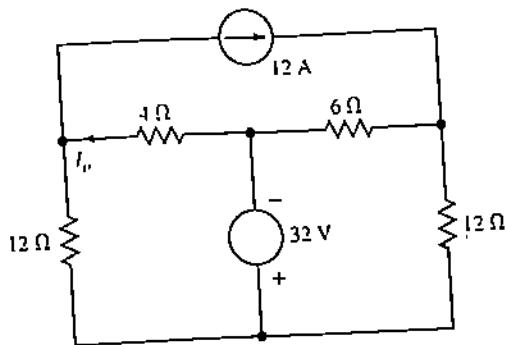2. 25 Pts. Use superposition to find  $I_o$  in the network in Fig. P5.9.



$I_{o1}$  due to the 12 A source ..

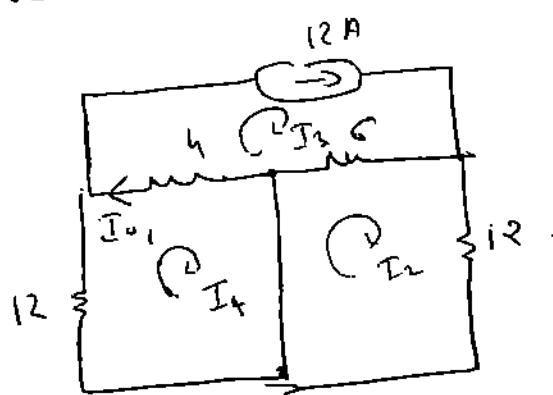

$$I_3 = 12 \text{ A}$$

$$4(I_1 - I_3) + 12I_1 = 0$$

$$4I_1 - 4I_3 + 12I_1 = 0$$

$$16I_1 = 4I_3$$


$$16I_1 = 4 \times 12$$

$$\boxed{I_1 = 3 \text{ A}}$$

$$I_{o1} = I_3 - I_1$$

$$= 12 - 3 = 9 \text{ A}$$

$I_{o2}$  due to the 32 V source

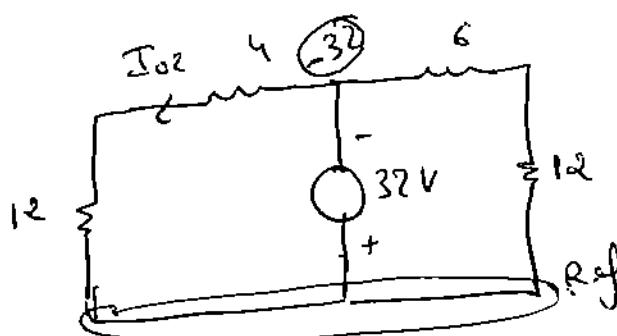

$$I_{o2} = -\frac{32}{16} = -2 \text{ A}$$

$$\Rightarrow I_o = I_{o1} + I_{o2}$$


$$= 9 - 2$$

$$= 7 \text{ A}$$

$$\boxed{I_o = 7 \text{ A}}$$

3. 25 Pts.


5.58. Determine the value of  $R_L$  in Fig. P5.58 for maximum power transfer.

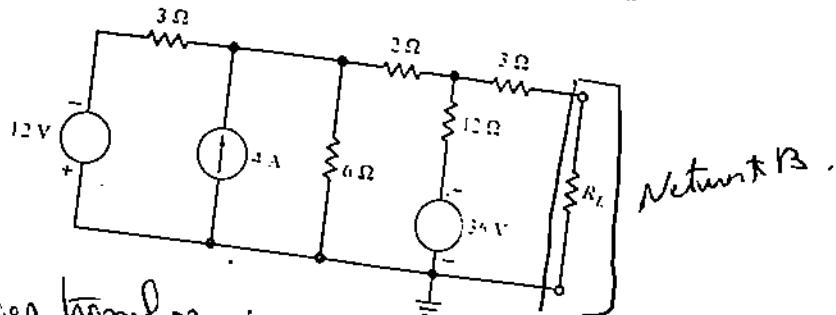

Network 13

for maximum power transfer


$$R_L = R + H$$

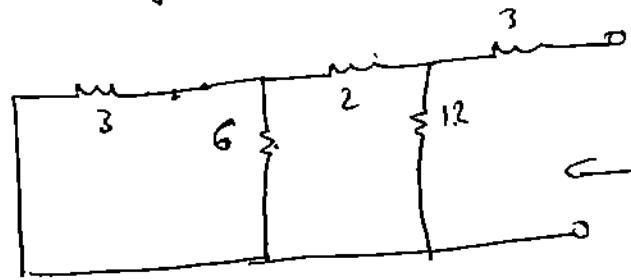

$R+H$

$$R+H = .6\Omega$$

$$R+H = R_L = 6\Omega$$

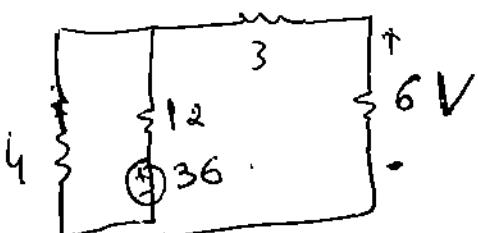

$$R_{eq} = \frac{36}{13} + 12 = \frac{132}{13}\Omega$$

$$I = \frac{(36)(13)}{132} A$$

$$V = \frac{(36)(13)}{132} \times \frac{4}{13} = \frac{3}{4} \times 6 = 4.5V$$

$$P = \frac{V^2}{R} = \frac{(4.5)^2}{6} = \frac{20.25}{6} W$$

$$P_{max} = 3.375 W$$

a

4. 25 Pts. 5.39. Use Thévenin's theorem to compute the current in  $R_L$  in Fig. P5.39.


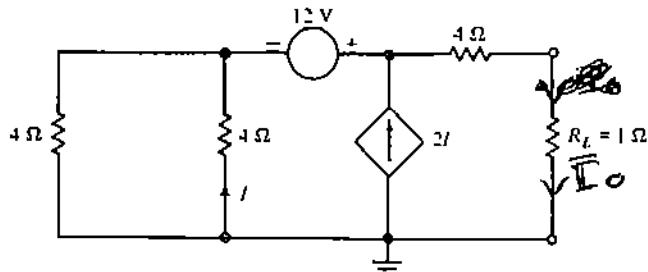


Figure P5.39

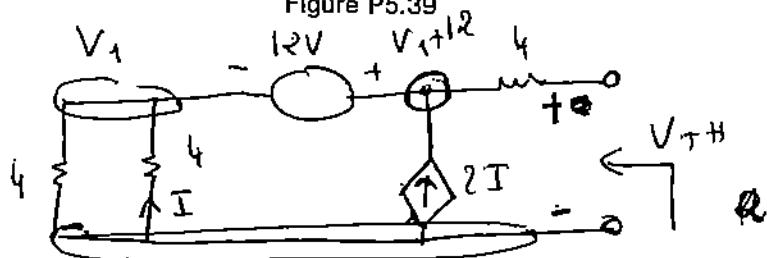

$R_{ref}$


$$I = -\frac{V_1}{4}$$

$$\frac{V_1}{4} + \frac{V_1}{4} - 2I = 0$$

$$V_1 + V_1 - 8I = 0$$

$$V_1 + V_1 + 2V_1 = 0 \Rightarrow V_1 = 0$$

$$V_{TH} = V_1 + 12 = 12V$$

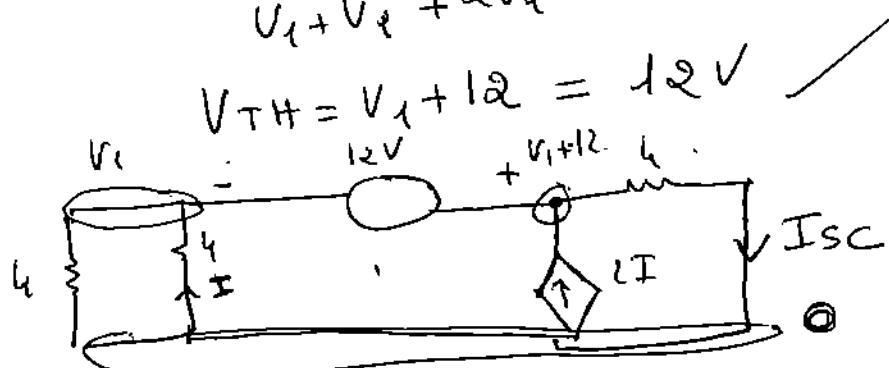

$$\frac{V_1}{4} + \frac{V_1}{4} - 2I + \frac{V_1 + 12}{4} = 0$$

$$R_{TH} = 5\Omega$$



$$V_0 = \frac{12}{6} = 2V$$

$$I_0 = \frac{2}{4} = 0.5A$$

$$I_{SC} = \frac{V_1 + 12}{4}$$

$$I_{SC} = \frac{-12 + 12}{4} = 0$$

$$= \frac{48}{20} = \frac{12}{5} A$$

$$3V_1 - 8I = -12$$

$$3V_1 + 2V_1 = -12$$

$$5V_1 = -12$$

$$V_1 = -\frac{12}{5} V$$

$$R_{TH} = \frac{12}{\frac{12}{5}} = 5\Omega$$