

Question 1. (10 points)

Encircle your answers of the following questions: (1 point each)

N.O.A = None Of the Above

1- The representation of BCD code 10011001 is

- a) 99 Decimal and 99 Hex b) 99 Decimal and 63 Hex
 c) 153 Decimal and 99 Hex d) 153 Decimal and 63 Hex e) N.O.A

2- XOR gate can be realized by using NAND gates.

- a) F b) T

3- The binary representation of 2.25 is

- a) 10.00100101 b) 10.11001 c) 0100.0100 d) 10.0100 e) N.O.A

4- How many combinations, can we build with 8 bits?

- a) 256 b) 255 c) 512 d) 511 e) N.O.A

5- The result of this addition, $(10001000_2 + 10001000_2)$, using 8-bit calculator, is:

- a) 00010000₂ b) 00000000₂ c) 10001000₂ d) 00010001₂ e) N.O.A

6- The result of multiplication 8 bits by 8 bits is

- a) 64 bits b) 16 bits c) 8 bits d) 24 bits e) N.O.A

7- A NOR gate can be realized using AND gates.

- a) F b) T

8- If the result $F = A \text{ AND } B$ is equal 1010 and $B = 1011$, so A is equal to

- a) 1100 b) 1010 c) 1011 d) 0101 e) N.O.A

9- $(x \oplus x')x + x = 1$

- a) F b) T


10- $A'BC + A(B' + C') = A \oplus B \oplus C$

- a) F b) T

Question 2. (10 points)


a) Complete the truth table of the following circuit:

Cin	A1	A0	B1	B0	S1	S0	Cout
0	0	0	0	0	0	0	0
0	0	0	0	1	0	1	0
0	0	0	1	0	1	0	0
0	0	0	1	1	1	1	0
0	0	1	0	0	0	1	0
0	0	1	0	1	1	0	0
0	0	1	1	0	1	1	0
0	0	1	1	1	0	0	1
0	1	0	0	0	1	0	0
0	1	0	0	1	1	1	0
0	1	0	1	0	0	0	1
0	1	0	1	1	0	1	1
0	1	1	0	0	1	1	0
0	1	1	0	1	0	0	1
0	1	1	1	0	1	0	1
1	0	0	0	0	0	0	1
1	0	0	0	1	1	1	0
1	0	0	1	0	1	0	0
1	0	0	1	1	0	1	0
1	0	1	0	0	0	1	1
1	0	1	0	1	0	0	1
1	0	1	1	0	1	1	0
1	1	0	0	0	1	0	0
1	1	0	0	1	0	1	1
1	1	0	1	1	1	1	0
1	1	1	0	0	1	1	0
1	1	1	1	0	0	1	1
1	1	1	1	1	0	0	1

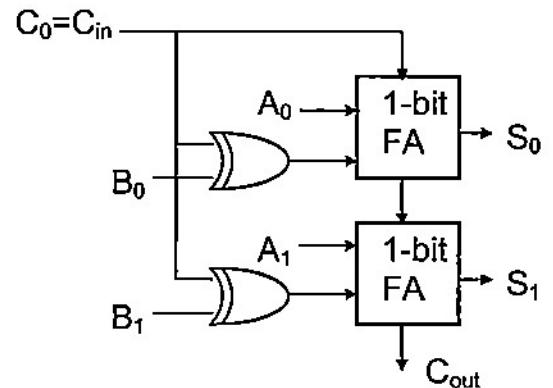

b) What this circuit does?


It adds $A+B$, When $Cin = 0$
Otherwise $A-B$ (when $Cin = 1$)

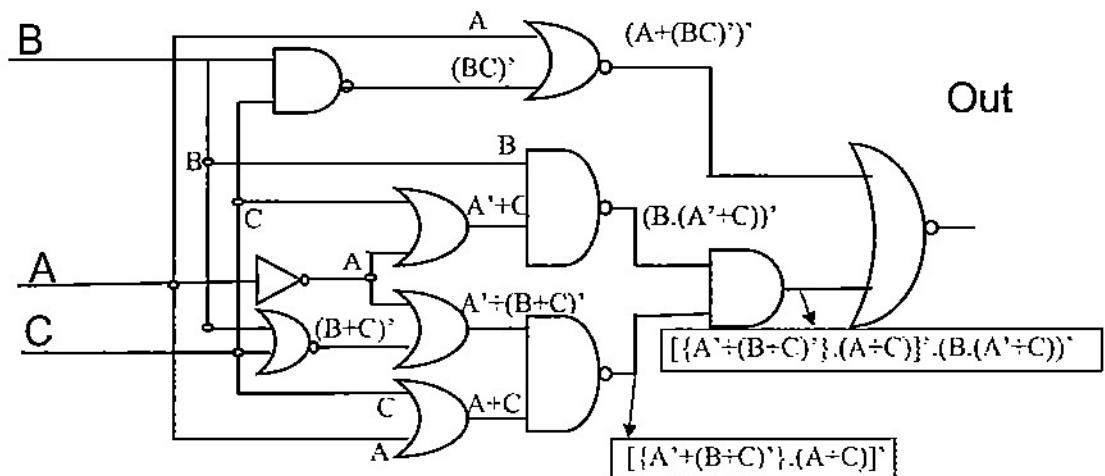Question 3. (15 points)**a) Write the output expression of the following circuit: (5 points)**

$$\overline{\overline{\overline{\text{Out}}}} = \overline{(A + BC)} + \{ \overline{[(A + (B+C)) . (A + C)]} . \overline{[B . (A+C)]} \}$$

b) Reduce to maximum the above circuit. (10 points)

$$\begin{aligned}
 \overline{\overline{\overline{\text{Out}}}} &= \overline{(A + BC)} . \{ \overline{[(A + (B+C)) . (A + C)]} + \overline{[B . (A+C)]} \} \\
 &= (A + \overline{BC}) . \{ \overline{[(A + (B+C)) . (A + C)]} + \overline{[B . (A+C)]} \} \\
 &= (A + \overline{B} + \overline{C}) . \{ \overline{(\overline{A} + \overline{B} \ \overline{C}) . (A + C)} + \overline{AB + BC} \} \\
 &= (A + \overline{B} + \overline{C}) . \{ \overline{AC} + \overline{A} \ \overline{B} \ \overline{C} + \overline{A} \ B + B \ C \} \\
 &= A \ \overline{B} \ \overline{C} + A \ B \ C + \overline{A} \ \overline{B} \ \overline{C} + \overline{A} \ B \ \overline{C} \\
 &= A \ (\overline{B} \oplus C) + \overline{A} \ (B \oplus C) \\
 &= A \oplus B \oplus C
 \end{aligned}$$

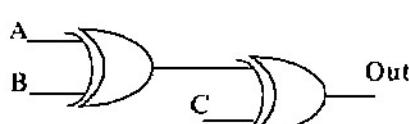

Question 4. (15 points)Find the minimum expressions (F and F') of the following k-maps:

AB \ CD	00	01	11	10
00	1	0	0	1
01	0	1	1	0
11	0	1	1	0
10	1	0	0	1

$$\begin{aligned} F &= BD + B'D' = (B \oplus D)' \\ F' &= B \oplus D \end{aligned}$$

AB \ CD	00	01	11	10
00	1	1	1	1
01	0	1	1	1
11	0	1	1	1
10	1	0	0	1

$$\begin{aligned} F &= AB' + AC' + AD + BC' \\ F' &= (A'B'D) + (BCD') \end{aligned}$$

AB \ CD	00	01	11	10
00	0	0	0	0
01	0	1	1	0
11	0	0	0	0
10	0	0	0	0

$$\begin{aligned} F &= BC'D \\ F' &= B' + C + D' \end{aligned}$$

AB \ CD	00	01	11	10
00	X	X	X	X
01	0	X	0	0
11	0	0	1	1
10	1	X	1	1

$$\begin{aligned} F &= D' + AC \\ F' &= (A'C')D \end{aligned}$$

AB \ CD	00	01	11	10
00	1	X	X	1
01	X	X	X	X
11	X	X	X	X
10	1	X	X	1

$$\begin{aligned} F &= 1 \\ F' &= 0 \end{aligned}$$

AB \ CD	00	01	11	10
00	X	0	0	0
01	0	X	1	0
11	0	0	X	0
10	0	0	0	X

$$\begin{aligned} F &= BC'D \\ F' &= B' + C + D' \end{aligned}$$

Simplify in maximum the following expressions (you can use K-maps):

$$1- X = AB'C' + A'D + D' = A' + D' + B'C$$

$$2- Y = A'C + AD + BCD = A'C + AD + \cancel{CD} \xrightarrow{\text{Add Redundant}} \cancel{A'C + AD + BCD} = A'C + AD + \cancel{AD} \xrightarrow{\text{Remove Redundant}} A'C + AD$$

$$3- Z = AD' + BD \text{----- NO CHANGE}$$


AB \ CD	00	01	11	10
00	1	1	1	1
01	1	1	0	1
11	1	1	0	0
10	1	1	1	1

AB \ CD	00	01	11	10
00				
01				
11				
10				

AB \ CD	00	01	11	10
00			1	1
01		1	1	
11		1	1	
10		1	1	1

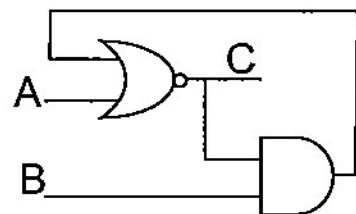Question 5. (Bonus: 5 points)

Complete the truth table of the following circuit:



A	B	C
0	0	1
0	1	C_p'
1	0	0
1	1	0

When $A = 1 \Rightarrow C = 0$