

NOTE1: OPEN BOOK, CLOSED NOTES.

NOTE2: SHOW ALL WORK IN ORDER TO RECEIVE FULL CREDIT.

1. 15 Pts. Perform the base conversions and binary operations indicated below.

$$(1040.9375)_{10} = (\quad)_{16} = (\quad)_{8} = (\quad)_{2}$$

$(1007.1)_8 - (1FF.C)_{16}$. Use two's complement addition.

2. 25 Pts. Which of the following four variable functions are equivalent? Justify your answer.

$$\begin{aligned} F_1 &= \sum m(0, 2, 5, 7, 8, 10, 13, 15) \\ F_2 &= (A + B)' + CD(A' + B') + ((B'C'D')(ABC'D')(ABCD'))' \\ F_3 &= ((B + D)(B' + D'))' + ABD + (B' + C' + D')' \\ F_4 &= \prod M(4, 5, 6, 9, 10, 12, 15) \\ F_5 &= AB' + CD + A'D + A'BC + A'B'C \\ F_6 &= (B' + C + D)(A' + B' + C)(A + B + C' + D) \end{aligned}$$

3. 20 Pts. Find the minterm and maxterm list forms for the function defined by the logic diagram in Fig.P3.

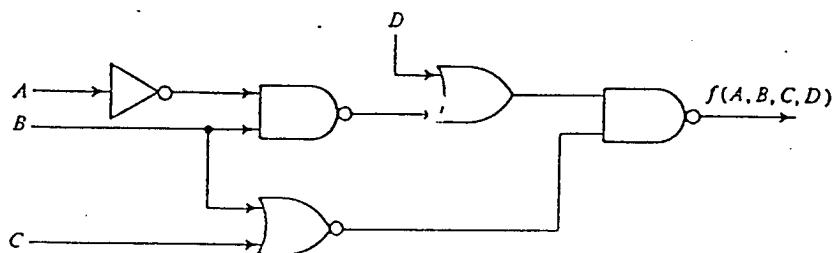


Fig.P3.

4. 20 Pts. $F(A, B, C, D, E) = \prod M(0, 3, 6, 9, 11, 19, 20, 24, 25, 26, 27, 28, 29, 30)$
 $\cdot \prod D(1, 2, 12, 13)$

- a. Find two minimum sum-of-products expressions for F.

b. Underline the essential prime implicants in your answer.

5.20 Pts. Design a switching network which has five input variables and one output variable. Four of the input variables represent BCD digits, while the fifth is a control line. While the control line is a logic 0, the output should be logic 1 only if the BCD digit is greater than or equal to 5. While the control line is high, the output should be logic 1 only if the BCD digit is less than or equal to 5.

Solution

Summer 2002

EEN 220

LOGIC DESIGN







Test 1

$$y(1040.9375)_{10} = (10000010000.1111)_2 (2020, 34)_8 = (410, f)_{16}$$




$$(1002.1)_8 - (1FF.C)_{16} =$$

$$- \begin{array}{r} 1000\ 000\ 111.0010 \\ 0111\ 111\ 111.1100 \end{array}$$

$$\begin{array}{r} 0 | 1000000111.0010 \\ 1 | 10000000000.0100 \\ \hline 100000000111.0110 \end{array}$$

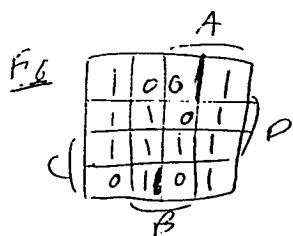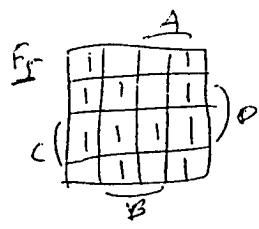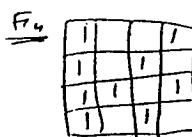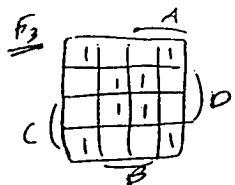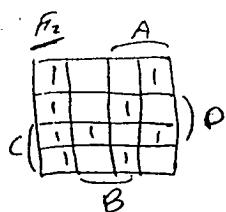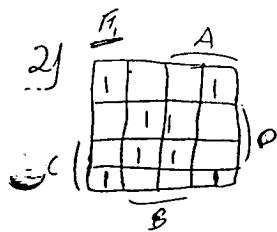
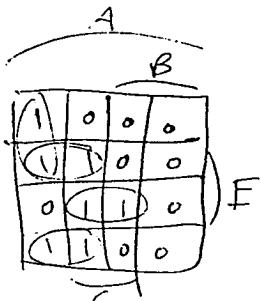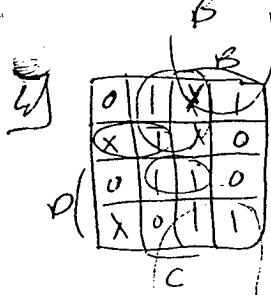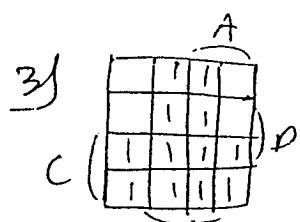
$$\left\{ \begin{array}{l} f_5 = f_6 \\ f_1 = f_3 \\ f_2 = f_4 \end{array} \right.$$



$$\Sigma (2, 3, 4, 5, 6, 7, 10, 11, 12, 13, 14, 15)$$

$$\Pi M (0, 1, 8, 9)$$

$$\frac{A'CD'}{A'CD'} + \frac{A'BE'}{A'CD'} + \frac{CDE}{CDE} + \frac{B'D'E}{AB'C'D'} \text{ essential}$$

$$A'CD' + A'BE' + CDE + AB'C'D' + B'D'E + AB'DE'$$

$$A'CD' + A'BE' + CDE + AB'C'D' + B'D'E + AB'CD$$

		X	1
	1	X	1
D	1	X	X
	1	X	X
C			

		X	1
	1	X	
	1	X	
E	1	X	X
C			

with X:

$$F(A, B, C, D, E) = A'B + AB'C' + A'CE + A'CD + ACD'$$

~~no X!~~

Ec control line

		A	
	1	1	1
C	1	1	1
	1	1	1
B			

$$AB'C' + AB'D' + A'BC'b' + A'B'CD + A'B'CE$$

		E	A	B	C	D
	1	1				
	1	1				
	1	1				
	1	1				
B						

$$AE' + A'B'F + A'C'E + BDE' + BCE'$$