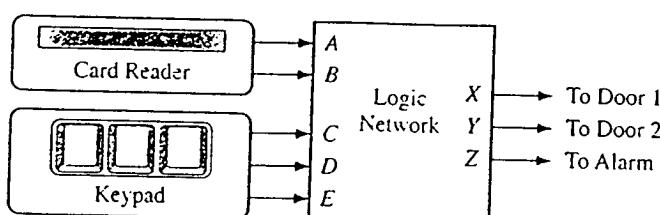


Note 1: Open book, open Notes, Closed Neighbours

Note 2: Show all work in order to receive full credit.

Note 3: Start each problem on a new page.

- 1:25 Pts A simple security system for two doors consists of a card reader and a keypad.



A person may open a particular door if he or she has a card containing the corresponding code, and enters an authorized keypad code for that card. The outputs from the card reader are as follows:

	<u>A</u>	<u>B</u>
No card inserted	0	0
Valid code for door 1	0	1
Valid code for door 2	1	1
Invalid card code	1	0


To unlock a door, a person must hold down the proper keys on the keypad and then insert the card in the reader. The authorized keypad codes for door 1 are 101 and 110, and the authorized keypad codes for door 2 are 101 and 011. If the card has an invalid code or if the wrong keypad code is entered, the alarm will ring when the card is inserted. If the correct keypad code is entered, the corresponding door will be unlocked when the card is inserted.

Design the logic network for this simple security system. Your network's inputs will consist of a card code AB, and a keypad code CDE. The network will have three outputs XYZ (if X or Y = 1, door 1 or 2 will be opened; if Z=1, the alarm will sound). Design your network and implement in NAND/NAND form.



2. 20 Pts. Realize the function

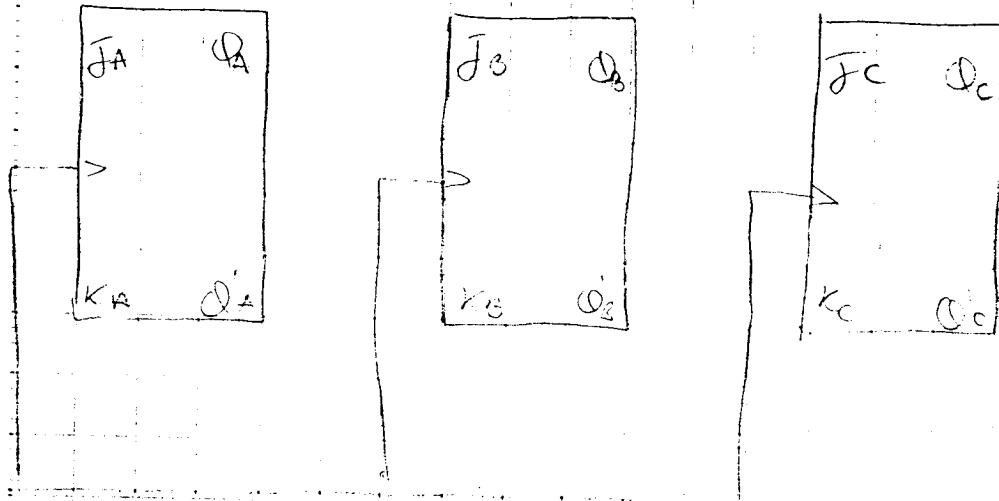- (a) using a 16-to-1 MUX with control inputs A,B,C, and D
- (b) using an 8-to-1 MUX with control inputs A, B, and C and added gates

$$F(A,B,C,D,E) = \sum m(0,2,6,7,8,10,11,12,13,14,16,18,19,29,30) + \sum d(4,9,21)$$




$CLK \rightarrow$

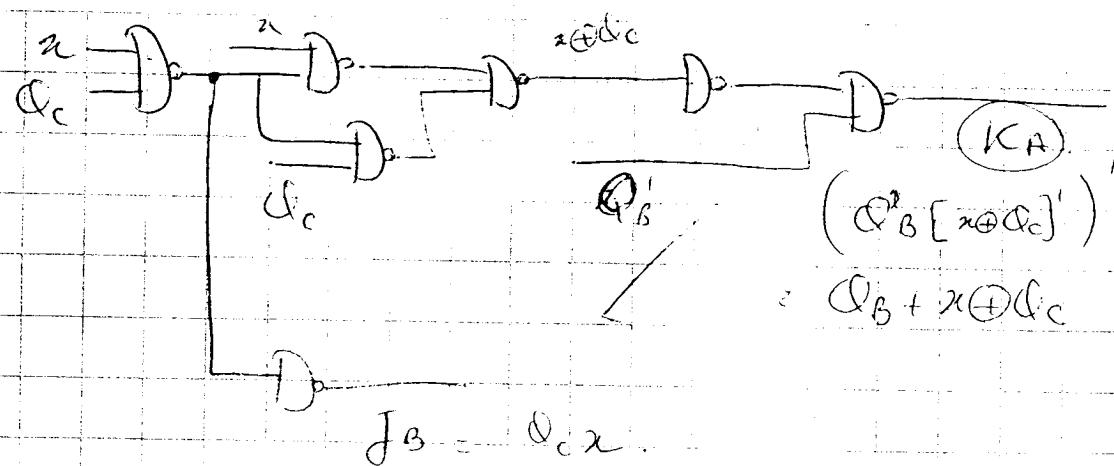
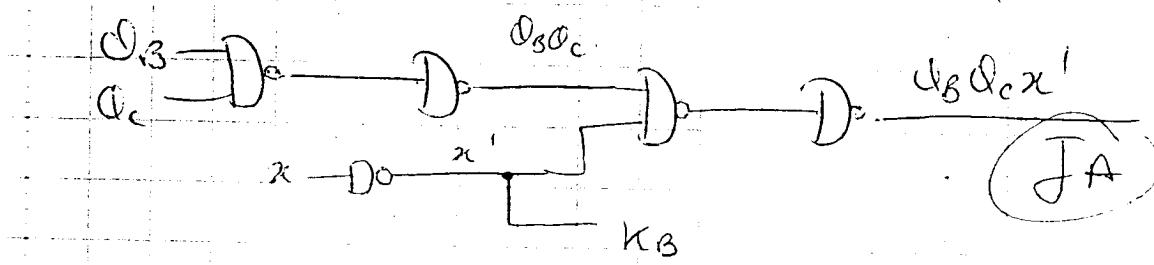


$$(Q_B' [x \oplus Q_C])'$$

$$Q_B + x \oplus Q_C$$

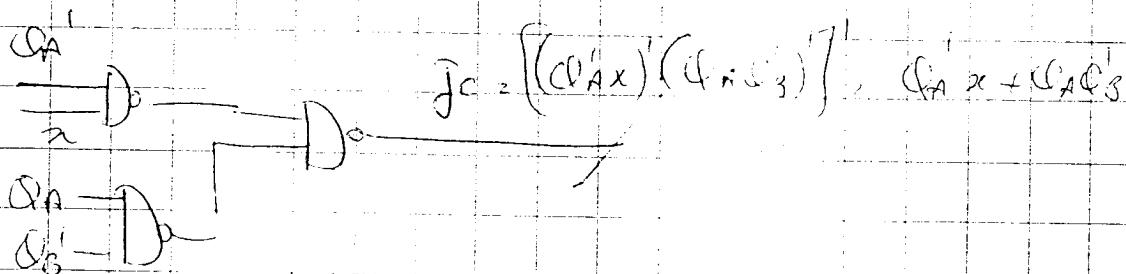
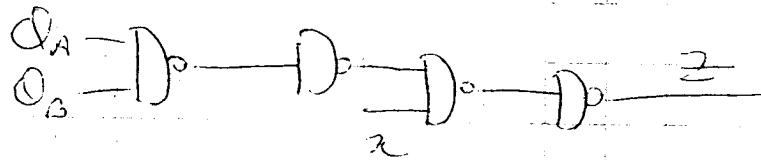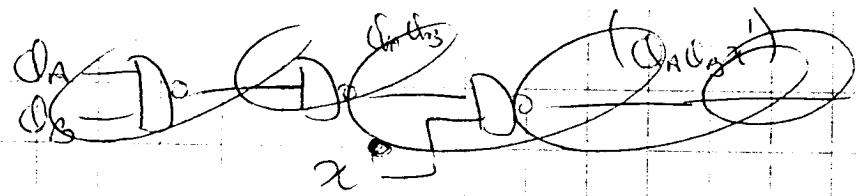
$$J_C = [(Q_A x) (Q_B x')] \quad (Q_A x + Q_A Q_B)$$



Don't Care States
for $D_A, D_B, \text{ and } x$

$J_K = K_A$ $J_K = K_B$ $J_K = K_C$ $C_A C_B + C_C$

1 1 1 0	1 1 0 1 0 1 0 0 0 0 0
1 1 1 1	0 1 1 0 0 0 0 1 0 1 1

\Rightarrow The circuit counts out 7 don't care states: from 110 \rightarrow

If $x = 0$ $11 \rightarrow 00$ ✓

$x = 1$ $11 \rightarrow 01$ ✓



Name: _____

Section: _____

A

(3)

b	x	
c	x	x
d	x	x b
e	db	x
f	x	b hg x
g	hg	x
h	v	a d a d a ga
	a b c d e f g	

Electronics

Copy Centre

03/970742

a =

b =

c =

d =

e =

f =

g =

h =

i =

j =

k =

l =

m =

n =

o =

p =

q =

r =

s =

t =

u =

v =

w =

x =

y =

z =


Rectangular

$$\begin{aligned} F &= D \\ B &= E \end{aligned}$$


10

a	a/1	c/0
b	c/0	d/1
c	a/0	b/0
d	f/0	a/0
e	c/0	f/1
f	f/0	a/0

4 Sheets

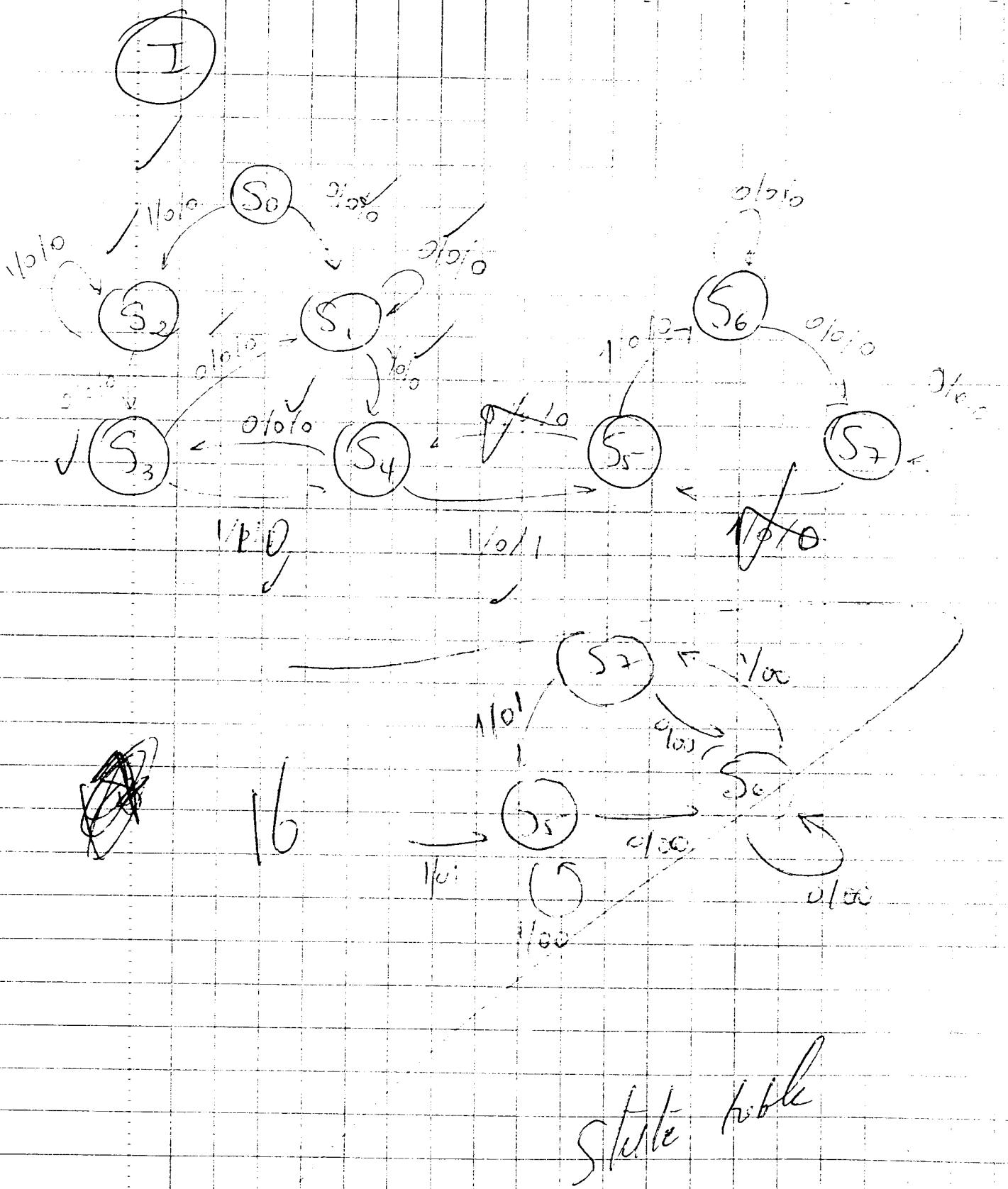


state table

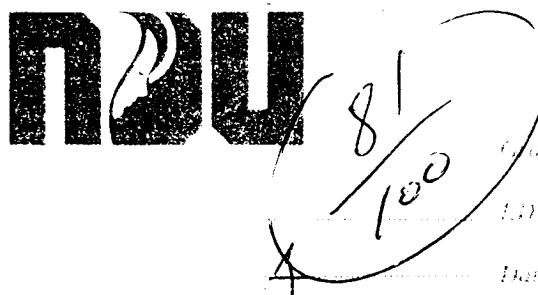

16 2) State Table

	0	1
A	A/0	B/0
B	A/0	C/0
C	A/0	D/0
D	E/0	D/0
E	F/0	B/0
F	A/0	G/0
G	A/0	C/1

S _A S _B S _C	0	1
000	000/0	001/0
001	000/0	010/0
010	000/0	011/0
011	100/0	011/0
100	101/0	001/0
101	000/0	110/0
110	000/0	010/1

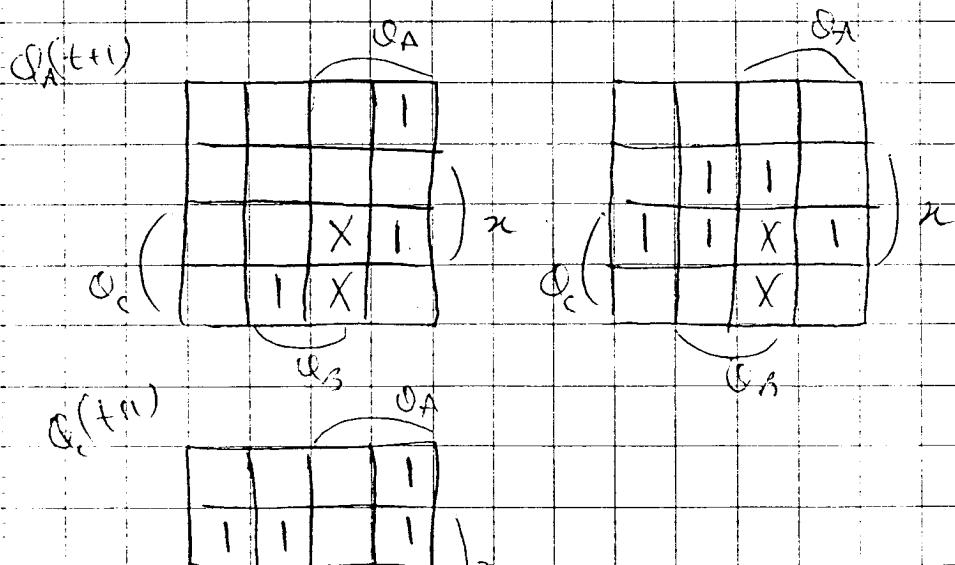

$$J_A = Q_C \left(\begin{array}{|ccc|} \hline & X & X \\ & X & X \\ X & X & X \\ \hline 1 & X & X \\ \hline \end{array} \right) x$$

Q_1

Q_2

Q_3

$$K_A = Q_C \left(\begin{array}{|ccccc|} \hline & X & X & 1 & 1 \\ & X & X & 1 & 1 \\ & X & X & X & X \\ X & X & X & X & 1 \\ \hline \end{array} \right) x$$

Q_1

Q_2

Q_3

$$J_B = Q_B Q_C x$$

$$K_A = Q_3 + x \oplus Q_C$$

$$J_B = Q_C \left(\begin{array}{|ccc|} \hline & X & X \\ & X & X \\ X & X & X \\ \hline 1 & X & X \\ \hline \end{array} \right) x$$

Q_1

Q_2

Q_3

$$K_B = Q_C \left(\begin{array}{|cccc|} \hline & X & 1 & 1 & Y \\ & X & & & X \\ & X & & X & X \\ X & 1 & X & X \\ \hline \end{array} \right) x$$

Q_1

Q_2

Q_3

$$J_B = Q_C x$$

$$K_B = x'$$

$$J_C = Q_C \left(\begin{array}{|ccc|} \hline & & 1 \\ & & 1 \\ 1 & 1 & 1 \\ \hline Y & X & X & X \\ X & X & X & X \\ \hline \end{array} \right) x$$

Q_1

Q_2

Q_3

$$K_C = Q_C \left(\begin{array}{|cccc|} \hline & Y & X & X & X \\ & X & X & X & X \\ 1 & & Y & 1 & \\ \hline 1 & 1 & V & 1 & \\ \hline \end{array} \right) x$$

Q_1

Q_2

Q_3

$$J_C = Q_A' x + Q_A Q_S$$

$$K_C = Q_B' + x' + (Q_3 x)'$$

$$Z = Q_A Q_S x$$

$$Z = Q_A Q_S x$$

-3. 25 pts. Reduce the following state table to a minimum number of states.

Present State	Next State		Present Output	
	X = 0	X = 1	X = 0	X = 1
a	b	c	1	0
b	c	d	0	1
c	b	a	0	0
d	f	a	0	0
e	c	d	0	1
f	f	g	0	0
g	h	c	1	0
h	a	c	1	0



b	α						
c	α	α					
d	α	α	b b				
e	α	df	α	bb			
f	α	bb	bb	bb	α	α	α
g	bb	α	α	α	α	α	α
h	α	α	α	α	α	α	α


Handwritten notes around the table:

- Above the first column: $A_2 \rightarrow a \Rightarrow g$
- To the right of the second column: (d, f, b, e)
- Below the last row: $g \rightarrow a, g \rightarrow g$


$$3) x = A'B'D + C'D + AB' + AB'C'D'$$

$$y = A'B'D + BCD + AB'$$


$$z = A'B'D + BCD + ABC + AB'C'D'$$

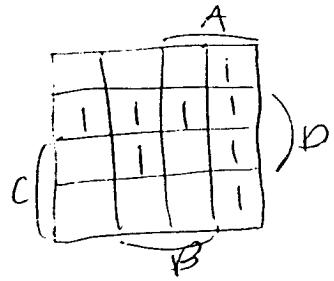

$$x = AB' + C'D + A'D$$

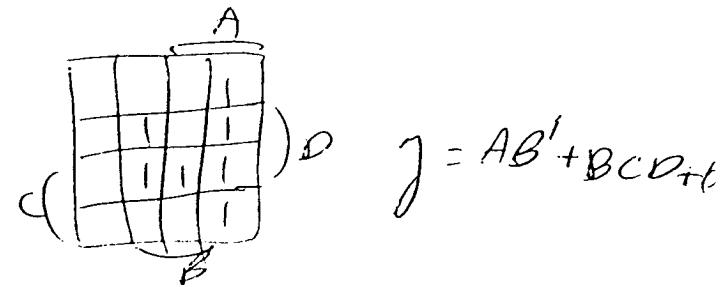

$$y = AB' + BCD + C'D$$

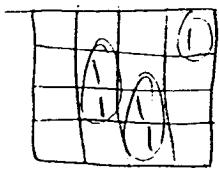


$$z = A'B'D + ABC + AB'C'D'$$



$$x = \Sigma m(1, 5, 7, 8, 9, 10)$$

$$y = \Sigma m(5, 7, 8, 9, 10, 11, 12)$$



$$z = \Sigma m(5, 7, 8, 14, 15)$$

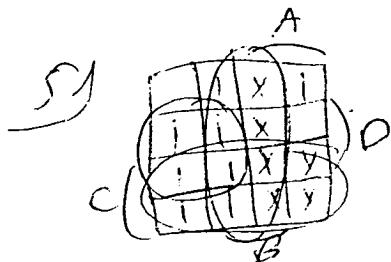

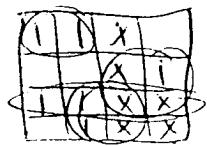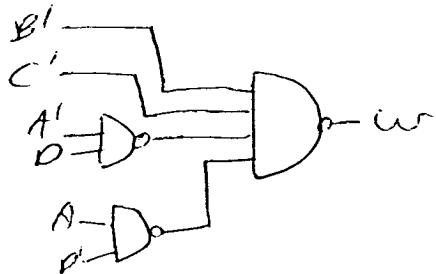
$$w = C + B + A'D + AD' = (B'C'(A'D)'(AD'))'$$



$$x = AD + BC + CD + A'C'D'$$

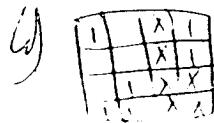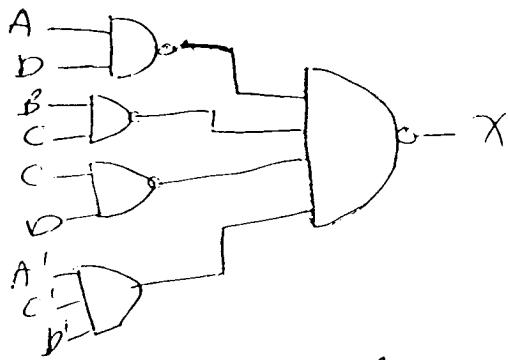

$$z = A + B'D' + BC$$

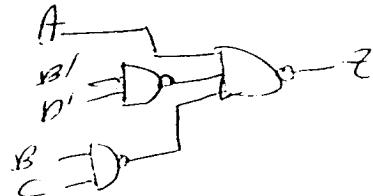

$$c'D + D' - f$$

Solution SPRING 2001

Logic Design



Test 2

$$Y = A'B'C'D'E + A'B'C'D'E'$$

$$J = ABCD'E + ABC'D'E$$

$$Z = AB' + A'B \left(E_m (0, 1, 2, 3, 4, 7) \right) + AB \left(E_m (0, 1, 2, 4, 6, 7) \right)$$
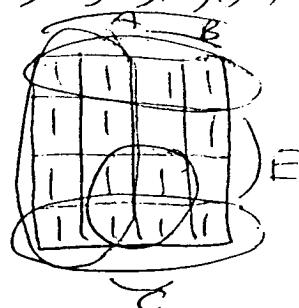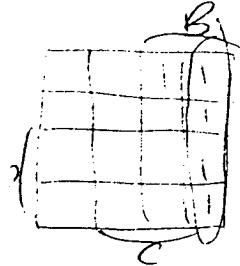
$$Z = AB' + E_m (8, 9, 10, 11, 12, 15) + E_m (24, 25, 26, 28, 30, 31)$$



$$Z = AB' + AE' + A'B'C' + ACD + AC'D' + BD'E'$$



$$Z = ((AB')'(AE')'(A'B'C')'(ACD)'(AC'D')'(BD'E'))'$$

$$X = ((A'BCD'E)'(A'BCDE'))'$$

$$J = ((ABC'D'E)'(ABC'DE))'$$

$$Z = AB' + C'D'E' + C'D'E + C'D'E' + C'D'E' + CDE$$

$$Z = AB' + C'D' + C'E' + D'E' + CDE$$

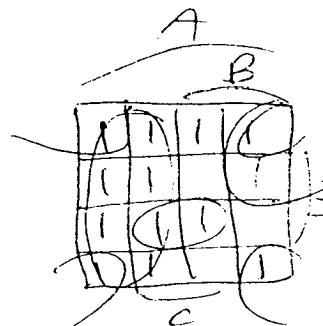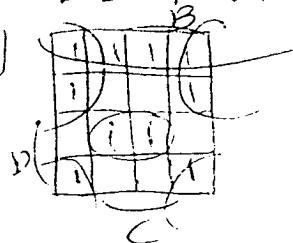

$$2) F(A, B, C, D, E) = E_m (0, 2, 6, 7, 8, 10, 11, 12, 13, 14, 16, 18, 19, 29, 30) + E_d (4, 9,$$

E	1	0
E'	1	1
0	1	1
1	1	1
1	1	1
1	1	1
1	1	1
1	1	1
1	1	1
1	1	1
1	1	1
1	1	1
1	1	1
1	1	1
1	1	1
1	1	1
1	1	1

$\rightarrow F$



I ¹	1	0
C ₁	1	1
I ₂	1	1
(DE)'	1	1
(D'E)'	1	1
O	0	1
O	0	1
R(D'E)	1	1