

Department of Electrical and Computer  
Engineering

**EEN 205 – Electric Circuit**  
**Exam 1 – April 8, 2010**  
**Exam Duration: 60 minutes**

59+5

64

Student Name: \_\_\_\_\_


Section: \_\_\_\_\_

Student ID No.: \_\_\_\_\_

Note:

- You have **7 problems, 8 pages** Exam including the first page.
- No cell phones are allowed in the exam room
- All questions **should be answered on the space below each question.**
- All answers are to be **explained in detail.**
- Reverse side** of each paper sheet is to be **used for scratch paper.**
- Illegible** answers may **not be graded.**
- Underline** intermediate answers and **box your final answer.**
- Penalty** will be applied to any student who **fails to submit** the Exam in full to the instructor within **15 seconds** of the announcement of the **end of the exam.**

1. (15 points) Find the Current  $I$  Supplied by the 50-V Source.

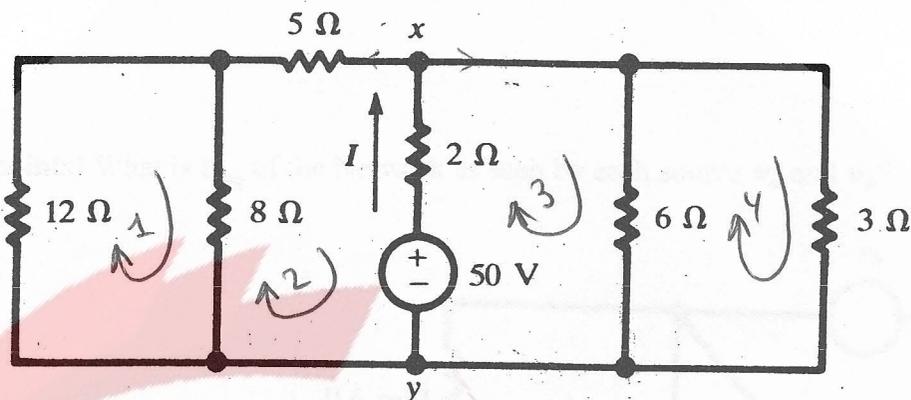

mesh 1

$$-12i_1 - 8(i_1 - i_2) = 0 \quad (1)$$

mesh 2

$$-8(i_2 - i_1) - 5(i_2) - 2(i_2 - i_3) - 50 = 0 \quad (2)$$

mesh 3

$$-2(i_3 - i_2) - 6(i_3 - i_4) + 50 = 0 \quad (3)$$

mesh 4

$$-6(i_4 - i_3) - 3i_4 = 0 \quad (4)$$

$$\begin{aligned} (4) \rightarrow -6i_4 + 6i_3 - 3i_4 &= 0 \\ -9i_4 &= -6i_3 \\ i_4 &= \frac{6}{9}i_3 \rightarrow i_4 = 0.666i_3 \end{aligned}$$

$$\begin{aligned} -20i_1 + 8i_2 &= 0 \\ 8i_1 - 15i_2 + 2i_3 &= 50 \\ 2i_2 - 4.004i_3 &= -50 \end{aligned}$$

$$I = i_3 - i_2 = 13.65$$

$$i_1 = -0.926 \text{ A}$$

$$i_2 = -2.316 \text{ A}$$


$$i_3 = 11.33 \text{ A}$$

$$i_4 = 7.54 \text{ A}$$


$$\text{and } I = i_2 + i_3 = -2.316 + 11.33$$

$$I = 9.014 \text{ A}$$

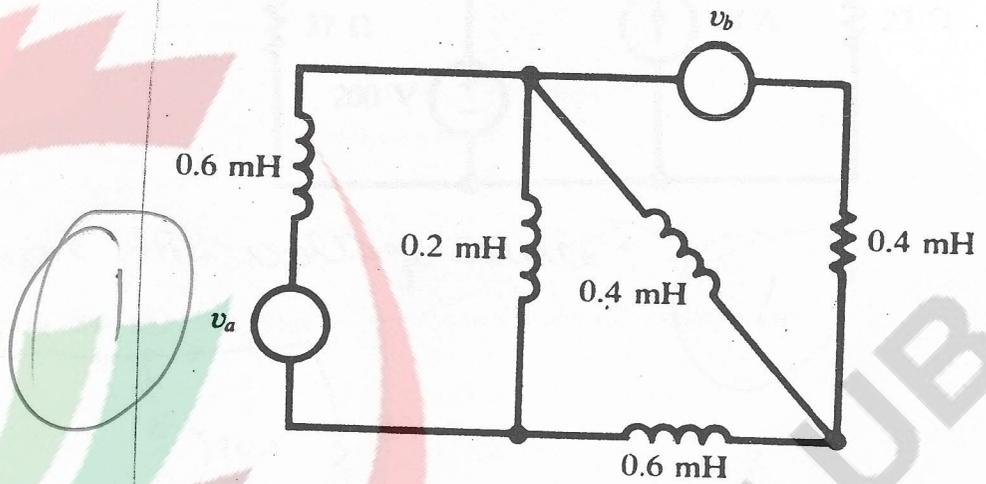2. (5 points) What is  $L_{eq}$  of the Network as seen by each source  $v_a$  and  $v_b$ ?




Seen by source  $v_a$

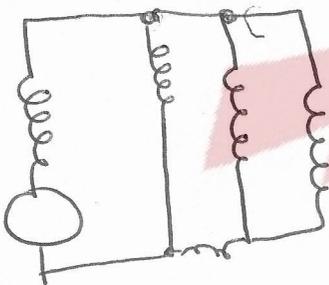


$$(0.2 + 0.6) \parallel 0.6 \parallel 0.4 \parallel 0.4$$

$$\boxed{0.12 \text{ mH}}$$

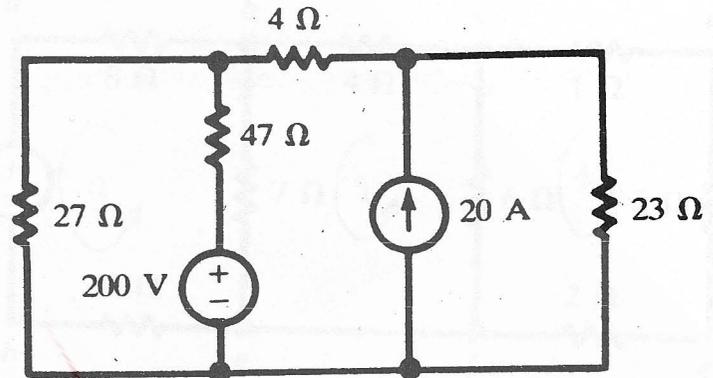3. (15 points) Compute the Current in the  $23\Omega$  resistor by applying the superposition principle. Show all work including equivalent Circuits.



if we remove the voltage source:

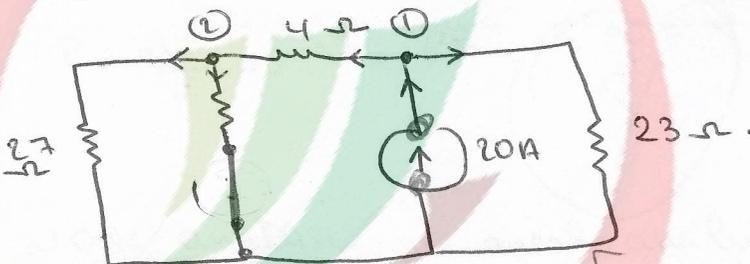

mode analysis: at mode 1

$$20 = \frac{v_1}{23} + \frac{v_1 - v_2}{4} \quad (1)$$

at mode 2

$$\frac{v_1 - v_2}{4} = \frac{v_2}{47} + \frac{v_2}{27} \quad (2)$$


$$\begin{cases} 0.29 v_1 - 0.25 v_2 = 20 \\ 0.25 v_1 - 0.308 v_2 = 0 \end{cases}$$

$$v_1 = 229.67 \text{ V}$$

$$v_2 = 186.42 \text{ V}$$

$$v_1 = 23 \times i \Rightarrow i_1 = \frac{229.67}{23} = 9.98 \text{ A}$$

If we remove the current source:

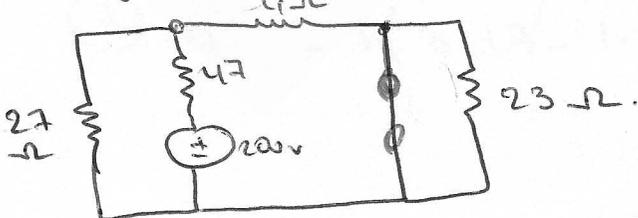


$$i_2 = 0$$

$$\Rightarrow i = i_1 + i_2 = 9.98 + 0 \Rightarrow i = 9.98 \text{ A}$$

4. Find the Source voltage  $V_s$  that result in power of  $P = 3W$  in the  $3\Omega$  resistor

(15 points)

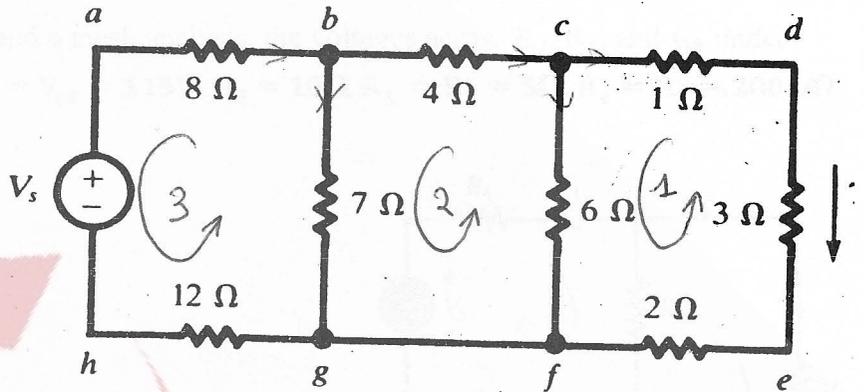

$$R = 3\Omega \rightarrow P = 3W$$

$$P = \frac{V^2}{R} \Rightarrow V^2 = PR$$

$$V = \sqrt{PR}$$

$$\Rightarrow V_{3\Omega} = \sqrt{3 \times 3} = 3V$$

$$i_{3\Omega} = \sqrt{\frac{P}{R}} = \sqrt{\frac{3}{3}} = 1A$$

~~Node analysis~~

~~node b~~

$$\frac{V_s - V_b}{8}$$

mesh analysis

$$\textcircled{1} \quad -3i_1 - 1i_1 - 6(i_1 - i_2) - 2i_1 = 0$$

$$\textcircled{2} \quad -6(i_2 - i_1) - 4i_2 - 7(i_2 - i_3) = 0$$

$$\textcircled{3} \quad -7(i_3 - i_2) - 8(i_3) - V_s - 12i_3 = 0$$

$$\textcircled{1} \rightarrow -3 - 1 - 6 + 6i_2 - 2 = 0$$

$$6i_2 = 10 \rightarrow i_2 = 1.66A$$

$$\textcircled{2} \rightarrow -6(1.66 - 1) - 4(1.66) - 7(1.66) + 7i_3 = 0$$

$$7i_3 = 22.2 \rightarrow i_3 = 3.17A$$

$$\textcircled{3} \rightarrow -7(3.17 - 1.66) - (8 \times 3.17) - V_s - (12 \times 3.17) = 0$$

$$V_s = 7$$

$$V_s = -73.97V$$

94. V = 14

5. (20 points) Under normal condition the fuses F1 and F2 in the circuit below are modeled as a short circuit. However, if excess current flows through a fuse, its element melt and the fuse blows.

Determine, using KVL and a mesh analysis, the voltages across  $R_1$ ,  $R_2$ , and  $R_3$  under normal conditions.  $V_{s1} = V_{s2} = 115V$ ,  $R_3 = 10\Omega$ ,  $R_1 = R_2 = 5\Omega$ ,  $R_4 = R_5 = 200m\Omega$

mesh analysis

$$V_{s1} - R_4 i_1 - R_1(i_1 - i_3) = 0$$

$$\textcircled{1} \quad 115 - 0.2 i_1 - 5(i_1 - i_3) = 0$$

$$V_{s2} - R_2(i_2 - i_3) - R_5 i_2 = 0$$

$$\textcircled{2} \quad 115 - 5(i_2 - i_3) - 0.2 i_2 = 0$$

$$-R_1(i_3 - i_1) - R_1(i_3 - i_2) - R_3 i_3 = 0$$

$$\textcircled{3} \quad -5(i_3 - i_1) - 5(i_3 - i_2) - 10 i_3 = 0$$

$$-5.2 i_1 + 5 i_3 = -115$$

$$-5.2 i_2 + 5 i_3 = -115$$

$$5 i_1 + 5 i_2 - 20 i_3 = 0$$

$$i_1 = 42.59 \text{ A}$$

$$i_2 = 42.59 \text{ A}$$


$$i_3 = 21.29 \text{ A}$$

$$V_1 = R_1 i_1 = 42.59 \times 5 \Rightarrow V_1 = 212.95 \text{ V}$$

$$V_2 = R_2 i_2 = 5 \times 42.59 \Rightarrow V_2 = 212.95 \text{ V}$$



$$V_3 = R_3 i_3 = 10 \times 21.29 \Rightarrow V_3 = 212.9 \text{ V}$$

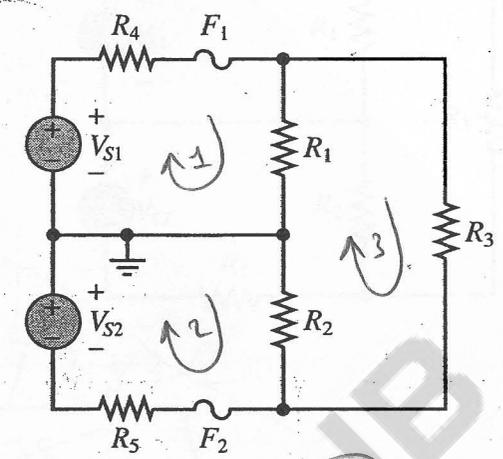similarly for  $V_{R_2}$   
( $i_2 - i_3$ )




12

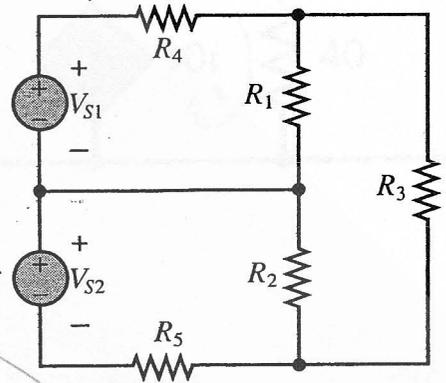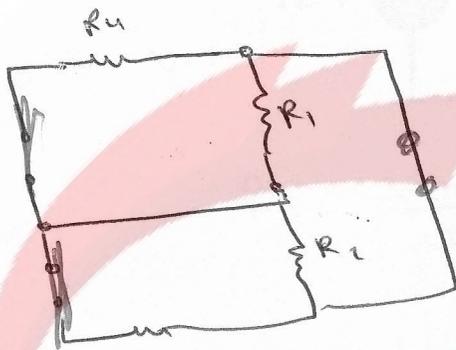6. (20 points) Find the Thevenin equivalent circuit resistance seen by  $R_3$  in the circuit below. Compute the Thevenin voltage and the Norton Current when  $R_3$  is the load.  
 $V_{s1} = V_{s2} = 450V$ ,  $R_3 = 10\Omega$ ,  $R_1 = 7\Omega$ ,  $R_2 = 5\Omega$ ,  $R_4 = R_5 = 1\Omega$



$$R_{eq} = (R_4 \parallel R_1) + (R_2 \parallel R_5) = 1.7083 \Omega$$

$$= 0.875 + 5 = \boxed{5.875 \Omega}$$

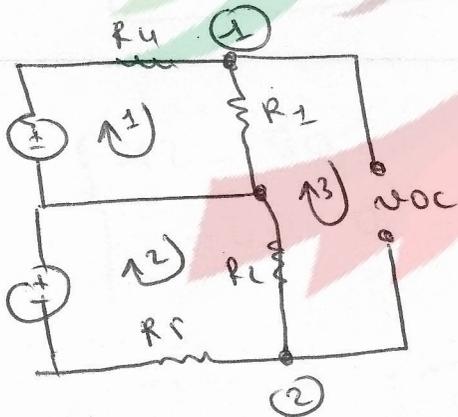

mesh analysis

at node 1

$$\frac{450 - v_1}{1} = \frac{v_1}{7}$$


$$450 = 1.14 v_1$$

$$v_1 = 393.75V$$

at node 2

$$v_{oc} = 393.75V$$

$$v_2? \quad v_{oc} = v_1 - v_2$$

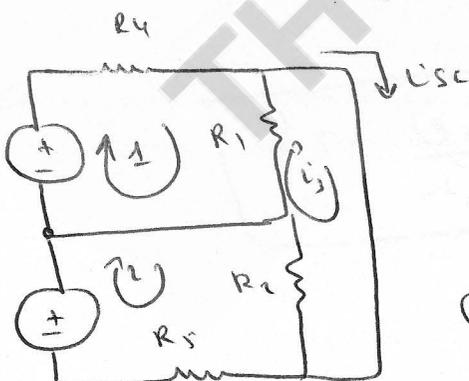

mesh analysis

$$\textcircled{1} \quad 450 - 1i_1 - 7(i_1 - i_{sc}) = 0$$

$$\textcircled{2} \quad 450 - 5(i_2 - i_{sc}) - 1i_2 = 0$$

$$\textcircled{3} \quad -7(i_{sc} - i_1) - 5(i_{sc} - i_2) = 0$$

$$\begin{cases} 8i_1 + 7i_{sc} = -450 \\ -6i_2 + 5i_{sc} = -450 \\ 7i_1 + 5i_2 - 12i_{sc} = 0 \end{cases}$$

pg. 7

next page  
continues

14

$$i_1 = 450 \text{ A}$$

$$i_2 = 450 \text{ A}$$


$$i_3 = i_{sc} = 450 \text{ A}$$



THE DEBATE CLUB

$0.450 - 0.450 = 0$   
 $0.450 - 0.450 = 0$   
 $0.450 - 0.450 = 0$

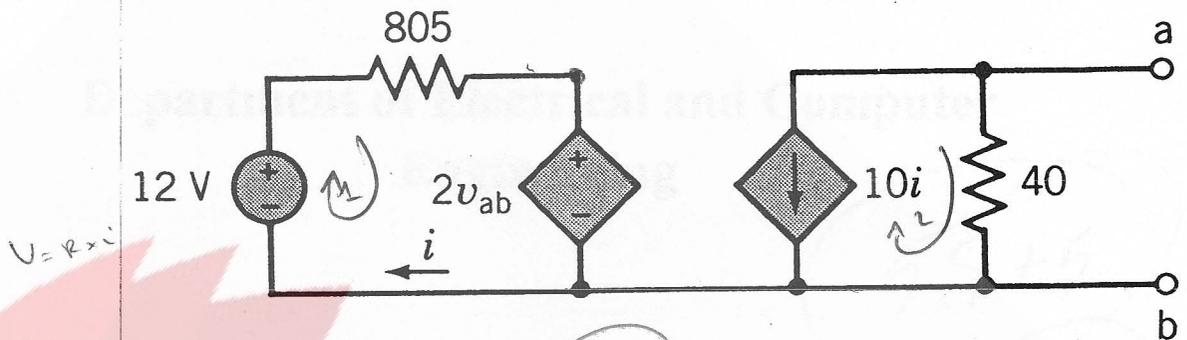7. (10 points) Find the Norton equivalent Circuit.



$$R_T = \frac{V_{oc}}{i_{sc}}$$

7

$$i = \frac{12}{805} = 0.014 \text{ A}$$

$$I_{sc} = 10 \times 0.014 = 0.14 \text{ A}$$

$$V_{oc} = -960 \text{ V}$$

$$R_T = \frac{V_{oc}}{i_{sc}}$$

$$= 6.442 \text{ k}\Omega$$

$$\begin{cases} 12 - 805i + 2v_{ab} = 0 \\ -40 \times 10i = v_{ab} \rightarrow -i = \frac{v_{ab}}{400} \end{cases}$$

~~$$i = -\frac{v_{ab}}{400}$$~~

$$12 - 805\left(\frac{v_{ab}}{400}\right) - 2v_{ab} = 0$$

$$12 - 4.0125v_{ab} = 0$$

$$v_{ab} = 2.99 \text{ V}$$

$$R_T = \frac{v_{ab}}{i_{sc}} = \frac{2.99}{0.14} = 21.36 \Omega$$