

EEN 105 201  
CIRCUIT ANALYSIS

TEST 1  
50 MINUTES

NDU  
ECCE DEPARTMENT  
NON ECCE

NOTE 1: OPEN BOOK, OPEN NOTES.

NOTE 2: SHOW ALL WORK TO RECEIVE FULL CREDIT

1. 15 pts. Determine the power that is absorbed or supplied by the elements in Fig. P1. Check for power conservation law.

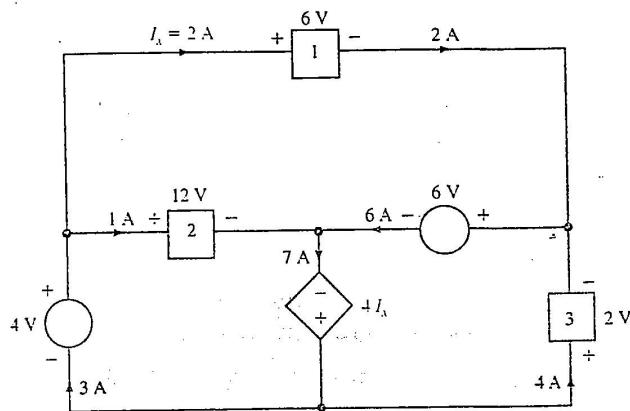


Fig. P1

2. 15 pts. In the network in Fig. P2, if  $V_0 = 12\text{ V}$ , find  $V_s$ .

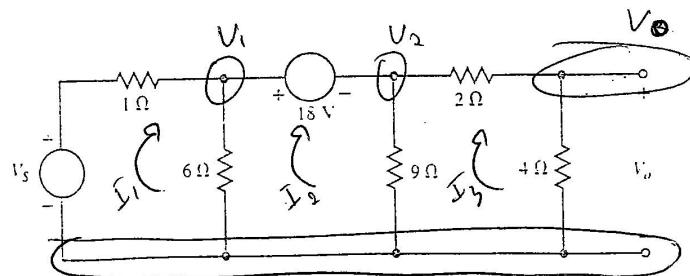


Fig. P2

$$V_s = 47\text{ V}$$

$$V_s = 11 \times 1 + 36$$

$$\boxed{V_s = 47\text{ V}}$$

3. 20 pts. Use loop analysis to find  $V_0$  in the network in Fig P3.

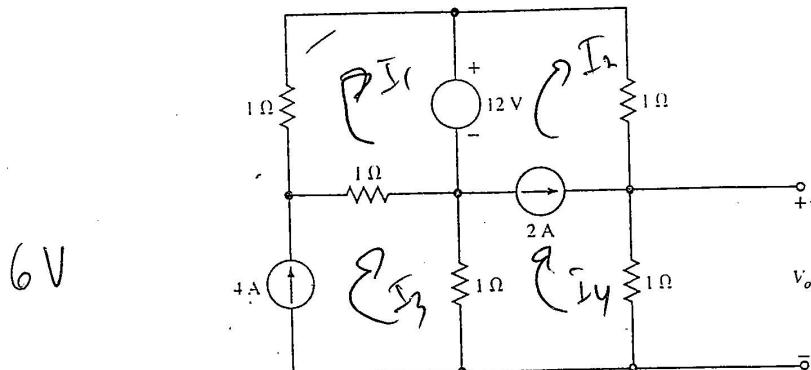


Fig. P3

4. 30 pts. Apply Thevenin's theorem to find  $V_0$  in the circuit in Fig. P4.

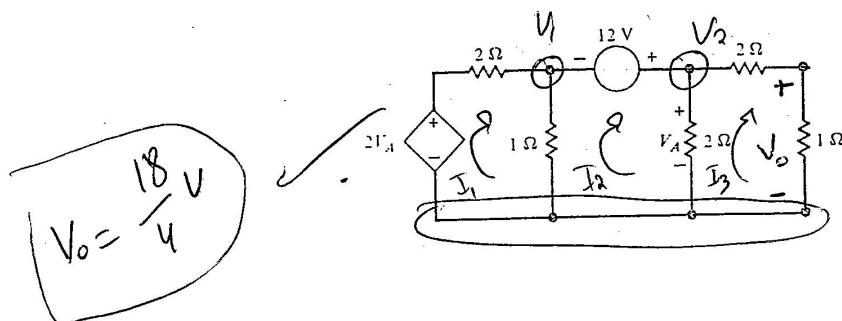


Fig. P4

*Source TRANS.*  
5. 20 pts. Use \_\_\_\_\_ to find  $V_0$  in the Fig. P5.

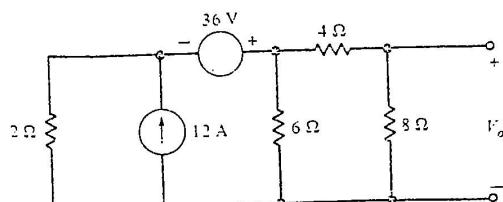


Fig. P5

$$V_0 = 26.6 \text{ or } \frac{80}{3}$$