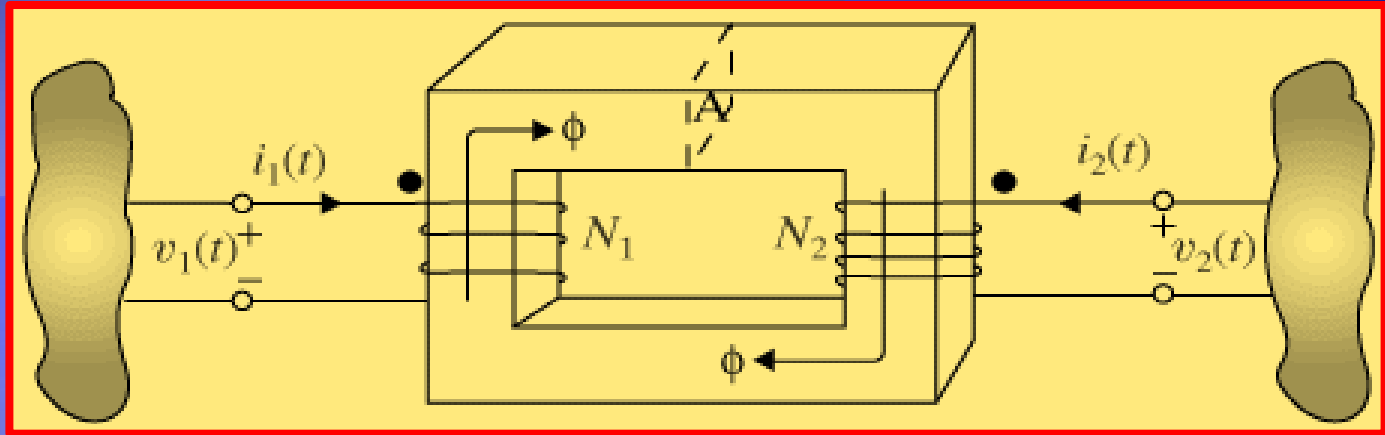


IDEAL TRANSFORMER



If we consider the particular situation where the two coupled coils are wound around a single closed magnetic core, with the **same core flux, ϕ , linking all the turns of both coils**, we could write:

$$v_1(t) = N_1 \frac{d\phi}{dt} \text{ and } v_2(t) = N_2 \frac{d\phi}{dt}$$

Which means that:


$$\frac{v_1}{v_2} = \frac{N_1}{N_2}$$

On the other hand, if we consider that the **wire resistance of the coils is negligible**, we deduce that the transformer under consideration is **lossless**:


$$v_1(t)i_1(t) + v_2(t)i_2(t) = 0$$

$$\Rightarrow \frac{i_1}{i_2} = -\frac{N_2}{N_1}$$

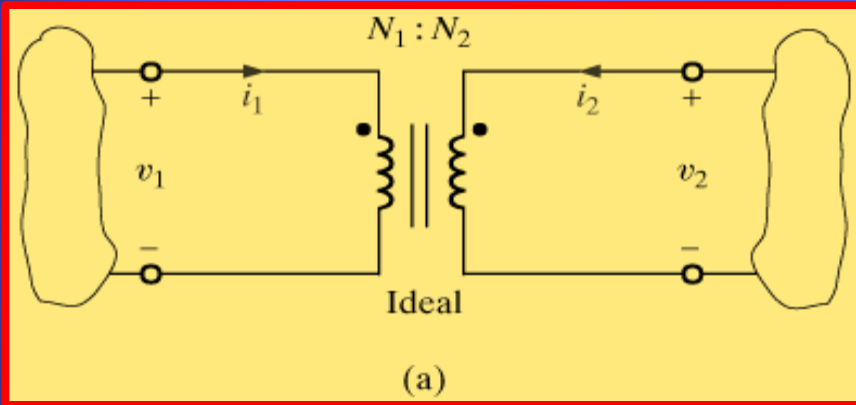These equations are applicable when **both currents are flowing into the dots and both voltages are positive at the dots**, as shown in the following Figure:



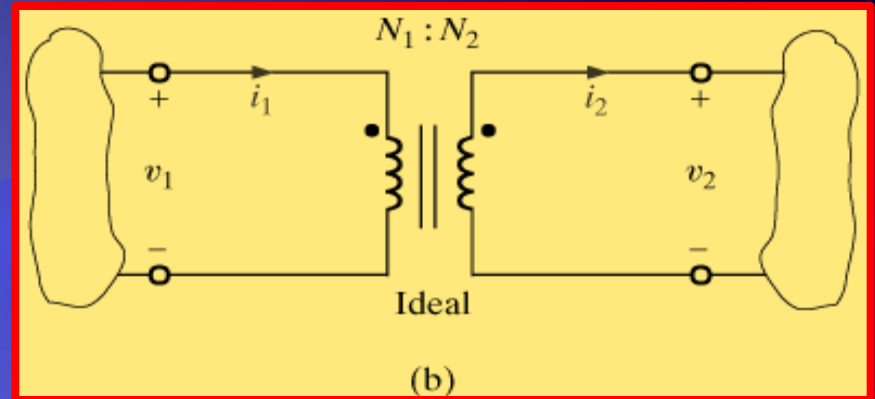However, the normal power flow through such coil combination takes place **from an input current in the primary to an output current in the secondary**, as shown in the following Figure. In this case, the corresponding voltage and current equations could be written as:



$$\frac{v_1}{v_2} = \frac{N_1}{N_2}$$


$$\text{and : } \frac{i_1}{i_2} = \frac{N_2}{N_1}$$

In both cases, such coil combination is called **Ideal Transformer**. It is modeled using the word “Ideal” under the two coils, **two vertical lines** representing the common core, and **two numbers N_1 and N_2** representing the **turns ratio** of the transformer.

We note that although the voltage and current levels change through an ideal transformer, **the power levels do not!**

Note that **practical transformers** do not use dots as such. Instead, they use **markings** specified in the US by the National Electrical Manufacturers Association (**NEMA**). These markings are conceptually equivalent to the dots.

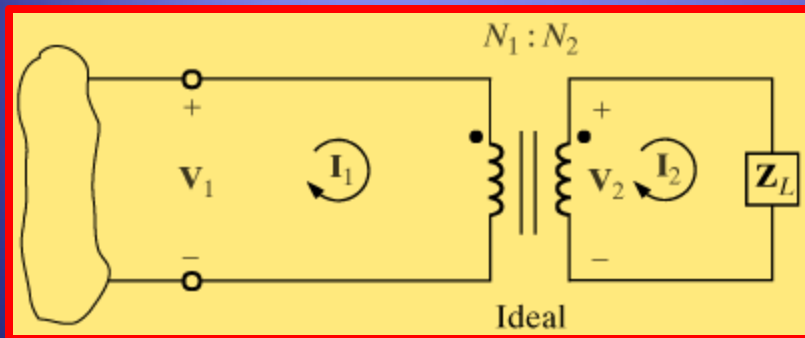Now, if we consider the following phasor-domain circuit:



Since **both voltage phasors are positive at the dots**, we could write:

$$\frac{\mathbf{V}_1}{\mathbf{V}_2} = \frac{N_1}{N_2}$$

And since **one current phasor enters the dot while the other leaves the dot**:

$$\frac{\mathbf{I}_1}{\mathbf{I}_2} = \frac{N_2}{N_1}$$

In other words:

$$\mathbf{V}_1 = \frac{N_1}{N_2} \mathbf{V}_2 \quad \text{and} \quad \mathbf{I}_1 = \frac{N_2}{N_1} \mathbf{I}_2$$

Therefore, the input impedance is:

$$\mathbf{Z}_1 = \frac{\mathbf{V}_1}{\mathbf{I}_1} = \left(\frac{N_1}{N_2} \right)^2 \frac{\mathbf{V}_2}{\mathbf{I}_2} = \left(\frac{N_1}{N_2} \right)^2 \mathbf{Z}_L$$

Which means that the load impedance, \mathbf{Z}_L is **reflected** into the primary side **by the square of the turns ratio**.

If we designate the turns ratio as n :

$$n = \frac{N_2}{N_1}$$


The previous equations could be rewritten as:

$$V_1 = \frac{V_2}{n} ; I_1 = nI_2 ; \text{ and } Z_1 = \frac{Z_2}{n^2}$$

When using these equations, **care must be taken** regarding the **polarities of voltages**, the **directions of currents**, and the **positions of dots**.

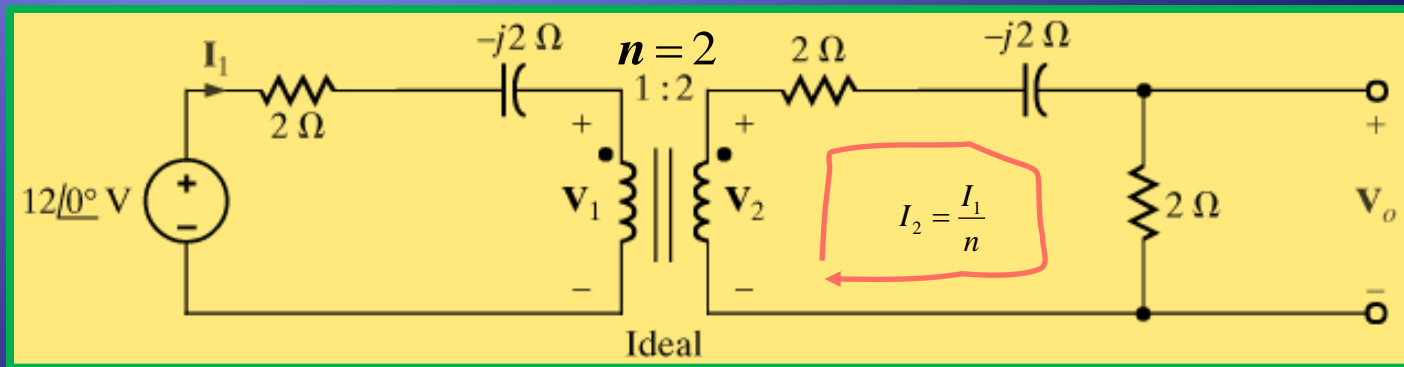
Example 10.8 – Voltages and Currents in an Ideal Transformer

E 10.6 – Reflecting Load Impedance into the Primary



Strategy: reflect impedance into the primary side and make transformer “transparent to user.”
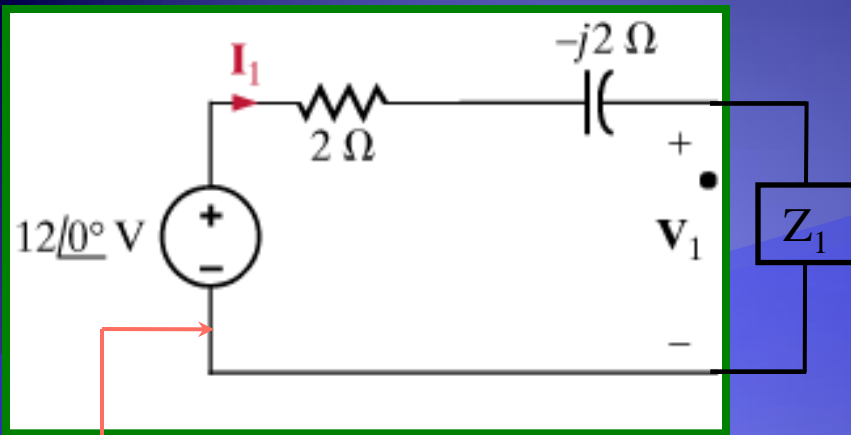
$$Z_1 = \frac{Z_L}{n^2} = \frac{4 - j2}{4} = 1 - j0.5\ \Omega$$




$$Z_i = 3 - j2.5 \Omega$$

$$I_1 = \frac{12 \angle 0^\circ}{3 - j2.5}$$

$$I_1 = \frac{12 \angle 0^\circ}{3.91 \angle -39.81^\circ} = 3.07 \angle 39.81^\circ (\text{A})$$

Using Thevenin's Theorem: Reflecting into the Secondary

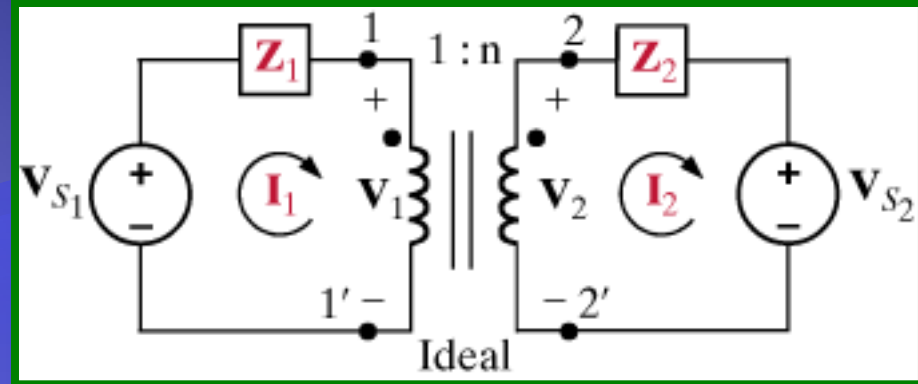
It is possible to use the **Thévenin or Norton Theorems** to replace the transformer and the primary circuit by their equivalent circuit.



Considering the voltage polarities and the current directions in the above circuit, we could write:

$$I_1 = nI_2; \text{ and } V_1 = \frac{V_2}{n}$$

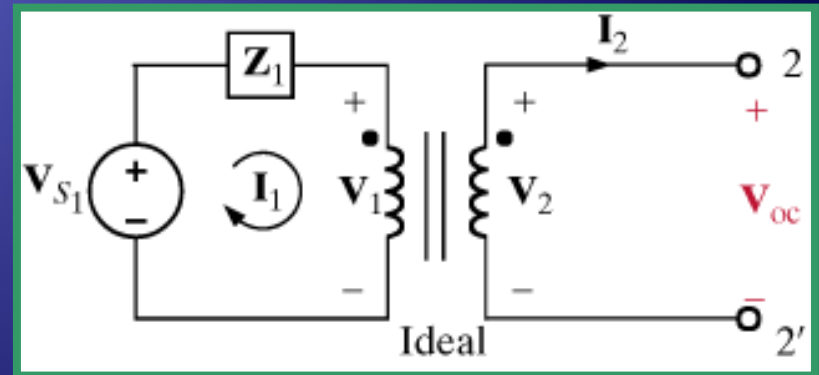
Looking into the circuit to the left of nodes 2-2', we could write:



$$I_2 = 0 \Rightarrow I_1 = 0, \text{ and :}$$


$$V_{OC} = V_2 = nV_1 = nV_{S1}$$

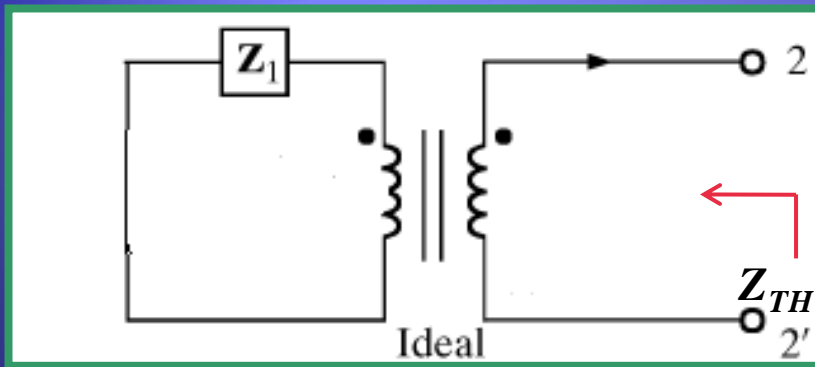On the other hand, the Thévenin equivalent impedance is calculated using the following circuit:




$$\Rightarrow Z_{Th} = n^2 Z_1$$

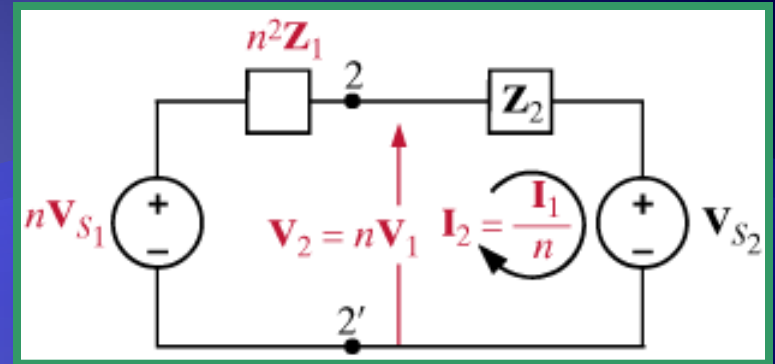The resulting equivalent circuit with the **transformer made “transparent”** and **reflected**, along with the primary **into the secondary** becomes:



Using Thevenin's Theorem: Reflecting into the Primary

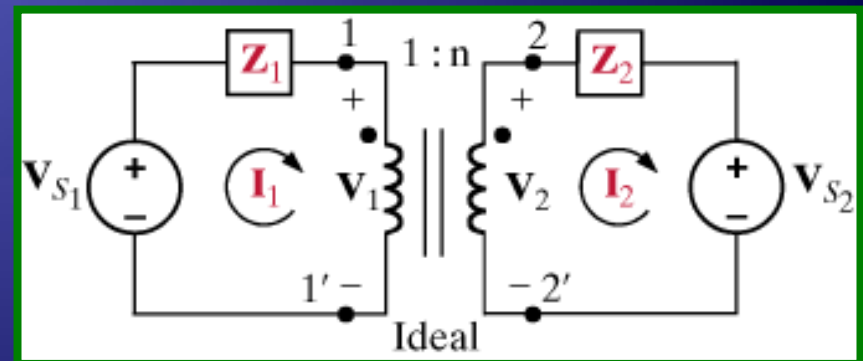In a similar fashion, it is possible to use the **Thévenin Theorem** to replace the transformer and the secondary circuit by their equivalent circuit. In this case, we replace the circuit to the right of nodes 1-1' :



In this case, we could write:


$$\mathbf{I}_1 = 0 \Rightarrow \mathbf{I}_2 = 0, \text{ and :}$$

$$\mathbf{V}_{\text{OC}} = \mathbf{V}_1 = \frac{\mathbf{V}_2}{n} = \frac{\mathbf{V}_{s_2}}{n}$$

On the other hand, the Thévenin equivalent impedance is the secondary impedance reflected into the primary:

$$\Rightarrow Z_{\text{Th}} = Z_1 = \frac{Z_2}{n^2}$$

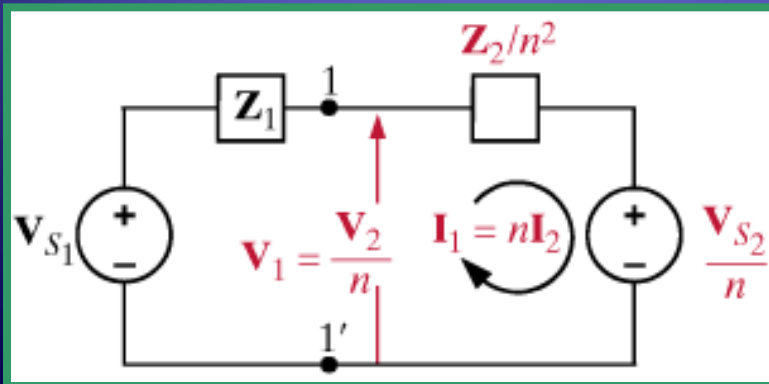The resulting equivalent circuit becomes:



As a general rule, when finding the equivalent circuit for the transformer and its primary circuit, **each primary voltage is multiplied by n , each primary current is divided by n , and each primary impedance is multiplied by n^2** , and conversely.

However, **powers are the same** whether calculated on the primary or the secondary side.

We note that **if the location of one of the dots is different** from that shown in the present circuit, the turns ratio n will need to be replaced by $-n$.

We also note that **if the transformer circuit is different from the typical circuit** shown in the present circuit, Thévenin Theorem is typically applied to reduce the circuit to its present form.

Example 10.9 – Determining the Equivalent Circuits

PROBLEM SOLVING STRATEGY

Step 1: Examine the **voltage polarities and current directions** with respect to the transformer dots:

➤ If both voltages are **positive at the dots**: $v_1/v_2 = N_1/N_2$,
otherwise: $v_1/v_2 = -N_1/N_2$

➤ If **one current enters the dotted terminal and the other leaves the dotted terminal**:

$$i_1/i_2 = N_2/N_1,$$

otherwise:


$$i_1/i_2 = -N_2/N_1$$

Step 2: For a typical circuit, made up of a single primary mesh and a single secondary mesh, **reflect the primary into the secondary** or vice versa, using the reflection equations, solve the resulting circuit using common circuit analysis techniques, then **reflect back to the original circuit** to determine the required variables – Note that impedances are scaled in magnitude only

Step 3: For more complex circuits, with unconnected windings, use Thévenin Theorem to reduce the circuit to a typical circuit.


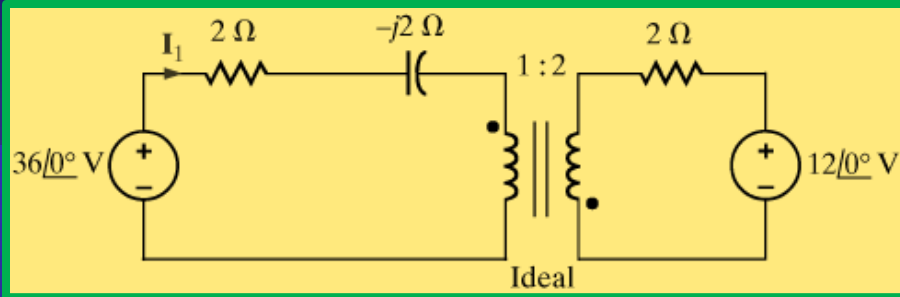
Example 10.10 – Working With an Atypical Circuit

E 10.8 – Calculation of Primary Current in a Typical Circuit



We note that **if the ideal transformer has its windings electrically connected, the equivalent circuit techniques** (primary to secondary and vice-versa) **cannot, in general, be used**. Instead, nodal and mesh analysis is used, along with the transformer voltage and current transformation equations.

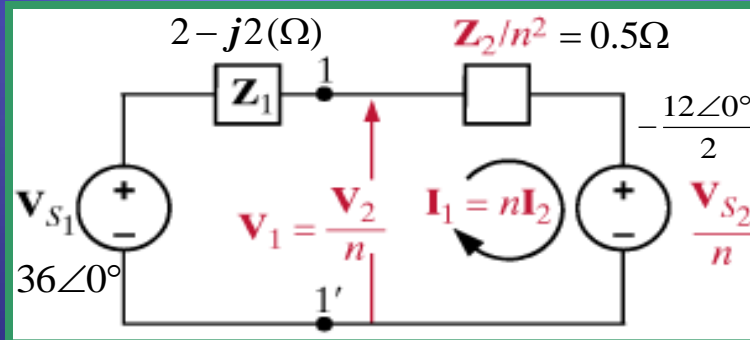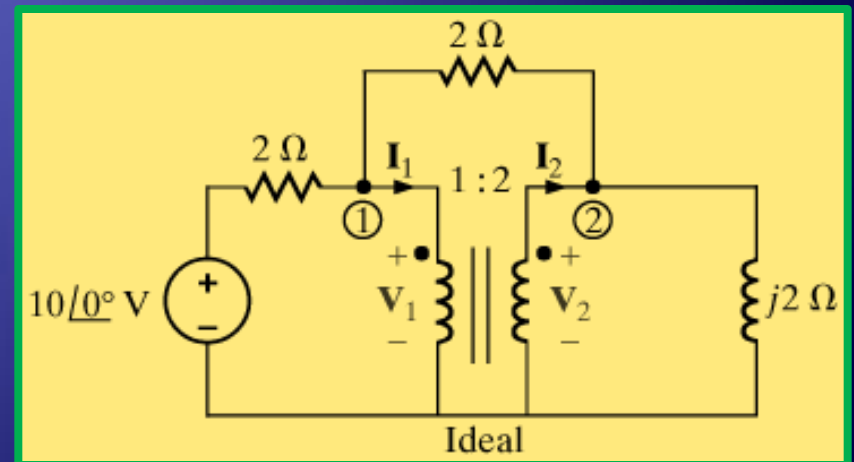Example 10.11 – Ideal Transformer with Connected Windings



$$I_1 = \frac{36\angle 0^\circ + 6\angle 0^\circ}{2.5 - j2}$$

$$I_1 = \frac{42\angle 0^\circ}{3.2\angle -38.66^\circ}$$

Phasor transformation equations for ideal Transformer:

$$V_1 = \frac{V_2}{2}$$

$$I_1 = 2I_2$$

Nodal equations:

$$\text{@ Node 1: } \frac{V_1 - 10\angle 0^\circ}{2} + \frac{V_1 - V_2}{2} + I_1 = 0$$

$$\text{@Node 2: } \frac{V_2 - V_1}{2} + \frac{V_2}{j2} - I_2 = 0$$

Solving:

$$\begin{aligned} 2V_1 - V_2 + 2I_1 &= 10\angle 0^\circ \\ -V_1 + (1-j)V_2 - 2I_2 &= 0 \\ V_2 &= 2V_1 \\ I_1 &= 2I_2 \end{aligned}$$

$$\Rightarrow I_1 = 5\angle 0^\circ$$

$$I_2 = 2.5\angle 0^\circ$$

$$-V_1 + (1-j)(2V_1) = 5\angle 0^\circ$$

$$V_1 = \frac{5\angle 0^\circ}{1-j2} = \frac{5\angle 0^\circ}{2.24\angle -63.43^\circ}$$

$$\Rightarrow V_1 = \sqrt{5}\angle 63.43^\circ \text{ V}$$

$$\text{and } V_2 = 2\sqrt{5}\angle 63.43^\circ \text{ V}$$

**END OF
CHAPTER**