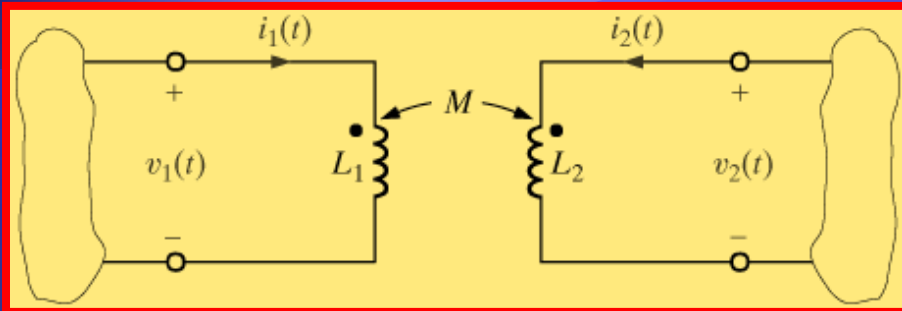


When the **voltages and currents are sinusoidal**, we work in the **phasor domain** where the coupling equations become:



$$V_1 = j\omega L_1 I_1 + j\omega M I_2$$

$$V_2 = j\omega M I_1 + j\omega L_2 I_2$$

Example 10.3 – Equivalent inductance of two mutually coupled coils (Cases 2 and 3)


CASE 2

$$V = V_1 - V_2$$

$$V_1 = j\omega L_1 I - j\omega M I$$


$$V_2 = j\omega M I - j\omega L_2 I$$
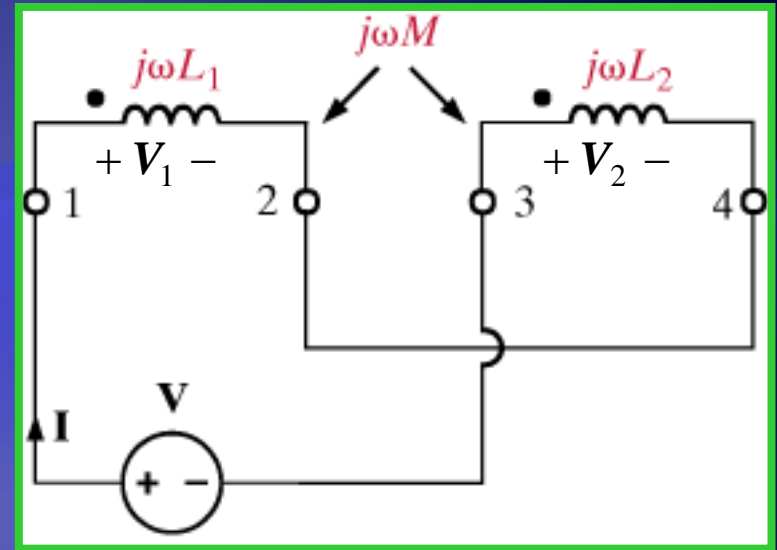
$$V = j\omega \underbrace{(L_1 - 2M + L_2)}_{L_{eq}} I$$



$L_{eq} \geq 0$ imposes a **physical constraint** on the value of M .

CASE 3

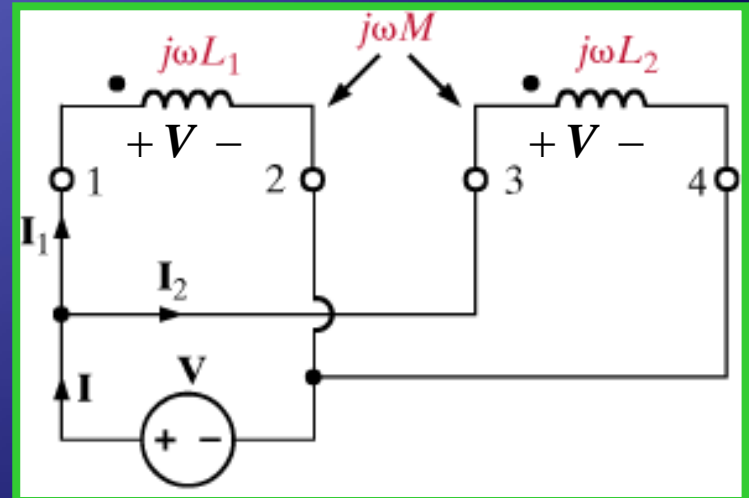

$$I = I_1 + I_2 \Rightarrow I_2 = I - I_1$$

$$V = j\omega L_1 I_1 + j\omega M I_2$$

$$V = j\omega M I_1 + j\omega L_2 I_2$$

$$V = j\omega L_1 I_1 + j\omega M (I - I_1)$$

$$V = j\omega M I_1 + j\omega L_2 (I - I_1)$$

$$V = j\omega(L_1 - M)I_1 + j\omega M I \quad \times / (L_2 - M)$$

$$V = -j\omega(L_2 - M)I_1 + j\omega L_2 I \quad \times / (L_1 - M)$$


$$(L_1 + L_2 - 2M)V = j\omega(M(L_2 - M) + L_2(L_1 - M))I$$

$$V = j\omega \underbrace{\frac{L_1 L_2 - M^2}{L_1 + L_2 - 2M}}_{L_{eq}} I$$

Example 10.4 – Output voltage of a circuit with two coupled coils

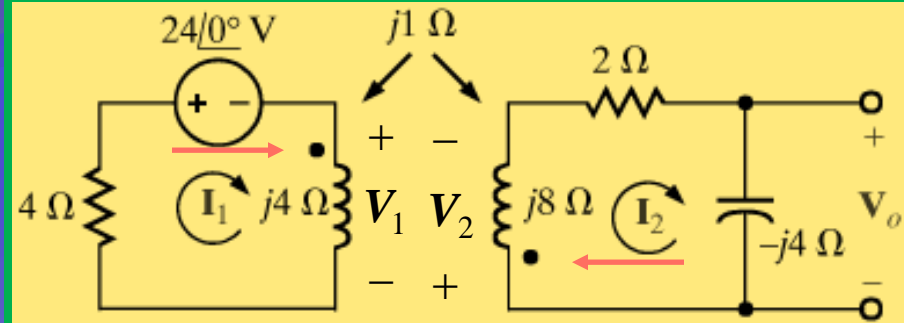Example 10.5 – Mesh equations of a three-mesh circuit with 2 coupled coils

E 10.2 – Currents and output voltage in a circuit with two coupled coils



1. Define variables for coupled inductors

2. Loop equations:

$$V_S + V_1 + 4I_1 = 0$$

$$V_2 + (2 - j4)I_2 = 0$$

3. Coupled inductors equations:

$$V_1 = j4I_1 + jI_2$$

$$V_2 = jI_1 + j8I_2$$

4. Replace and rearrange:

$$(4 + j4)I_1 + jI_2 = -V_S$$

$$jI_1 + (2 + j4)I_2 = 0$$

$$\Rightarrow (1 + 8(1 + j)(1 + 2j))I_2 = jV_S$$

4. Deduce I_2 , I_1 ,
and V_0 :

$$I_2 = \frac{jV_s}{-7 + 24j} \times \frac{-j}{-j} = \frac{24\angle 0^\circ}{24 + 7j} = \frac{24\angle 0^\circ}{25\angle 16.26^\circ}$$

$$I_2 = 0.96\angle -16.26^\circ (\text{A})$$

$$jI_1 + (2 + j4)I_2 = 0 / \times j \Rightarrow I_1 = j(2 + j4)I_2$$


$$I_1 = 1\angle 90^\circ \times 4.47\angle 63.43^\circ \times 0.96\angle -16.26^\circ$$

$$I_1 = 4.29\angle 137.17^\circ (\text{A})$$

$$V_0 = -j4I_2 = 1\angle -90^\circ \times 4 \times 0.96\angle -16.26^\circ$$

$$V_0 = 3.84\angle -106.26^\circ (\text{V})$$

E 10.3 – Two-mesh Circuit

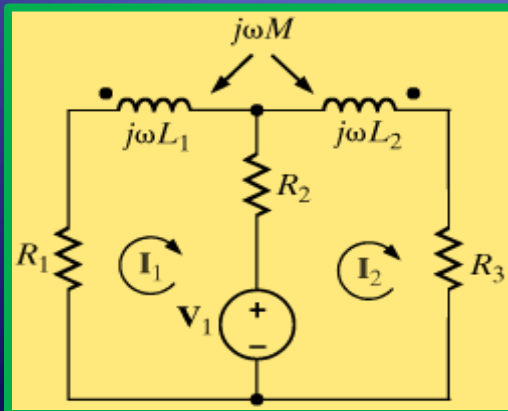

1. Define variables for coupled inductors

2. Loop equations in terms of inductor voltages:

$$V_a + R_2(I_1 - I_2) + V_1 + R_1I_1 = 0$$

$$-V_b + R_3I_2 - V_1 + R_2(I_2 - I_1) = 0$$

3. Equations for coupled inductors:

$$V_a = j\omega L_1 I_1 + j\omega M(-I_2)$$


$$V_b = j\omega M I_1 + j\omega L_2(-I_2)$$

4. Replace into loop equations and rearrange:

$$(R_1 + R_2 + j\omega L_1)I_1 - (R_2 + j\omega M)I_2 = -V_1$$

$$-(R_2 + j\omega M)I_1 + (R_2 + R_3 + j\omega L_2)I_2 = V_1$$

Example 10.6 – Impedance Seen by Source

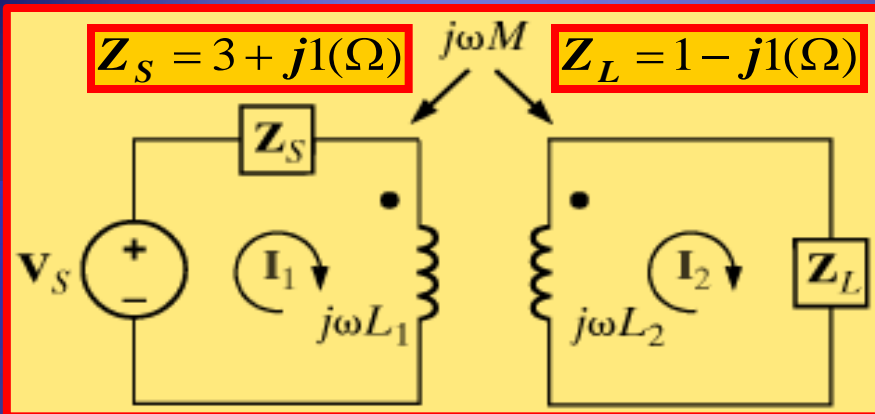

$$j\omega L_1 = j2(\Omega)$$

$$j\omega L_2 = j2(\Omega)$$

$$j\omega M = j1(\Omega)$$

1. Variables for coupled inductors:

2. Loop equations in terms of coupled inductors voltages:

$$\mathbf{Z}_S \mathbf{I}_1 + \mathbf{V}_1 = \mathbf{V}_S$$

$$-\mathbf{V}_2 + \mathbf{Z}_L \mathbf{I}_2 = 0$$

3. Equations for coupled inductors:

$$\mathbf{V}_1 = j\omega L_1 \mathbf{I}_1 + j\omega M (-\mathbf{I}_2)$$

$$\mathbf{V}_2 = j\omega M \mathbf{I}_1 + j\omega L_2 (-\mathbf{I}_2)$$

4. Replace and do the algebra:

$$(\mathbf{Z}_S + j\omega L_1) \mathbf{I}_1 - (j\omega M) \mathbf{I}_2 = \mathbf{V}_S \quad \times / (\mathbf{Z}_L + j\omega L_2)$$

$$-(j\omega M) \mathbf{I}_1 + (\mathbf{Z}_L + j\omega L_2) \mathbf{I}_2 = 0 \quad \times / j\omega M$$

$$\begin{aligned} & ((\mathbf{Z}_S + j\omega L_1)(\mathbf{Z}_L + j\omega L_2) - (j\omega M)^2) \mathbf{I}_1 \\ & = (\mathbf{Z}_L + j\omega L_2) \mathbf{V}_S \end{aligned}$$


$$\mathbf{Z}_i = \frac{\mathbf{V}_S}{\mathbf{I}_1} = (\mathbf{Z}_S + j\omega L_1) - \frac{(j\omega M)^2}{\mathbf{Z}_L + j\omega L_2}$$

$$\mathbf{Z}_i = 3 + j3 - \frac{(j1)^2}{1 + j1} = 3 + j3 + \frac{1}{1 + j} \quad \times \frac{1 - j}{1 - j}$$

$$\mathbf{Z}_i = 3 + j3 + \frac{1 - j}{2} = 3.5 + j2.5(\Omega)$$

$$\mathbf{Z}_i = 4.30 \angle 35.54^\circ (\Omega)$$

E 10.4 – Impedance Seen by Source

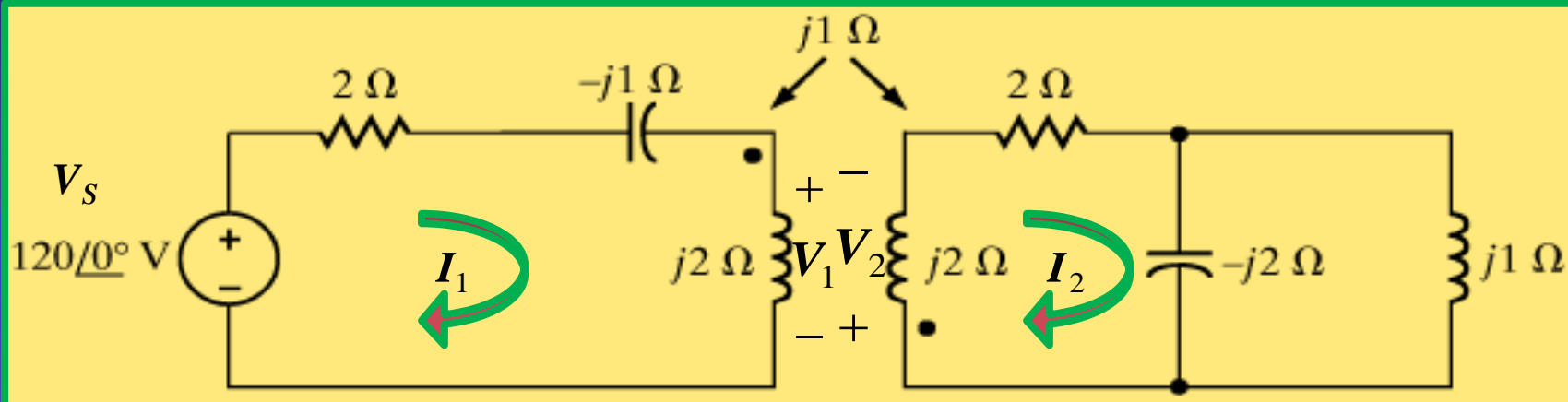

$$\mathbf{Z}_S = 2 - j1(\Omega)$$

$$\mathbf{Z}_L = 2 + (-j2 \parallel j1)$$

$$\mathbf{Z}_L = 2 + \frac{2}{-j} = 2 + 2j(\Omega)$$

1. Variables for coupled inductors

2. Loop equations

$$\mathbf{V}_1 + \mathbf{Z}_S \mathbf{I}_1 = \mathbf{V}_S$$

$$\mathbf{V}_2 + \mathbf{Z}_L \mathbf{I}_2 = 0$$

3. Equations for coupled inductors

$$\mathbf{V}_1 = j\omega L_1 \mathbf{I}_1 + j\omega M \mathbf{I}_2$$

$$\mathbf{V}_2 = j\omega M \mathbf{I}_1 + j\omega L_2 \mathbf{I}_2$$

4. Replace and do the algebra

$$\mathbf{Z}_i = \frac{\mathbf{V}_S}{\mathbf{I}_1} = (\mathbf{Z}_S + j\omega L_1) - \frac{(j\omega M)^2}{\mathbf{Z}_L + j\omega L_2}$$


$$\mathbf{Z}_i = [(2 - j1) + j2] - \frac{(j1)^2}{(2 + 2j) + 2j}$$

$$= (2 + j) + \frac{1}{2(1 + 2j)} \times \frac{(1 - 2j)}{(1 - 2j)}$$

$$\mathbf{Z}_i = 2 + j + \frac{1 - 2j}{2(1 + 2^2)} = 2.1 + 0.8j(\Omega)$$

$$\mathbf{Z}_i = 2.25 \angle 20.85^\circ(\Omega)$$

ENERGY ANALYSIS

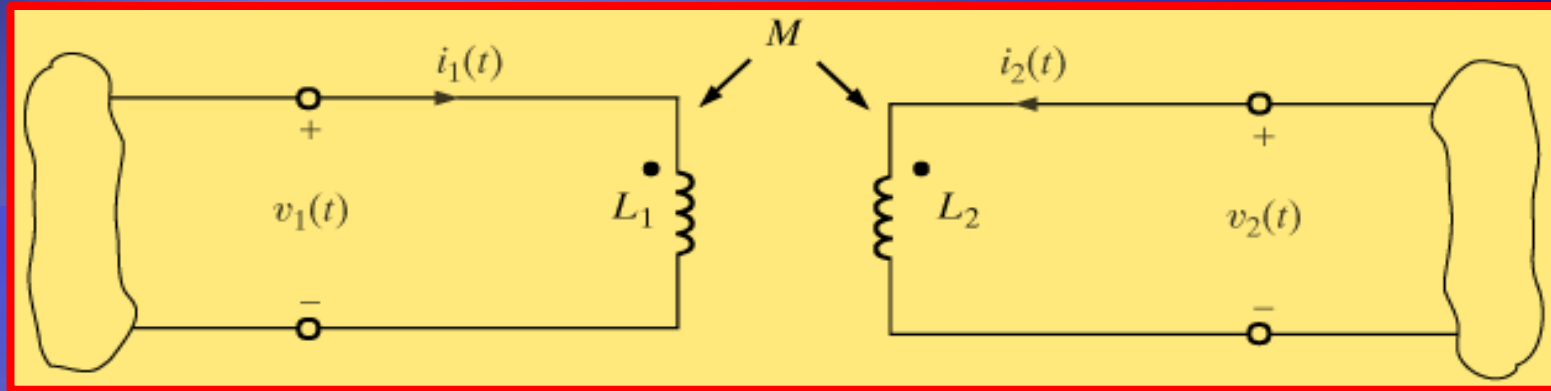

In the following, a small **experiment** will be conducted on the above circuit, where the two coils, L_1 and L_2 , are mutually coupled. The experiment will be conducted in **two phases**:

Phase 1:

In this phase, we leave the **right side terminal open**, i.e. $i_2(t) = 0$, and we increase the current $i_1(t)$ **from 0 to some value I_1** . In this case, whereas the power associated with the right side

will be zero, the **instantaneous power at the left-side terminals** could be calculated as:

$$p(t) = v_1(t)i_1(t) = \left[L_1 \frac{di_1}{dt} \right] i_1(t)$$

When $i_1(t)$ reaches I_1 at a certain time, t_1 , **the energy stored within the coupled circuit** could be found as:

$$\int_0^{t_1} v_1(t)i_1(t)dt = \int_0^{I_1} L_1 i_1(t)di_1(t) = \frac{1}{2} L_1 I_1^2$$

Phase 2:

In this phase, while **holding** $i_1(t)$ **constant at** I_1 , we increase the current $i_2(t)$ **from 0 to a certain value** I_2 . Consequently, we could calculate the **energy associated with the right-side terminals**:

$$\int_{t_1}^{t_2} v_2(t) i_2(t) dt = \int_0^{I_2} L_2 i_2(t) di_2(t) = \frac{1}{2} L_2 I_2^2$$

At the same time, it is possible to calculate **the voltage and the energy at the left-side terminals**:

$$v_1(t) = L_1 \frac{di_1}{dt} + M \frac{di_2}{dt} = M \frac{di_2}{dt}$$

since $i_1(t)$ remains constant at I_1 , and:

$$\begin{aligned} \int_{t_1}^{t_2} v_1(t) i_1(t) dt &= \int_{t_1}^{t_2} M \frac{di_2}{dt} I_1 dt \\ &= M I_1 \int_0^{I_2} di_2 = M I_1 I_2 \end{aligned}$$

The **total energy stored** in the circuit from time zero until time t_2 passing by time t_1 is:

$$w = \frac{1}{2} L_1 I_1^2 + \frac{1}{2} L_2 I_2^2 + M I_1 I_2$$

If the dot on one of the coils is **reversed**, however, we could calculate the total energy to be:

$$w = \frac{1}{2} L_1 I_1^2 + \frac{1}{2} L_2 I_2^2 - M I_1 I_2$$

Also, **for an arbitrary time, t** , the expression of the total energy could be shown to be:

$$w(t) = \frac{1}{2} L_1 [i_1(t)]^2 + \frac{1}{2} L_2 [i_2(t)]^2 \pm M i_1(t) i_2(t)$$

Since the two coils represent a passive network, this energy must be nonnegative:

To the expression of the instantaneous energy, we can **add and subtract** the following term:

$$\frac{1}{2} \frac{M^2}{L_2} i_1^2$$

After rearranging, we find the following expression:

$$w(t) = \frac{1}{2} \left(L_1 - \frac{M^2}{L_2} \right) i_1^2 + \frac{1}{2} L_2 \left(i_2 + \frac{M}{L_2} i_1 \right)^2$$

Since the second term in the above equation is **a square**, we deduce that the condition for $w(t)$ to be nonnegative is:

$$M \leq \sqrt{L_1 L_2}$$

which specifies an **upper limit on the value of M** .

If we define the **coefficient of coupling** as:

$$k = \frac{M}{\sqrt{L_1 L_2}}$$


The **condition on the coefficient of coupling** could be stated as:

$$0 \leq k \leq 1$$

Hence, this coefficient indicates **how much flux in one coil affects the other coil**, and vice versa. For **$k = 0$** , there is **no coupling** between the two coils, and for **$k = 1$** , the two coils are said to be **fully coupled**. In this respect, **if $k > 0.5$** the two coils are said to be **tightly coupled**, whereas **if $k < 0.5$** the two coils are said to be **loosely coupled**.

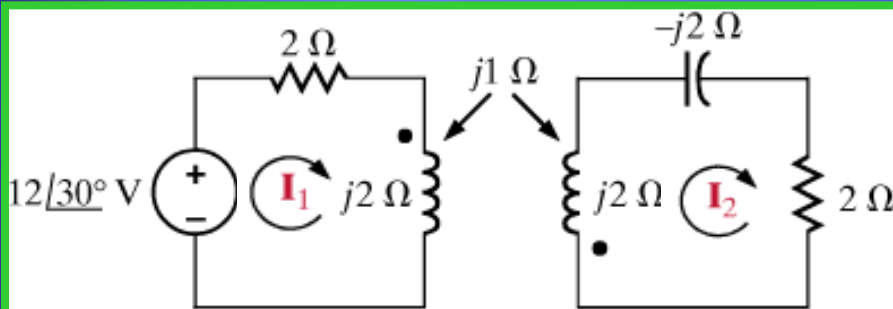Example 10.7 – Calculation of Stored Energy

E 10.5 – Calculation of Stored Energy in Mutually Coupled Coils



$$f = 60 \text{ Hz} \Rightarrow \omega = 377 (\text{s}^{-1})$$

$$\omega L_1 = 2 \Rightarrow L_1 = 0.00528 (\text{H}) = L_2$$

$$M = 0.00264 (\text{H})$$

$$2I_1 + (j2I_1 + j1I_2) = 12\angle 30^\circ$$

$$(j1I_1 + j2I_2) + (2 - j2)I_2 = 0$$

$$(2 + j2)I_1 + jI_2 = 12\angle 30^\circ$$

$$jI_1 + 2I_2 = 0$$

$$\Rightarrow I_2 = -0.5jI_1$$

$$(2 + j2 + 0.5)I_1 = 12\angle 30^\circ$$

$$I_1 = \frac{12\angle 30^\circ}{2.5 + j2} = \frac{12\angle 30^\circ}{3.20\angle 38.66^\circ}$$

$$= 3.75\angle -8.66^\circ (\text{A})$$

$$I_2 = -0.5jI_1 = 0.5\angle -90^\circ \times 3.75\angle -8.66^\circ$$

$$= 1.875\angle -98.66^\circ$$

Go back to time domain:

$$i_1(t) = 3.75 \cos(377t - 8.66^\circ) (\text{A})$$

$$i_2(t) = 1.875 \cos(377t - 98.66^\circ) (\text{A})$$

$$377 (\text{rad/sec}) \times 0.010 (\text{sec}) = 3.77 (\text{rad}) = 216^\circ$$

$$i_1(0.010) = -3.3 (\text{A}) \text{ and } i_2(0.010) = -0.86 (\text{A})$$

$$w(t) = \frac{1}{2} L_1 i_1^2(t) + M i_1(t) i_2(t) + \frac{1}{2} L_2 i_2^2(t)$$

$$w(0.010) = 0.5 * 0.00528 * (-3.3)^2$$

$$+ 0.00264 * (-3.3)(-0.86)$$

$$+ 0.5 * 0.00528 * (0.86)^2 (\text{J})$$

$$w(0.010) = 0.00264 * (3.3^2 + (3.3)(0.86) + 0.86^2)$$

$$w(0.010) = 0.038 \text{ J} = 38 \text{ mJ}$$