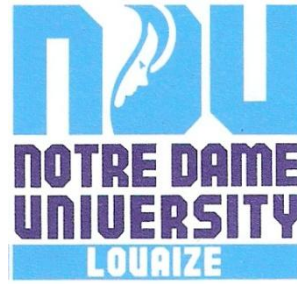



NOTRE DAME UNIVERSITY



FACULTY OF ENGINEERING

**Department of Electrical, Computer
& Communication Engineering**

EEN 202

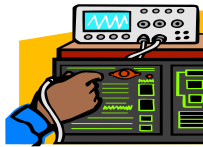

Circuits Analysis II

Solution* for HW 3

* Problem Solutions Extracted from the Solution Manual of:
“Basic Engineering Circuit Analysis”, by J.D. Irwin and R. M. Nelms, 9th Edition, Wiley, 2008

Instructor: G. Hassoun

9.3 The voltage and current at the input of a circuit are given by the expressions

$$v(t) = 170 \cos(\omega t + 30^\circ) \text{ V}$$

$$i(t) = 5 \cos(\omega t + 45^\circ) \text{ A}$$

Determine the average power absorbed by the circuit.

SOLUTION:

$$V(t) = 170 \cos(\omega t + 30^\circ) \text{ V}$$

$$i(t) = 5 \cos(\omega t + 45^\circ) \text{ A}$$

$$P = \frac{V_m I_m}{2} \cos(\theta_v - \theta_i)$$

$$P = \frac{170(5)}{2} \cos(30^\circ - 45^\circ)$$

$$P = 410.52 \text{ W}$$

9.7 Calculate the power absorbed by each element in the circuit in Fig. P9.7.

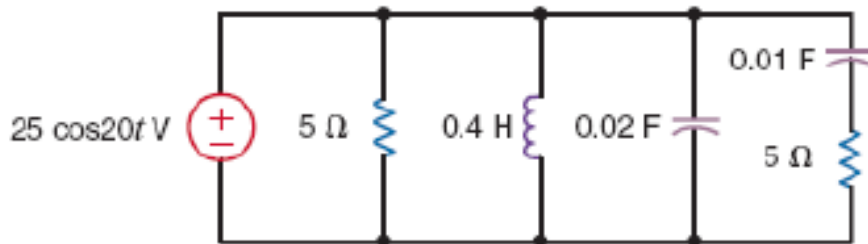



Figure P9.7

SOLUTION:

$$\bar{Z}_L = j\omega L = j(20)(0.4) = j8\Omega$$

$$\bar{Z}_{C_1} = \frac{1}{j\omega C_1} = \frac{1}{j(20)(0.02)} = -j2.5\Omega$$
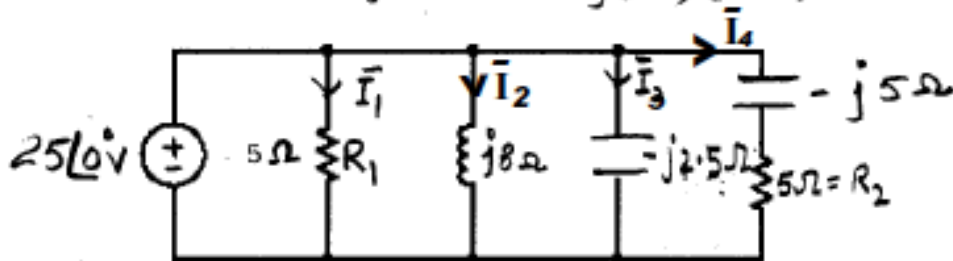
$$\bar{Z}_{C_2} = \frac{1}{j\omega C_2} = \frac{1}{j(20)(0.01)} = -j5\Omega$$



$$\bar{I}_1 = \frac{25\angle 0^\circ}{5} = 5\angle 0^\circ \text{ A}$$

$$\bar{I}_2 = \frac{25\angle 0^\circ}{j8} = 3.125\angle -90^\circ \text{ A}$$

$$\bar{I}_3 = \frac{25\angle 0^\circ}{-j2.5} = 10\angle 90^\circ \text{ A}$$

$$\bar{I}_4 = \frac{25 \angle 0^\circ}{5 - j5} = 3.54 \angle 45^\circ \text{ A}$$

$$P_{R_1} = \frac{I_4^2 R}{2} = \frac{5^2 (5)}{2}$$

$$P_{R_1} = 62.5 \text{ W}$$

$$P_{R_2} = \frac{I_4^2 R}{2} = \frac{(3.54)^2 (5)}{2}$$

$$P_{R_2} = 31.33 \text{ W}$$

9.14 Given the network in Fig. P9.14, find (a) the power supplied and the average power absorbed by each element ((b) 1- Ω resistor, (c) 2- Ω resistor, (d) inductor, (e) capacitor).

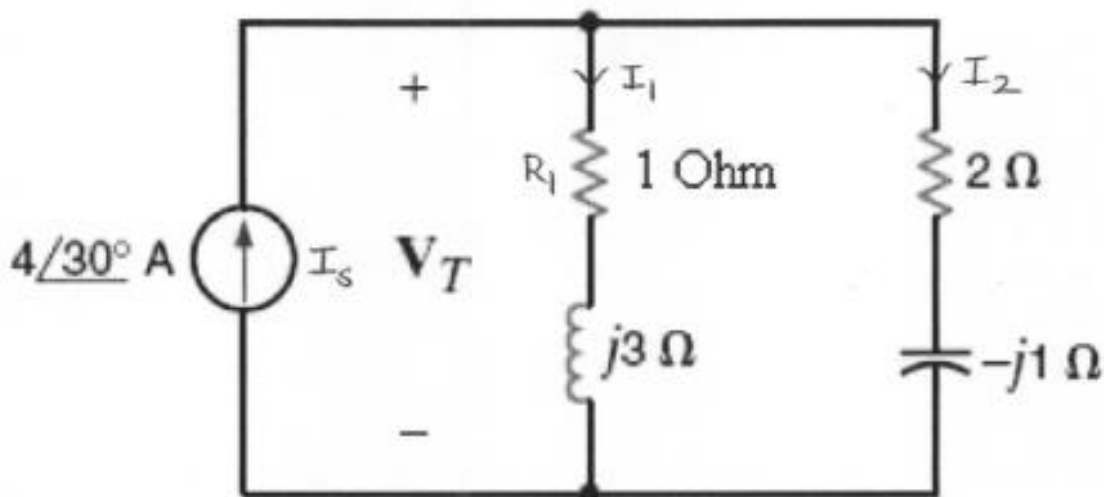


Figure P9.14

Find the power supplied at $t = 0$.

Solution: 9.14

(a) Let, $z_1 = 1 + j3 \Omega$ and $z_2 = 2 - j1 \Omega$

$$\text{and } z_T = \frac{z_1 z_2}{z_1 + z_2} = 1.961 \angle 11.31^\circ \Omega$$

$$V_T = 4 \angle 30^\circ z_T = 7.844 \angle 41.31^\circ \text{ V}$$

For the source

$$P_s(t) = \frac{4(7.844)}{2} [\cos(2\omega t + 71.31^\circ) + \cos 11.31^\circ]$$

$$= 15.688 [\cos(2\omega t + 71.31^\circ) + 0.981]$$

$$P_s(0) = 15.39 \text{ W}$$

$$P_S(0) = 15.4 \text{ W}$$

$$(b) I_1 = V_T / z_1 = 2.481 \angle -30.26^\circ \text{ A}$$

$$P_{R_1} = \frac{I_{1M}^2}{2} R_1 = 3.078 \text{ W}$$

$$P_{R_1} = 3.08 \text{ W}$$

$$(c) I_2 = V_T / z_2 = 3.508 \angle 67.875^\circ \text{ A}$$

$$P_{R_2} = \frac{I_{2M}^2}{2} R_2 = 12.306 \text{ W}$$

$$P_{R_2} = 12.3 \text{ W}$$

$$(d) P_L = 0 \text{ W}$$

$$(e) P_C = 0 \text{ W}$$

9.16 Given the network in Fig. P9.16, show that the power supplied by the sources is equal to the power absorbed by the passive elements.

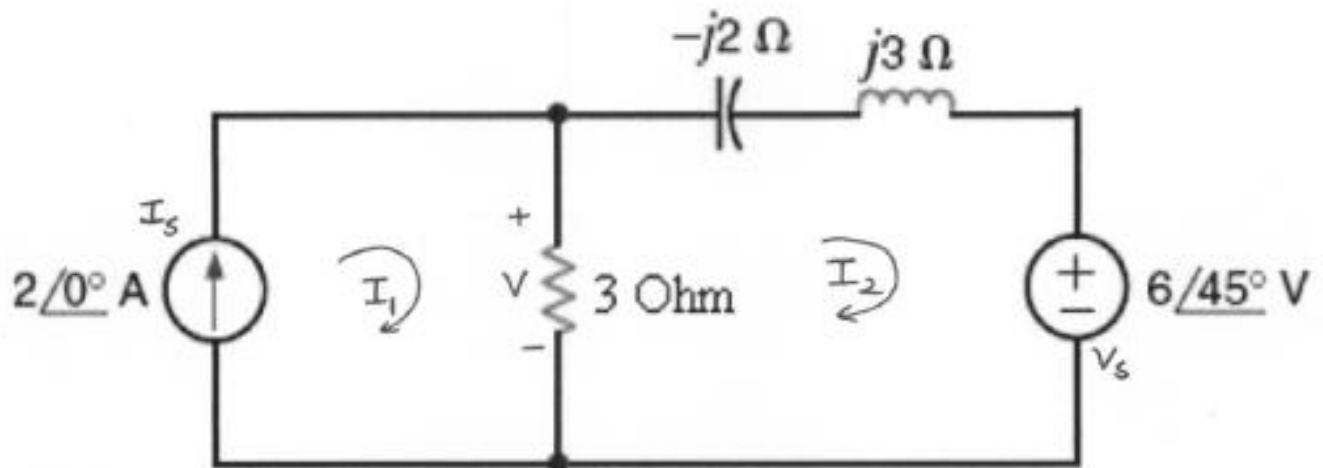


Figure P9.16

Find (a) power absorbed and (b) power supplied.

Solution: 9.16

$$I_1 = 2 \angle 0^\circ \text{ A} \quad \text{---} \quad \textcircled{1}$$

$$-3I_1 + I_2(3 + j1) = -6 \angle 45^\circ \quad \text{---} \quad \textcircled{2}$$

From equations ① and ②, we get

$$\begin{bmatrix} 1 & 0 \\ -3 & 3 + j1 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} 2 \angle 0^\circ \\ -6 \angle 45^\circ \end{bmatrix}$$

$$\Rightarrow I_2 = 1.453 \angle -85.941^\circ \text{ A}$$

$$V = 3(I_1 - I_2) = 7.161 \angle 37.374^\circ \text{ V}$$

$$I_s \text{ supplies } P_{I_s} = \frac{I_{sM} V_M}{2} \cos(\theta_V - \theta_{I_s})$$

$$\Rightarrow P_{I_s} = 5.691 \text{ W}$$

$$V_s \text{ absorbs } P_{V_s} = \frac{V_{sM} I_{2M}}{2} \cos(\theta_{V_s} - \theta_{I_2})$$

$$= -2.856 \text{ W}$$

So, V_s actually delivers 2.856 W

$$P_R = \frac{V_M^2}{2R} = 8.547 \text{ W}$$

$$P_L = P_C = 0 \text{ W}$$

$$\text{Power supplied} = 5.691 + 2.856 = 8.547 \text{ W}$$

$$\text{Power absorbed} = P_R = 8.547 \text{ W}$$

\therefore Power supplied = Power absorbed

(a) $\boxed{\text{Power supplied} = 8.55 \text{ W}}$

(b) $\boxed{\text{Power absorbed} = 8.55 \text{ W}}$

9.22 Determine the average power absorbed by a $2\text{-}\Omega$ resistor connected at the output terminals of the network shown in Fig. P9.22.


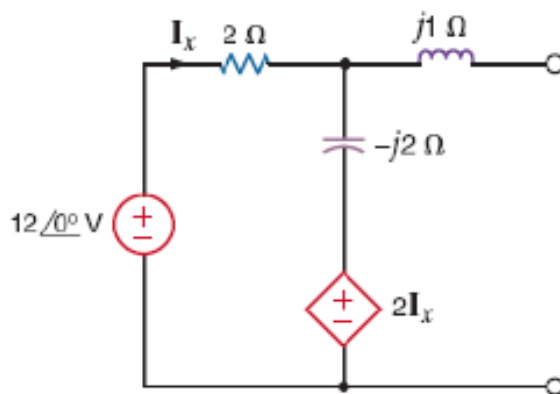


Figure P9.22

SOLUTION:

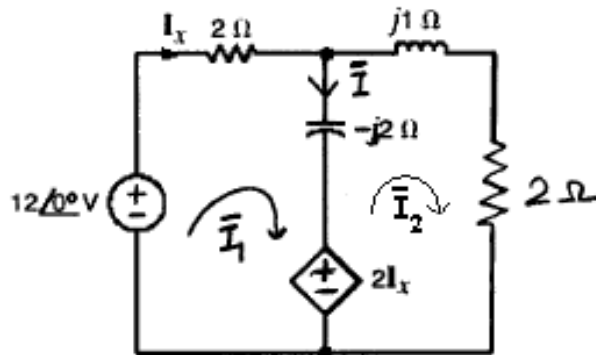

$$\text{KCL: } \bar{I}_1 = \bar{I} + \bar{I}_2 \quad \bar{I} = \bar{I}_1 - \bar{I}_2$$

KVL around left loop:

$$2\bar{I}_1 - j2\bar{I} + 2\bar{I}_x = 12\angle 0^\circ$$

$$\bar{I}_x = \bar{I}_1$$

$$2\bar{I}_1 - j2(\bar{I}_1 - \bar{I}_2) + 2\bar{I}_1 = 12\angle 0^\circ$$

$$(4 - j2)\bar{I}_1 + j2\bar{I}_2 = 12\angle 0^\circ$$

KVL around right loop:

$$j1\bar{I}_2 + 2\bar{I}_2 - j2(-\bar{I}_1) = 2\bar{I}_x$$

$$j1\bar{I}_2 + 2\bar{I}_2 + j2(\bar{I}_1 - \bar{I}_2) = 2\bar{I}_1$$

$$(-2 + j2)\bar{I}_1 + (2 - j1)\bar{I}_2 = 0$$

$$(4 - j2)\bar{I}_1 + j2\bar{I}_2 = 12\angle 0^\circ$$

$$(-2 + j2)\bar{I}_1 + (2 - j1)\bar{I}_2 = 0$$

$$\bar{I}_1 = 2.49\angle -4.76^\circ \text{ A}$$

$$\bar{I}_2 = 3.15\angle -23.2^\circ \text{ A}$$

$$P_{2\Omega} = \frac{I_2^2 R}{2} = \frac{(3.15)^2 (2)}{2} = 9.92 \text{ W}$$

9.30 Determine the impedance Z_L ((a) determine the real part, (b) determine the imaginary part) for maximum average power transfer and (c) the value of the maximum average power absorbed by the load in the network shown in Fig. P9.30.


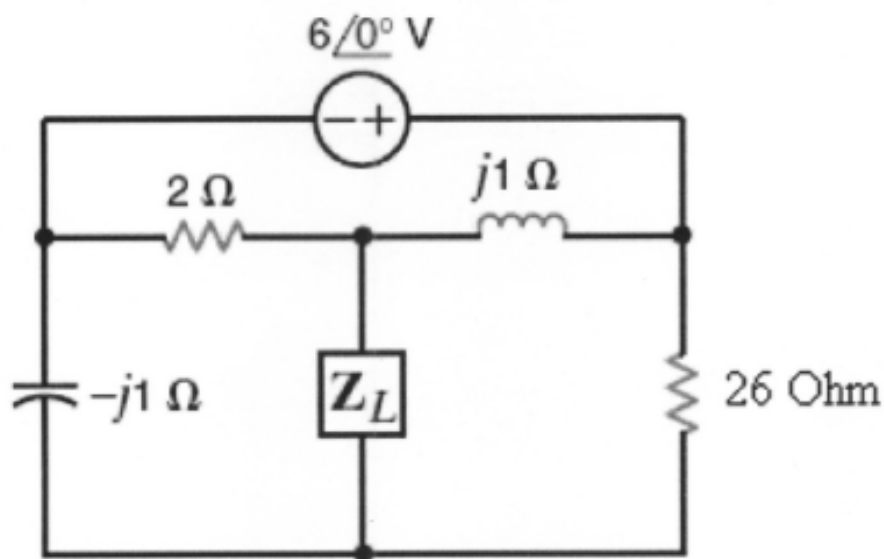



Figure P9.30

Solution: 9.30

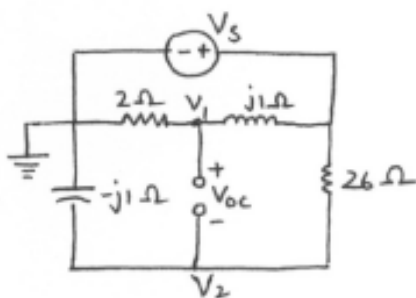

$$V_1 = V_s \left[\frac{2}{2+j1} \right] \quad V_2 = V_s \left[\frac{-j1}{26-j1} \right]$$
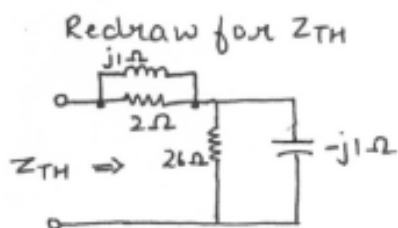
$$V_{oc} = V_1 - V_2 = 5.26 \angle -24.37^\circ \text{ V}$$




$$\begin{aligned} Z_{TH} &= \frac{2(j1)}{2+j1} + \frac{26(-j1)}{26-j1} \\ &= 0.438 - j0.198 \, \Omega \\ &= 0.48 \angle -24.85^\circ \, \Omega \end{aligned}$$

For maximum power transfer

$$Z_L = Z_{TH}^* = 0.438 + j0.198 \, \Omega$$

$$I = \frac{V_{oc}}{Z_{TH} + Z_L} = 5.98 \angle -24.37^\circ \text{ A}$$
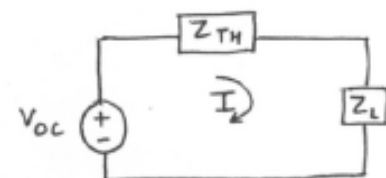
$$P_L = \frac{I_m^2}{2} R_L = 7.87 \text{ W}$$



(a) $R_L = 0.438 \, \Omega$

(b) $X_L = 0.198 \, \Omega$

(c) $P_L = 7.87 \text{ W}$

9.33 In the network in Fig. P9.33, find Z_L for maximum average power transfer and the maximum average power transferred.


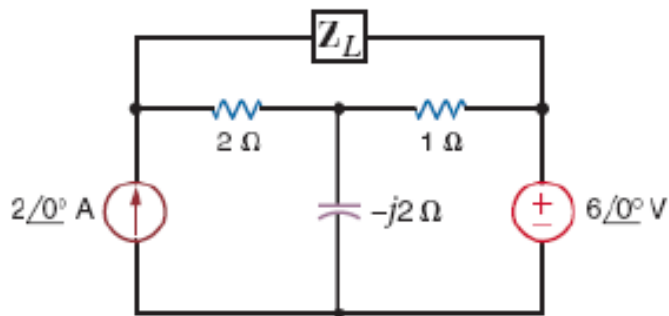


Figure P9.33

SOLUTION:

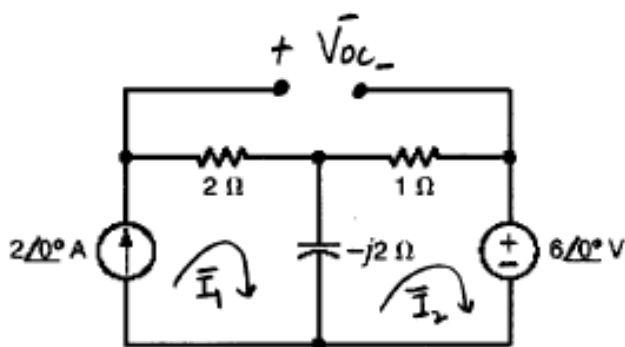

$$\text{KCL: } \bar{I}_1 = \bar{I} + \bar{I}_2$$

$$\bar{I} = \bar{I}_1 - \bar{I}_2$$

$$\text{KVL right loop: } 1(\bar{I}_2) + 6\angle 0^\circ - j2(-\bar{I}) = 0$$

$$\bar{I}_2 + 6\angle 0^\circ + j2(\bar{I}_1 - \bar{I}_2) = 0$$

$$j2\bar{I}_1 + (1 - j2)\bar{I}_2 = -6\angle 0^\circ$$

$$\bar{I}_1 = 2\angle 0^\circ \text{ A}$$


$$(1 - j2)\bar{I}_2 = -6\angle 0^\circ - j2(2\angle 0^\circ)$$

$$\bar{I}_2 = 3.22\angle -82.87^\circ \text{ A}$$

$$V_{OC} = \bar{I}_1(2) + \bar{I}_2(1)$$

$$\bar{V}_{oc} = (2 \angle 0^\circ)(2) + (3.22 \angle -82.87^\circ)(1)$$
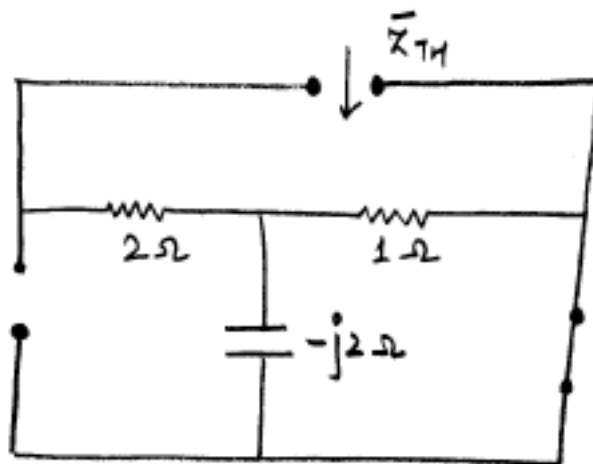
$$\bar{V}_{oc} = 5.44 \angle -36^\circ \text{ V}$$




$$\bar{Z}_{TH} = 1 \parallel -j2 + 2$$

$$\bar{Z}_{TH} = \frac{1(-j2)}{1-j2} + 2 = 2.83 \angle -8.13^\circ \Omega$$

$$\bar{Z}_{TH} = 2.8 - j0.4 \Omega$$
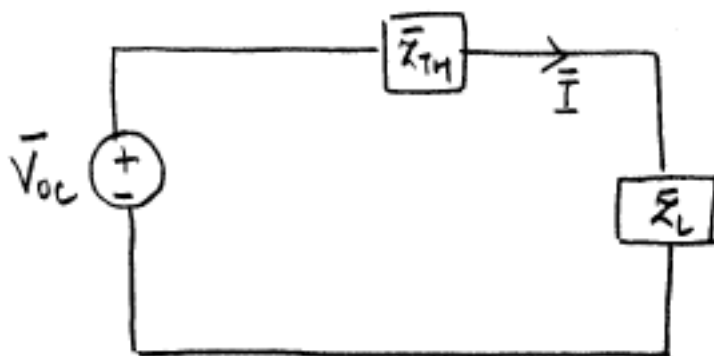
$$\bar{Z}_L = \bar{Z}_{TH}^* = 2.8 + j0.4 \Omega$$



$$\bar{I} = \frac{5.44 \angle -36^\circ}{2.8 - j0.4 + 2.8 + j0.4}$$

$$\bar{I} = 0.97 \angle -36^\circ \text{ A}$$

$$P_{\max} = \frac{I^2 R_L}{2} = \frac{(0.97)^2 (2.8)}{2}$$

$$P_{\max} = 1.32 \text{ W}$$