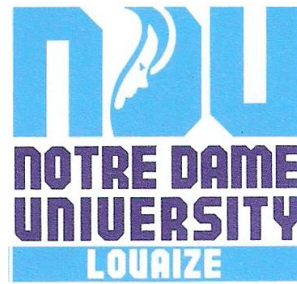


**NOTRE DAME UNIVERSITY**



**FACULTY OF ENGINEERING**

**Department of Electrical, Computer  
& Communication Engineering**

**EEN 202**



**Circuits Analysis II**

**Solutions\* for HW2**

**Chapter 8**

**AC Steady-State Analysis**

\* Problem Solutions Extracted from the Solution Manual of:  
“Basic Engineering Circuit Analysis”, by J.D. Irwin and R. M. Nelms, 9<sup>th</sup> Edition, Wiley, 2008

**Instructor: G. Hassoun**

8.58 In the network in Fig. P8.58  $v_o$  is known to be  $4\angle 45^\circ$ . Find  $Z$ .


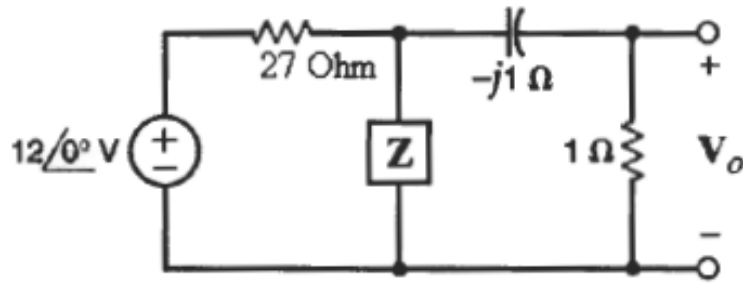


Figure P8.58

- (a) Find the real part of  $Z$ .  
 (b) Find the imaginary part of  $Z$ .

Solution: 8-58

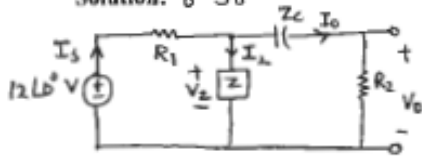

$$\begin{aligned} R_1 &= 27\ \Omega \\ R_2 &= 1\ \Omega \\ Z_c &= -j1\ \Omega \end{aligned}$$

$$I_o = \frac{v_o}{R_2} = 4\angle 45^\circ\ \text{A}$$

$$V_z = I_o (R_2 + Z_c) = 5.656\angle 0^\circ\ \text{V}$$

$$\text{KVL: } -12\angle 0^\circ + I_s R_1 + V_z = 0$$

$$I_s = \frac{12\angle 0^\circ - V_z}{R_1} = 0.2349\ \text{A}$$

$$I_z = I_s - I_o = -2.5935 - j2.8284\ \text{A}$$

$$Z = \frac{V_z}{I_z} = -0.996 + j1.086\ \Omega$$

$$\boxed{\text{Re}(Z) = -0.996\ \Omega}$$

$$\boxed{\text{Im}(Z) = 1.09\ \Omega}$$

8.63 Using nodal analysis, find  $I_o$  in the circuit in Fig. P8.63.


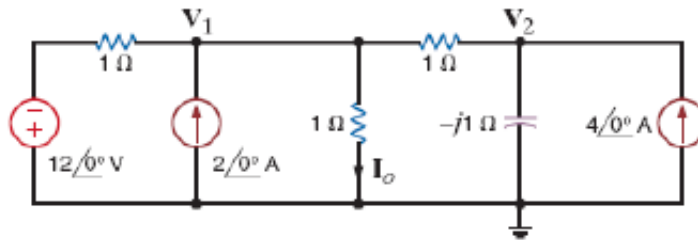


Figure P8.63

**SOLUTION:**

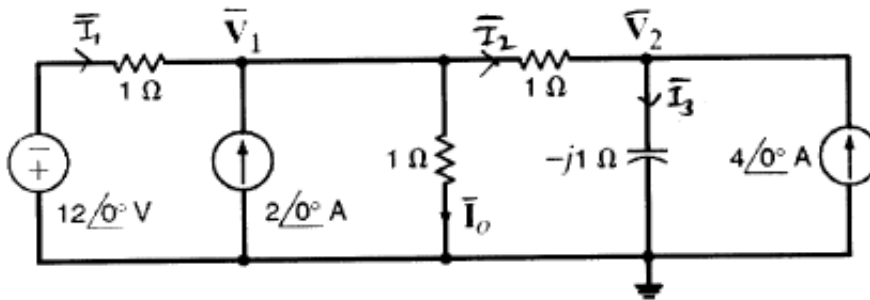

$$\text{KCL at } \textcircled{1} : \bar{I}_1 + 2\angle 0^\circ = \bar{I}_o + \bar{I}_2$$

$$\frac{-12\angle 0^\circ - \bar{V}_1}{1} + 2\angle 0^\circ = \frac{\bar{V}_1}{1} + \frac{\bar{V}_1 - \bar{V}_2}{1}$$

$$-12\angle 0^\circ - \bar{V}_1 + 2\angle 0^\circ = \bar{V}_1 + \bar{V}_1 - \bar{V}_2$$

$$3\bar{V}_1 - \bar{V}_2 = 10\angle 180^\circ$$

$$\text{KCL at } \textcircled{2} : \bar{I}_2 + 4\angle 0^\circ = \bar{I}_3$$

$$\frac{\bar{V}_1 - \bar{V}_2}{1} + 4\angle 0^\circ = \frac{\bar{V}_2}{-j1}$$

$$-j1(\bar{V}_1 - \bar{V}_2) - j1(4\angle 0^\circ) = \bar{V}_2$$

$$-j1\bar{V}_1 + (-1+j1)\bar{V}_2 = 4\angle 90^\circ$$

$$3\bar{V}_1 - \bar{V}_2 = 10\angle 180^\circ$$

$$-j1\bar{V}_1 + (-1+j1)\bar{V}_2 = 4\angle 90^\circ$$

$$\bar{V}_1 = 3.23\angle -177.3^\circ \text{ V}$$

$$\bar{V}_2 = 0.55\angle -56.3^\circ \text{ V}$$

$$\bar{I}_0 = \frac{\bar{V}_1}{1}$$

$$\bar{I}_0 = \frac{3.23\angle -177.3^\circ}{1}$$

$$\bar{I}_0 = 3.23\angle -177.3^\circ \text{ A}$$

8.73 Find the voltage across the inductor in the circuit shown in Fig. P8.73 using nodal analysis.


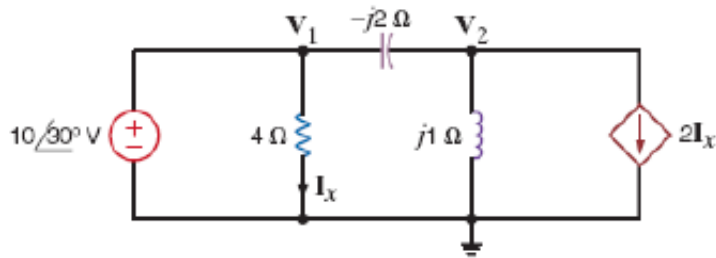


Figure P8.73

**SOLUTION:**

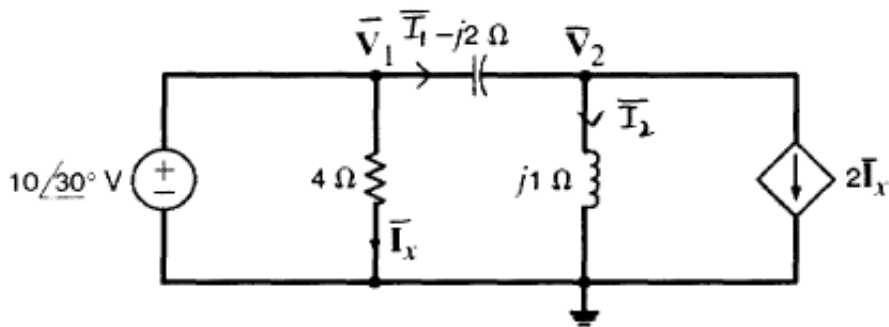

$$\bar{I}_x = \frac{10\angle 30^\circ}{4} = 2.5\angle 30^\circ \text{ A}$$

$$\text{KCL at } \textcircled{2} : \bar{I}_1 = \bar{I}_2 + 2\bar{I}_x$$

$$\frac{10\angle 30^\circ - \bar{V}_2}{-j2} = \frac{\bar{V}_2}{j1} + 2(2.5\angle 30^\circ)$$

$$10\angle 30^\circ - \bar{V}_2 = -2\bar{V}_2 + 2(2.5\angle 30^\circ)(-j2)$$

$$\bar{V}_2 = 14.14\angle -105^\circ \text{ V}$$

8.75 Use mesh analysis to find  $v_o$  in the circuit shown in Fig. P8.75.

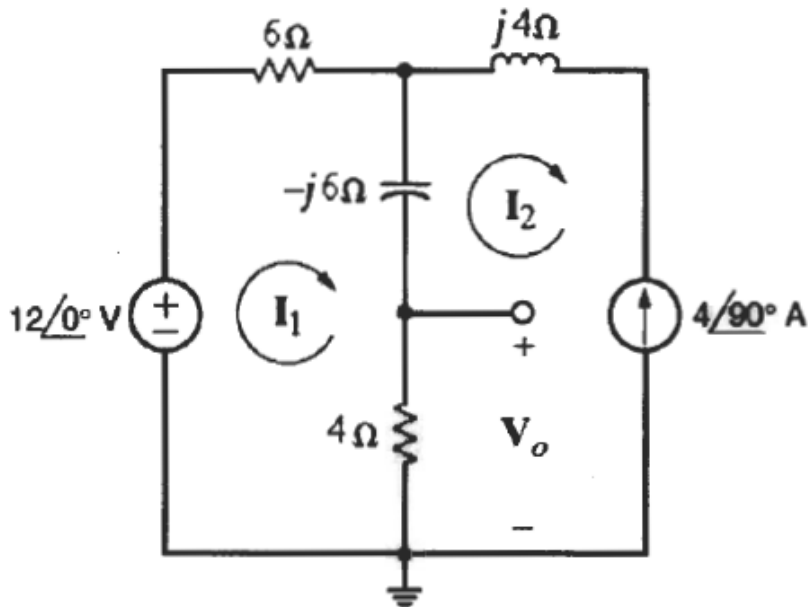


Figure P8.75

Enter (a) the amplitude and (b) the angle of phase. The angle of phase must be in the interval  $(-180^\circ, 180^\circ)$ .

Solution: 8.75

$$\text{KVL @ } I_1: -12\angle 0^\circ + I_1(6 - j6 + 4) - I_2(4 - j6) = 0$$

$$I_1(10 - j6) + I_2(-4 + j6) = 12$$

$$I_2 = -4\angle 90^\circ = -j4 \text{ A}$$

$$\begin{bmatrix} 10 - j6 & -4 + j6 \\ 0 & 1 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} 12 \\ -j4 \end{bmatrix}$$

$$I_1 = -0.176 - j1.7059 \text{ A}$$


$$I_2 = -j4 \text{ A}$$

$$\begin{aligned} V_o &= (I_1 - I_2)4 = 4(-0.1765 - j2.2941) \\ &= -0.706 - j9.1764 \text{ V} \end{aligned}$$

(a) Amplitude of  $V_o = 9.20 \text{ V}$

(b) Angle of phase of  $V_o = 85.6^\circ$

Solution: 8.84

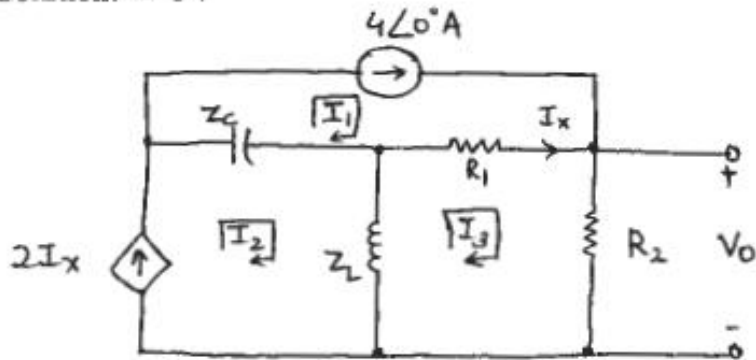

$$R_1 = 1\Omega, R_2 = 7\Omega, Z_c = -j1\Omega, Z_L = j1\Omega$$

$$I_1 = 4\angle 0^\circ \text{ A} \quad \text{--- (1)}$$

$$I_x = I_3 - I_1$$

$$I_2 = 2I_x$$

$$\Rightarrow I_2 = 2I_3 - 2I_1 \Rightarrow 2I_1 + I_2 - 2I_3 = 0 \quad \text{--- (2)}$$

8.84 Find  $v_o$  in the network in Fig. P8.84.

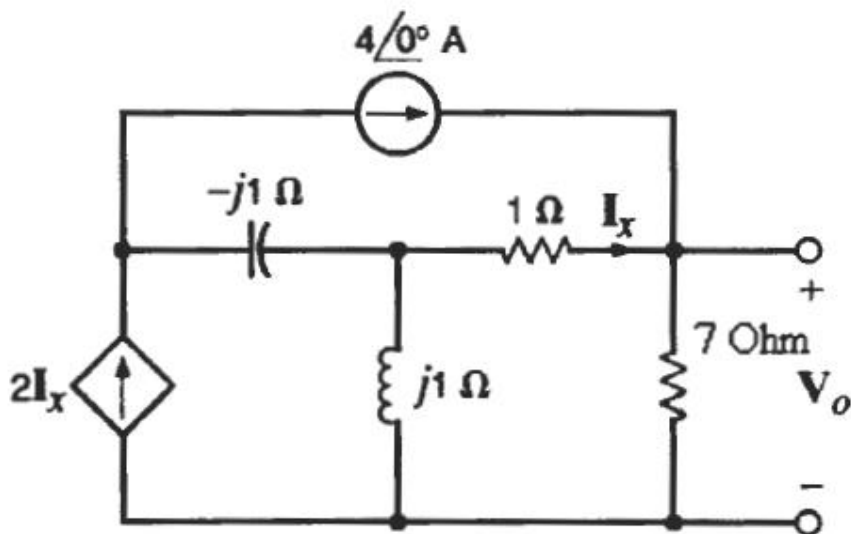


Figure P8.84

- (a) Find the real part of  $v_o$ .
- (b) Find the imaginary part of  $v_o$ .

$$\text{KVL @ } I_3 : (I_3 - I_2)(j1) + (I_3 - I_1)1 + 7I_3 = 0$$

$$-I_1 - jI_2 + I_3(8+j) = 0 \quad \text{--- (3)}$$

From equations (1), (2) and (3), we get

$$\begin{bmatrix} 1 & 0 & 0 \\ 2 & 1 & -2 \\ -1 & -j & 8+j \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 4 \\ 0 \\ 0 \end{bmatrix}$$

$$V_0 = 7I_3 = 4.31 - j6.46 \text{ V}$$

(a)  $\text{Re}(V_0) = 4.31 \text{ V}$

(b)  $\text{Im}(V_0) = -6.46 \text{ V}$

8.88 Using superposition, find  $v_o$  in the circuit in Fig. P8.88.


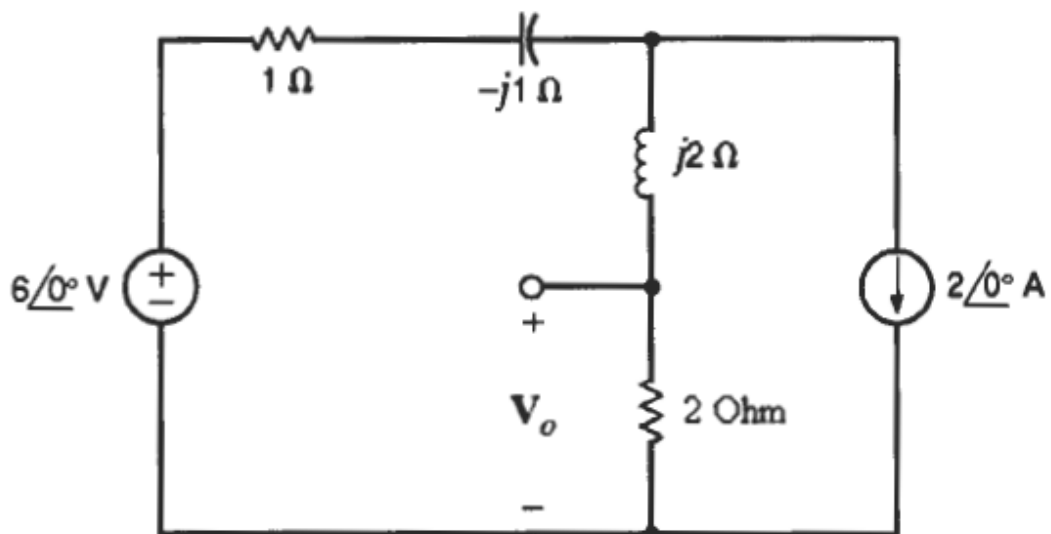


Figure P8.88

- (a) Find the real part of  $v_o$ .  
 (b) Find the imaginary part of  $v_o$ .

Solution: 8.88

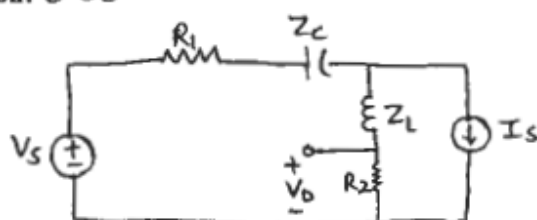


$$R_1 = 1 \Omega, R_2 = 2 \Omega, Z_c = -j1 \Omega,$$

$$Z_L = j2 \Omega$$

$$V_s = 6 \angle 0^\circ \text{ V}$$


$$I_s = 2 \angle 0^\circ \text{ A}$$



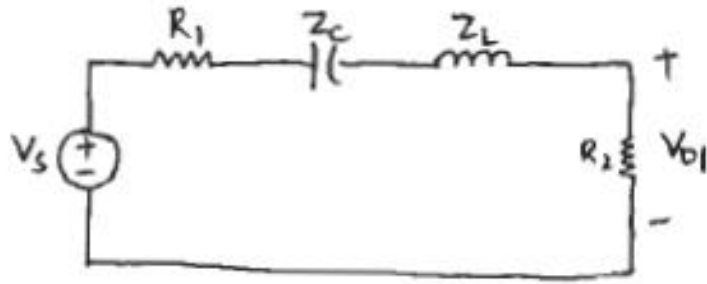

$$V_{o1} = V_s \frac{R_2}{R_1 + R_2 + Z_c + Z_L}$$

$$V_{o1} = 3.6 - j1.2 \text{ V}$$

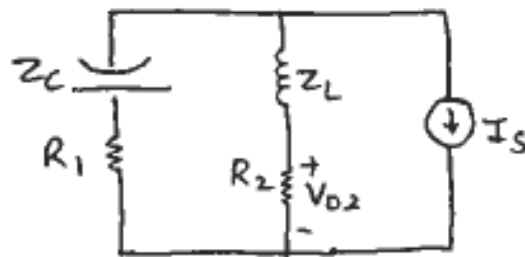

$$V_{o2} = -I_s \cdot \frac{R_1 + Z_c}{R_1 + R_2 + Z_c + Z_L} \cdot R_2$$

$$V_{o2} = -0.8 + j1.6 \text{ V}$$

$$V_o = V_{o1} + V_{o2} = 2.8 + j0.4 \text{ V}$$

(a)  $\boxed{\text{Re}(V_o) = 2.8 \text{ V}}$

(b)  $\boxed{\text{Im}(V_o) = 0.4 \text{ V}}$

8.93 Use source exchange to determine  $v_o$  in the network in Fig. P8.93.


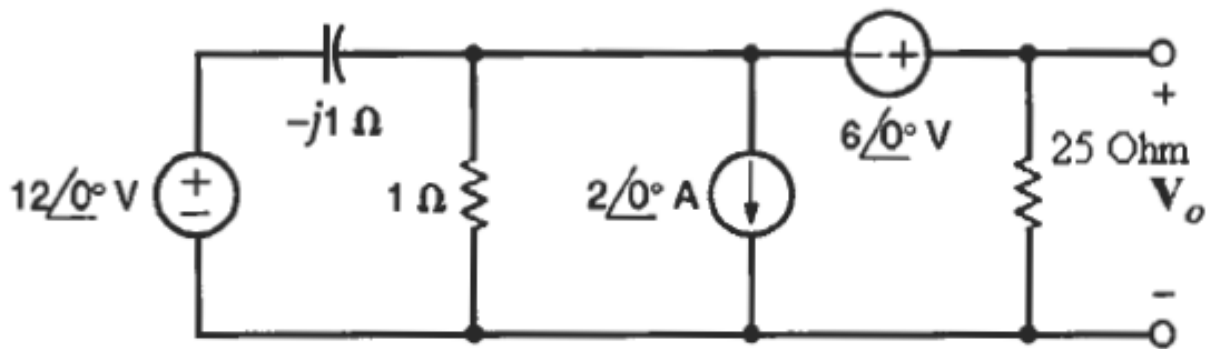




Figure P8.93

- (a) Find the real part of  $v_o$ .  
 (b) Find the imaginary part of  $v_o$ .


Solution:

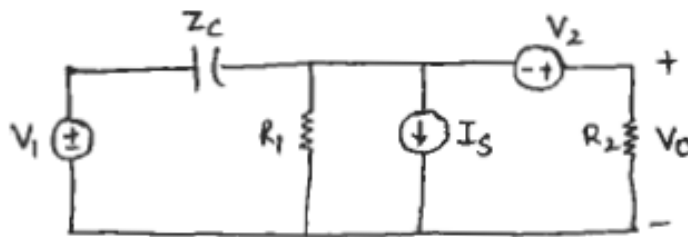
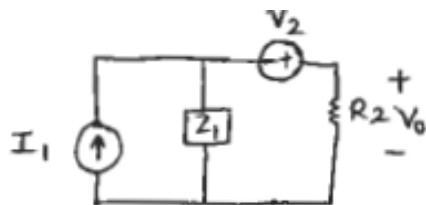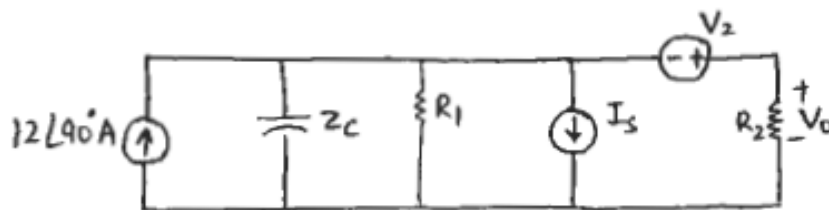
$$\begin{aligned} V_1 &= 12 \angle 0^\circ \text{ V} \\ V_2 &= 6 \angle 0^\circ \text{ V} \\ I_S &= 2 \angle 0^\circ \text{ A} \\ R_1 &= 1 \Omega \\ R_2 &= 25 \Omega \\ Z_c &= -j1 \Omega \end{aligned}$$


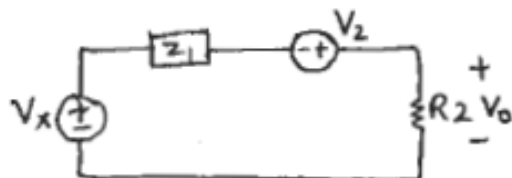
$$\begin{aligned} I_1 &= -2 + j12 \text{ A} \\ Z_1 &= Z_c \parallel R_1 = (-j1) \parallel 1 = \frac{-j1}{1-j1} \\ Z_1 &= 0.5 - j0.5 \end{aligned}$$



$$\begin{aligned} V_x &= I_1 Z_1 \\ &= 5 + j7 \text{ V} \end{aligned}$$

$$v_o = (V_x + V_2) \frac{R_2}{R_2 + Z_1} = 10.6 + j7.07 \text{ V}$$

$$\boxed{\text{Re}(v_o) = 10.6 \text{ V}}$$

$$\boxed{\text{Im}(v_o) = 7.07 \text{ V}}$$

8.104 Find  $v_o$  in the network in Fig. P8.104 using Thévenin's theorem.


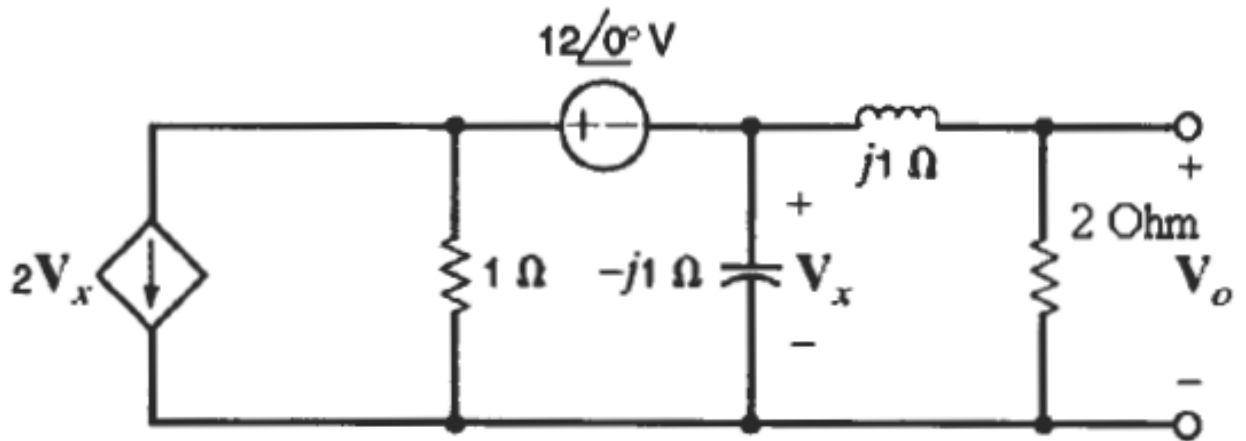


Figure P8.104

- (a) Find the real part of  $v_o$ .  
 (b) Find the imaginary part of  $v_o$ .

Solution: 8.104

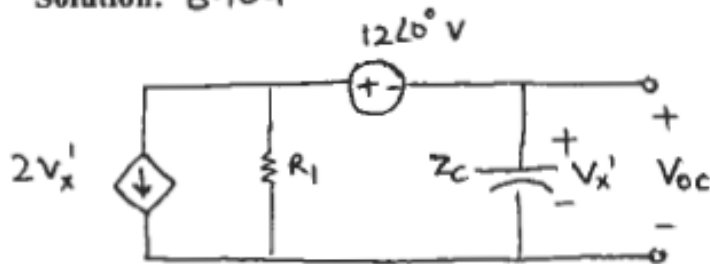


$$R_1 = 1\Omega, R_2 = 2\Omega,$$

$$Z_C = -j1\Omega, Z_L = j1\Omega$$

$$V_{x'} = V_{oc}$$

$$2V_{oc} + \frac{V_{oc} + V_1}{R_1} + \frac{V_{oc}}{Z_C} = 0$$


$$V_{oc} = -3.6 + j1.2 \text{ V}$$

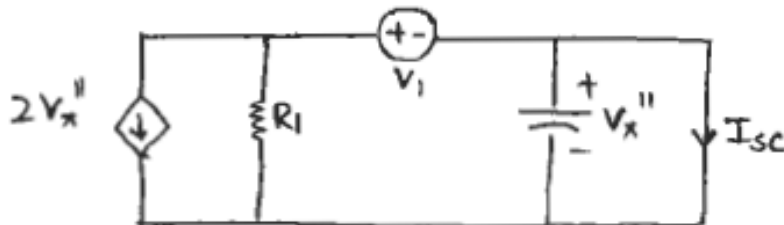

$$V_{x''} = 0$$

$$\frac{V_1}{R_1} + I_{sc} = 0$$
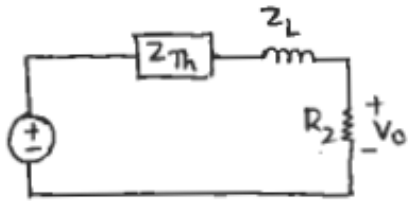
$$I_{sc} = -12 \angle 0^\circ \text{ A}$$



$$Z_{Th} = \frac{V_{oc}}{I_{sc}} = 0.3 - j0.1 \Omega$$

$$V_0 = V_{oc} - \frac{R_2}{R_2 + Z_L + Z_{Th}}$$

$$= -2.36 + 1.97 V$$

(a)  $\text{Re}(V_0) = -2.36 V$

(b)  $\text{Im}(V_0) = 1.97 V$

8.105 Find the Thévenin's equivalent for the network in Fig.P8.105 at terminals A-B.


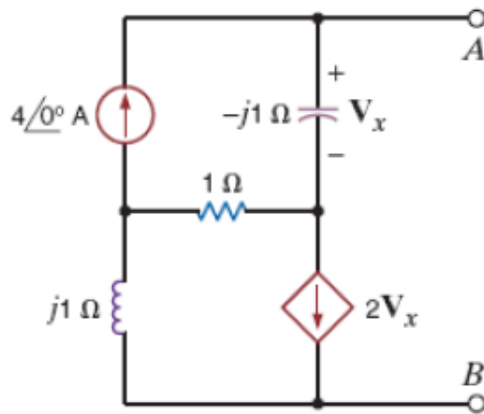


Figure P8.105

**SOLUTION:**

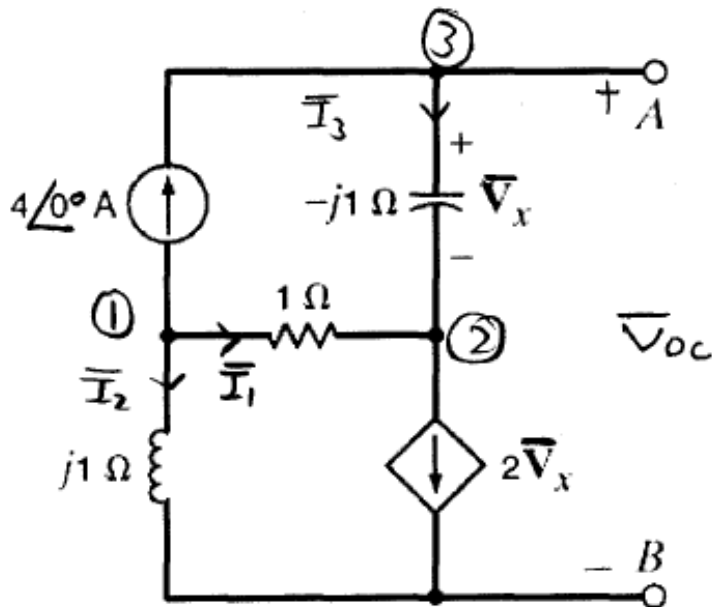

$$\text{KCL at } \textcircled{1} : 4\angle 0^\circ + \bar{I}_1 + \bar{I}_2 = 0$$

$$\frac{\bar{V}_1 - \bar{V}_2}{1} + \frac{\bar{V}_1}{j1} = -4\angle 0^\circ$$

$$j1(\bar{V}_1 - \bar{V}_2) + \bar{V}_1 = j1(-4\angle 0^\circ)$$

$$(1 + j1)\bar{V}_1 - j1\bar{V}_2 = 4\angle -90^\circ$$

$$\text{KCL at } \textcircled{2} : \bar{I}_3 + \bar{I}_1 = 2\bar{V}_x$$


---

$$\bar{V}_x = \bar{V}_{oc} - \bar{V}_2$$

$$\frac{\bar{V}_{oc} - \bar{V}_2}{-j1} + \frac{\bar{V}_1 - \bar{V}_2}{1} = 2[\bar{V}_{oc} - \bar{V}_2]$$

$$\bar{V}_{oc} - \bar{V}_2 - j1(\bar{V}_1 - \bar{V}_2) = -j2[\bar{V}_{oc} - \bar{V}_2]$$

$$-j1\bar{V}_1 + (-1-j1)\bar{V}_2 + (1+j2)\bar{V}_{oc} = 0$$

$$\text{KCL at } \textcircled{3}: \bar{I}_3 = 4\angle 0^\circ$$

$$\frac{\bar{V}_{oc} - \bar{V}_2}{-j1} = 4\angle 0^\circ$$

$$-\bar{V}_2 + \bar{V}_{oc} = 4\angle -90^\circ$$

$$(1+j1)\bar{V}_1 - j1\bar{V}_2 = 4\angle -90^\circ$$


$$-j1\bar{V}_1 + (-1-j1)\bar{V}_2 + (1+j2)\bar{V}_{oc} = 0$$

$$-\bar{V}_2 + \bar{V}_{oc} = 4\angle -90^\circ$$

$$\bar{V}_1 = 8\angle 180^\circ \text{ V}$$

$$\bar{V}_2 = 8.94\angle 116.6^\circ \text{ V}$$
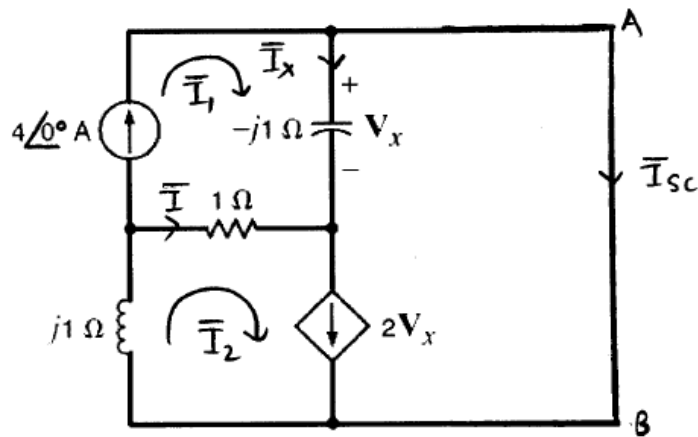
$$\bar{V}_{oc} = 5.66\angle 135^\circ \text{ V}$$



$$\text{KCL: } \bar{I}_2 = \bar{I} + \bar{I}_1$$

$$\bar{I} = \bar{I}_2 - \bar{I}_1$$

$$\text{KCL: } 4\angle 0^\circ = \bar{I}_x + \bar{I}_{sc}$$

$$\bar{I}_x = 4\angle 0^\circ - \bar{I}_{sc}$$

$$\text{KVL: } 1(\bar{I}) - j1(-\bar{I}_x) + j1(\bar{I}_2) = 0$$

$$\bar{I}_2 - \bar{I}_1 + j1(4\angle 0^\circ - \bar{I}_{sc}) + j1\bar{I}_2 = 0$$

$$-\bar{I}_1 + (1+j1)\bar{I}_2 - j1\bar{I}_{sc} = 4\angle -90^\circ$$

$$\text{KCL: } 2\bar{V}_x + \bar{I}_{sc} = \bar{I}_2$$

$$\bar{V}_x = -j1(4\angle 0^\circ - \bar{I}_{sc})$$

$$-j2(4\angle 0^\circ - \bar{I}_{sc}) + \bar{I}_{sc} = \bar{I}_2$$

$$-\bar{I}_2 + (1+j2) \bar{I}_{sc} = 8 \angle 90^\circ$$

$$\bar{I}_1 = 4 \angle 0^\circ \text{ A}$$

$$(1+j1) \bar{I}_2 - j1 \bar{I}_{sc} = 5.66 \angle -45^\circ$$


$$-\bar{I}_2 + (1+j2) \bar{I}_{sc} = 8 \angle 90^\circ$$

$$\bar{I}_2 = 2.53 \angle 71.6^\circ \text{ A}$$

$$\bar{I}_{sc} = 2.53 \angle 18.43^\circ \text{ A}$$

$$\bar{Z}_{TH} = \frac{\bar{V}_{oc}}{\bar{I}_{sc}} = \frac{5.66 \angle 135^\circ}{2.53 \angle 18.43^\circ}$$
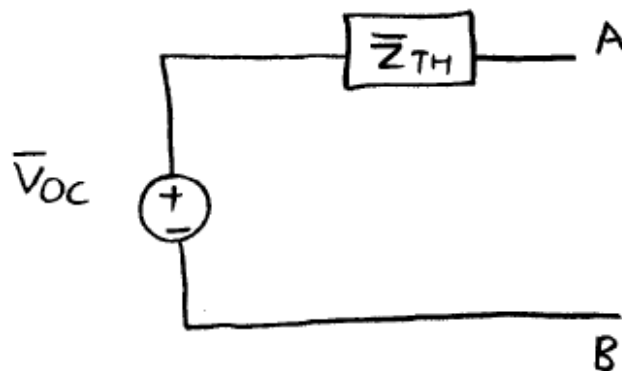
$$\bar{Z}_{TH} = 2.24 \angle 116.57^\circ \Omega$$





8.110 Find  $V_o$  using Norton's theorem for the circuit in Fig. P8.110.


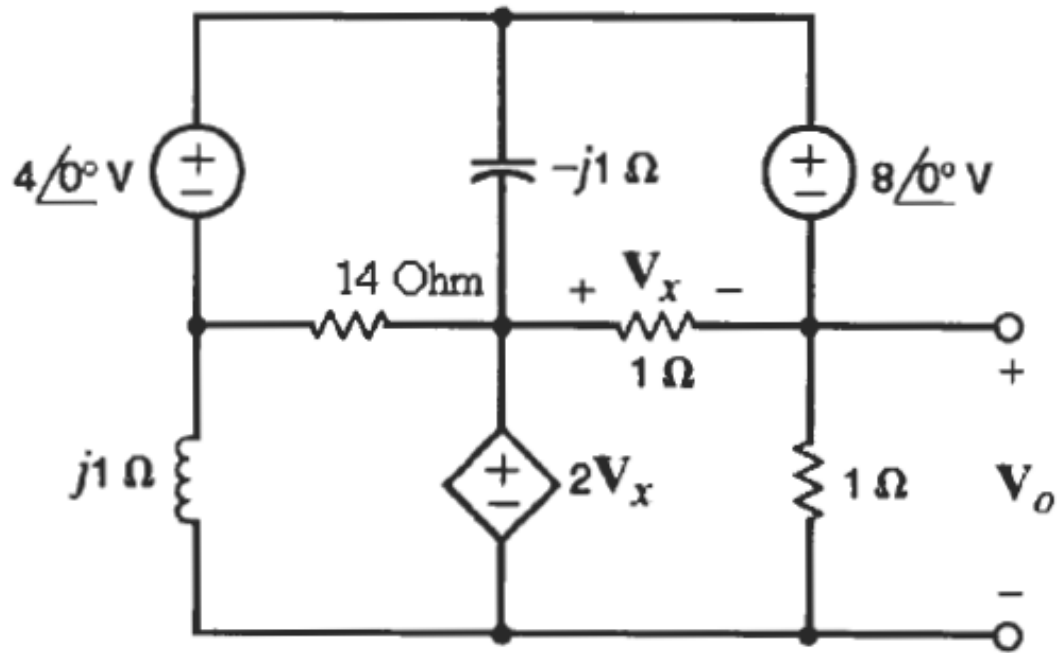


Figure P8.110

- (a) Find the real part of  $V_o$ .  
 (b) Find the imaginary part of  $V_o$ .

Solution: 8-110

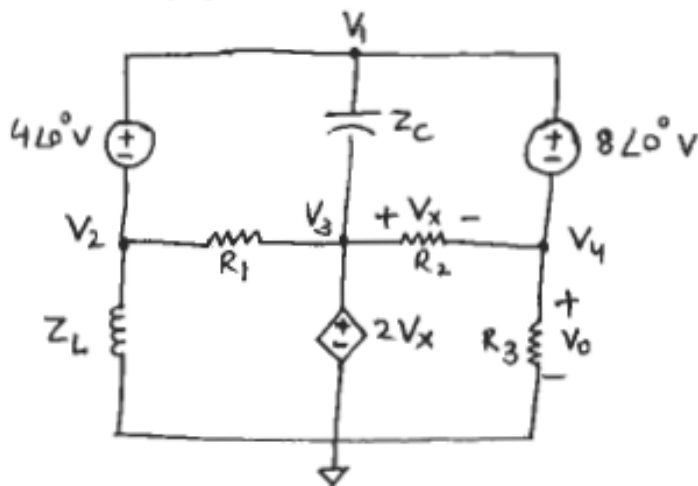

$$R_1 = 14 \Omega$$

$$R_2 = R_3 = 1 \Omega$$

$$Z_c = -j1 \Omega$$

$$Z_L = j1 \Omega$$


$$V_1 - V_2 = 4 \angle 0^\circ \text{ V}$$

$$V_1 - V_4 = 8 \angle 0^\circ \text{ V}$$

$$V_1 = 8 + V_4 \quad \text{--- (1)}$$

$$V_2 = V_1 - 4$$

$$V_2 = V_4 + 4 \quad \text{--- (2)}$$

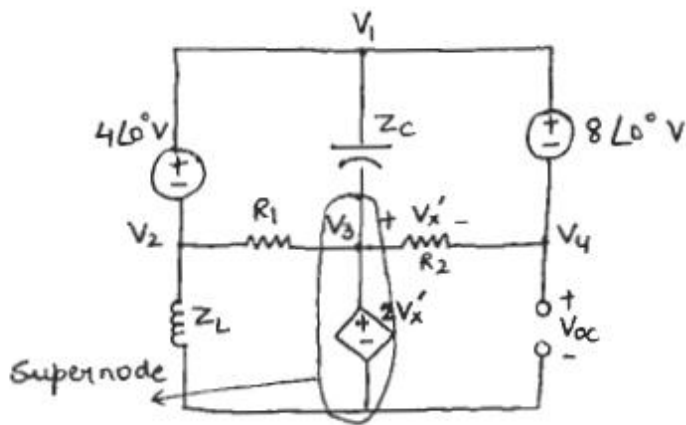

$$2V_x' = V_3$$

$$V_x' = V_3 - V_4$$

$$V_3 = 2(V_3 - V_4)$$

$$\Rightarrow V_3 = 2V_4 \quad \text{--- (3)}$$

KCL @ supernode:  $\frac{V_3 - V_2}{R_1} + \frac{V_3 - V_1}{Z_c} + \frac{V_3 - V_4}{R_2} - \frac{V_2}{Z_L} = 0$


$$\frac{V_3 - V_2}{14} + \frac{V_3 - V_1}{-j1} + \frac{V_3 - V_4}{1} - \frac{V_2}{j1} = 0$$

$$V_4 (15 + 28j) - (56j + 4) = 0$$

$$V_4 = 1.613 + j 0.7215 \text{ V}$$

$$V_{oc} = V_4$$

$$V_{oc} = 1.613 + j 0.7215 \text{ V}$$

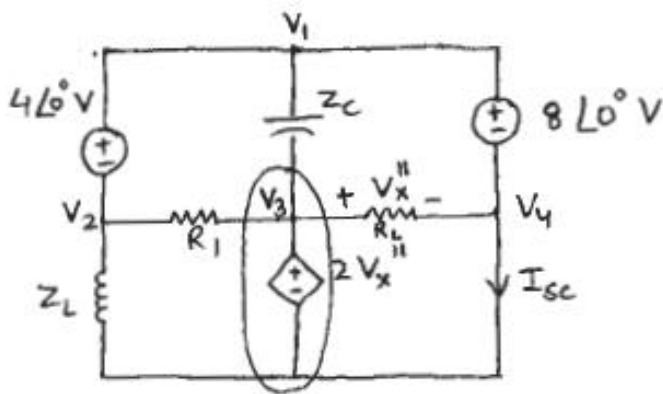

$$V_4 = 0 \quad V_3 - V_4 = V_x'' \text{ and } V_3 = 2V_x''$$

$$\Leftrightarrow V_3 = 0$$

$$V_1 - V_4 = 8 \angle 0^\circ$$

$$\Rightarrow V_1 = 8 \text{ V}$$

$$V_1 - V_2 = 4 \angle 0^\circ$$

$$V_2 = 4 \angle 0^\circ \text{ V}$$

KCL @ supernode:

$$\frac{V_3 - V_1}{Z_C} + \frac{V_3 - V_4}{R_L} + \frac{V_3 - V_2}{R_1} - \frac{V_2}{Z_L} = I_{sc}$$

$$\Rightarrow I_{sc} = -0.2857 - 4j \text{ A}$$

$$Z_{Th} = \frac{V_{oc}}{I_{sc}} = -0.208 + j0.388 \ \Omega$$

$$V_o = I_{sc} \frac{Z_{Th} \cdot R_3}{Z_{Th} + R_3}$$

$$\Rightarrow V_o = 2.0 + j0.071 \text{ V}$$

(a)  $\boxed{\text{Re}(V_o) = 2.0 \text{ V}}$

(b)  $\boxed{\text{Im}(V_o) = -0.071 \text{ V}}$