



# Notre Dame University

## ECCE Department

Exam #1

Spring Semester (2004-2005)

## Microprocessor Design Systems EEN324

Name: \_\_\_A.Kassem

Student ID: \_\_\_\_\_ **Solution**

Question1

Question2

Question3




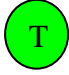

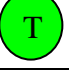

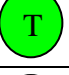
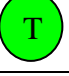
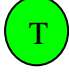
Question4

Total

	10
	25
	10
	15
	/60


**Question 1. (10 points)**

Answer True or False for each of the following statements (1 point each)

1. An instruction that has 2 machine cycles would require 2 clock cycles to complete	T	
2. All registers in the 8085 are 8-bits	T	
3. Memory stores information in Hexadecimal format.	T	
4. The microprocessor (8085) is made up of a Control Unit, an Arithmetic and Logic Unit, and Registers.		F
5. Only one device can be connected to a unidirectional bus.	T	
6. It is possible to have F130H as the first address of a 1K memory chip.		F
7. An 8-bit microprocessor (8085) has 8 address lines.	T	
8. A register is very fast memory located inside the microprocessor.		F
9. A 2 Mega Byte memory chip has 21 address lines and 8 data lines.		F
10. ALL Arithmetic and Logic operations in the 8085 use the accumulator.	T	F
11. The Operating System is the first program to execute after startup and the last program to quit.		F

**Question 2. (25 points)**

An existing memory system has the memory map shown in Figure 1.

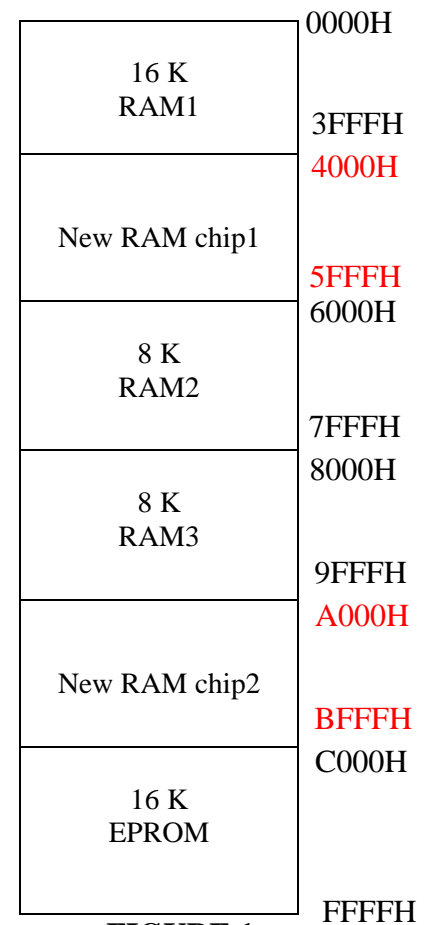
**FIGURE 1**

2.1 Determine the starting and ending addresses for each of the new memory chips. (10 Points)


$$\text{RAM1} = 2^{13} = 8\text{K} \quad \begin{array}{l} \text{From: } 4000\text{H} \\ \text{To: } 5\text{FFFH} \end{array}$$

$$\text{RAM2} = 2^{13} = 8\text{K} \quad \begin{array}{l} \text{From: } \text{A000H} \\ \text{To: } \text{BFFFH} \end{array}$$

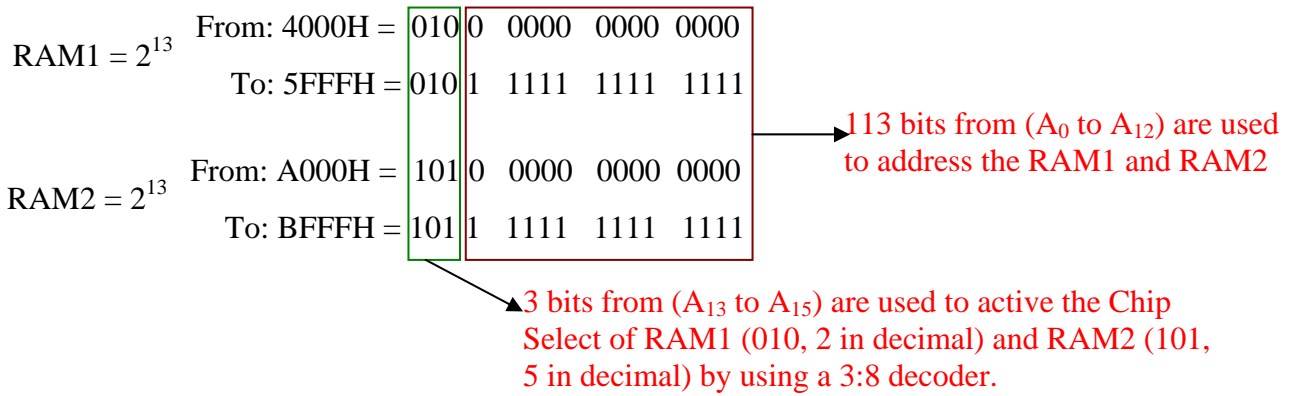2.2 Determine the combinations needed for the chip select of the new memory chips. (7 Points)



2.3 Draw the circuit. (you can use logic gates plus the decoder) (8 Points)

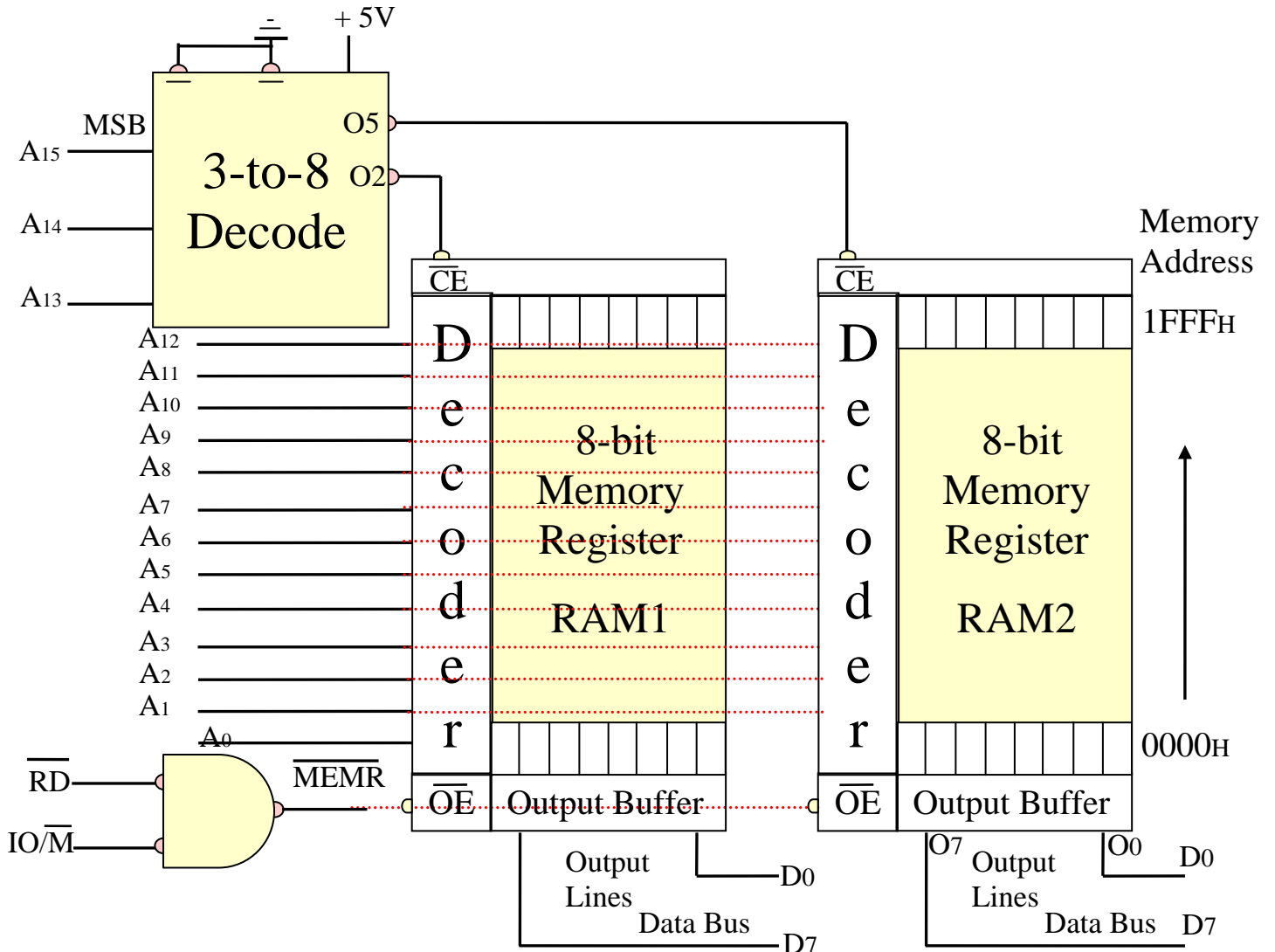


**Question 3. (15 points)**

Using the following timing diagram, find the instructions executed by the 8085 microprocessor.

And what is the address at the M6 machine cycle?

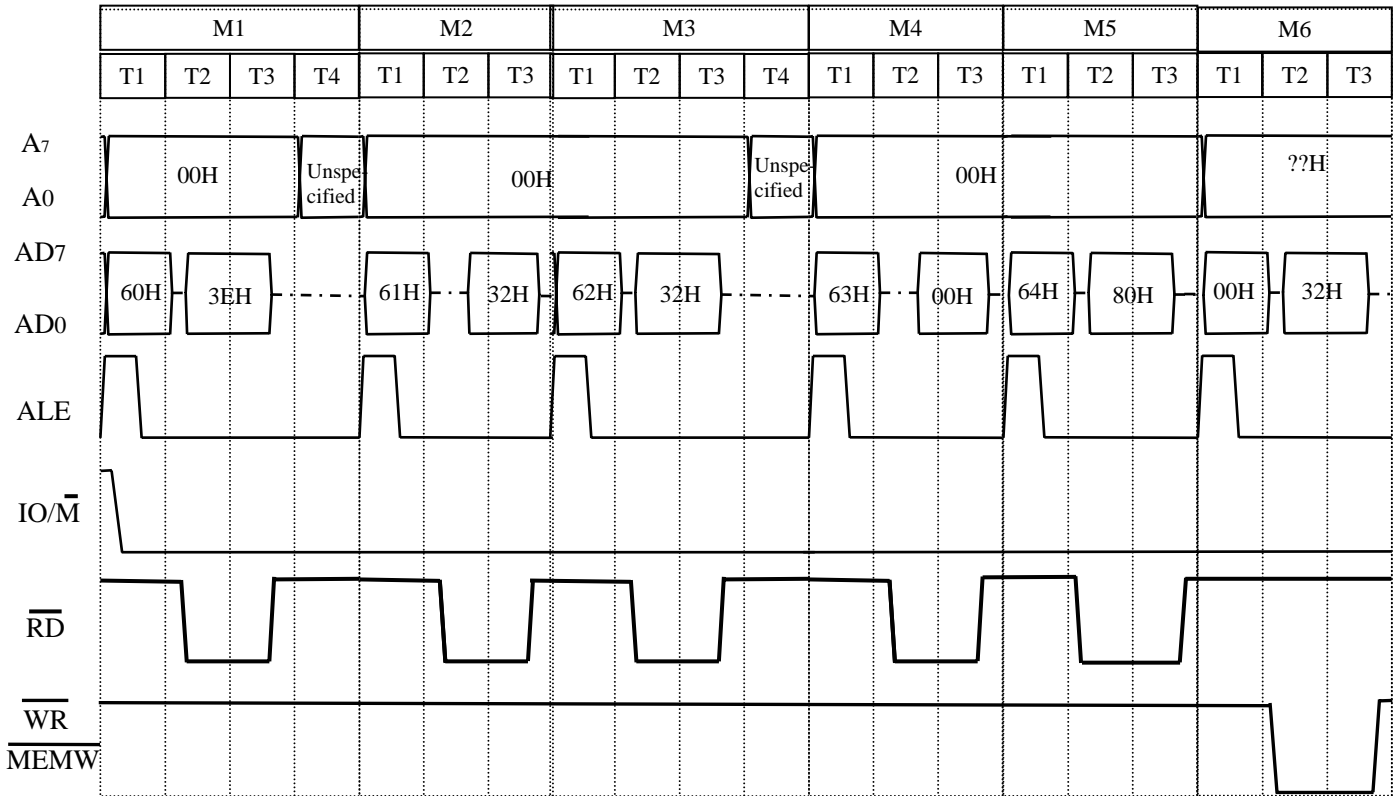Refer to the following table to find the instructions, **not all are used**.



<p><b>MVI A, 32</b> <b>STA 8000</b></p>	Hex. OpCode	Mnemonics	#T-States
	00	NOP	4
	32	STA	13
	3E	MVI A,	7
	60	MOV H,B	4
	61	MOV H,C	4
	62	MOV H,D	4
	63	MOV H,E	4
	64	MOV H,H	4
80	ADD B	4	

**Question 4. (15 points)**

Design an I/O system for the 8085 microprocessor with the following characteristics:

- An input peripheral-mapped port with address 42H.
- An output memory-mapped port with address 4x3xH (x means don't care).

Assume that the device selection input for both ports is active low.

*You are limited to the following chips (Max):*

Chip type	Count
3:8 Decoder	1
Octal Latch gate	1
Octal D-Flip-Flop	1
4-inputs NAND gate	5
4-inputs OR gate	3
Inverter gate	6

