

NDU
Computer Organization & assembly language
CSC 222 Midterm exam.
Duration 1 hour 30 minutes.

Name: _____

1. Perform the subtraction of the following **SIGNED** numbers using the complement method:
 Show your work. (5 pts each)

a. $10010 - 10$ (Binary)

b. $18AF - 2BBB$ (Hexadecimal)

c. $76543 - 7777$ (octal)

2. Perform the following conversions: Show all the steps (5 pts each)

Decimal	Binary	Hexadecimal	Octal
		AB.CD	
			47.25

3. What is the capacity of each of the following memories; what is the number of the input/output data lines, and the number of the address lines? (2.5 pts each)

a. $256K \times 128$

b. $1024M \times 256$

4. Let $F(A,B,C,D) = \sum(0,1,3,5,6,7,9,10,11,12,13,15)$.

- a. Draw the karnaugh map. (5 pts)
- b. Derive the simplified equation. (5 pts)
- c. Draw the logic circuit using NAND gates. (5 pts)
- d. Draw the same circuit using one 8x1 MUX. (5 pts)


5. Simplify the following expression using Boolean algebra:

$F = xy'z + x'yz' + x'y' + xz' + z'y'$. (7.5 pts)

6. Get the complement of the following expression (F'):

$F = xy'z + x'yz' + x'y' + xz' + z'y'$. (7.5 pts)

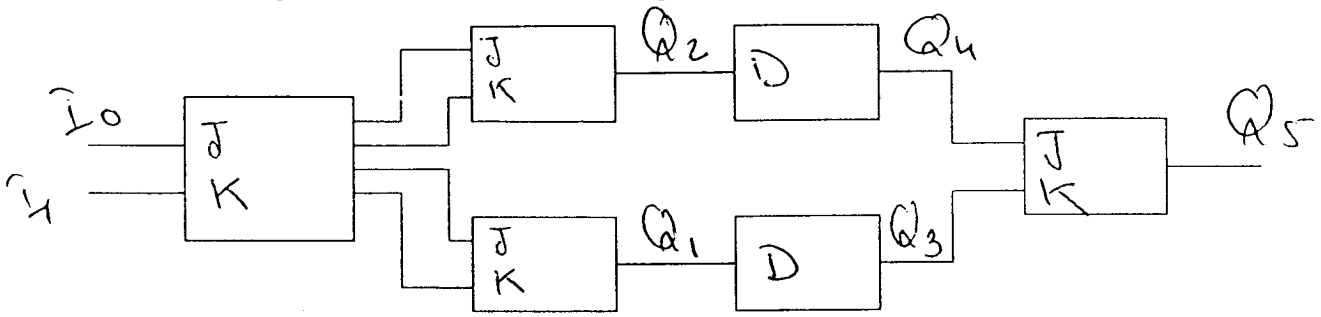7. For the following circuits, what will be the output of Q5 for each input of I0 & I1? (15 pts)



I0	I1	Q5
0	0	
0	0	
0	1	
1	1	
1	1	
0	0	
1	1	
0	1	
1	0	
1	0	