
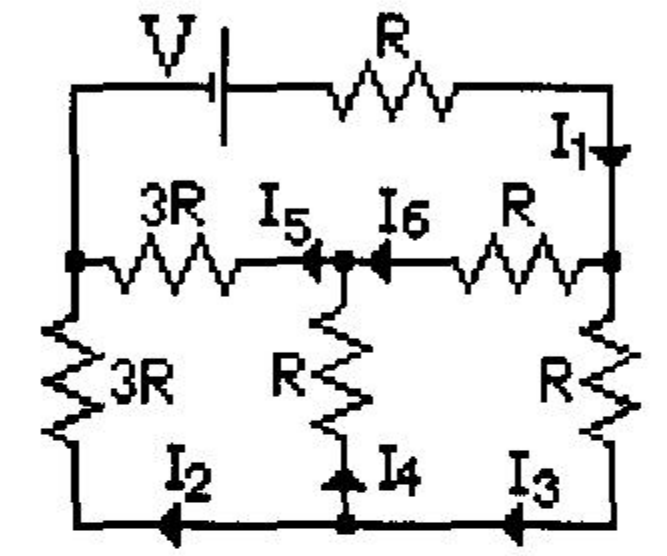


PHY 218
Quiz I

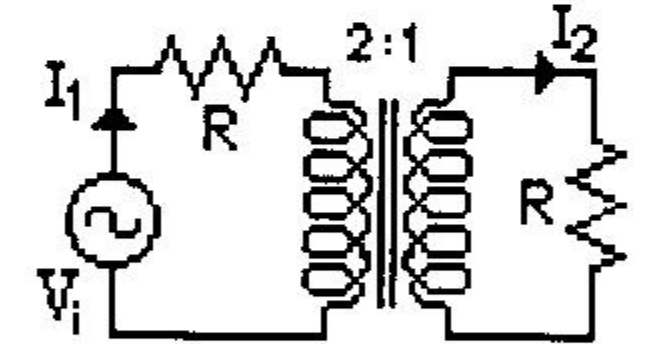
1. For the circuit shown in the figure
 - a. Write down the KCL equations. (4 pts)
 - b. Write down the KVL equations. (9 pts)
 - c. Argue (without algebra) that $I_4 = 0$ (4 pts)
 - d. Show that $I_1 = 40\text{mA}$ for $R=100\Omega$ & $V=12\text{v}$ (3 pts)




2. Take $R = 1.5\text{K}$ and $V_i = 15\text{v}$
 - a. Calculate the current I_1 . (12 pts)
 - b. Is impedance matching satisfied? Explain briefly. (3 pts)



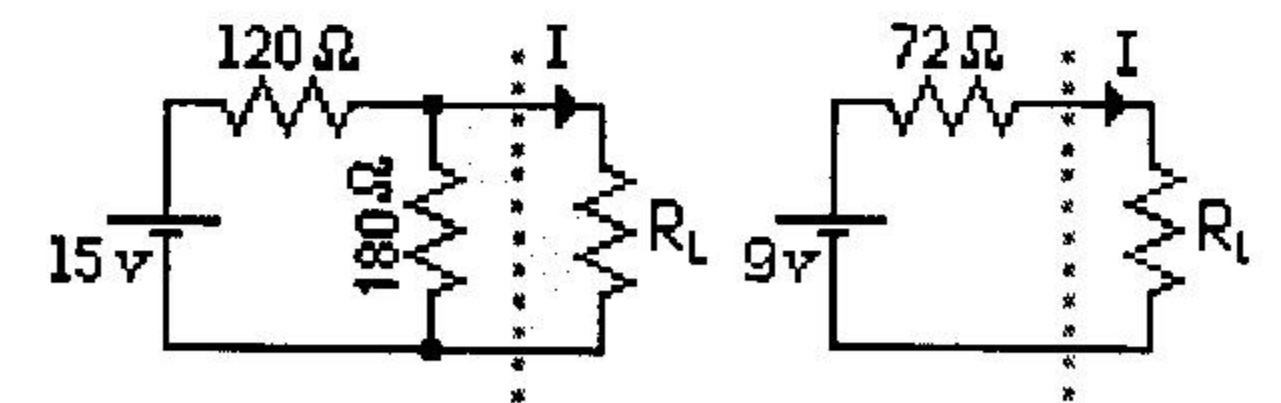3. Use the Thevenin's Theorem to show that circuit (b) is equivalent to circuit (a). Note: NO points for other methods. (15 points)




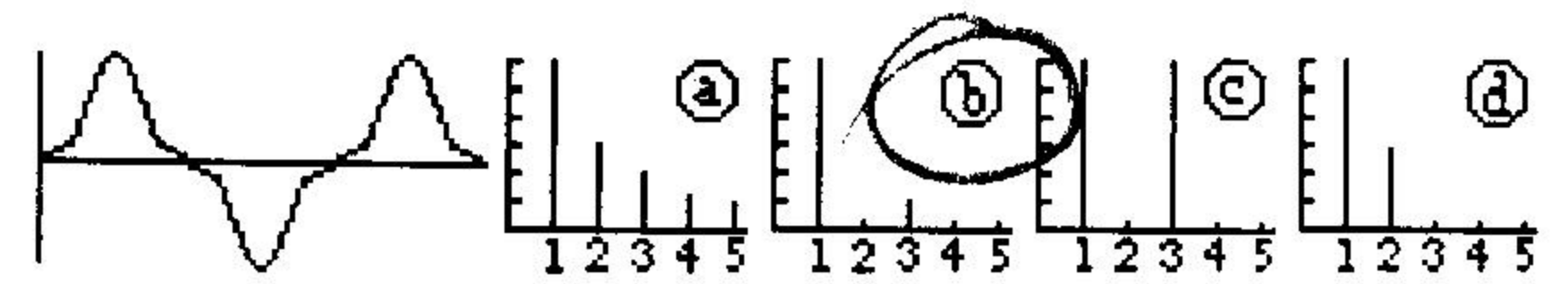4. Which of the four spectra belongs to the waveform? Explain your answer clearly. (No explanation, no points) (8 points)



5. Answer 7 of the following 11 questions. The 8th answer will be ignored. (7x6 = 42 points)

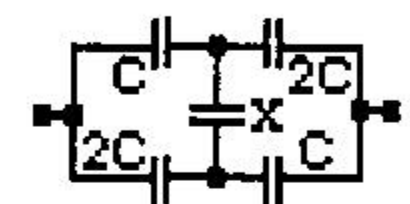
- a. Why do transmission lines have capacitance and inductance?
- b. What is the value of a resistor marked as 3K3? **3.3KΩ**
- c. Why does the size of capacitors increase with their value, whereas that of resistors does not?
- d. Why the value of an electrolytic capacitor is depends a little on voltage?



- e. Argue that $C_e \sim 1.4C$ is an "educated guess" for the connection shown, irrespective of X.

- f. How is a data "written" on a CD?

- g. Mention three uses of transformers.

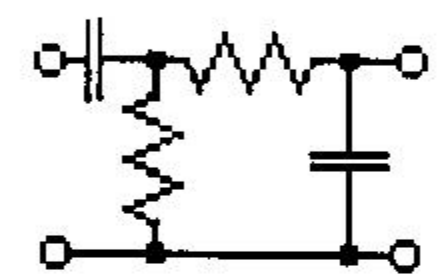

- h. What is the shape of the Bode diagram for the filter shown?



- i. Define "termination" in transmission lines

- j. What is the approximate value of a current that causes painful shock? **9 mA**

- k. Complete the following: Quality factor $Q = (\text{energy } \triangle) / (\text{energy } \square)$

Good Luck!

20 + 2x15 + 8 + 42 = 100