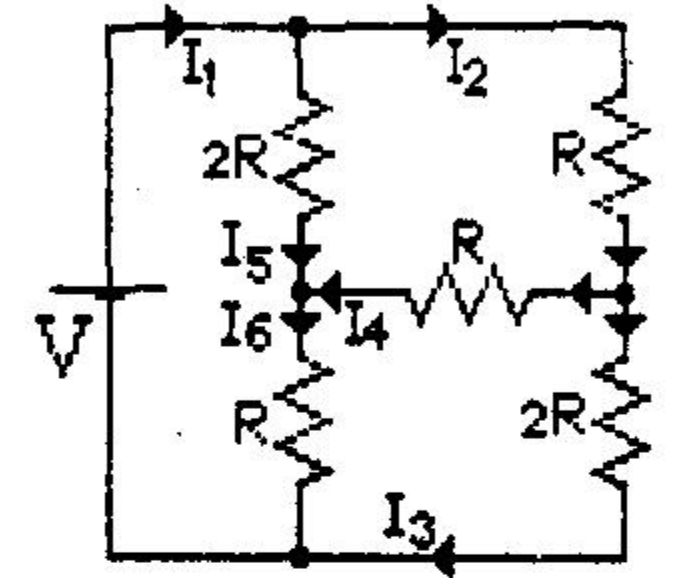


PHY 218

Quiz I

$I_1 = I_2 + I_5$
 $I_5 + I_4 = I_6$
 $I_2 = I_4 + I_3$




$V - 2RI_5 - RI_6 = 0$

1. For the circuit shown in the figure

- a. Write down the KCL equations. (6 points)
- b. Write down the KVL equations. (12 points)
- c. Argue (without algebra) that $I_2 = I_6$ and $I_3 = I_5$ (3 points)

Flip it mirror

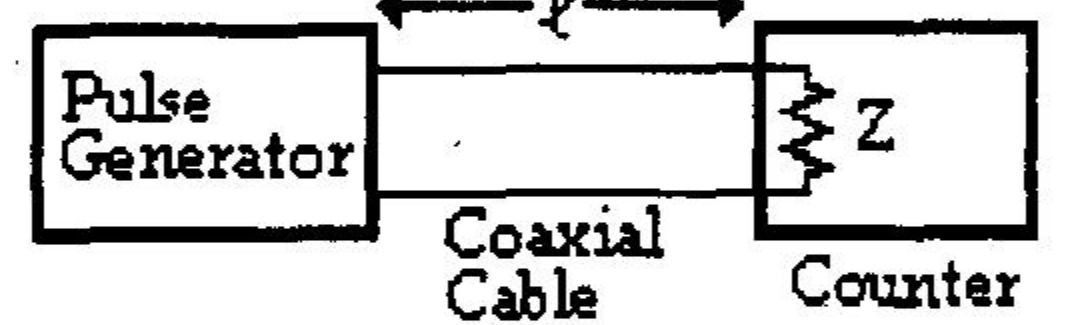2. A pulse generator is connected to a counter of resistance $Z = 300\Omega$ by a cable of $Z_0 = 60\Omega$ and length $l = 2m$. Take $v = 2.5 \times 10^8$ m/s.



- a. Calculate the upper limit of the signal frequency. (5 points)
- b. Calculate the value of the resistance that must be used to terminate the cable. (5 points)
- c. Show that the reflection coefficient is $2/3$. (5 points)


a) $f \leq \frac{v}{2l}$

b) $\frac{1}{300} + \frac{1}{R} = \frac{1}{60}$

c) $\frac{Z - Z_0}{Z + Z_0}$


3. For the RC filter shown answer 3 of the 4 questions below (3x5=15 pts.)

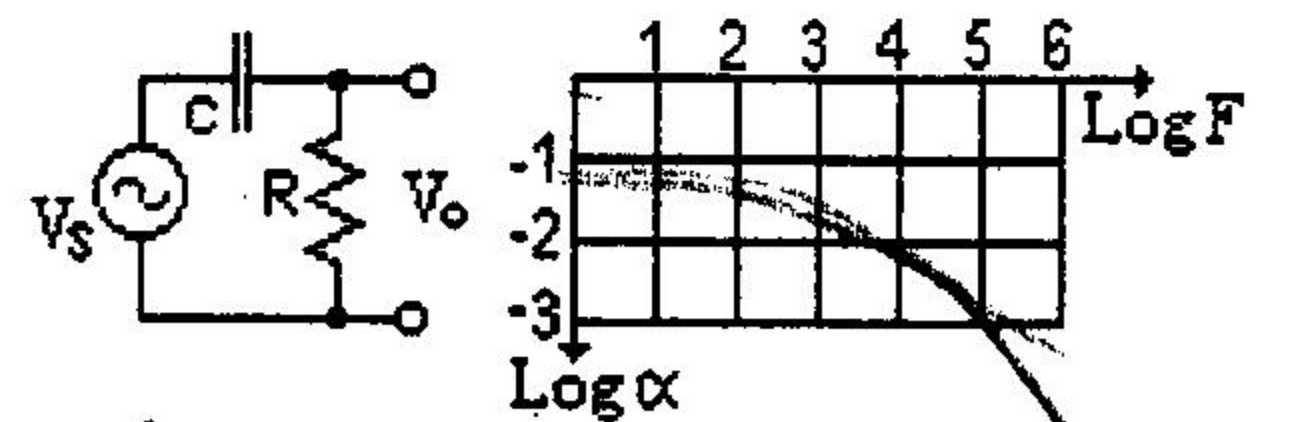- a. Argue that it is a low pass and hence $\alpha = 1/[1+(f_0/f)^2]^{1/2}$
- b. Take $C = 0.47\mu F$, $R = 339\Omega$ and show that $f_0 \approx 1KHz$
- c. Will the circuit integrate or differentiate the input V_s ? What is the condition that must be satisfied, $T \gg \tau$ or $T \ll \tau$? Explain briefly.
- d. Draw the Bode diagram on the graph provided.




$f_0 = \frac{1}{2\pi RC}$

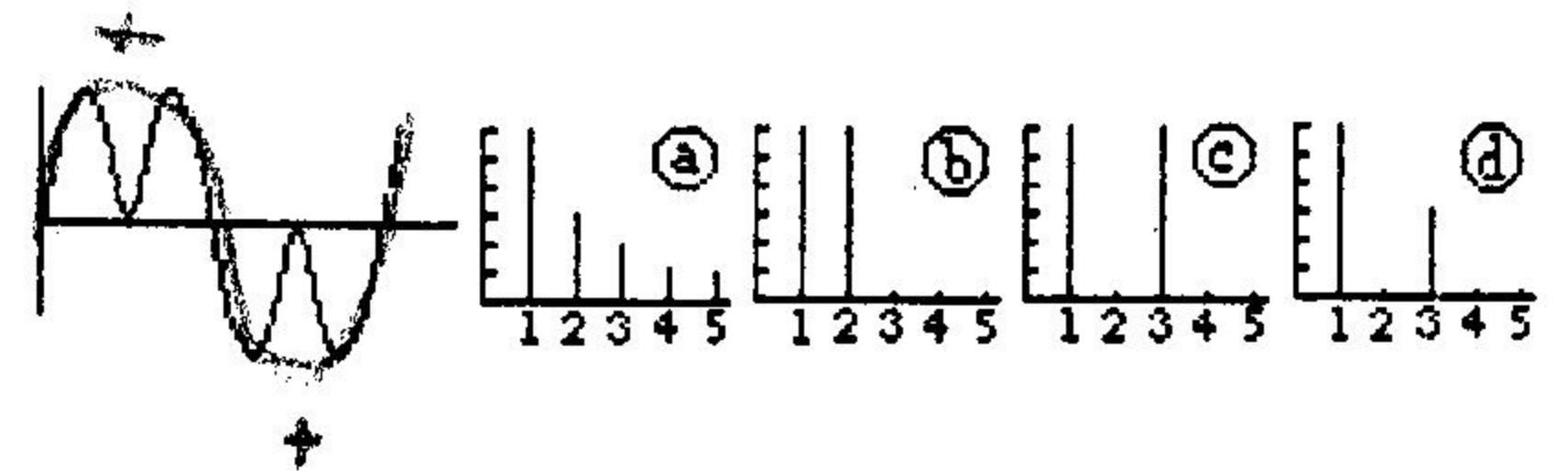4. Which of the four spectra (a,b,c, or d) belongs to the waveform shown in the figure? Explain your answer clearly. (No explanation, no points) (9 points)



5. Answer 5 of the following 7 questions. (5 X 8 = 40 points)
 Note: The 6th answer will be ignored.

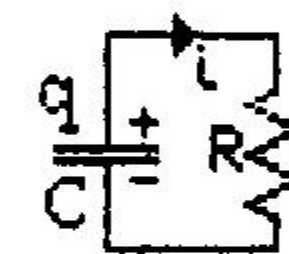- a. Define impedance matching and give an example.
- b. Why does the size of capacitors increase with their value, whereas the size of resistors is independent of their value?
- c. Give two reasons why chips cannot contain inductors.
- d. For the discharge in the figure opposite show that $dq/dt = -q/RC$
- e. Define magnetic flux linkage in transformers
- f. Describe the construction of 3 types of commercial resistors
- g. For the circuit of question 1. Take $V = 14$ volt and $R = 1 K\Omega$ and show that $I_1 = 10$ mA
 Note: You may use the result of part 1c above.



$\frac{q}{C} + Ri = 0$
 $\frac{q}{C} = -R \frac{dq}{dt}$
 $\frac{dq}{dt} = -\frac{q}{RC}$

Good Luck

$21 + 2 \times 15 + 9 + 40 = 100$

g) $V = 14, R = 1K$

$V - 2RI_5 - RI_2 = 0$
 $14 - 2000I_5 - 1000I_2 = 0$

$2000I_5 + 1000I_2 = 14$
 $2I_5 + I_2 = 14/1000$