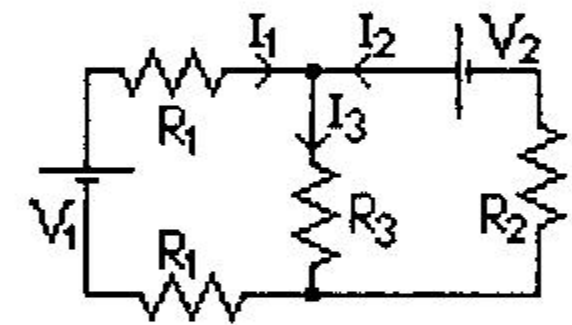


PHY 218
Quiz I

Note: Cellular phones and programmable calculators are not allowed.


1. For the circuit shown in the figure

- a. Write down the Kirchhoff Current and Voltage Laws. (14 pts.)
- b. Take $V_1=9v$, $V_2=6v$, $R_1=R_2=R_3=12\Omega$. Calculate I_2 . (6 pts.)




2. For the circuit shown in the figure take $V_s = 15v$, $R_1 = R_2 = 60\Omega$.

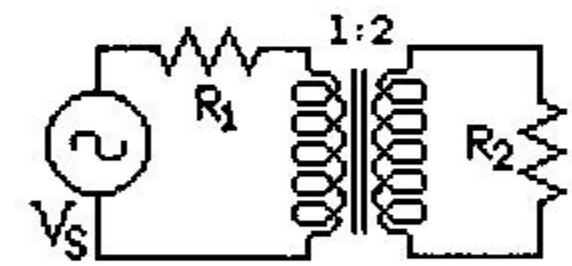- a. Follow any method of your choice to calculate I_1 . (10 pts.)
- b. Calculate the power dissipated in (R_2) (7 pts.)
- c. Is Impedance Matching satisfied? Explain briefly. (3 pts.)



3. For the RC filter circuit shown in the figure

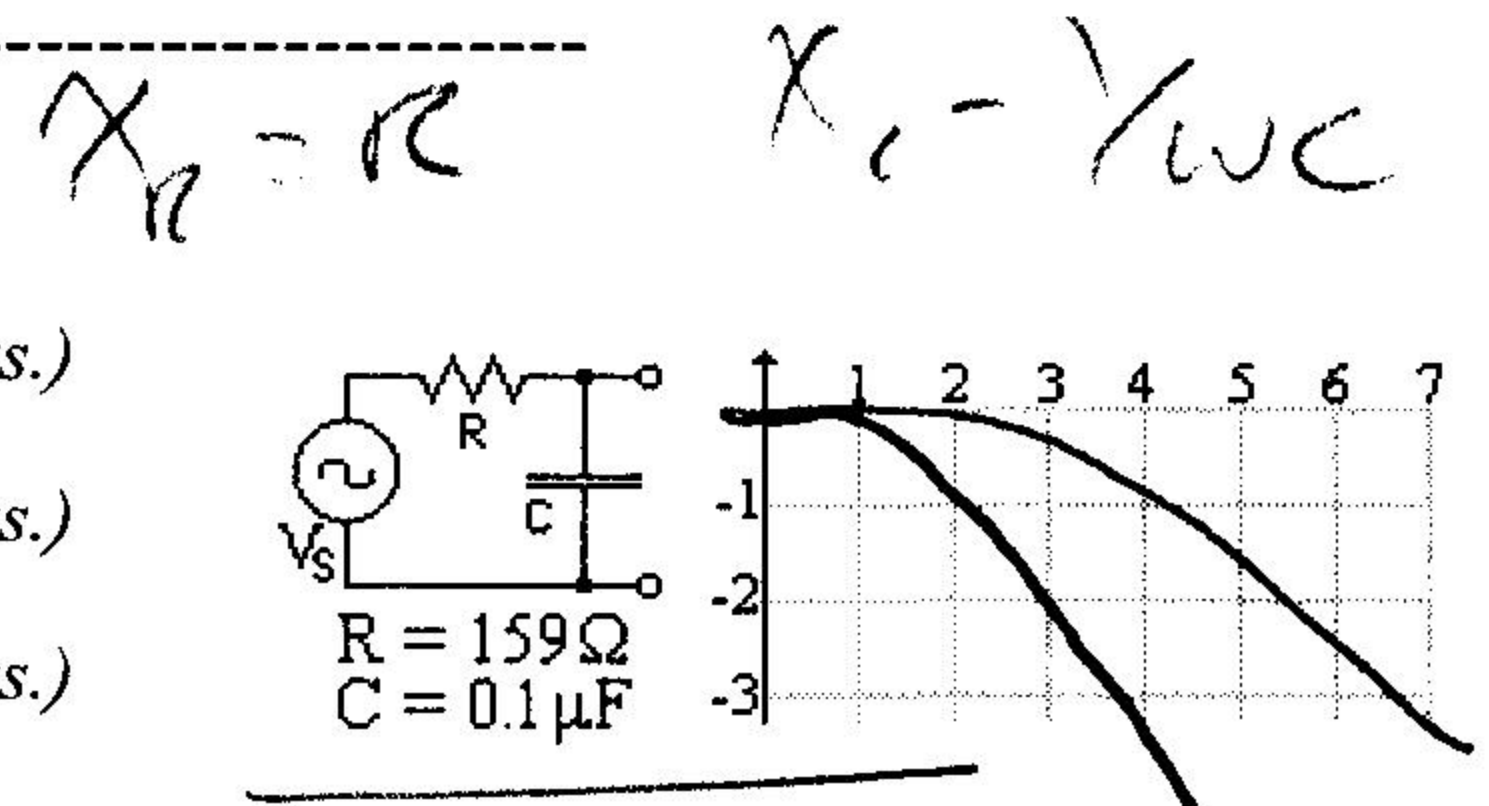- a. Show that $f_0 = 10\text{ KHz}$ (5 pts.)
- b. Argue that $\alpha = 1/[1 + (f/f_0)^2]^{1/2}$ (6 pts.)
- c. Draw the Bode Diagram for $10\text{Hz} < f < 10\text{ MHz}$ (7 pts.)




Note: You may save time by drawing on the figure itself.

4. Answer 6 of the following 9 questions briefly. (6x7 = 42 pts.)

Note: The 7th answer will be ignored.

- a. Which type of resistors is the cheapest and which most expensive?
- b. Why is the physical size of capacitors proportional to its value, whereas this relation does not hold for resistors?
- c. Why did we use ODD Fourier harmonics only to construct a "square wave" *down*
- d. When the characteristic Impedance (Z_0) of a transmission line does NOT match that of the receiver, there will be reflections. Why does that impose an UPPER (not a lower) limit on the frequency?
- e. Why is a coaxial cable rather than a parallel pair of wires used in communications? *it prevents magnetic variations*
- f. Define Thevenin's Theorem and give an example.
- g. For which frequencies will the filter in question 3 act an analogue computer? Explain briefly.
- h. Give two reasons explaining why inductors can't be used in chips.
- i. Why do transmission lines have capacitance and inductance? *vertical*

Good Luck!

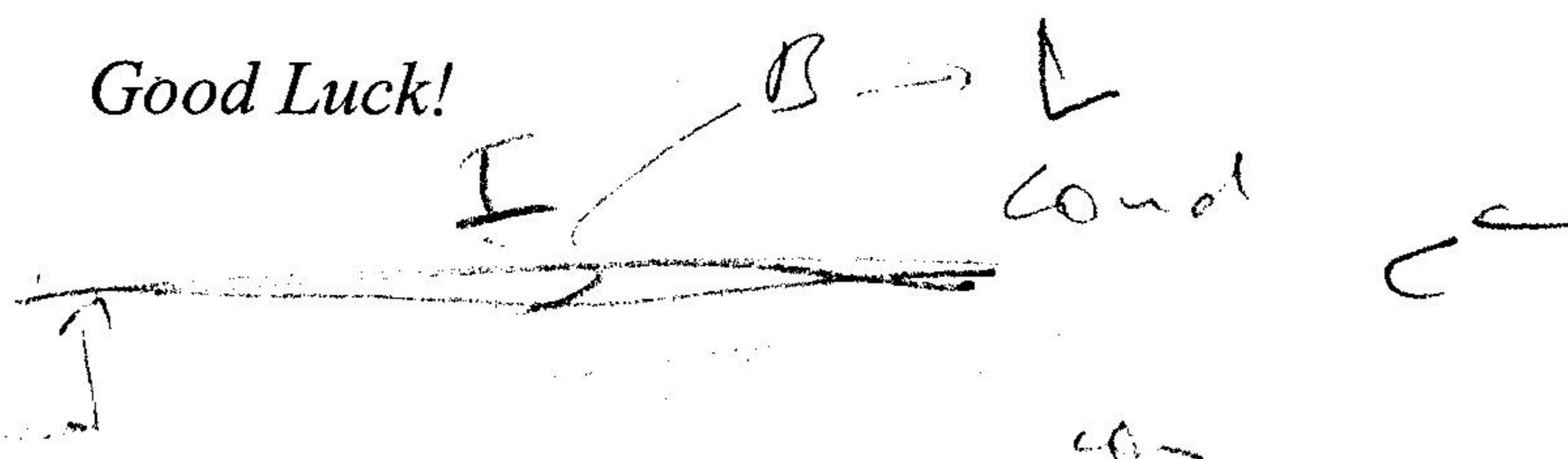

$2 \times 20 + 18 + 42 = 100$