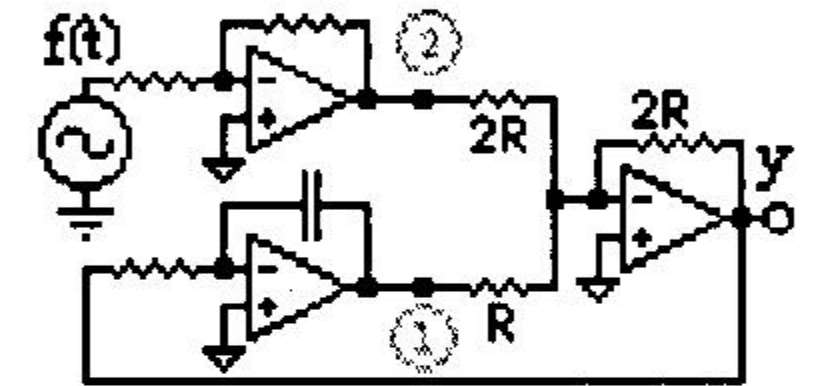


PHY 218
FINAL


1. Assume that all unmarked resistors in the Analogue computation circuit shown are equal, and that $\tau = 1$. Take $f(t) = 2\cos 3t$.

- a. Write down the voltages at the nodes 1 and 2 (5 pts.)
- b. Write down the differential equation for (y). (5 pts.)




2. The circuit shown is an "azif component".

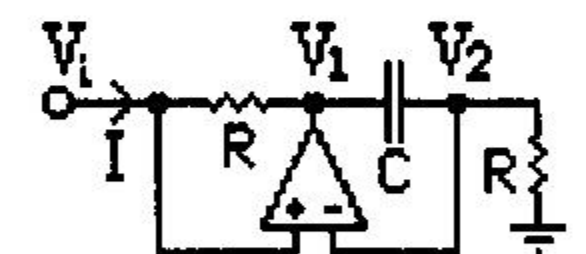- a. Write down the nodal equations for V_1 & V_2 and calculate V_i/I (12 pts.)
- b. V_i/I has the form $(-j\omega K)$ where (K) is a constant that depends on R&C. What does that practical meaning mean of K? (3 pts.)




3. Take $V_{cc} = 12v$, $V_E \sim 6v$, $R_E = 1k$, $R_S = 50\Omega$, $\beta = 100$, $F = 10KHz$, and $C = 0.47 \mu F$. ($1/\omega C \sim 34\Omega$)

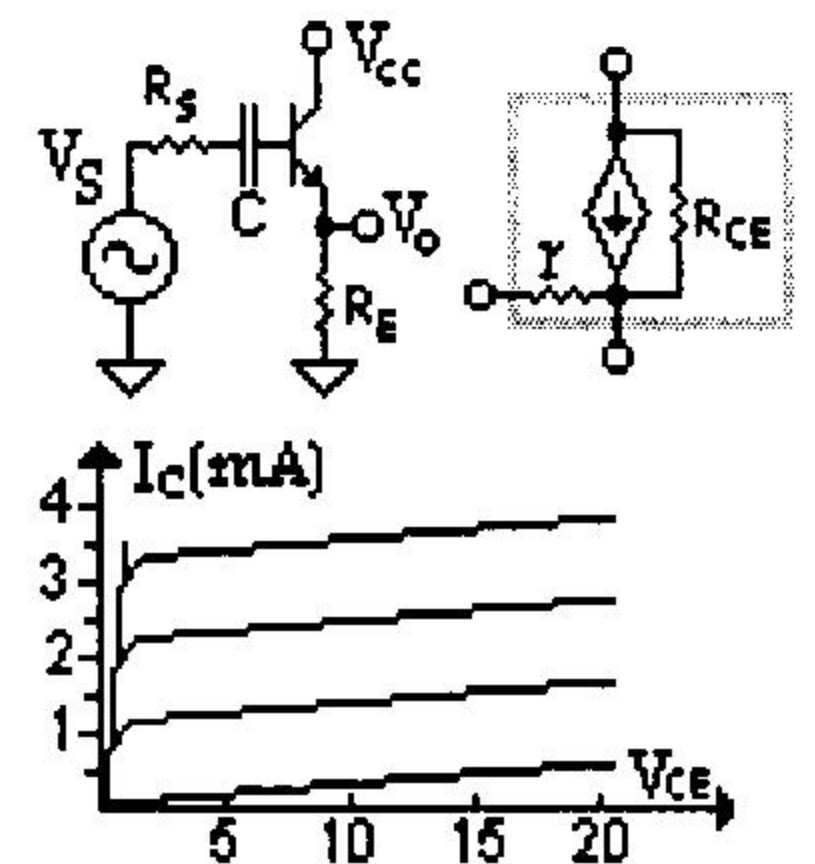- a. Draw the ac equivalent of the circuit (5 pts.)
- b. Calculate I_E and show that $r \sim 5\Omega$ (2 pts.)
- c. Use the I-V graph to argue that $R_{CE} > 40k$ (2 pts.)
- d. Simplify the circuit using the answers of parts b&c (2 pts.)
- e. Show that $V_o/V_s \sim A/(A+1)$ where $A = \beta R_E/R_s$ (4 pts.)




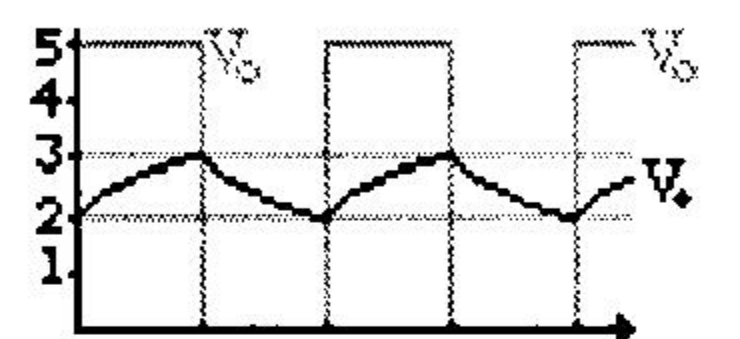4. Answer 3 of the following 4 problems. (3x9 = 27 pts.)
Note: The 4th answer will be ignored.


4A. Assume that the two halves of the cycle of the RC oscillator have equal length. Show that the period is given by $T \sim 0.81\tau$



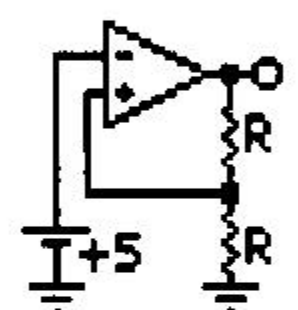
4B. Assume that the opamp shown is ideal except for common mode rejection. Take $CMRR = 104$ and show that $DV_o = 10mv$. Show your steps clearly.



4C. Calculate V_o in terms of x and y.

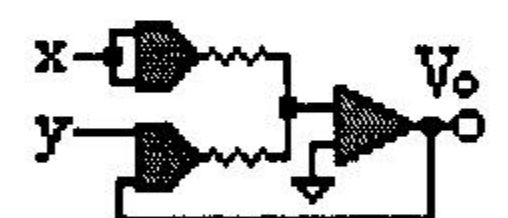

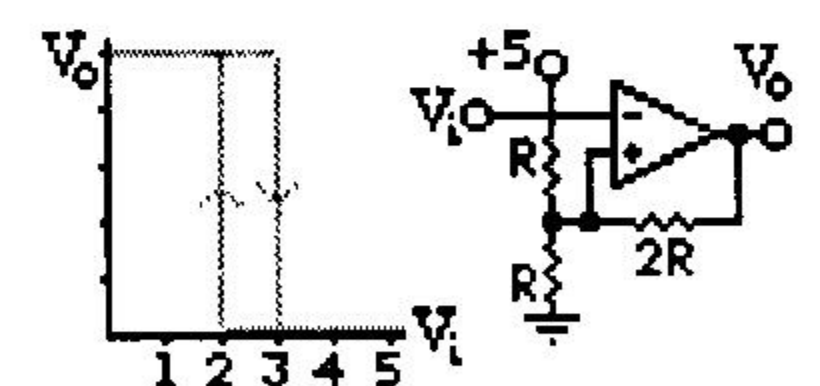4D. Identify the circuit (2 pts.) and show that the reference voltage ($V+$) alternates between the does have the values 2v, 3v




Note: You may answer the following questions on the sheet itself to save time.

5. Answer 5 of the following 7 questions briefly. The 6th answer will be ignored. (5x4=20 pts.)


- How does one write on a CD?
- Draw a CMOS Totem Pole
- Why are voltage followers used as "buffers"?
- Why is the characteristic impedance of a transmission cable weakly dependent on its diameter?
- Why is the input resistance of an FET very large?
- What are the factors that limit the integration time of Analogue computers?
- What would be an educated guess for the resistivity of a semiconductor, if ρ of conductors were $\rho_m = 10^{-9} \Omega m$ and that of insulators $\rho_i = 10^{13} \Omega m$? Is the answer you found realistic?

6. Answer 2 of the following 3 questions briefly. The 3rd answer will be ignored. (2x5 = 10 pts.)

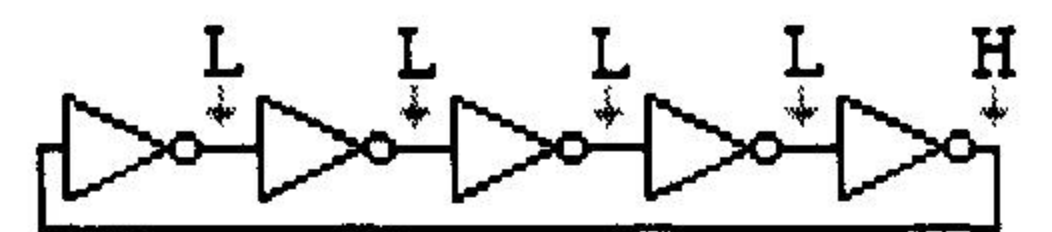
- a. The circuit shown is in the (00001) state. What is its next state?



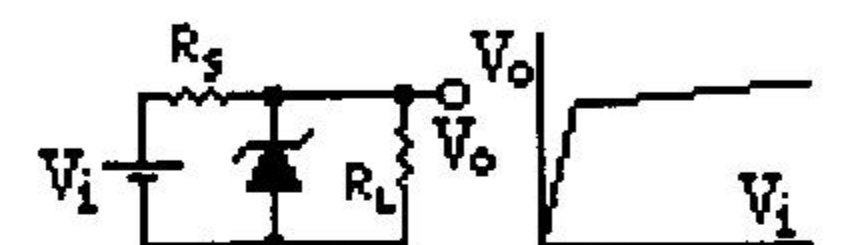
- b. Why is the initial steep slope of the regulator shown independent of the Zener diode used, whereas the flatter part is determined by the diode?



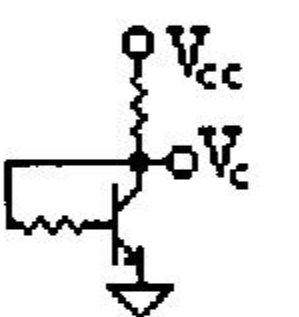- c. Complete the "nonsense sentence": $V_c \uparrow \dots \dots V_c \downarrow$, which indicates that the operating point tends to be stable.



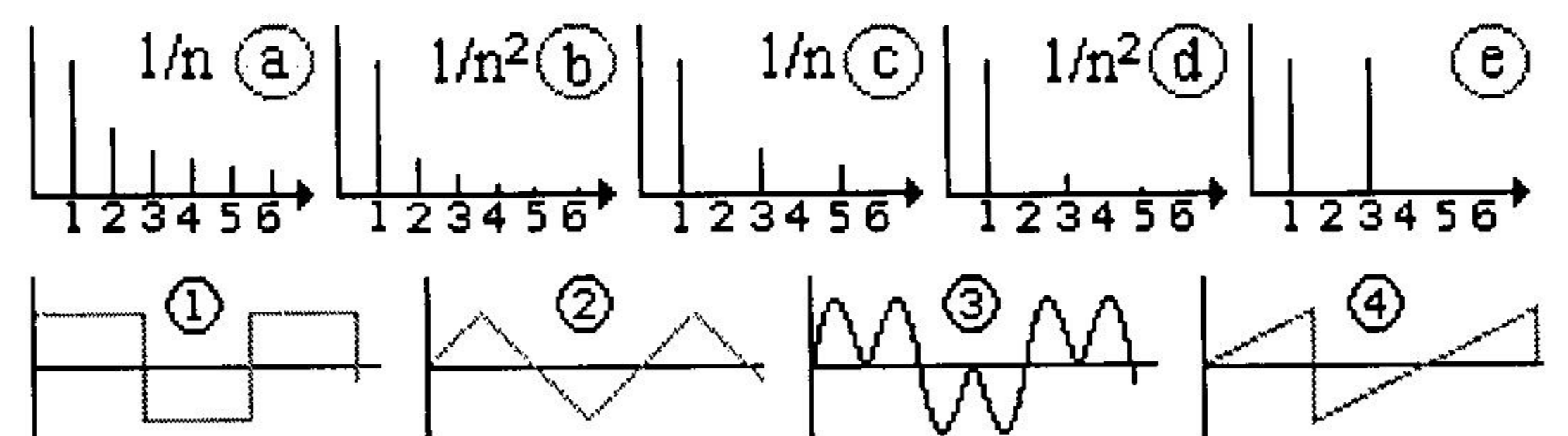- d. Associate each of the the 4 waveforms with one of the spectra. Double penalty for wrong answers.



-
-
-
-

Good Luck!

$$\dots\dots/10 + \dots\dots/2x15 + \dots\dots/30 + \dots\dots/20 + \dots\dots/10 = \dots\dots/100$$