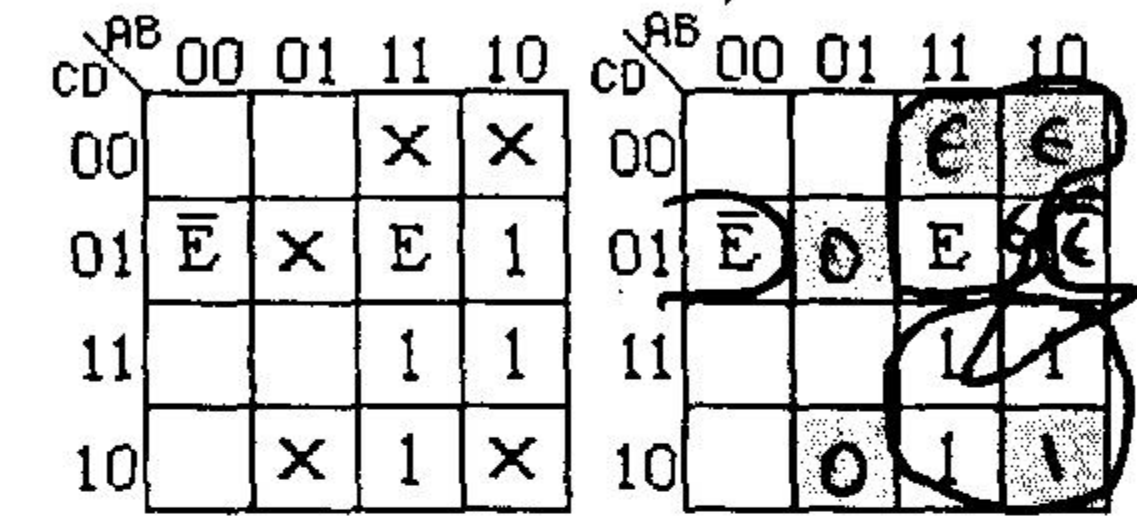


PHY 233
Quiz I

1. In the Karnaugh map shown the blanks are zeros. Replace the "Don't Cares" with appropriate values, and write down the minimized logic function. Fill in the values of the X's explicitly in the blank map given. (Correctness: 9 pts. Minimalism: 6 pts.)




2. Follow the Quine-McCluskey method to minimize the function (F) shown below. Show all your steps clearly. Indicate the redundant group(s). (Minimized function: 10pts + Redundant groups: 5pts = 15 pts.)


$$F = m_0 + m_1 + m_5 + m_7 + m_{10} + m_{11} + m_{13} + m_{15}$$

	m_0	m_1	m_5	m_7	m_{10}	m_{11}	m_{13}	m_{15}
000-	x	x						
0-01		x	x					
01-1			x	x		x	x	x
101-					x	x		
1-11								

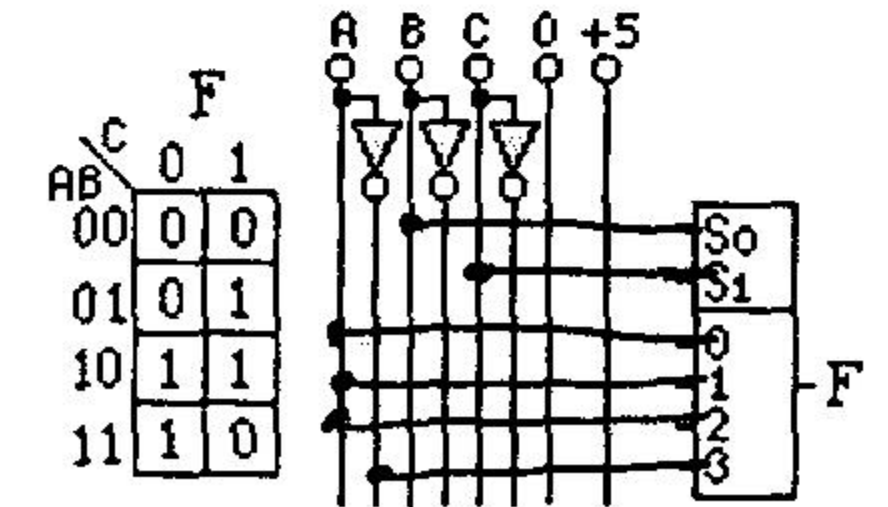3. Show how the 3 variable Karnaugh Map can be realized using the 2-bit Address Multiplexer given. You can save time answering on this sheet. (10 pts)






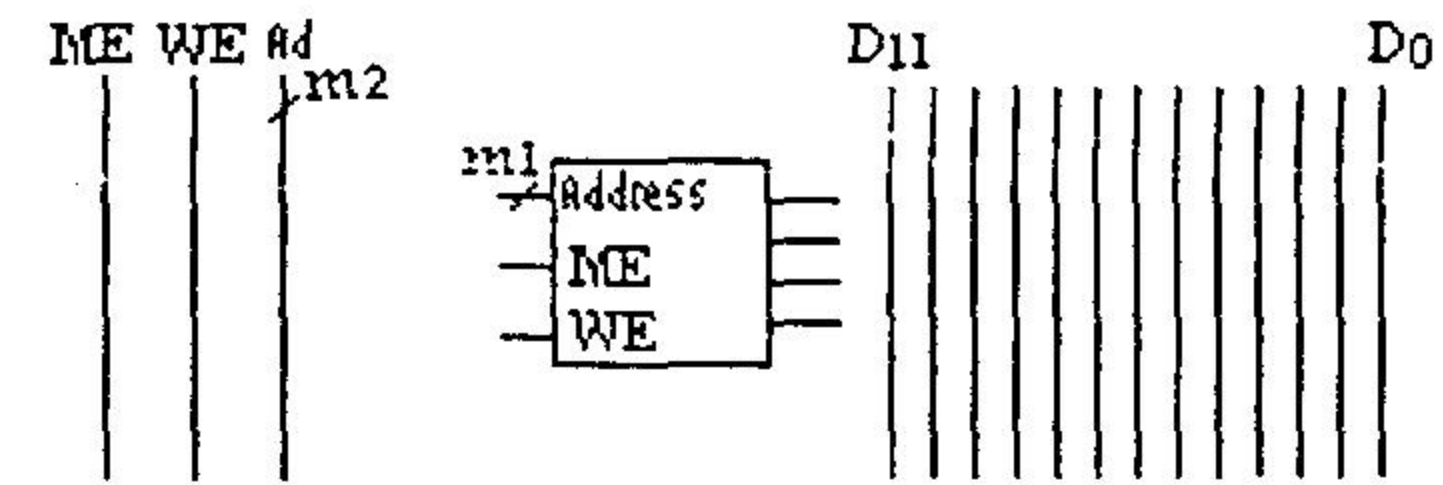4. Figure shows an 8x4 memory chip. Indicate the values of m_1 and m_2 . Show how can use it to construct a 16x12 memory "chip". You must connect I/O and the address to the appropriate buses. Note: Redraw the figure in your answer booklet. (12 pts)



5. Answer 6 of the following 8 questions briefly. The 8th answer will be ignored. (6x8 = 48)

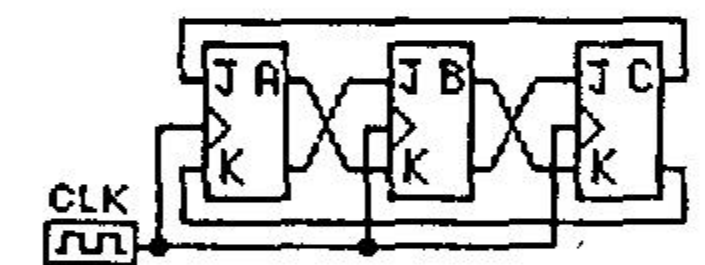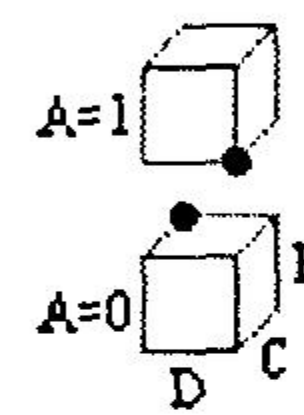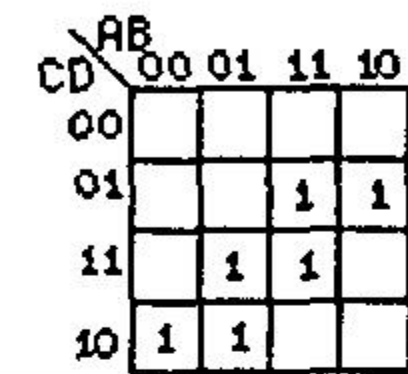- a. Perform the Binary division 101010/110 EXPLICITLY. (No points for answers like $42/6 = 7$)
- b. State the gate(s) that must be included in the realization of the map to ensure Hazard Cover. Explain your answer briefly. No points for the other gates
- c. When will a counter be suicidal? Explain with the aid of a diagram
- d. Calculate the distance between the two numbers shown by heavy dots.
- e. Draw a Debouncer and describe its function
- f. When will a hazard be dynamic?
- g. Draw the circuit of a range detector that tests whether $3 < N < 11$ is satisfied.
- h. Calculate the cycles of the counter given.



Good Luck!

$$2 \times 15 + 10 + 12 + 49 = 101$$

* Bonus 1: How can one use the the Quine-McCluskey method when there are "don't cares"?

* Bonus 2: Show that if the number of functions of N variables is M, then that of (N+1) variables is M^2 .