

1. (10 points) **Answer by TRUE or FALSE.**

- (a) An npn transistor having $V_C = 10V$, $V_B = 1.2V$, and $V_E = 1V$ is in cut-off.

- (b) In the active region, when the collector-emitter voltage increases, the collector current decreases.

- (c) In saturation mode, a BJT has $I_C \leq \beta I_B$.



- (d) The power dissipated by the zener diode is greater when the load current is less.

- (e) Zener regulators are mostly efficient for applications that require low current to the load.

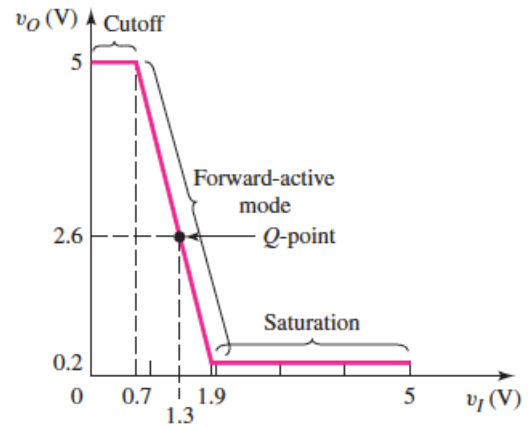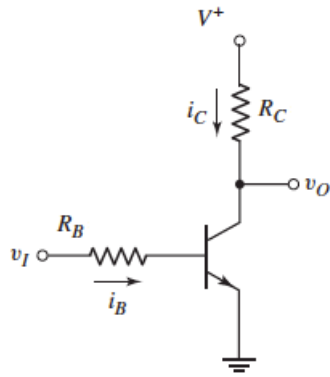2. (15 points) **Transistor Design.**

Consider the simple transistor circuit shown below along with its voltage characteristics.

Let $\beta = 120$ and $I_{C(sat)} = 960\mu A$.




1. (5 pts) What is the transistor's voltage gain?
2. (10 pts) Find R_B and R_C .

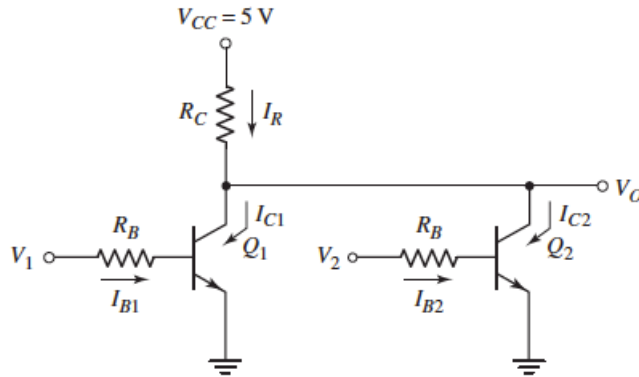3. (25 points) **Digital Gate**

Consider the following two cascaded transistors Q_1 and Q_2 forming a digital logic gate with inputs V_1 and V_2 . Let $R_C = 1k\Omega$ and $R_B = 20k\Omega$.


Assume the transistor parameters are: $\beta = 50$, $V_{BE(on)} = 0.7V$ and $V_{CE(sat)} = 0.2V$. Fill out the following table. What kind of logic gate is that?



Gate Input	$V_0(V)$	$I_R(mA)$	$I_{B1}(mA)$	$I_{C2}(mA)$
$V_1 = 0, V_2 = 0$				
$V_1 = 5, V_2 = 0$				
$V_1 = 0, V_2 = 5$				
$V_1 = 5, V_2 = 5$				

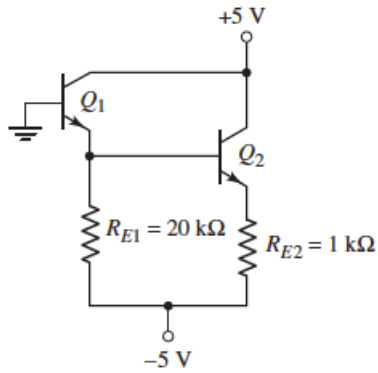
4. (20 points) **Current Gain.**

For each transistor in the following circuit $V_{BE(on)} = 0.7V$, and the current gain is given by β . Find β such that the collector current I_{C1} through Q_1 equals $256\mu A$.



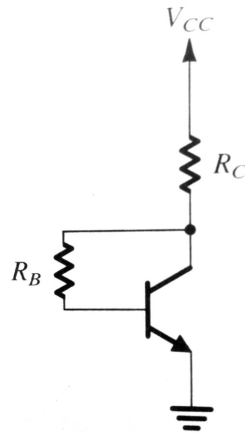
5. (15 points) **Common-Emitter Amplifier Design.**

Design the following circuit to attain an emitter current I_E that is insensitive to variations of β .



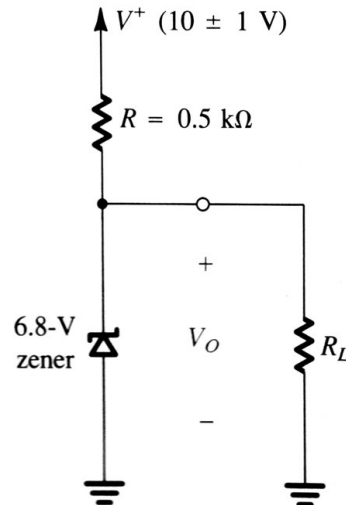6. (15 points) **Zener Circuit.**

The 6.8 V zener diode in the circuit shown below is specified to have $V_Z = 6.8V$ at $I_Z = 5mA$, $R_Z = 20\Omega$, and $I_{ZK} = 0.2mA$. The supply voltage V^+ is nominally 10V but can vary by $\pm 1V$.



1. (5 pts) Find V_0 with no load and with V^+ at its nominal value.
2. (5 pts) Find the change in V_0 resulting from the $\pm 1V$ change in V^+ .
3. (5 pts) Find the minimum value of R_L for which the diode still operates in breakdown region.

Bonus (10 points)

Consider the amplifier below, which amplifies the signal from a sensor with an internal resistance of $1K\Omega$. Assume all capacitances to be of very large values. Given an estimate for the amplification factor A_v .

