

**American University of Beirut
Department of Electrical and Computer
Engineering
EECE 290 – Analog Signal Processing**

Quiz I

**Closed Book
No Programmable Calculators
No Wireless Devices**

**90 minutes
March 11, 2019
Version A**

Name:

Instructor Name:

**Only this question sheet must be
returned.**

AJS

This exam has 11 problems, 50 pts, and 16 pages.

Problem 1(4 pts)

1. Why do we use Laplace transform in electrical circuits?

To transform signal of time domain to frequency domain.

To transform signal of time domain to s-domain.

To facilitate the complex differential calculations.

a and c.

all of the above.

2. If an input signal is applied to the inverting input of an op-amp with the noninverting input grounded, the output signal would have:

Same polarity with the input.

Opposite in polarity with the input.

Neutral polarity since the one of the inputs is grounded.

Cannot be determined without a numerical value of both inputs.

None of the above.

3. Reactive power:

Surges back and forth between electric devices.

It is stored in magnetic and electric fields.

Only occurs when E and I are out of phase.

All of the above

None of the above


4. In the power industry a common practice is to use parallel inductive elements to decrease the power factor just like parallel capacitors are used to increase the PF.

True

False

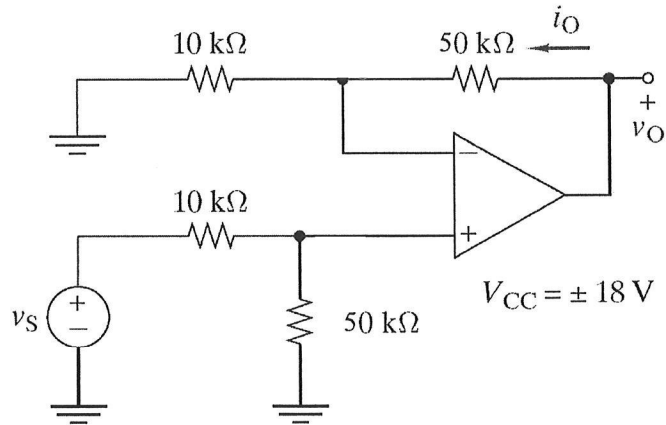Problem 2 (4 pts)


Find i_0 for $v_s = 1$ V. The Op-Amp is operating in its linear mode.



- 0.0333 mA
- 0.1667 mA
- 0.253 mA
- 0.0833 mA
- None of the above (specify your answer)

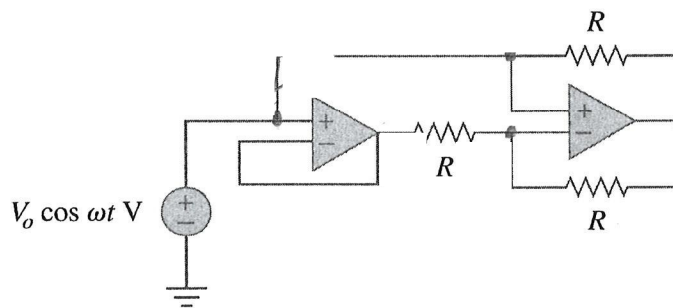Problem 3 (3 pts)


Find the total average power absorbed by the resistors. Both Op-Amp are operating in their linear modes.



- $V_0^2/2R$
- $V_0^2/3R$
- $V_0^2/4R$
- $V_0^2/6R$
- None of the above (specify your answer)

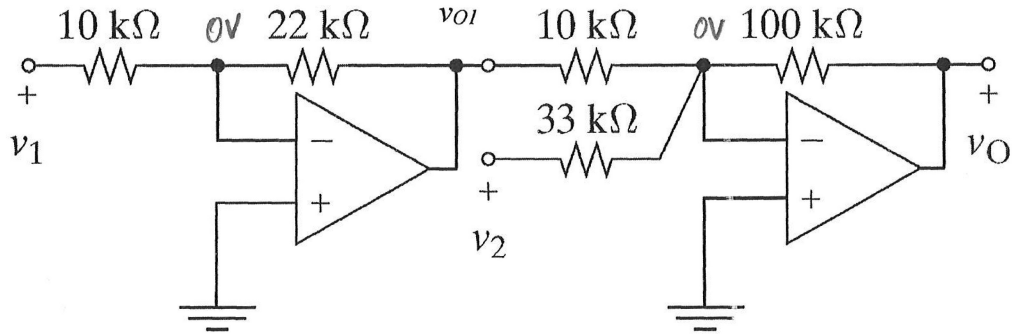Problem 4 (4pts)

Consider the following op-amp circuit where $v_1 = 1\text{ V}$ and $v_2 = 2\text{ V}$



1. Determine the output voltage v_{O1} of the first amplifier. (2pts)

-3.24 V

-1.32 V

-2.2 V

-1.76 V

None of the above (specify your answer)

2. Determine the output voltage v_O of the op-amp circuit. (2 pts)

10.87 V

12.43 V


16.81 V

15.94 V

None of the above (specify your answer)

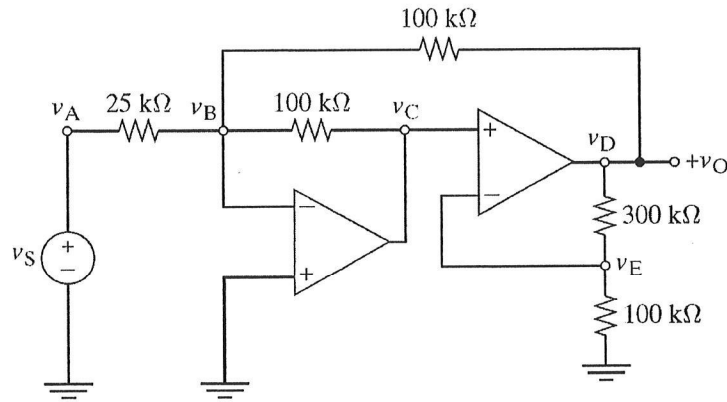Problem 5 (4 pts)

Consider the following op-amp circuit. Both Op-Amp are operating in their linear modes.




1. Determine a relationship between the output voltage v_O and the voltage v_C . (2 pts)

2. Determine the output voltage v_O in terms of v_S . (2 pts)

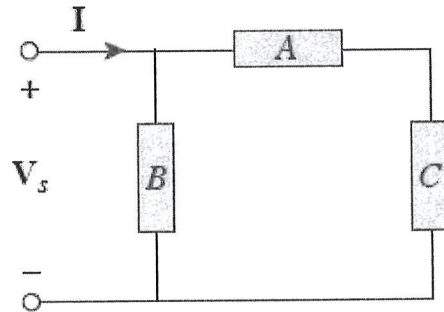Problem 6 (6 pts)

In the circuit shown below, load A receives 4 KVA at 0.8 pf lagging, device B receives 3 kVA at 0.4 pf leading, while device C is inductive and consumes 1 KW and receives 500 VAR.




1. Determine the complex power (S_A, S_B, S_C) received by each load, and the total complex power S_T received by the entire system. (3 pts)

2. Determine the power factor of the entire system. (1 pt)

3. Find \mathbf{I} , given that $\mathbf{V}_s = 240\angle 45^\circ \text{ V (rms)}$. (2 pt)

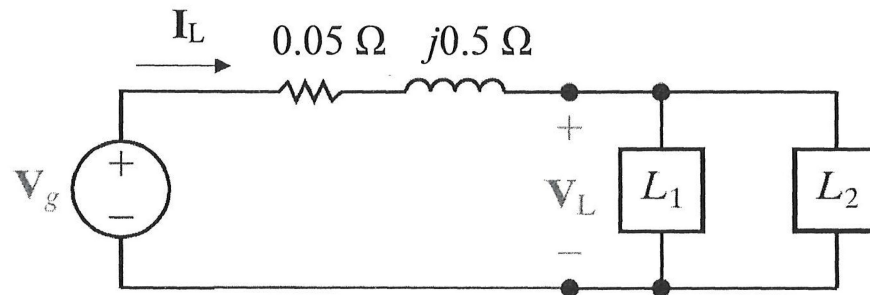Problem 8 4(pts)

Load L_1 absorbs an average power of 10 kW at a 0.9 power factor leading; Load L_2 has an impedance of $60 + j80 \Omega$. The voltage at the terminals of the loads is $1000\sqrt{2} \cos 100\pi t$ V.



1. Find the rms value of the total load current I_L in amperes. (2 pts)

2. Calculate the rms voltage V_g of the source. Does the load voltage lead or lag the source voltage and by how many degrees? What is the active and reactive power supplied by the source? (2 pts)

3. Let $Y(s) = X_1(s) \cdot X_2(s)$. Determine $y(t)$ by the inverse Laplace transform of $Y(s)$. (2 pts)

Problem 10 (4 pts)

The Laplace transform function representing the output voltage of a network is expressed as


$$V_0(s) = \frac{120}{s(s + 10)(s + 20)}$$

1. Determine the value of this voltage at $t = 1$ s. (Hint solve for $v_0(t)$) (3 pts)

2. Find the final value of the voltage without solving for $v_0(t)$. (1 pts)

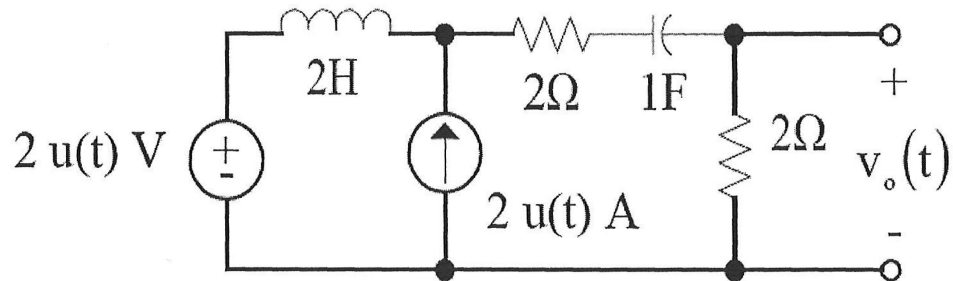Problem 11 (7 pts)

Consider the following circuit diagram where it is required to determine the voltage $v_0(t)$ for $t > 0$, with the initial conditions being zero.



1. Draw the s-domain equivalent circuit (2 pt)

2. Solve for the s-domain voltage $V_0(s)$ (2pts)

3. Obtain a time-domain expression for the voltage $v_0(t)$ (3 pts)

TABLE 12.2 An Abbreviated List of Operational Transforms

Operation	$f(t)$	$F(s)$
Multiplication by a constant	$Kf(t)$	$KF(s)$
Addition/subtraction	$f_1(t) + f_2(t) - f_3(t) + \dots$	$F_1(s) + F_2(s) - F_3(s) + \dots$
First derivative (time)	$\frac{df(t)}{dt}$	$sF(s) - f(0^-)$
Second derivative (time)	$\frac{d^2f(t)}{dt^2}$	$s^2F(s) - sf(0^-) - \frac{df(0^-)}{dt}$
n th derivative (time)	$\frac{d^n f(t)}{dt^n}$	$s^n F(s) - s^{n-1}f(0^-) - s^{n-2}\frac{df(0^-)}{dt} - \dots - \frac{d^{n-1}f(0^-)}{dt^{n-1}}$
Time integral	$\int_0^t f(x) dx$	$\frac{F(s)}{s}$
Translation in time	$f(t-a)u(t-a), a > 0$	$e^{-as}F(s)$
Translation in frequency	$e^{-at}f(t)$	$F(s+a)$
Scale changing	$f(at), a > 0$	$\frac{1}{a}F\left(\frac{s}{a}\right)$
First derivative (s)	$tf(t)$	$-\frac{dF(s)}{ds}$
n th derivative (s)	$t^n f(t)$	$(-1)^n \frac{d^n F(s)}{ds^n}$
s integral	$\frac{f(t)}{t}$	$\int_s^\infty F(u) du$

TABLE 12.1 An Abbreviated List of Laplace Transform Pairs

Type	$f(t)$ ($t > 0^-$)	$F(s)$
(impulse)	$\delta(t)$	1
(step)	$u(t)$	$\frac{1}{s}$
(ramp)	t	$\frac{1}{s^2}$
(exponential)	e^{-at}	$\frac{1}{s + a}$
(sine)	$\sin \omega t$	$\frac{\omega}{s^2 + \omega^2}$
(cosine)	$\cos \omega t$	$\frac{s}{s^2 + \omega^2}$
(damped ramp)	te^{-at}	$\frac{1}{(s + a)^2}$
(damped sine)	$e^{-at} \sin \omega t$	$\frac{\omega}{(s + a)^2 + \omega^2}$
(damped cosine)	$e^{-at} \cos \omega t$	$\frac{s + a}{(s + a)^2 + \omega^2}$

TABLE 12.3 Four Useful Transform Pairs

Pair Number	Nature of Roots	$F(s)$	$f(t)$
1	Distinct real	$\frac{K}{s + a}$	$Ke^{-at}u(t)$
2	Repeated real	$\frac{K}{(s + a)^2}$	$Kte^{-at}u(t)$
3	Distinct complex	$\frac{K}{s + \alpha - j\beta} + \frac{K^*}{s + \alpha + j\beta}$	$2 K e^{-\alpha t} \cos(\beta t + \theta)u(t)$
4	Repeated complex	$\frac{K}{(s + \alpha - j\beta)^2} + \frac{K^*}{(s + \alpha + j\beta)^2}$	$2t K e^{-\alpha t} \cos(\beta t + \theta)u(t)$

Note: In pairs 1 and 2, K is a real quantity, whereas in pairs 3 and 4, K is the complex quantity $|K| \angle \theta$.