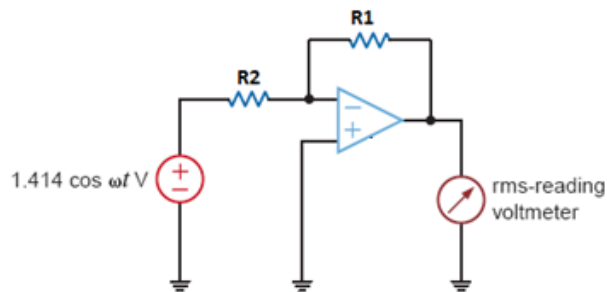


**American University of Beirut**  
**Department of Electrical and Computer Engineering**  
**EECE 290 – Analog Signal Processing**  
**Quiz I – Solution**

**Problem 1(4 pts)**

An rms-reading voltmeter is connected to the output of the op-amp shown below. The Op-Amp is operating in its linear mode. Determine the meter reading.




$V_p = 0 = V_n$ . Writing Nodal equation at the negative terminal of the op-Amp, we obtain

$$\frac{0 - V_{in}}{R_2} + \frac{0 - V_o}{R_1} = 0 \text{ and } V_o = -\frac{R_1}{R_2} V_{in}$$

- a. If  $R_1=36 \text{ k}\Omega, R_2=12\text{k}\Omega$ , and  $V_{in}=1.414\angle 00$  Volts, then  $V_o=3*\sqrt{2}\angle 180^0$  Volts and rms Value = 3 Volts
- b. If  $R_1=24 \text{ k}\Omega, R_2=6 \text{ K}\Omega$ , and  $V_{in}=1.414\angle 00$  Volts, then  $V_o=4*\sqrt{2}\angle 180^0$  Volts and rms Value = 4 Volts
- c. If  $R_1=12 \text{ k}\Omega, R_2=2 \text{ K}\Omega$ , and  $V_{in}=1.414\angle 00$  Volts, then  $V_o=6*\sqrt{2}\angle 180^0$  Volts and rms Value = 6 Volts

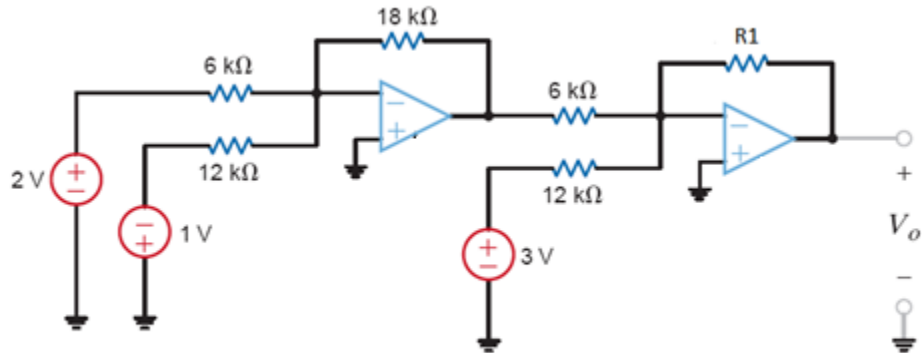**Problem 2 (4 pts)**

Determine the output voltage  $V_o$  of the summing op-amp circuit shown below. Both op-amps are operating in their linear modes.



For the left Op-Amp:  $V_p = 0 = V_n$ . Writing Nodal equation at the negative terminal of the op-Amp, we obtain

$$\frac{0-2}{6,000} + \frac{0+1}{12,000} + \frac{0-V_1}{18,000} = 0$$

Solve, we obtain  $V_1 = -4.5$  Volts.

For the right Op-Amp,  $V_p = 0 = V_n$ . Writing Nodal equation at the negative terminal of the op-Amp, we obtain


$$\frac{0+4.5}{6,000} + \frac{0-3}{12,000} + \frac{0-V_o}{R_1} = 0$$

Solve, we obtain  $V_o = 0.5 * 10^{-3} * R_1$

- For  $R_1 = 36 \text{ K}\Omega$ ,  $V_o = 18$  Volts
- For  $R_1 = 18 \text{ K}\Omega$ ,  $V_o = 9$  Volts
- For  $R_1 = 9 \text{ K}\Omega$ ,  $V_o = 4.5$  Volts

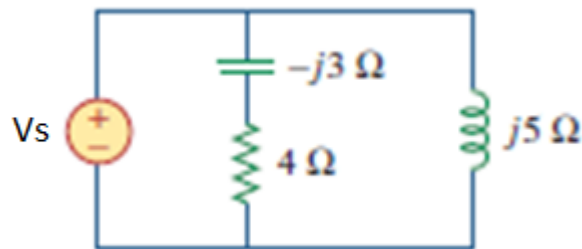**Problem 3 (4 pts)**


Find the complex power delivered by voltage source if  $V_s = x \angle y^\circ V$



- a. If  $V_s = 8 \angle -20^\circ V$ , then  $S = 11.456 \angle 26.58^\circ VA$
- b. If  $V_s = 16 \angle -20^\circ V$ , then  $S = 45.82 \angle 26.58^\circ VA$
- c. If  $V_s = 24 \angle -20^\circ V$ , then  $S = 103.1 \angle 26.58^\circ VA$

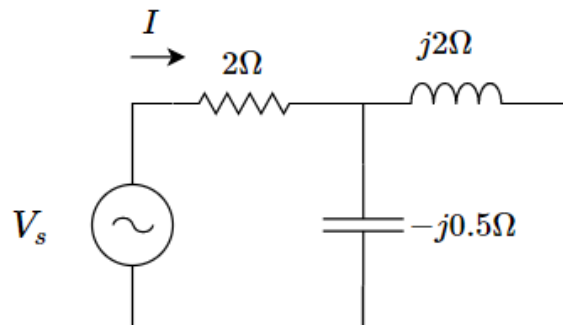**Problem 4 (4 pts)**


For the given circuit, determine the complex power delivered by the voltage source if  $V_s = K V RMS$  is:



- a. If  $V_s = 10 V rms$ , then  $S = (45 - j15) VA$
- b. If  $V_s = 20 V rms$ ,  $S = (180 - j60) VA$
- c. If  $V_s = 30 V rms$ , then  $S = (405 - j135) VA$
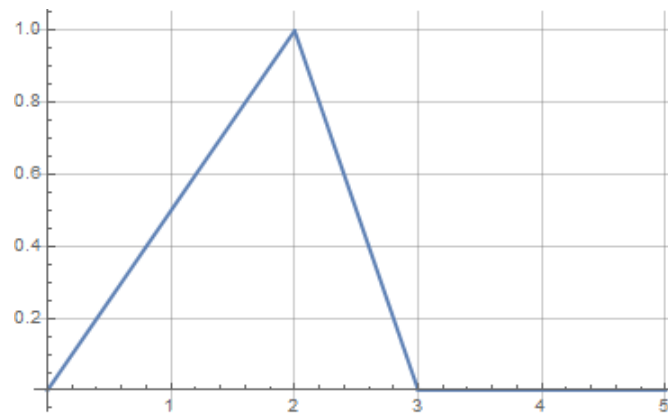
### **Problem 5 (4 pts) – Solution to Version A**

Find the Laplace Transform of the function shown below



$$f(t) = (0.5t)[u(t)-u(t-2)] + (-t+3)[u(t-2)-u(t-3)]$$

$$\begin{aligned} \frac{df(t)}{dt} &= \frac{1}{2}[u(t) - u(t-2)] + (0.5t)[\delta(t) - \delta(t-2)] - [u(t-2) - u(t-3)] \\ &\quad + (-t+3)[\delta(t-2) - \delta(t-3)] \end{aligned}$$

$$\frac{df(t)}{dt} = \frac{1}{2}[u(t) - u(t-2)] - \delta(t-2) - [u(t-2) - u(t-3)] + \delta(t-2)$$

$$\frac{df(t)}{dt} = \frac{1}{2}u(t) - \frac{3}{2}u(t-2) + u(t-3)$$

The Laplace Transform of the derivative of  $f(t)$  is :

$$sF(s) = \frac{1}{2s} - \frac{3}{2s}e^{-2s} + \frac{1}{s}e^{-2s}$$

Therefore,

$$F(s) = \frac{1}{2s^2} - \frac{3e^{-3s}}{2s^2} + \frac{e^{-3s}}{s^2}$$

**Problem 6 (4 pts)**

The Laplace transform function for the output voltage of a network is expressed in the following form:

$$V_o(s) = \frac{12(s + 2)}{s(s + 1)(s + 3)(s + 4)}$$


Determine the final value of this voltage that is,  $v_o(t)$  as  $t \rightarrow \infty$ .

The final value theorem states that the limit of  $v_o(t)$  as  $t \rightarrow \infty$  is the limit of  $sV_o(s)$  as  $s$  goes to zero provided that  $sV_o(s)$  has no poles either in the rhp nor on the  $j\omega$  axis


As  $sV_o(s)$  satisfies the above criterion, than the limit  $v_o(t)$  as  $t \rightarrow \infty$  is 2 V.

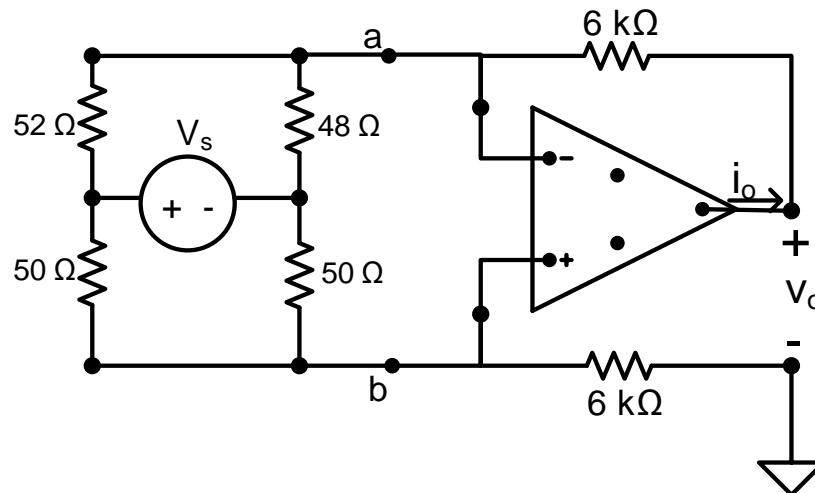**Problem 7 (10 pts)**


Assume that the Op-Amp operates in the linear region.  $V_s = \text{---- V}$



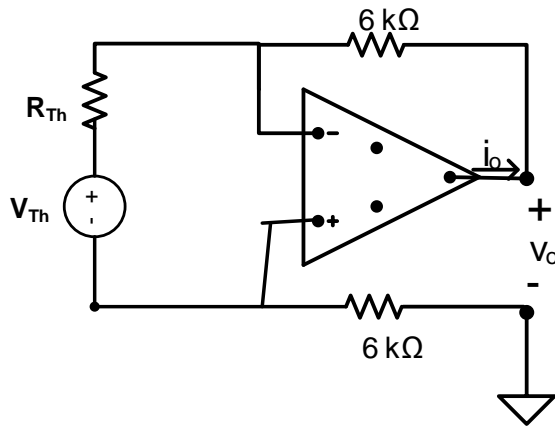1. Replace the circuit left of the nodes a-b with a Thevenin equivalent circuit. Draw the new circuit completely. (2 pts)



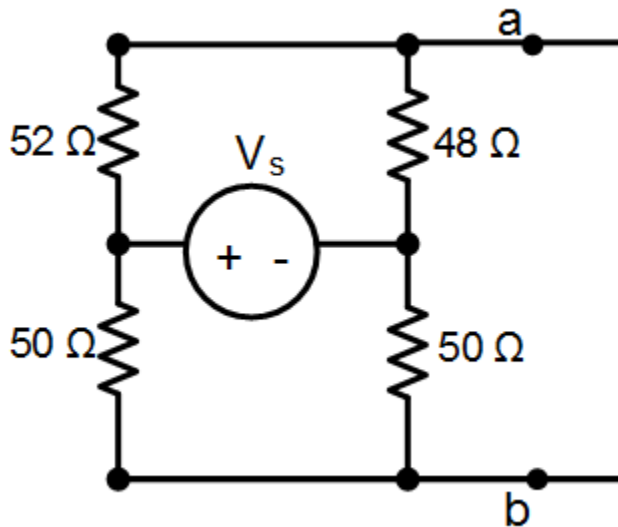2. Find the values of  $V_{Th}$  and  $R_{Th}$ . (4 pts)



If you ground the negative terminal of the voltage, and apply nodal equations at node a, we obtain

$$\frac{V_a - V_s}{52} + \frac{V_a}{48} = 0$$

The above implies,

$$V_a = \frac{48}{100} V_s$$

Applying nodal equations at node b, we obtain

$$\frac{V_b - V_s}{50} + \frac{V_b}{50} = 0$$

The above implies,

$$V_b = \frac{50}{100} V_s$$

$$V_{Th} = V_a - V_b = \frac{48-50}{100} V_s = -0.2V_s \text{ Volts}$$

And

$$R_{Th} = 48 // 52 + (50 // 50) = 49.96 \Omega$$

3. Find the value of  $i_o$ . (2 pts)

$$V_p = 0 = V_n$$

The current entering  $R_{Th}$  is the current  $i_o$  and found to be

Applying nodal equation at the negative terminal of the op-Amp, we obtain


$$i_o \frac{0 - V_{Th}}{R_{Th}} = \frac{-0.2V_s}{49.96}$$

4. Find the value of  $v_o$ . (2 pts)

$$i_o = \frac{V_o}{6 * 10^3} = \frac{-0.2V_s}{(49.96)(6 * 10^3)}$$

### Problem 8 (8 pts)

Given the network below:

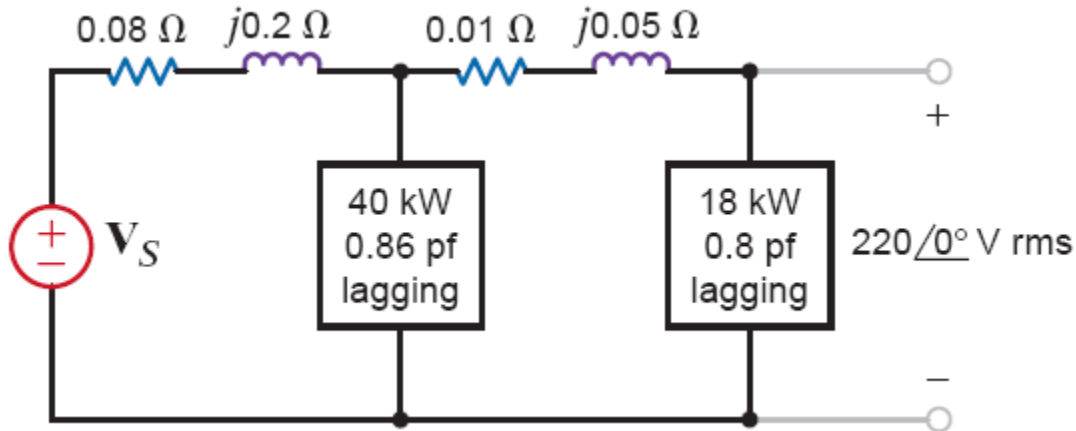

1. Find the current in the 18Kw load. (2 pts)

$$I_2 = \frac{P_2}{V_2 P_{f2}} = 102.3 \angle -36.86^\circ \text{ A (rms)}$$

The above equation is obtained based on the following facts:

$$p_f = \frac{P}{|S|} = \frac{P}{|V * I^*|} = \frac{P}{|V||I^*|} \xrightarrow{\text{yields}} |I| = |I^*| = \frac{P}{|V|P_f} = \frac{18000}{220 * 0.8} = 102.27$$

The angle of the current lags the angle of the voltage by an angle whose cosine is 0.8. Therefore the angle is  $36.86^\circ$

2. Find the current in the 40 KW Load. (2 pts)

Let  $V_1$  be the voltage across the 40 KW load. Using KVL in the right loop, we obtain

$$V_1 = (0.01 + j0.05)I_2 + V_2 = 223.91 \angle 0.8^\circ \text{ Volts (rms)}$$

Similar to the above,

$$I_1 = 207.7 \angle -30.68^\circ \text{ A (rms)}$$



3. Compute the input source voltage. (2 pts)

Using KCL, the current  $I_s$  flowing out of the source  $V_s$  is given by:

$$I_s = I_1 + I_2 = 309.6 \angle -32.7^\circ \text{ Volts (rms)}$$

4. Compute the input power factor. Is it leading or Lagging? (2 pts)


Using KVL in the left loop, we obtain

$$V_a = (0.08 + j0.2)I_s + V_1 = 281 \angle 8.62^\circ \text{ Volts (rms)}$$


$$P_f = \cos(\theta_{V_s} - \theta_{I_s}) = \cos(8.62 + 32.7) = 0.751 \text{ lagging}$$

### **Problem 9 (8 pts)**

Consider the circuit shown below.

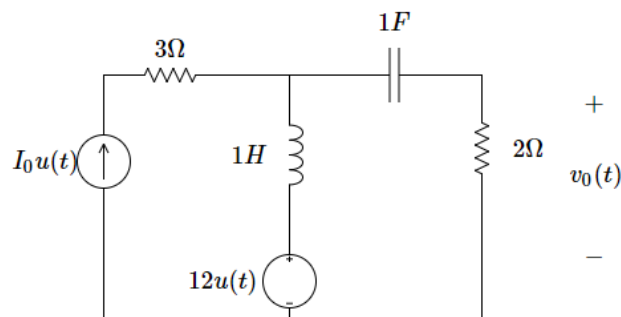

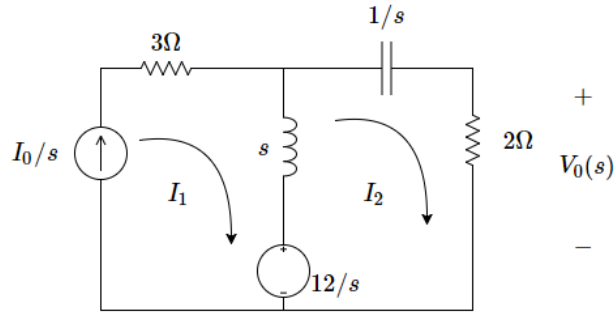Laplace transform, for zero Initial conditions, was used to convert the circuit to s-domain. The following is obtained



- a. Write mesh equation for the second mesh  $I_2(s)$ . Do not simplify. (2 pts)

$$-\frac{12}{s} + s \left( I_2(s) - \frac{I_0}{s} \right) + I_2(s) \left( \frac{1}{s} + 2 \right) = 0$$

- b. Write  $I_2(s)$  in fractional format. (2 pts)

$$I_2(s) = \frac{sI_0 + 12}{s^2 + 2s + 1}$$

- c. For  $I_0=1A$ , Determine  $v_0(t)$ . (4 pts)

$$V_0(s) = 2I_2(s) = \frac{2I_0s + 24}{s^2 + 2s + 1} = 2I_0 \frac{s}{(s+1)^2} + 24 \frac{1}{(s+1)^2}$$

$$\frac{1}{(s+1)^2} \xrightarrow{\text{yields}} te^{-t}u(t)$$

$$\frac{s}{(s+1)^2} \xrightarrow{\text{yields}} \frac{d}{dt} (te^{-t}u(t)) = (e^{-t} - te^{-1})u(t)$$

Therefore,

$$v_0(t) = 2I_0(e^{-t} - te^{-1})u(t) + 24te^{-t}u(t) \text{ Volts}$$