

**American University of Beirut
Department of Electrical and Computer Engineering
EECE 290 – Analog Signal Processing**

Quiz II

**Open Book and Notes
No Programmable Calculators
No Wireless Devices**

**90 minutes
April 10, 2018**

Name: _____

Instructor Name: _____


This question sheet must only be returned.

This exam has 12 problems, 50 pts, and 8 pages.

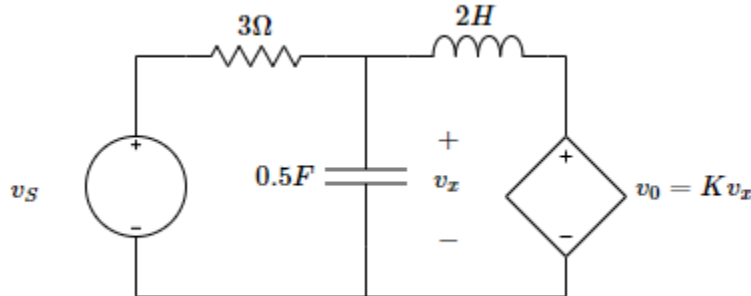Problem 1(4 pts)

Assume zero initial conditions for the inductance and for the capacitor. Find the transfer function


$H(s) = \frac{V_o(s)}{V_s(s)}$ of the circuit below for $K=0.5, 1, 3$



Version a	Version b	Version c
a. $H(s) = \frac{s}{3s^2+2s+4.5}$	a. $H(s) = \frac{s}{3s^2+2s+1.5}$	a. $H(s) = \frac{s}{3s^2+2s+1.5}$
b. $H(s) = \frac{1}{3s+1}$	b. $H(s) = \frac{1}{3s+1}$	b. $H(s) = \frac{1}{3s+1}$
c. $H(s) = \frac{2s}{3s^2+2s+6}$	c. $H(s) = \frac{2s}{3s^2+2s+6}$	c. $H(s) = \frac{2s}{3s^2+2s+6}$
d. $H(s) = \frac{6s}{3s^2+2s+12}$	d. $H(s) = \frac{6s}{3s^2+2s+12}$	d. $H(s) = \frac{6s}{3s^2+2s+12}$
e. None of the above	e. None of the above	e. None of the above

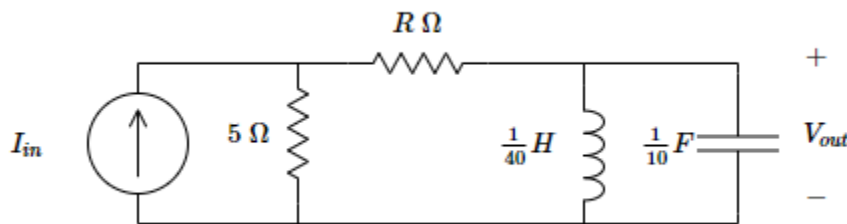Problem 2 (4 pts)

For the circuit shown below, let $I_{in}(s)$ be the input and $V_{out}(s)$ be the output. Determine the system transfer function $H(s) = \frac{V_{out}(s)}{I_{in}(s)}$ for $R=5, 10, 15 \Omega$, assuming zero initial conditions for both the inductor and capacitor.




(Hint: Convert the current source to a voltage source and back to a current source)

Version a	Version b	Version c
a. $\frac{V_{out}(s)}{I_{in}(s)} = \frac{50s}{15s^2+10s+6000}$	a. $\frac{V_{out}(s)}{I_{in}(s)} = \frac{50s}{10s^2+10s+4000}$	a. $\frac{V_{out}(s)}{I_{in}(s)} = \frac{50s}{20s^2+10s+8000}$
b. $\frac{V_{out}(s)}{I_{in}(s)} = \frac{50s}{10s^2+10s+4000}$	b. $\frac{V_{out}(s)}{I_{in}(s)} = \frac{50s}{20s^2+10s+8000}$	b. $\frac{V_{out}(s)}{I_{in}(s)} = \frac{50s}{10s^2+10s+4000}$

c. $\frac{V_{out}(s)}{I_{in}(s)} = \frac{50s}{20s^2+10s+8000}$	c. $\frac{V_{out}(s)}{I_{in}(s)} = \frac{50s}{25s^2+100s+1000}$	c. $\frac{V_{out}(s)}{I_{in}(s)} = \frac{50s}{15s^2+10s+6000}$
d. $\frac{V_{out}(s)}{I_{in}(s)} = \frac{50s}{25s^2+100s+1000}$	d. $\frac{V_{out}(s)}{I_{in}(s)} = \frac{50s}{15s^2+10s+6000}$	d. $\frac{V_{out}(s)}{I_{in}(s)} = \frac{50s}{25s^2+100s+1000}$
e. None of the above	e. None of the above	e. None of the above

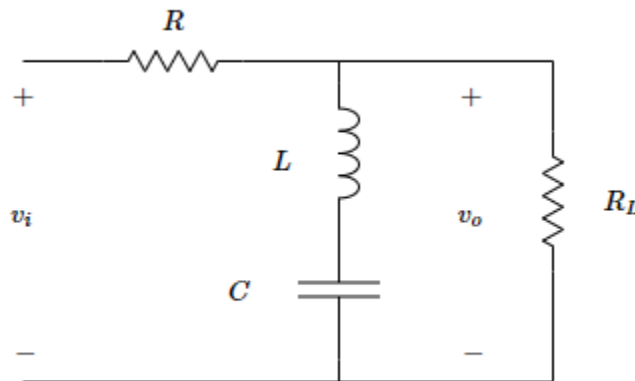
Problem 4 (4 pts)

If $R = \{10, 20, 30\} \Omega$, $L = 1 \mu F$, $C = 4 \text{ pF}$. Find the quality factor of the filter



Version a	Version b	Version c
a. $Q = 25 \left(1 + \frac{20}{R_L}\right)$	a. $Q = 50 \left(1 + \frac{10}{R_L}\right)$	a. $Q = 50 \left(1 + \frac{10}{R_L}\right)$
b. $Q = \frac{50}{3} \left(1 + \frac{30}{R_L}\right)$	b. $Q = 25 \left(1 + \frac{20}{R_L}\right)$	b. $Q = 25 \left(1 + \frac{20}{R_L}\right)$
c. $Q = \frac{50}{4} \left(1 + \frac{40}{R_L}\right)$	c. $Q = \frac{50}{3} \left(1 + \frac{30}{R_L}\right)$	c. $Q = \frac{50}{3} \left(1 + \frac{30}{R_L}\right)$
d. $Q = 50 \left(1 + \frac{10}{R_L}\right)$	d. $Q = \frac{50}{4} \left(1 + \frac{40}{R_L}\right)$	d. $Q = \frac{50}{4} \left(1 + \frac{40}{R_L}\right)$
e. None of the above	e. None of the above	e. None of the above

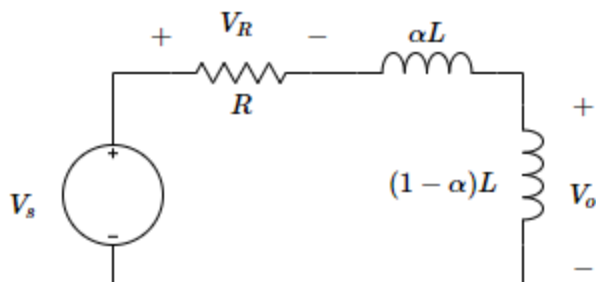The following figure represents the circuit to be used to solve Problem 5, 6 and 7. Note that $\alpha = 0.4, 0.6, 0.8$



Problem 5 (4 pts)

What is the transfer function of V_R/V_s ? What is the cutoff frequency?

Version a	Version b	Version c
a. $H(j\omega) = \frac{\alpha}{R+j\omega L}, \omega_c = \frac{L}{R}$	a. $H(j\omega) = \frac{\alpha}{R+j\omega L}, \omega_c = \frac{L}{R}$	a. $H(j\omega) = \frac{R}{R+j\omega L}, \omega_c = \frac{L}{R}$
b. $H(j\omega) = \frac{\alpha R}{R+j\omega L}, \omega_c = \frac{\alpha L}{R}$	b. $H(j\omega) = \frac{\alpha R}{R+j\omega L}, \omega_c = \frac{\alpha L}{R}$	b. $H(j\omega) = \frac{\alpha}{R+j\omega L}, \omega_c = \frac{\alpha L}{R}$
c. $H(j\omega) = \frac{R}{R+j\omega L}, \omega_c = \frac{L}{R}$	c. $H(j\omega) = \frac{R}{R+j\alpha\omega L}, \omega_c = \frac{\alpha L}{R}$	c. $H(j\omega) = \frac{\alpha R}{R+j\omega L}, \omega_c = \frac{\alpha L}{R}$
d. $H(j\omega) = \frac{R}{R+j\alpha\omega L}, \omega_c = \frac{\alpha L}{R}$	d. $H(j\omega) = \frac{R}{R+j\omega L}, \omega_c = \frac{L}{R}$	d. $H(j\omega) = \frac{R}{R+j\alpha\omega L}, \omega_c = \frac{L}{R}$
e. None of the above	e. None of the above	e. None of the above

Problem 6 (4 pts)

What is the transfer function of V_o/V_s ?

Version a	Version b	Version c
a. $H(j\omega) = \frac{\alpha j\omega L}{R+j\alpha\omega L}$	a. $H(j\omega) = \frac{(1-\alpha)j\omega L}{R+j\omega L}$	a. $H(j\omega) = \frac{\alpha j\omega L}{R+j\alpha\omega L}$
b. $H(j\omega) = \frac{(1-\alpha)j\omega L}{R+j(1-\alpha)\omega L}$	b. $H(j\omega) = \frac{\alpha j\omega L}{R+j\alpha\omega L}$	b. $H(j\omega) = \frac{(1-\alpha)j\omega L}{R+j\omega L}$
c. $H(j\omega) = \frac{\alpha j\omega L}{R+j\omega L}$	c. $H(j\omega) = \frac{(1-\alpha)j\omega L}{R+j(1-\alpha)\omega L}$	c. $H(j\omega) = \frac{(1-\alpha)j\omega L}{R+j(1-\alpha)\omega L}$
d. $H(j\omega) = \frac{(1-\alpha)j\omega L}{R+j\omega L}$	d. $H(j\omega) = \frac{\alpha j\omega L}{R+j\omega L}$	d. $H(j\omega) = \frac{\alpha j\omega L}{R+j\omega L}$
e. None of the above	e. None of the above	e. None of the above


Problem 7 (2 pts)

What is the gain of V_o/V_s at the cutoff frequency?

Version a	Version b	Version c
a. $0.6/\sqrt{2}$	a. $0.6/\sqrt{2}$	a. 0.2
b. $0.4/\sqrt{2}$	b. $0.4/\sqrt{2}$	b. $0.8/\sqrt{2}$
c. $1/\sqrt{2}$	c. $1/\sqrt{2}$	c. $0.2/\sqrt{2}$
d. 0.6	d. 0.4	d. $1/\sqrt{2}$
e. None of the above	e. None of the above	e. None of the above

The following figure represents the circuit to be used to solve Problem 8, 9 and 10.

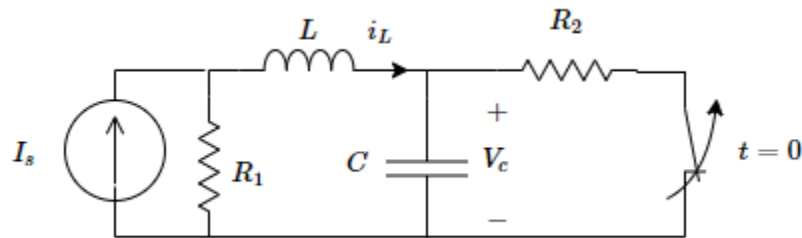If $I_s = \{3, 6, 9\}$ A, $R_1=6 \Omega$, $R_2=12 \Omega$, $L= 3$ H, $C= 1$ F. The switch opens at $t=0$, after having been closed for a long time.



Problem 8 (2 pts)

What is the value of $i_L(0^+)$?

Version a	Version b	Version c
a. 2 A	a. 1 A	a. 1 A
b. 1 A	b. 3 A	b. 2 A
c. 3 A	c. 2 A	c. 4 A
d. 4 A	d. 4 A	d. 3 A
e. None of the above	e. None of the above	e. None of the above

Problem 9 (2 pts)

What is the value of $v_C(0^+)$?

Version a	Version b	Version c
a. 9 V	a. 9 V	a. 36 V
b. 36 V	b. 24 V	b. 9 V
c. 12 V	c. 36 V	c. 12 V
d. 24 V	d. 12 V	d. 24 V
e. None of the above	e. None of the above	e. None of the above


Problem 10 (4 pts)

What is the expression for $I_L(s)$?

Version a	Version b	Version c
a. $\frac{6s+12}{3s^2+6s+1}$	a. $\frac{6s+12}{3s^2+6s+1}$	a. $\frac{3s+6}{3s^2+6s+1}$
b. $\frac{3s^2+6s+1}{9s+18}$	b. $\frac{3s^2+6s+1}{9s+18}$	b. $\frac{3s^2+6s+1}{9s+18}$
c. $\frac{3s^2+6s+1}{s+2}$	c. $\frac{3s^2+6s+1}{s+2}$	c. $\frac{3s^2+6s+1}{s+2}$
d. $\frac{3s^2+6s+1}{s+2}$	d. $\frac{3s^2+6s+1}{s+2}$	d. $\frac{3s^2+6s+1}{s+2}$
e. None of the above	e. None of the above	e. None of the above

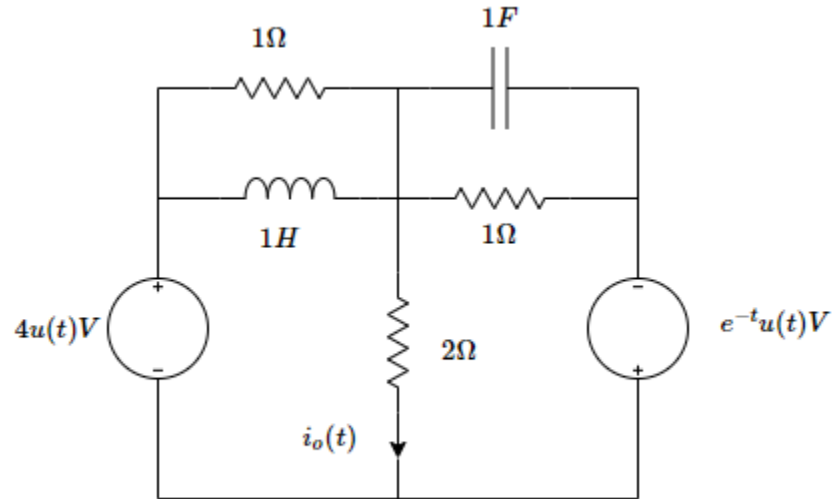Problem 11 (10 pts)

Consider the circuit shown below (initial conditions for the inductor and capacitor are zero).




1. Determine the s -domain representation of this circuit and re-draw the circuit (3pts)

2. Find $I_o(s)$, clearly and neatly show your work (4pts)

3. Deduce $i_o(t)$ flowing in the $2\ \Omega$ resistor (3 points)

Problem 12 (10 pts)

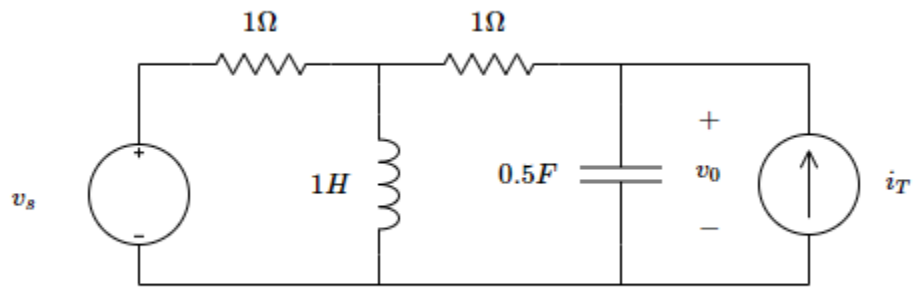

It is required to find $v_0(t)$ when the voltage and current source are respectively given by: $v_s(t) = K_1 u(t)$ and $i_T(t) = K_2 \delta(t)$. Assume no initial conditions on the capacitor and inductor