


Review for quiz 2

# Transfer functions

- Ratio of output quantity (V or I) to input quantity (V or I source) in s-domain:  $H(s)$
- If input is  $G(s)$ , then output is  $F(s)=H(s)G(s)$  (multiplication)
- ILT of  $H(s)$  is impulse response  $h(t)$ .
- If the input is  $g(t)$ , then the output is  $f(t)=h(t)*g(t)$  (convolution).






$$I_L(s)/I_S(s)=4/(s+4)$$
$$i_S(t)=\delta(t), i_L(t)= ?$$

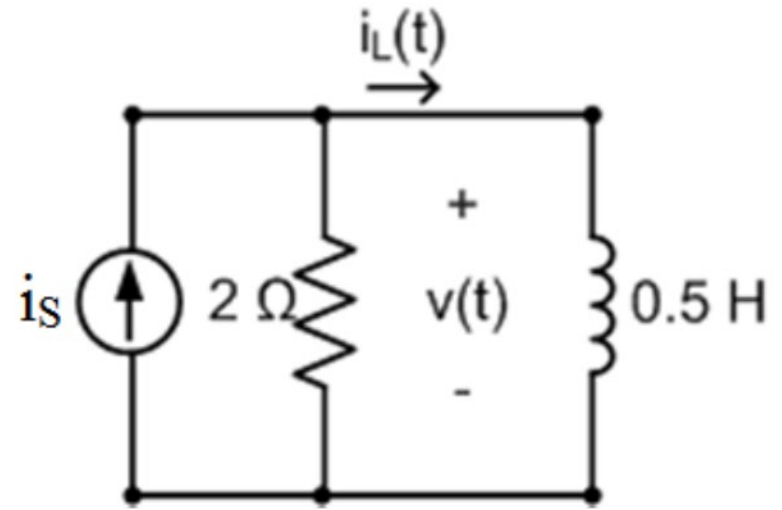- a. 12 A
- b. 6 A
- c.  $8 e^{-4t}$  A
- d.  $e^{-4t}$  A
- e.  $4 e^{-4t}$  A





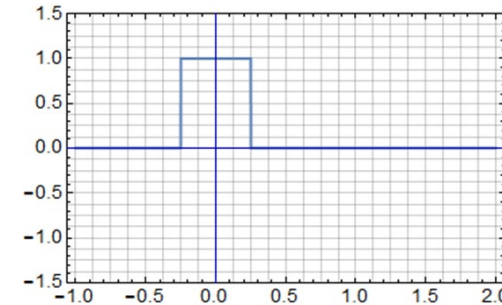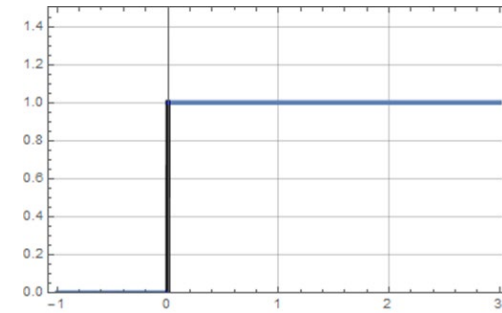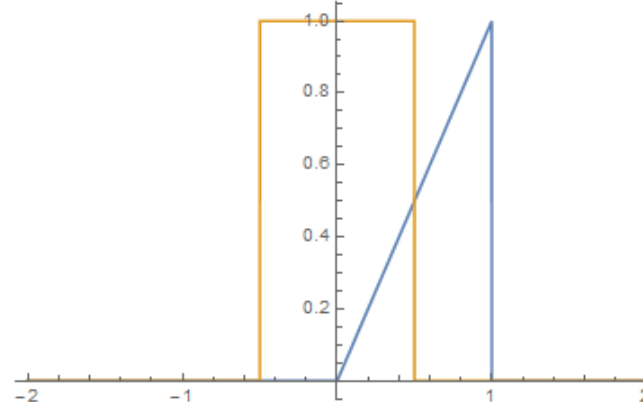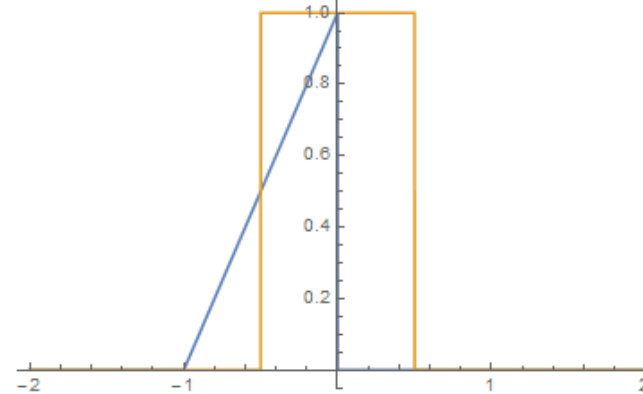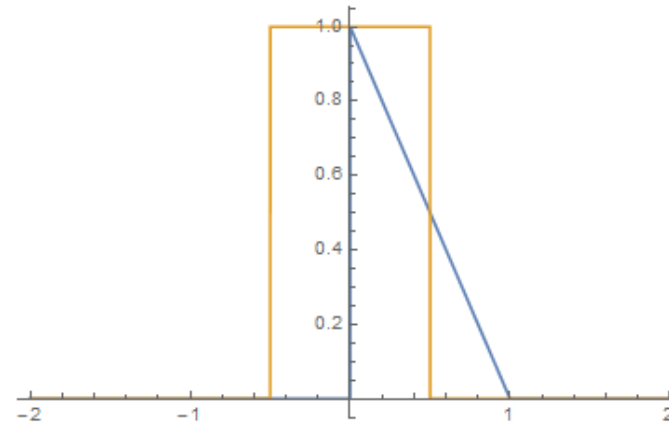
# Convolution



- Given  $g(t)$  and  $h(t)$
- $f = g * h = \int_{-\infty}^{\infty} g(\lambda) h(t - \lambda) d\lambda$
- Properties
  - Commutative
  - Associative
  - Distributive






A.  
B.  
C.

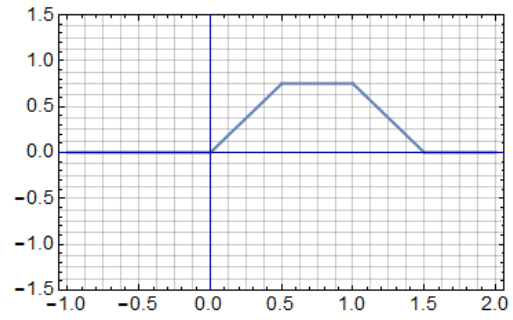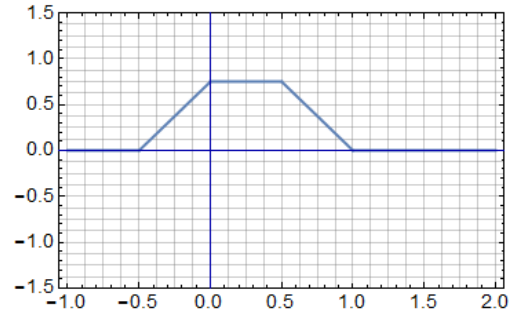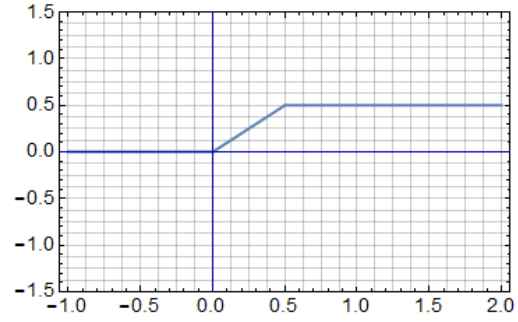


Convolve

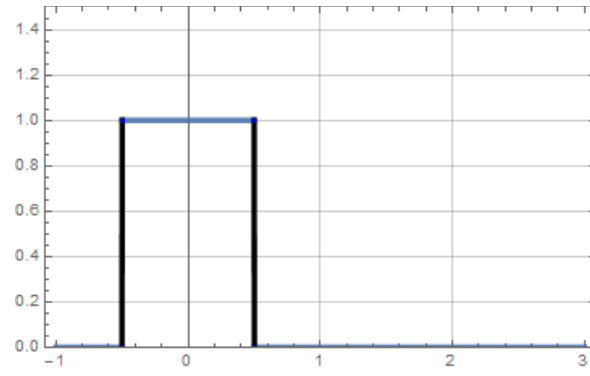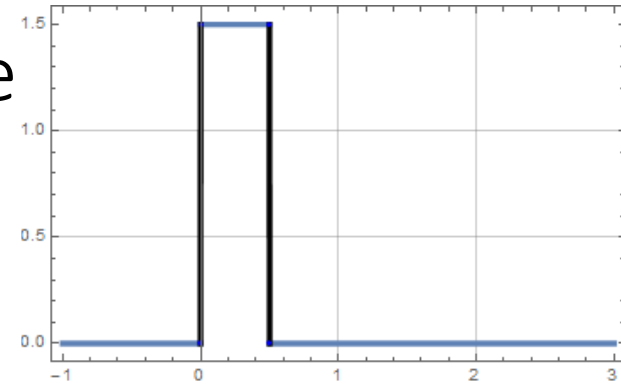

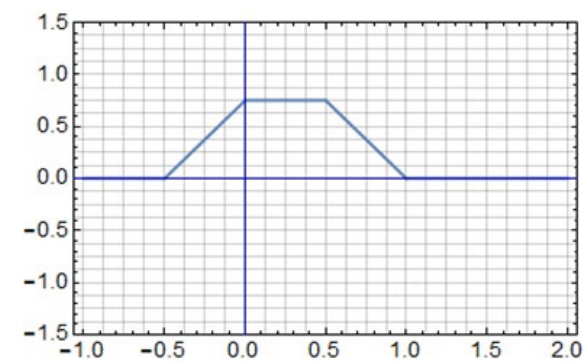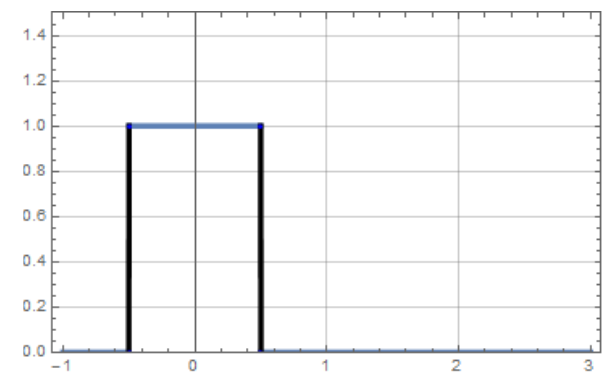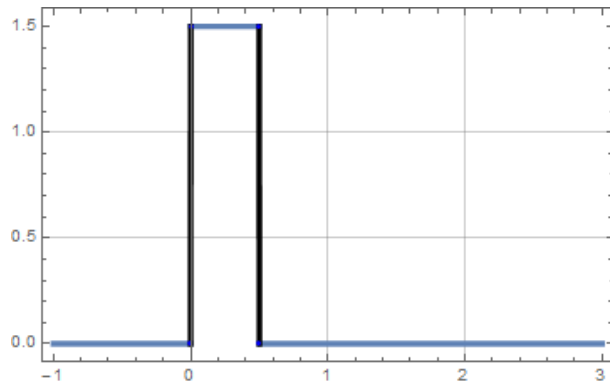


$t \ll -1/2$	$0$	
$-1/2 \leq t \leq 0$	$\int_0^{t+1/2} 1.5 \times 1 d\lambda = \frac{3}{2}t + \frac{3}{4}$	
$0 \leq t \leq 1/2$	$\int_0^{1/2} 1.5 \times 1 d\lambda = \frac{3}{4}$	
$1/2 \leq t \leq 1$	$\int_{t-1/2}^{1/2} 1.5 \times 1 d\lambda = -\frac{3}{2}t + \frac{3}{2}$	
$1 \leq t$	$0$	

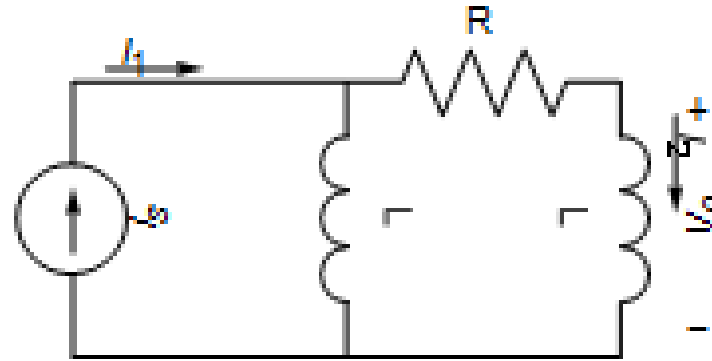$H(j\omega) = I_2/I_s$ ,  $R = 1 \text{ k}\Omega$ ,  
 $L = 0.5 \text{ mH}$ . The half  
power angular cut-off  
frequency  $\omega_c$  is



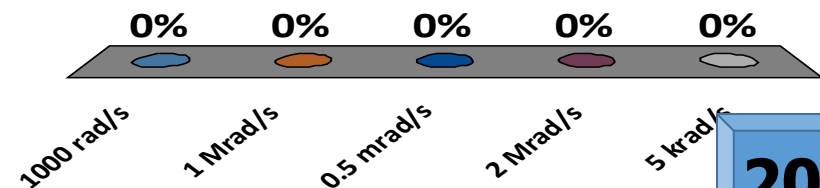- A. 1000 rad/s
- B. 1 Mrad/s
- C. 0.5 mrad/s
- D. 2 Mrad/s
- E. 5 krad/s



# Frequency responses: low pass, band pass, high pass, band stop

## first order: high pass or low pass


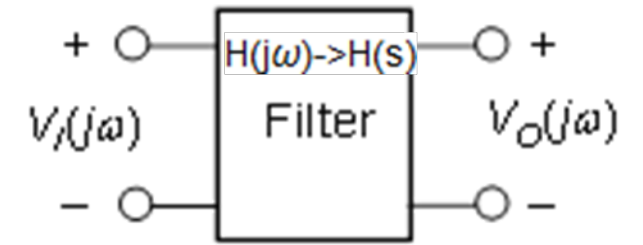
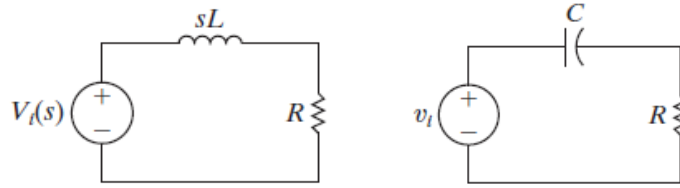
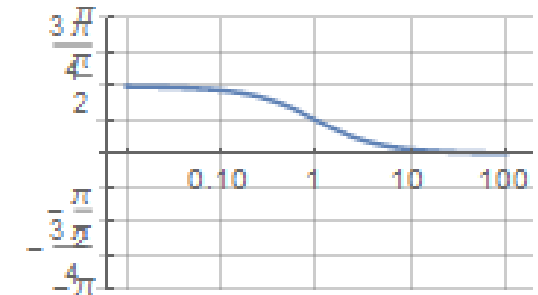


Figure 14.1.1

$$H(j\omega) = \frac{R}{R + 1/j\omega C} = \frac{j\omega RC}{j\omega RC + 1} = \frac{j\omega/\omega_c}{j\omega/\omega_c + 1}$$


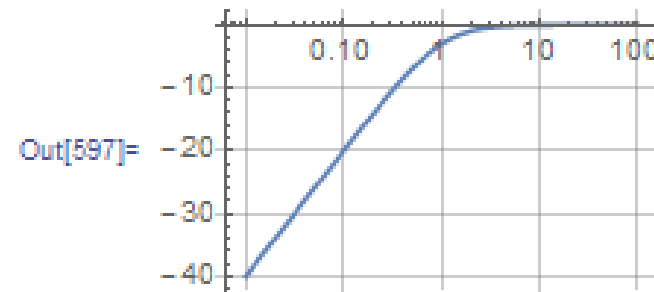
$$H(j\omega) = \frac{j\omega L}{R + j\omega L} = \frac{j\omega L/R}{j\omega L/R + 1} = \frac{j\omega/\omega_c}{j\omega/\omega_c + 1}$$



$$\omega_c = 1/\tau = 1/RC \text{ or } 1/GL = R/L$$

$$H(j\omega) = \frac{1/j\omega C}{R + 1/j\omega C} = \frac{1}{j\omega RC + 1} = \frac{1}{j\omega/\omega_c + 1}$$
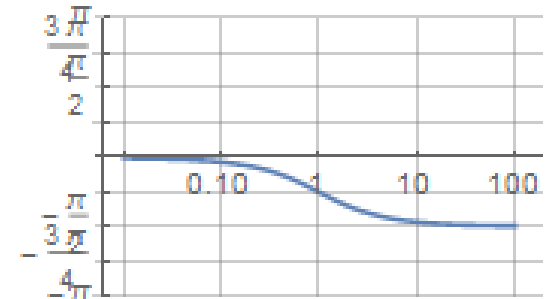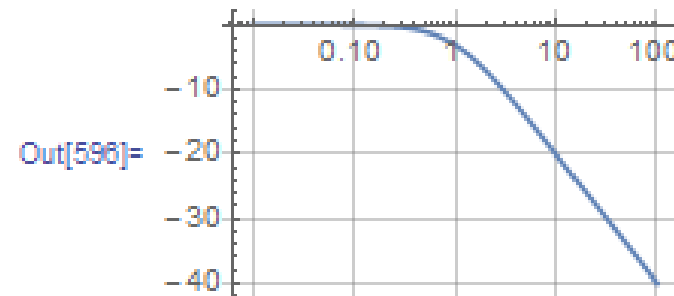
$$H(j\omega) = \frac{R}{R + j\omega L} = \frac{1}{j\omega L/R + 1} = \frac{1}{j\omega/\omega_c + 1}$$





# 2<sup>nd</sup> order frequency responses summary

$$j\omega \rightarrow s, B = \omega_2 - \omega_1, Q = \frac{\omega_0}{B}, \omega_1 \omega_2 = \omega_0^2$$


$$K \frac{s^2}{s^2 + Bs + \omega_0^2} \text{ highpass}$$

$$K \frac{Bs}{s^2 + Bs + \omega_0^2} \text{ bandpass}$$

$$K \frac{\omega_0^2}{s^2 + Bs + \omega_0^2} \text{ lowpass}$$

$$K \frac{s^2 + \omega_0^2}{s^2 + Bs + \omega_0^2} \text{ bandstop}$$
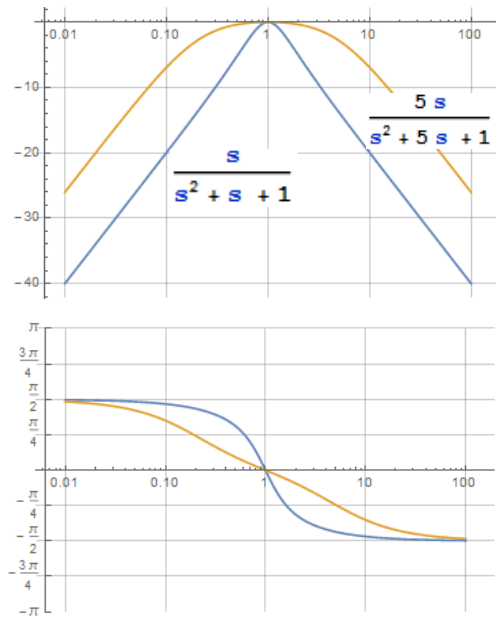
$$K \frac{s^2 - Bs + \omega_0^2}{s^2 + Bs + \omega_0^2} \text{ allpass}$$




$\omega_0$  is resonance frequency

B is bandwidth.

Q is quality factor.

$\omega_1, \omega_2$  are half power frequencies.
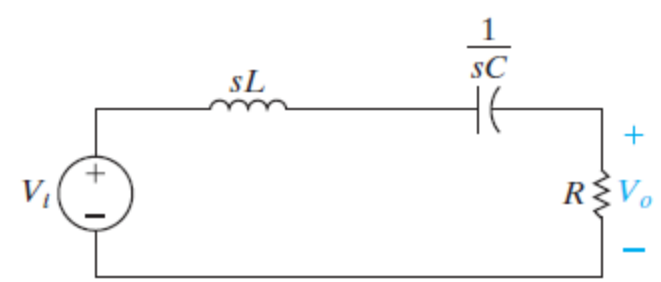
$$\omega_{1,2} = \mp \frac{B}{2} + \sqrt{\left(\frac{B}{2}\right)^2 + \omega_0^2}$$



$$\text{2 nd order : } \frac{R}{R + j\omega L + \frac{1}{j\omega C}} = \frac{\frac{R}{L} s}{s^2 + \frac{R}{L} s + \frac{1}{LC}}$$

Series RCL


$$\omega_0^2 = \frac{1}{LC}, B = \frac{R}{L}, Q = \omega_0 \frac{L}{R}$$

$$\omega_{1,2} = \mp \frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}}$$

Parallel GCL  $\rightarrow$  RCL

$$\omega_0^2 = \frac{1}{LC}, B = \frac{1}{RC}, Q = \omega_0 RC$$
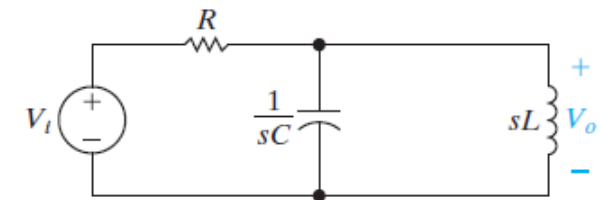
$$\omega_{1,2} = \mp \frac{1}{2RC} + \sqrt{\left(\frac{1}{2RC}\right)^2 + \frac{1}{LC}}$$




$$H(s) = \frac{s/RC}{s^2 + s/RC + 1/LC}$$

$$K \frac{s^2}{s^2 + Bs + \omega_0^2}$$


This response is

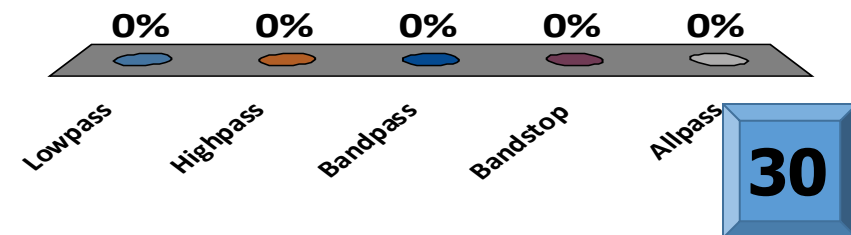- A. Lowpass
- B. Highpass
- C. Bandpass
- D. Bandstop
- E. Allpass



$$\frac{\square}{s^2 + Bs + \omega_0^2}; Q = \frac{\omega_0}{B}; \omega_0^2 = \frac{1}{LC}; Q = \frac{\omega_0 L}{R}$$

This response can be realized by

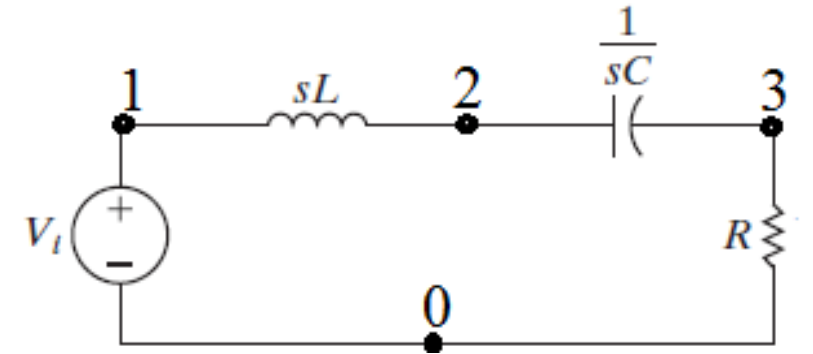

- A.  $V_{21}/V_i$
- B.  $V_{31}/V_i$
- C.  $V_{32}/V_i$
- D.  $V_{20}/V_i$
- E.  $V_{30}/V_i$

0%    0%    0%    0%    0%

Lowpass    Highpass    Bandpass    Bandstop    Allpass



**30**

# Use of dB's

$$A_{dB} = 20 \log_{10}(|H(s)|) = 10 \log_{10}(|H(s)|^2), \quad |H(s)| = 10^{A_{dB}/20}$$

TableForm=


signal ratio	power ratio	dB
0.1	0.01	-20.0
0.141421	0.02	-17.0
0.2	0.04	-14.0
0.3	0.09	-10.5
0.5	0.25	-6.0
0.707107	0.5	-3.0
1.	1.	0.0
1.41421	2.	3.0
2.	4.	6.0
3.	9.	9.5
5.	25.	14.0
7.07107	50.	17.0
10.	100.	20.0

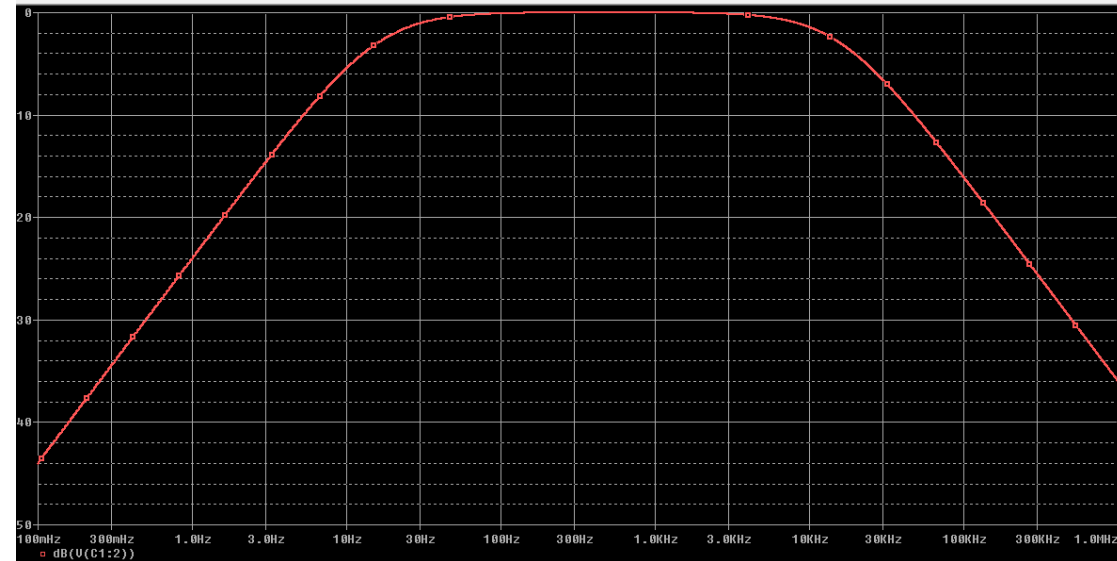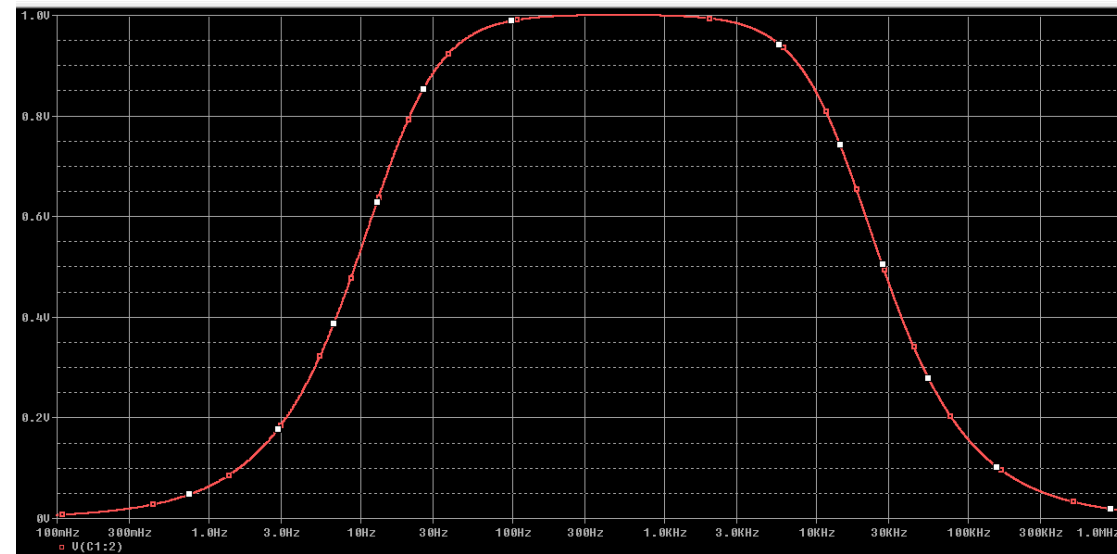

In cascaded circuits signal and power ratio's are multiplied, dB-values are added.

A signal of 10V is transmitted from an antenna to a mobile phone, where it is amplified with a factor of 500. This amplified signal of 1V is input to the phone's speaker. What is the gain in dB of the signal between the transmitter and the phone?

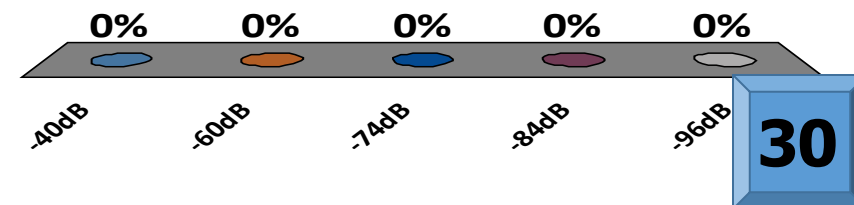- A. -40dB
- B. -60dB
- C. -74dB
- D. -84dB
- E. -96dB





# Scaling

## ^ circuit parameter expressions

$$R' = k_m R$$

$$L' = \frac{k_m}{k_f} L$$

$$C' = \frac{C}{k_m k_f}$$

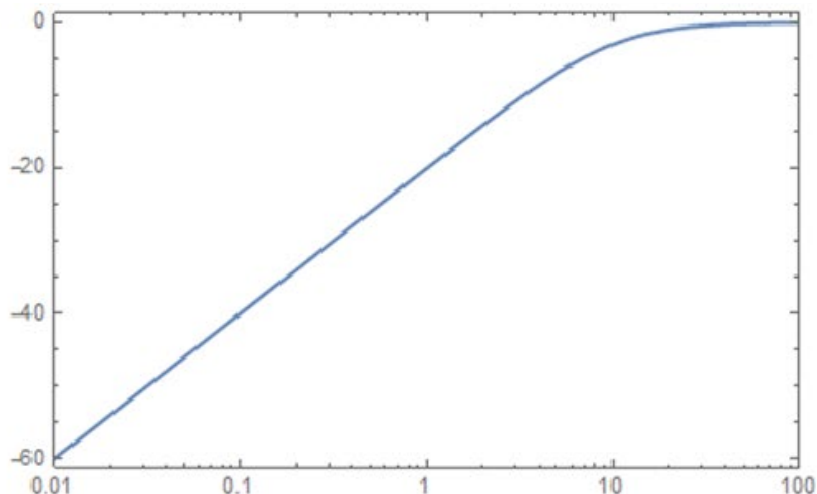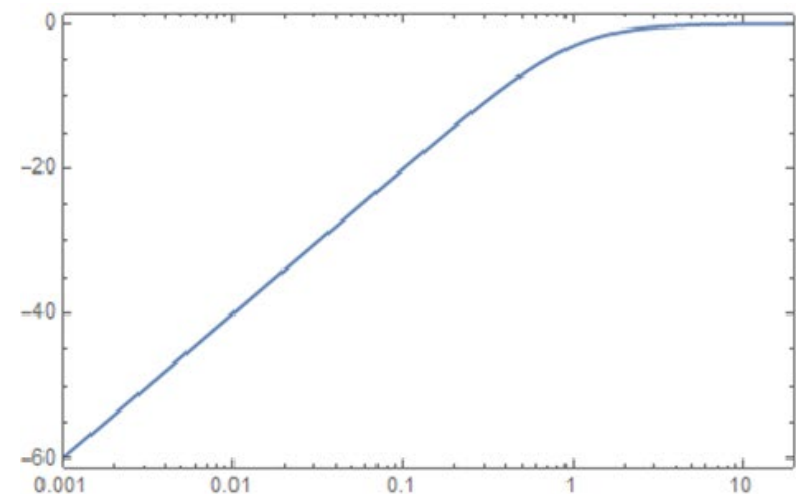

## ^ frequency expressions

$$\omega' = k_f \omega$$

$$B' = k_f B$$

$$\omega_0' = k_f \omega_0$$

$$Q' = \frac{\omega_0'}{B'} = Q$$

$$\frac{1}{R' C'} = \frac{k_f}{R C}$$

$$\frac{R'}{L'} = k_f \frac{R}{L}$$

$$\frac{1}{\sqrt{L' C'}} = k_f \frac{1}{\sqrt{L C}}$$


$$j \omega' L' = j k_m \omega L$$

$$\frac{1}{j \omega' C'} = \frac{k_m}{j \omega C}$$

$$R' = k_m R, \quad \omega' = k_f \omega, \quad L' = \frac{k_m}{k_f} L, \quad \text{and} \quad C' = \frac{1}{k_m k_f} C$$

For the normalized  $RL$  filter having  $\omega_c = 1$  rad/s,  $C = 1$  nF, and  $R = 1 \Omega$ , it is required to have  $\omega_c = 1$  krad/s and  $L = 10$  mH. What are the values of  $k_f$  and  $k_m$ ?

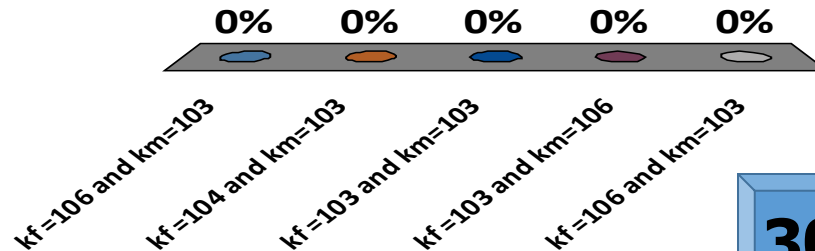
- A.  $k_f = 10^6$  and  $k_m = 10^3$
- B.  $k_f = 10^4$  and  $k_m = 10^3$
- C.  $k_f = 10^3$  and  $k_m = 10^3$
- D.  $k_f = 10^3$  and  $k_m = 10^6$
- E.  $k_f = 10^6$  and  $k_m = 10^3$


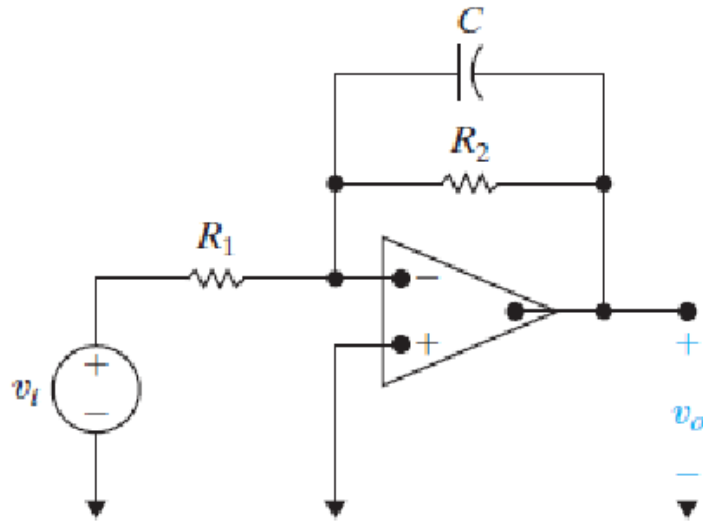
# Active filters

- 1st order


- Low-pass:  $K \frac{\omega_c}{s + \omega_c}$



$$\omega_c = \frac{1}{R_2 C}, K = \frac{R_2}{R_1}$$

$$\omega_c = \frac{1}{R_2 C}, K = \frac{R_2}{R_1}$$

- High-pass:  $K \frac{s}{s + \omega_c}$

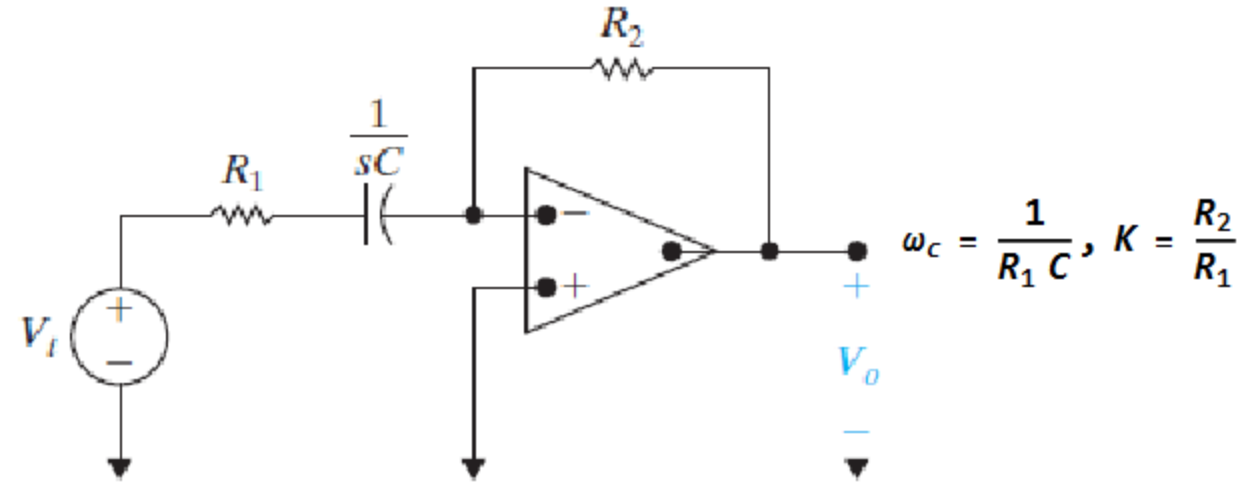


$$\omega_c = \frac{1}{R_1 C}, K = \frac{R_2}{R_1}$$

$$\omega_c = \frac{1}{R_1 C}, K = \frac{R_2}{R_1}$$



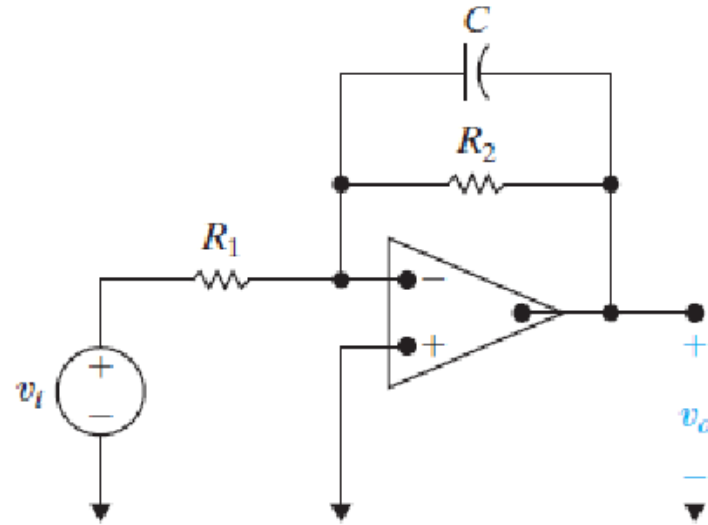$C' = 1\mu\text{F}$ ,  
 $\omega_c' = 10\text{krad/s}$   
 passband gain = 12  
 dB,  
 What is value of  
 $R_1'$ ?



$$R' = k_m R$$



$$L' = \frac{k_m}{k_f} L$$

$$C' = \frac{C}{k_m k_f}$$

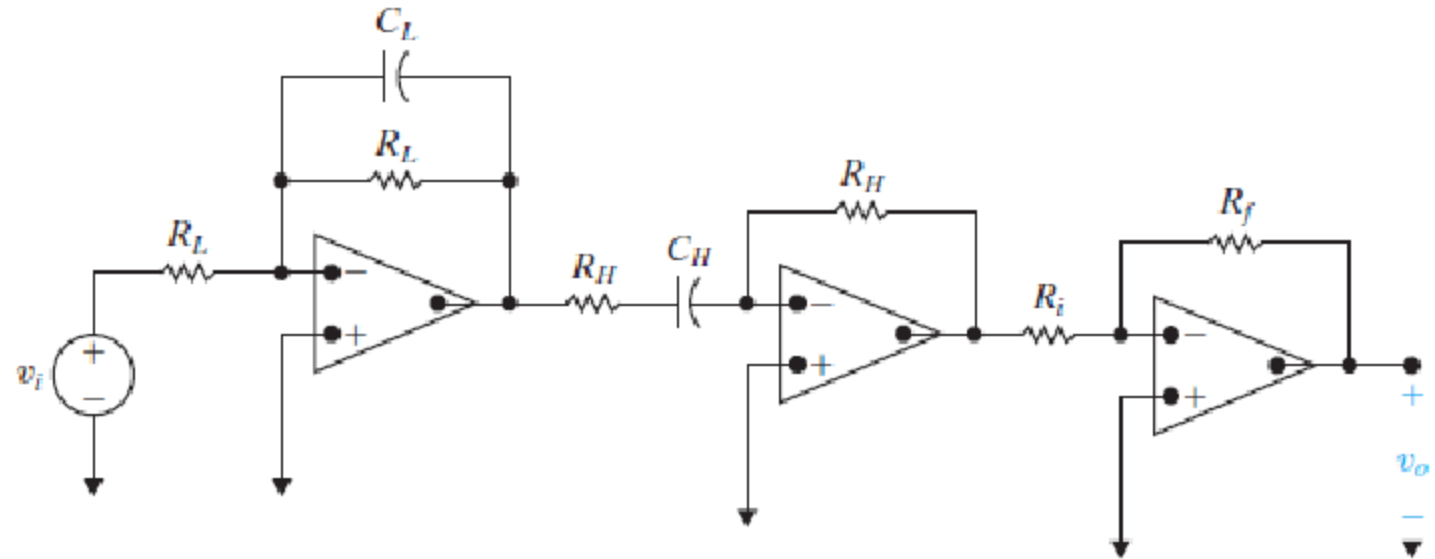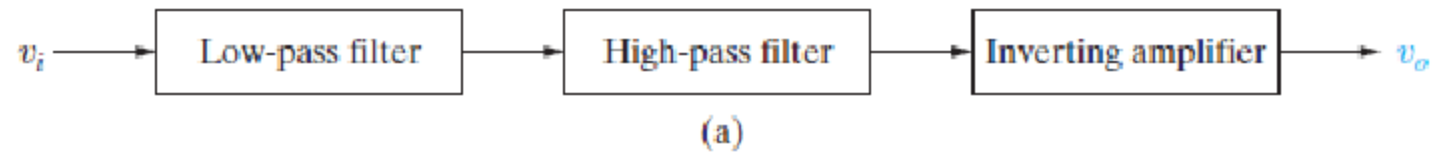- A. 10  $\Omega$
- B. 25  $\Omega$
- C. 100  $\Omega$
- D. 250  $\Omega$
- E. 1,000  $\Omega$

0% 0% 0% 0% 0%  
 100  $\Omega$  250  $\Omega$  1000  $\Omega$  250  $\Omega$  1000  $\Omega$   
**20**



- ^ Broadband band-pass with cascading LPF and HPF



$$\omega_{c2} \gg \omega_{c1}$$

$$H(s) = K \frac{Bs}{s^2 + Bs + \omega_c^2}, \quad \omega_{c1} = \frac{1}{R_H C_H}, \quad \omega_{c2} = \frac{1}{R_L C_L}, \quad B = \omega_{c1} + \omega_{c2} \approx \omega_{c2}, \quad K = -\frac{R_f}{R_i}$$

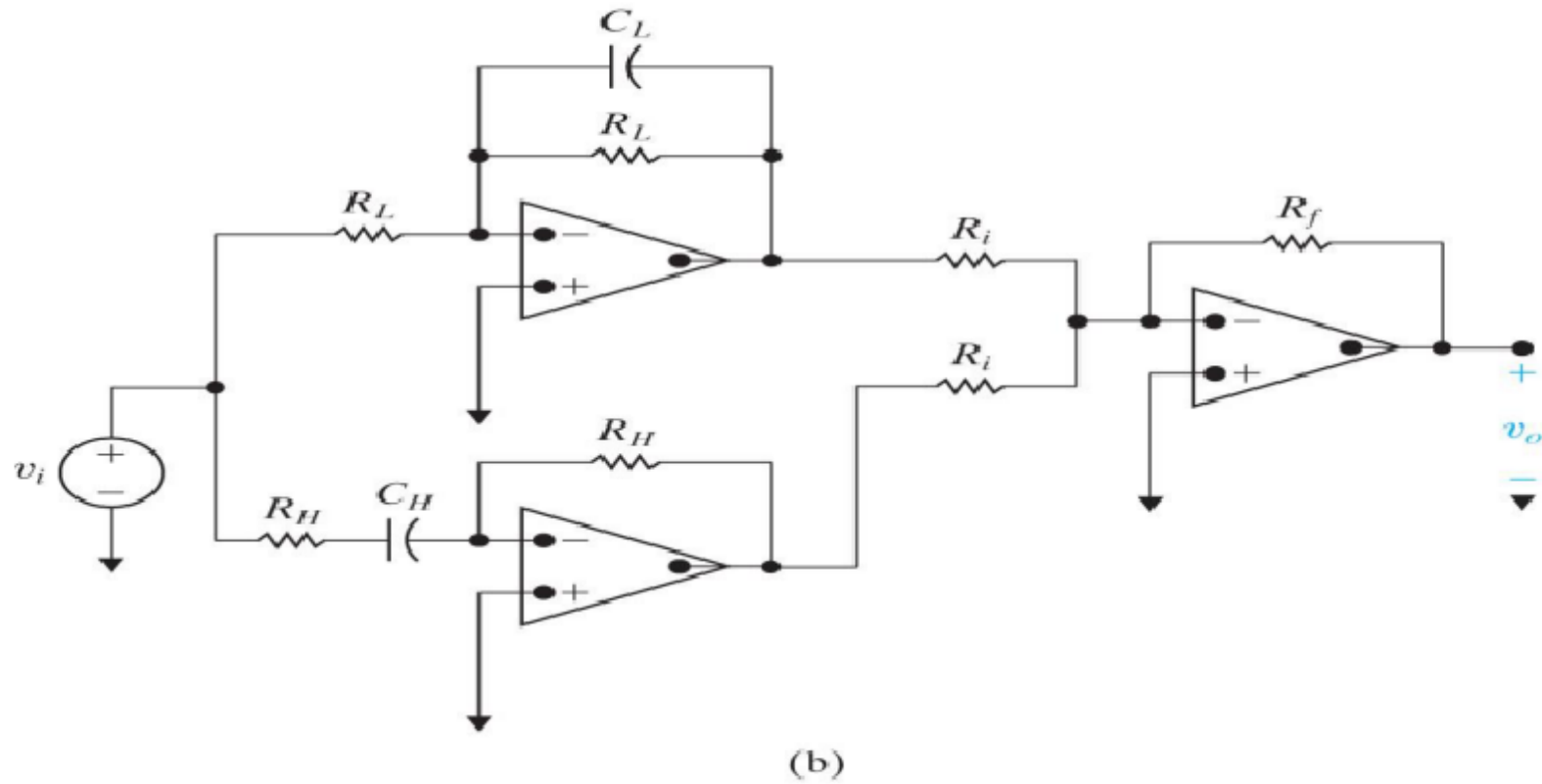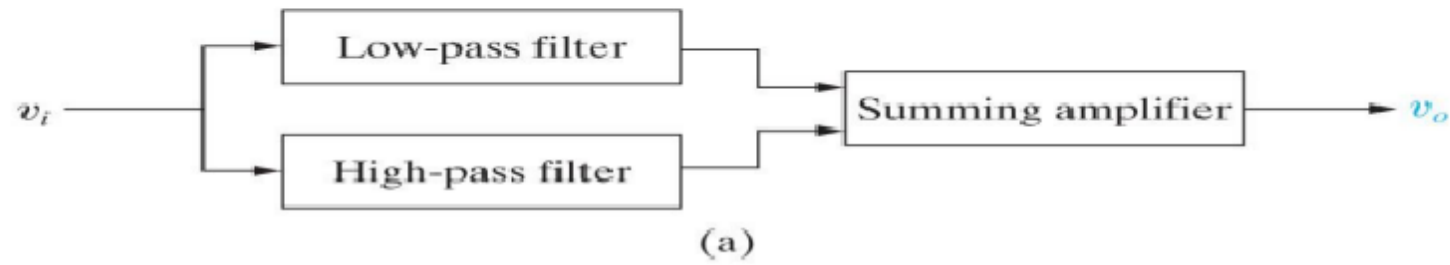^ Broadband band-reject with cascading LPF and HPF



$$\omega_{c2} \gg \omega_{c1}, \omega_{c1} = \frac{1}{R_L C_L}, \omega_{c2} = \frac{1}{R_H C_H}$$

passband gain:  $\frac{R_f}{R_i}$

## ^ Butterworth filters

$$\text{LPF: } H(s) = \frac{1}{B_n(s)}, \quad |H(s)| = \frac{1}{\sqrt{1 + \left(\frac{\omega}{\omega_c}\right)^{2n}}} = \frac{1}{\sqrt{1 + \left(\frac{f}{f_c}\right)^{2n}}}$$

$$\text{HPF: } H(s) = \frac{s^n}{B_n(s)}, \quad |H(s)| = \frac{\left(\frac{\omega}{\omega_c}\right)^n}{\sqrt{1 + \left(\frac{\omega}{\omega_c}\right)^{2n}}} = \frac{\left(\frac{f}{f_c}\right)^n}{\sqrt{1 + \left(\frac{f}{f_c}\right)^{2n}}}$$

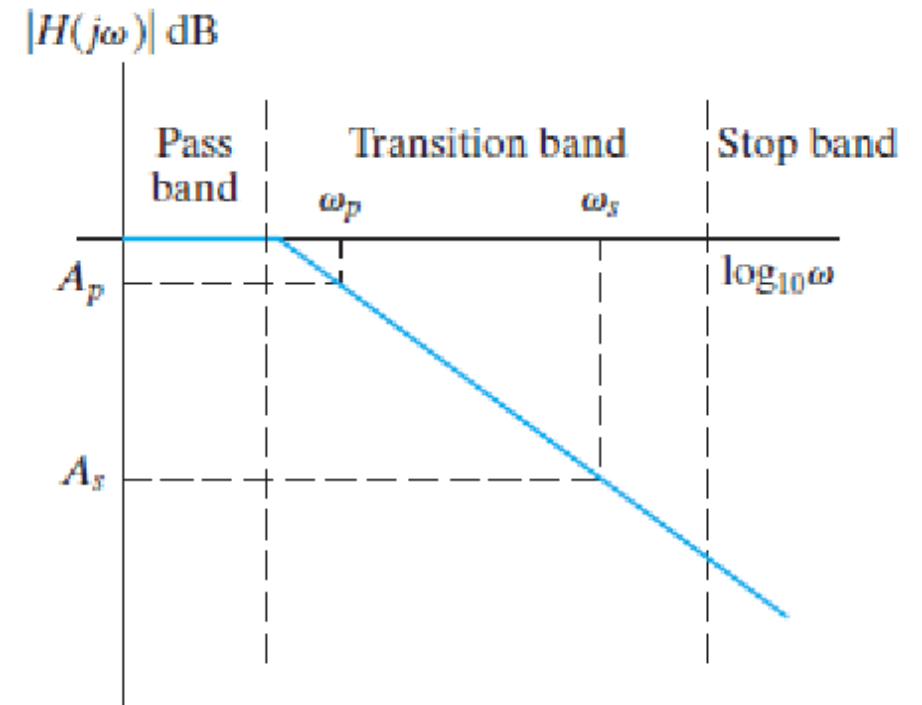


Table 15.2.2 Normalized Butterworth Polynomials of Order  $n$

$n$	Factors of Polynomial $B_n(s)$
1	$(s + 1)$
2	$(s^2 + 1.414s + 1)$ , where $\sqrt{2} = 1.414$
3	$(s + 1)(s^2 + s + 1)$
4	$(s^2 + 0.765s + 1)(s^2 + 1.848s + 1)$
5	$(s + 1)(s^2 + 0.618s + 1)(s^2 + 1.618s + 1)$
6	$(s^2 + 0.518s + 1)(s^2 + 1.414s + 1)(s^2 + 1.932s + 1)$
7	$(s + 1)(s^2 + 0.445s + 1)(s^2 + 1.247s + 1)(s^2 + 1.802s + 1)$
8	$(s^2 + 0.390s + 1)(s^2 + 1.111s + 1)(s^2 + 1.663s + 1)(s^2 + 1.962s + 1)$


$$\frac{\sqrt{10^{-0.1A_s} - 1}}{\sqrt{10^{-0.1A_p} - 1}} = \frac{\sigma_s}{\sigma_p},$$

$$n = \frac{\log_{10} \left( \frac{\sigma_s}{\sigma_p} \right)}{\log_{10} \left( \frac{\omega_s}{\omega_p} \right)}, \quad \text{approximation: } n = \frac{-0.05 A_s}{\log_{10} \left( \frac{\omega_s}{\omega_p} \right)}$$

For  $A_s = -20$  dB at  $\omega = 2\omega_p$ , find required  $n$ .

$$\frac{\sqrt{10^{-0.1A_s} - 1}}{\sqrt{10^{-0.1A_p} - 1}} = \frac{\sigma_s}{\sigma_p},$$
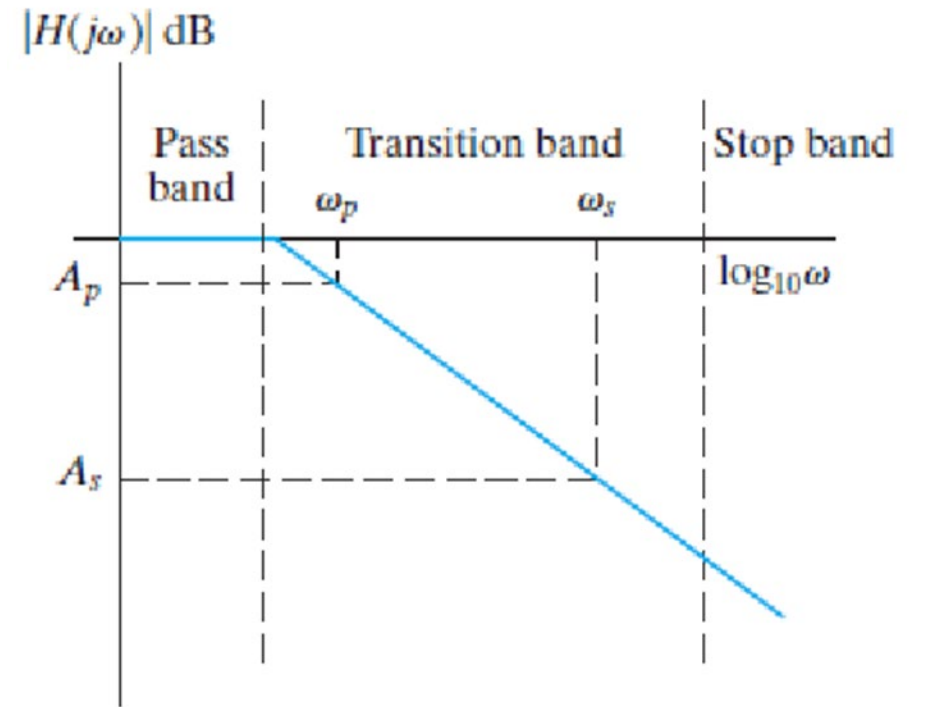
$$n = \frac{\log_{10}\left(\frac{\sigma_s}{\sigma_p}\right)}{\log_{10}\left(\frac{\omega_s}{\omega_p}\right)}, \text{ approximation : } n = \frac{-0.05 A_s}{\log_{10}\left(\frac{\omega_s}{\omega_p}\right)}$$



- A. 1
- B. 2
- C. 3
- D. 4
- E. 5
- F. 6