

# EECE 290, Problem solving



Session 10

# Use of dB's

$$A_{dB} = 20 \log_{10}(|H(s)|) = 10 \log_{10}(|H(s)|^2), \quad |H(s)| = 10^{A_{dB}/20}$$

TableForm=

signal ratio	power ratio	dB
0.1	0.01	-20.0
0.141421	0.02	-17.0
0.2	0.04	-14.0
0.3	0.09	-10.5
0.5	0.25	-6.0
0.707107	0.5	-3.0
1.	1.	0.0
1.41421	2.	3.0
2.	4.	6.0
3.	9.	9.5
5.	25.	14.0
7.07107	50.	17.0
10.	100.	20.0

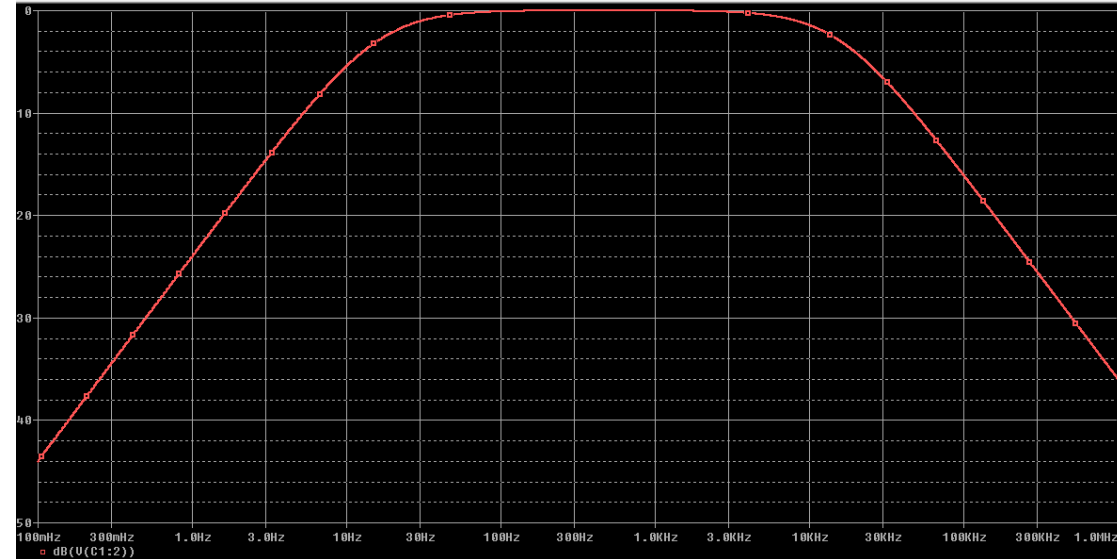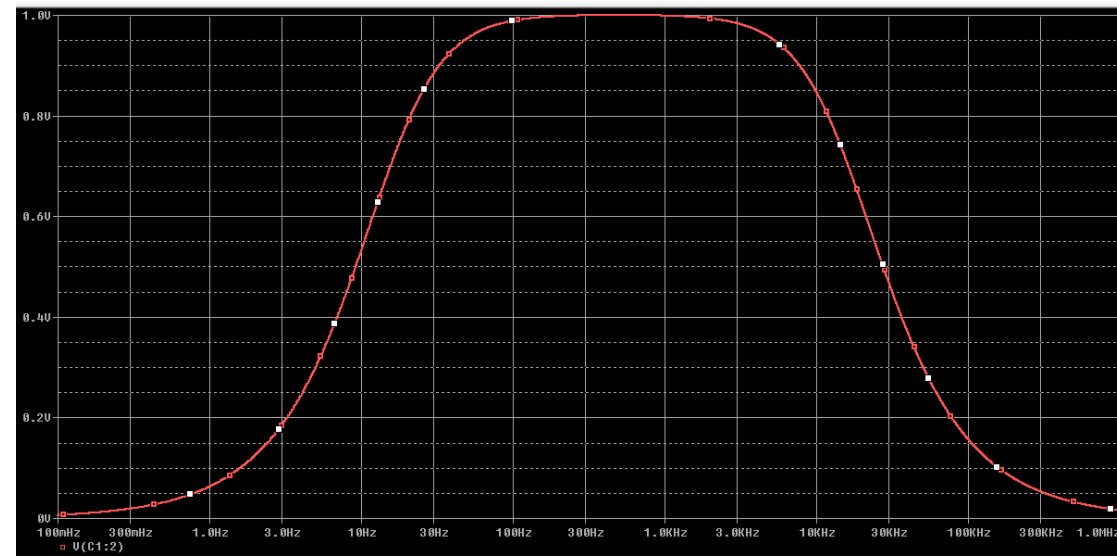

In cascaded circuits signal and power ratio's are multiplied, dB-values are added.


A factor of 4 in signal voltages corresponds to?

- A. -12 dB
- B. -6dB
- C. 3 dB
- D. 6 dB
- E. 12 dB

$$A_{dB} = 20 \log_{10}(|H(s)|) = 10 \log_{10}(|H(s)|^2),$$

TableForm=

signal ratio	power ratio	dB
0.1	0.01	-20.0
0.141421	0.02	-17.0
0.2	0.04	-14.0
0.3	0.09	-10.5
0.5	0.25	-6.0
0.707107	0.5	-3.0
1.	1.	0.0
1.41421	2.	3.0
2.	4.	6.0

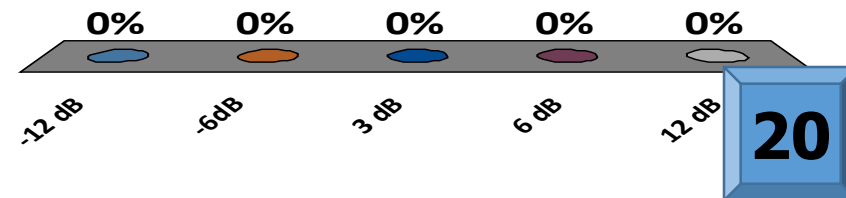


A factor of  
1/1000 in  
powers  
corresponds to?

- A. -60 dB
- B. -30 dB
- C. -15 dB
- D. 0 dB
- E. 30 dB

$$A_{dB} = 20 \log_{10}(|H(s)|) = 10 \log_{10}(|H(s)|^2),$$

TableForm=

signal ratio	power ratio	dB
0.1	0.01	-20.0
0.141421	0.02	-17.0
0.2	0.04	-14.0
0.3	0.09	-10.5
0.5	0.25	-6.0
0.707107	0.5	-3.0
1.	1.	0.0
1.41421	2.	3.0
2.	4.	6.0

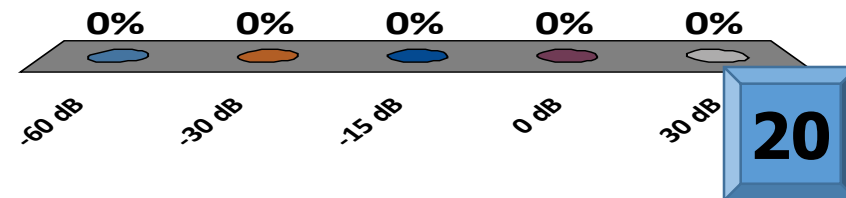


$$A_{dB} = 20 \log_{10}(|H(s)|) = 10 \log_{10}(|H(s)|^2),$$

- 2 dB  
corresponds to?

- A. 1/2 in powers
- B. 1/2 in voltages
- C. 0.7 in powers
- D. 0.8 in powers
- E. 0.7 in voltages
- F. 0.8 in voltages

TableForm=

signal ratio	power ratio	dB
0.1	0.01	-20.0
0.141421	0.02	-17.0
0.2	0.04	-14.0
0.3	0.09	-10.5
0.5	0.25	-6.0
0.707107	0.5	-3.0
1.	1.	0.0
1.41421	2.	3.0
2.	4.	6.0

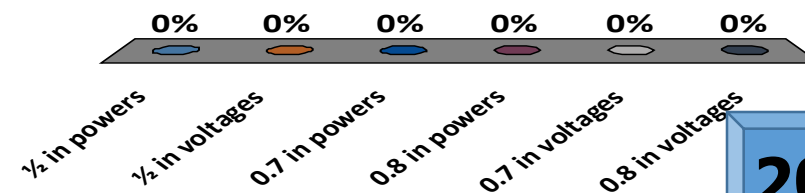


# Scaling

## ^ circuit parameter expressions

$$R' = k_m R$$

$$L' = \frac{k_m}{k_f} L$$

$$C' = \frac{C}{k_m k_f}$$

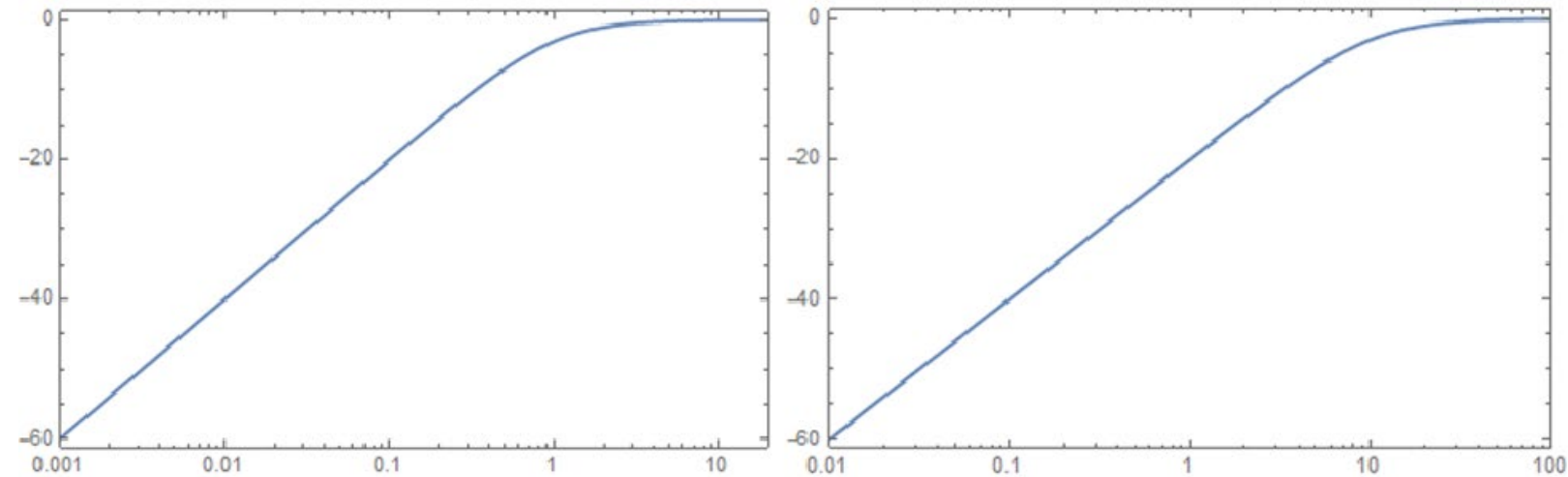

## ^ frequency expressions

$$\omega' = k_f \omega$$

$$B' = k_f B$$

$$\omega_0' = k_f \omega_0$$

$$Q' = \frac{\omega_0'}{B'} = Q$$

$$\frac{1}{R' C'} = \frac{k_f}{R C}$$

$$\frac{R'}{L'} = k_f \frac{R}{L}$$

$$\frac{1}{\sqrt{L' C'}} = k_f \frac{1}{\sqrt{L C}}$$


$$j \omega' L' = j k_m \omega L$$

$$\frac{1}{j \omega' C'} = \frac{k_m}{j \omega C}$$

$$R' = k_m R, \quad \omega' = k_f \omega, \quad L' = \frac{k_m}{k_f} L, \quad \text{and} \quad C' = \frac{1}{k_m k_f} C$$

For the normalized  $RL$  filter having  $\omega_c = 1$  rad/s,  $L = 1$  H, and  $R = 1 \Omega$ , it is required to have  $\omega_c = 1$  krad/s and  $L = 10$  mH. What are the values of  $k_f$  and  $k_m$ ?

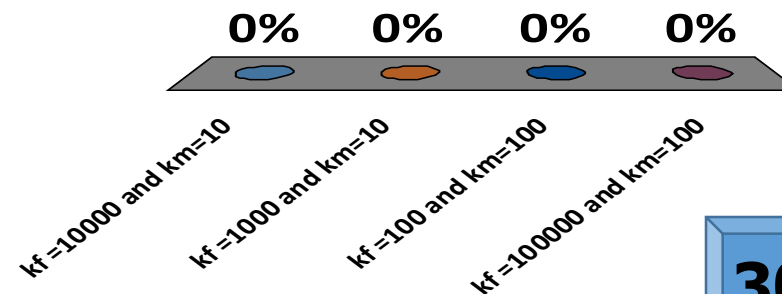
- A.  $k_f = 10000$  and  $k_m = 10$
- B.  $k_f = 1000$  and  $k_m = 10$
- C.  $k_f = 100$  and  $k_m = 100$
- D.  $k_f = 100000$  and  $k_m = 100$


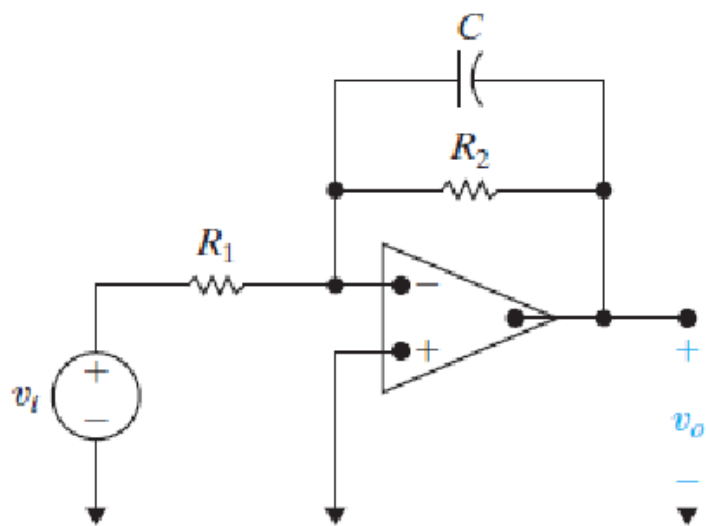
# Active filters


1st order

Low-pass:  $K \frac{\omega_c}{s + \omega_c}$



$$\omega_c = \frac{1}{R_2 C}, K = \frac{R_2}{R_1}$$


High-pass:  $K \frac{s}{s + \omega_c}$

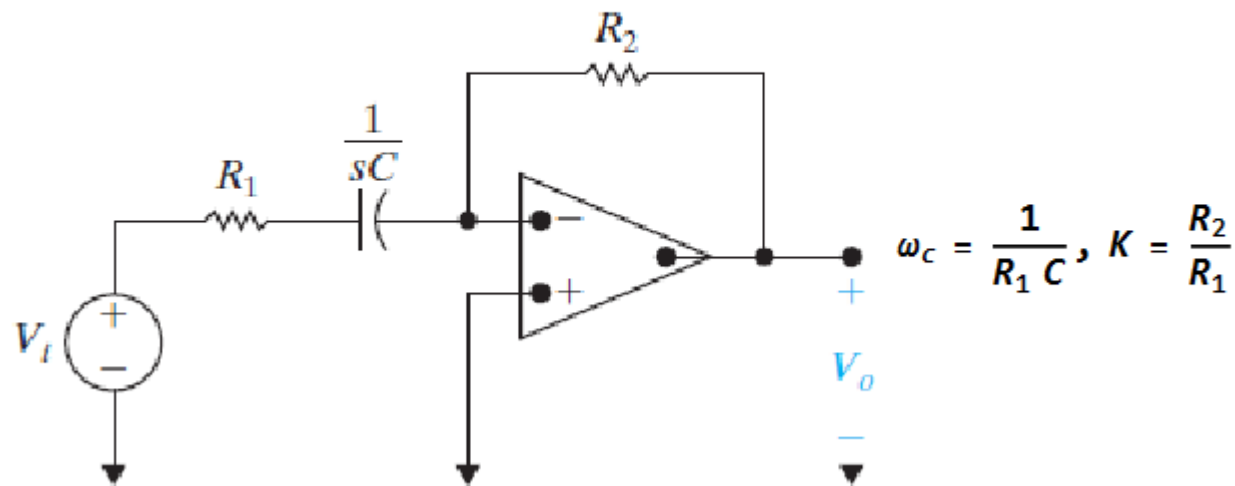

$$\omega_c = \frac{1}{R_1 C}, K = \frac{R_2}{R_1}$$



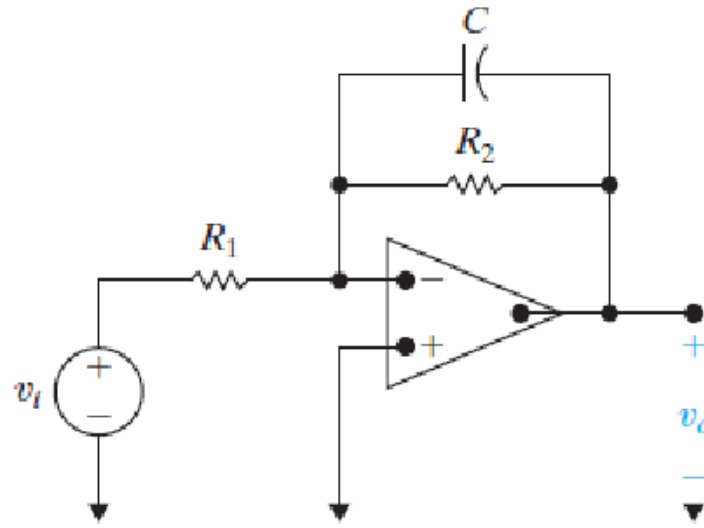$C=1\text{F}$ ,  $R_2=1\Omega$ ,  
 passband gain  
 $=12\text{ dB}$ ,  
 What is value of  
 $R_1$ ?



0.5	0.25	-0.0
0.707107	0.5	-3.0
1.	1.	0.0
1.41421	2.	3.0
2.	4.	6.0
3.	9.	9.5
5	25	14.0

- A.  $1\Omega$
- B.  $0.5\Omega$
- C.  $0.25\Omega$
- D.  $2\Omega$
- E.  $5\Omega$

0%    0%    0%    0%    0%


20    0.50    0.250    20    50

**20**

$$C' = 1\mu\text{F}$$

$$\omega_c' = 10\text{krad/s}$$

What is value of  $k_m$ ?

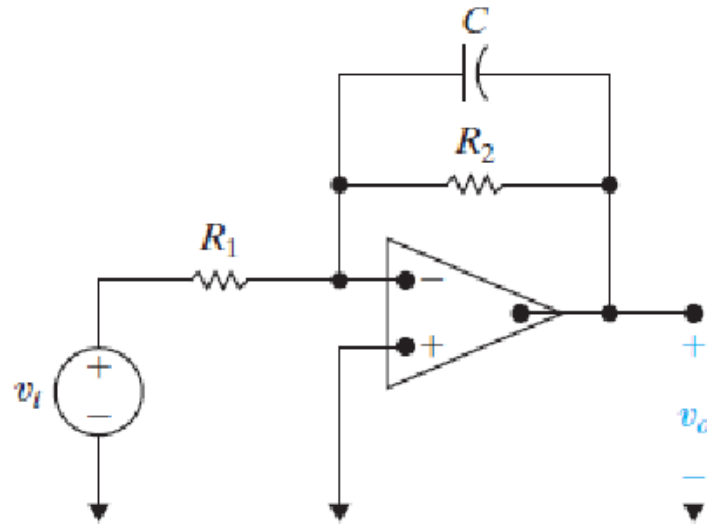


$$R' = k_m R$$

$$L' = \frac{k_m}{k_f} L$$

$$C' = \frac{C}{k_m k_f}$$

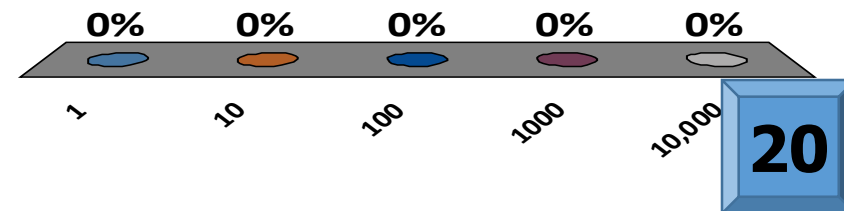
- A. 1
- B. 10
- C. 100
- D. 1000
- E. 10,000



$$C' = 1 \mu\text{F}$$

$$\omega_c' = 10 \text{krad/s}$$

What is value of  $R_1'$ ?

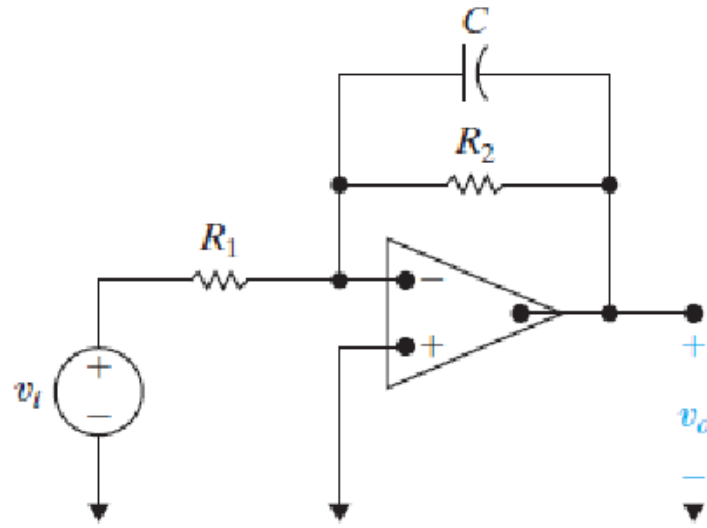

$$R' = k_m R$$

$$L' = \frac{k_m}{k_f} L$$

$$C' = \frac{C}{k_m k_f}$$

- A. 10  $\Omega$
- B. 25  $\Omega$
- C. 100  $\Omega$
- D. 250  $\Omega$
- E. 1,000  $\Omega$

