

EECE 290, Problem solving

Session 8

**Announcement: PSpice quiz will be on
April 23rd, 6 PM-8 PM in SRB**

$$u(t) * u(t) = ?$$

A. -1

B. 0

C. 1

D. t

E. t^2

F. $\frac{1}{2} t^2$

$$u(t) * t u(t) = ?$$

A. -1

B. 0




C. 1

D. t


E. t^2







F. $\frac{1}{2} t^2$

- A.
- B.
- C.
- D.
- E.
- F.

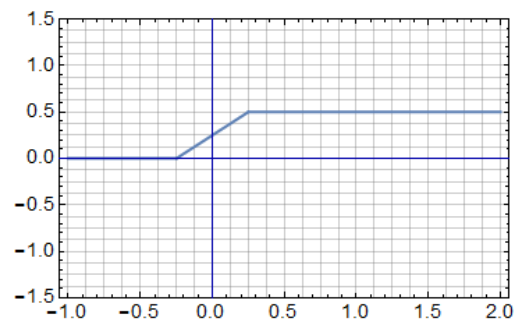
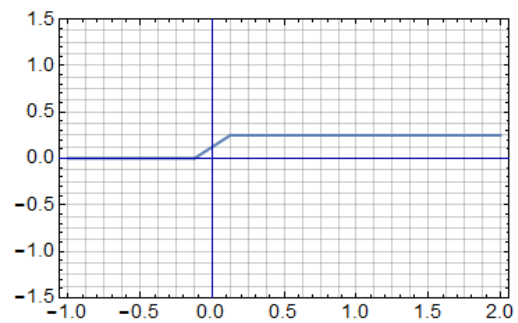
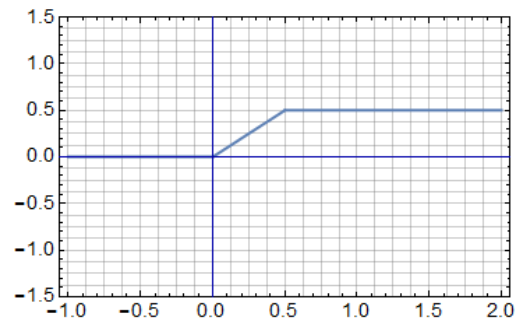


$$u(t)^*$$


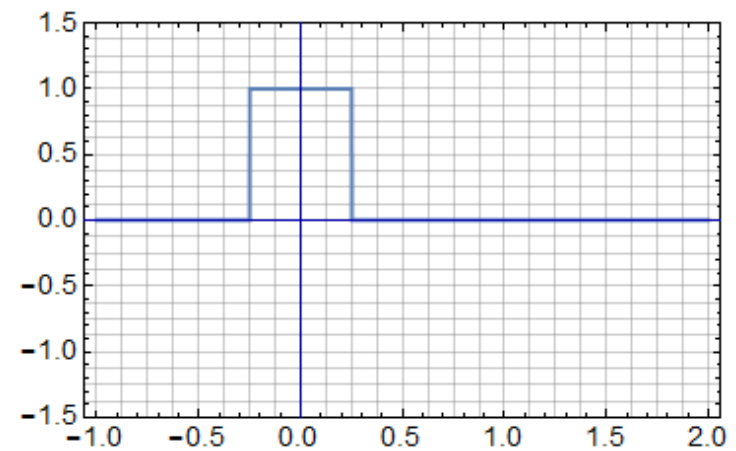


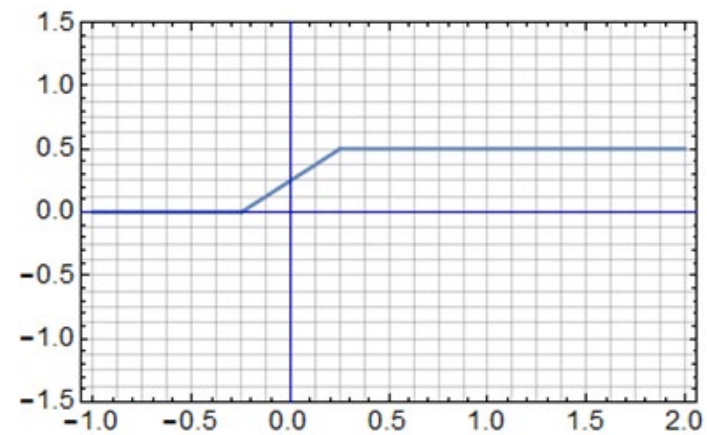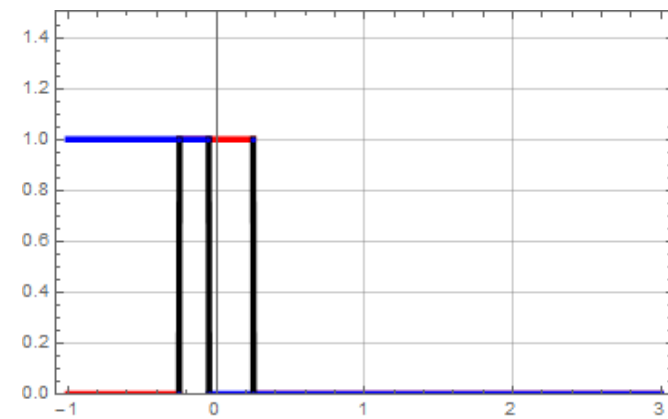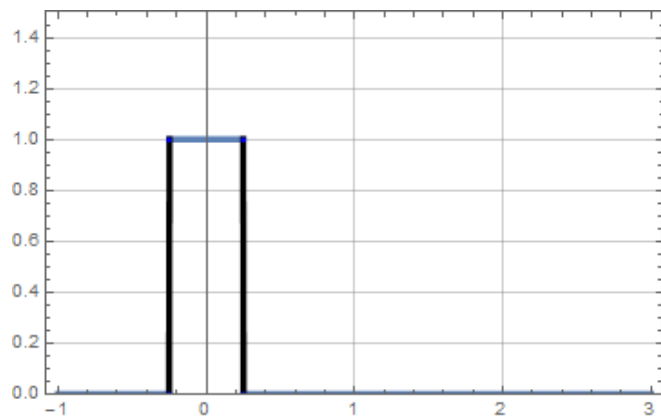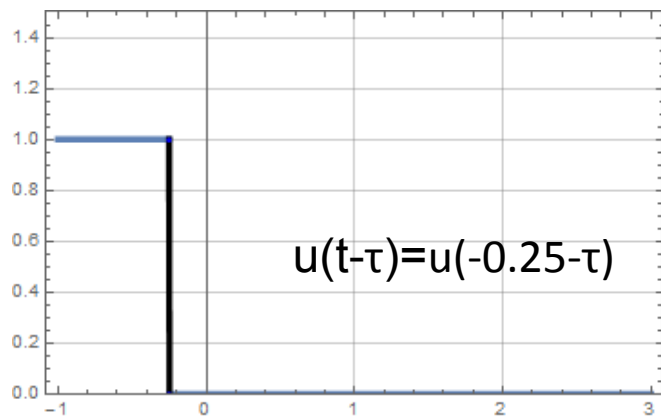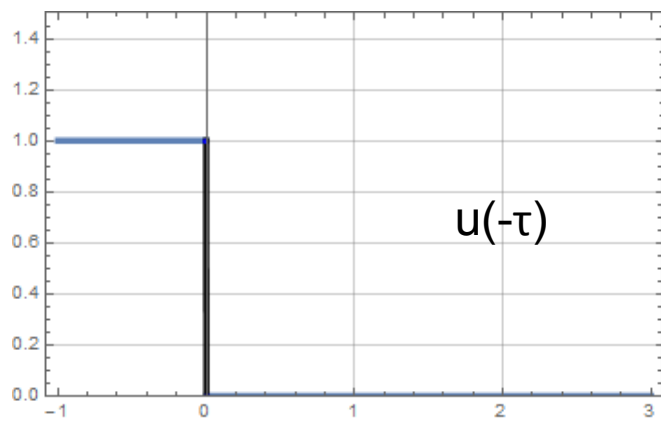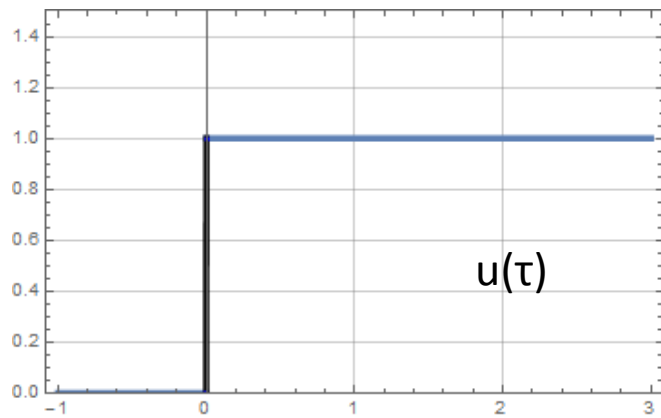

A.
B.
C.

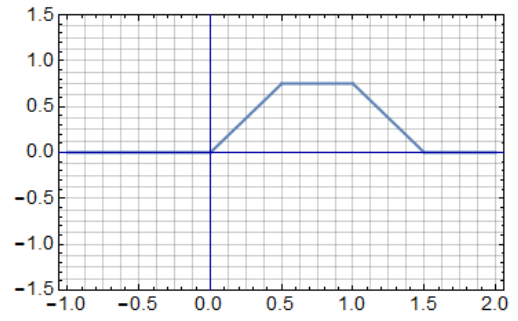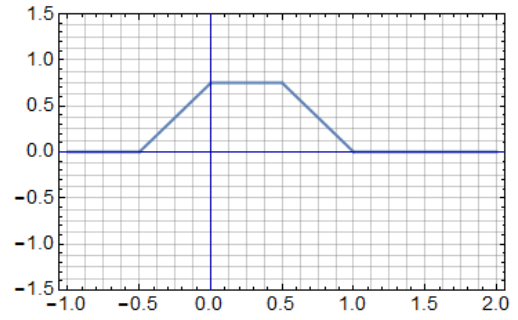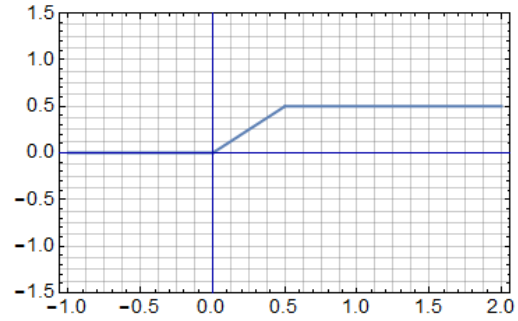


Convolve

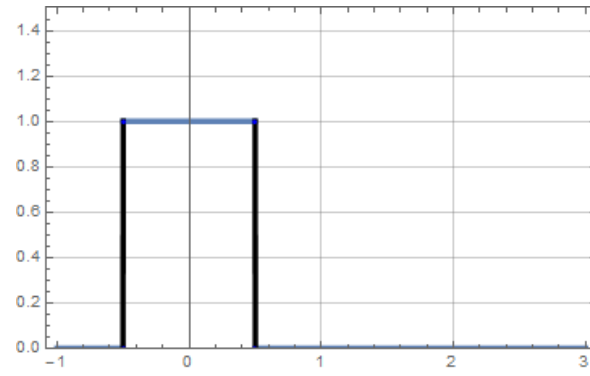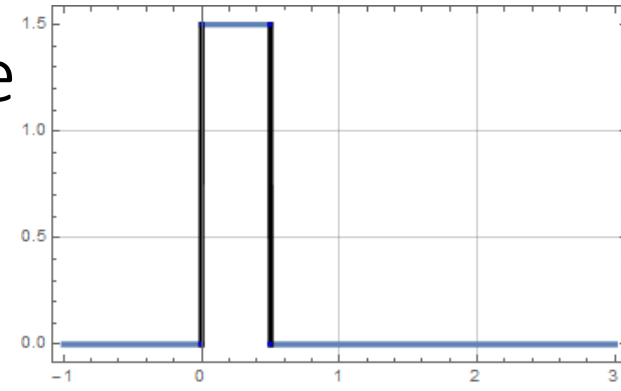


What is the extent in the time domain of the convolution?

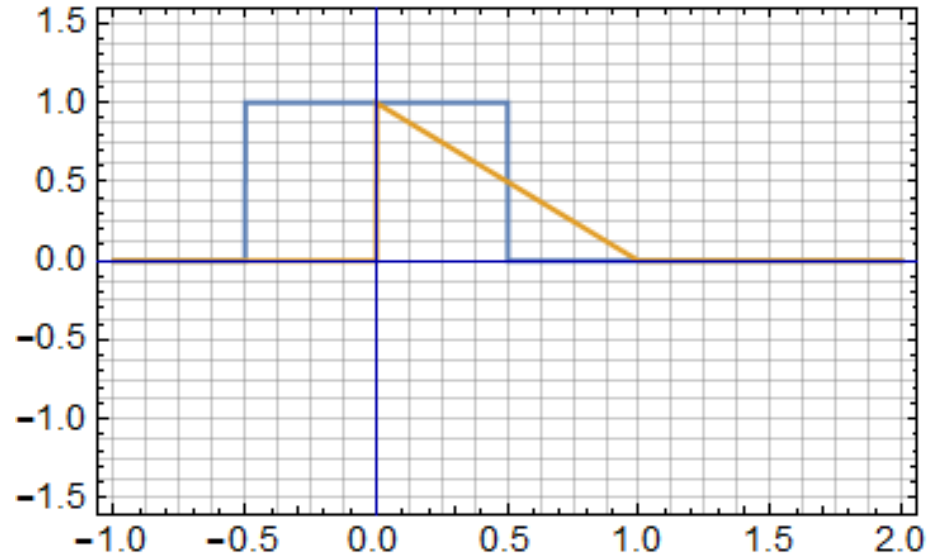- A. 0.5
- B. 1
- C. 1.5
- D. 2
- E. 2.5
- F. 3




$f(t)$ is the convolution of the functions shown. What is the value of $f(3)$?

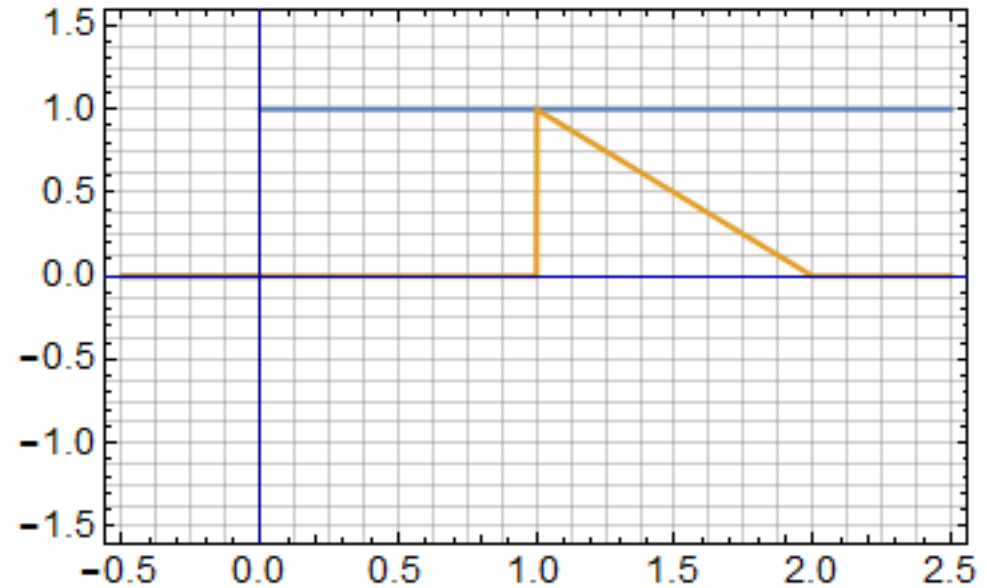- A. 0.5
- B. 1
- C. 1.5
- D. 2
- E. 2.5
- F. 3




The response of this circuit is

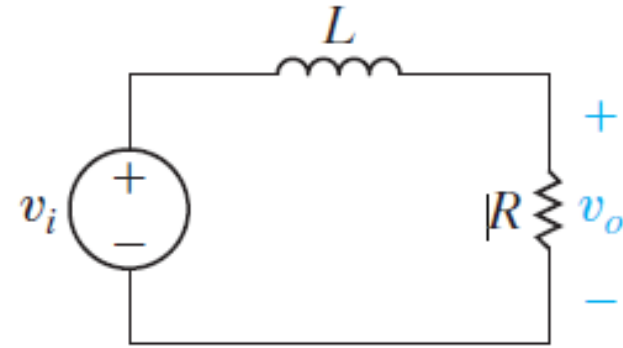

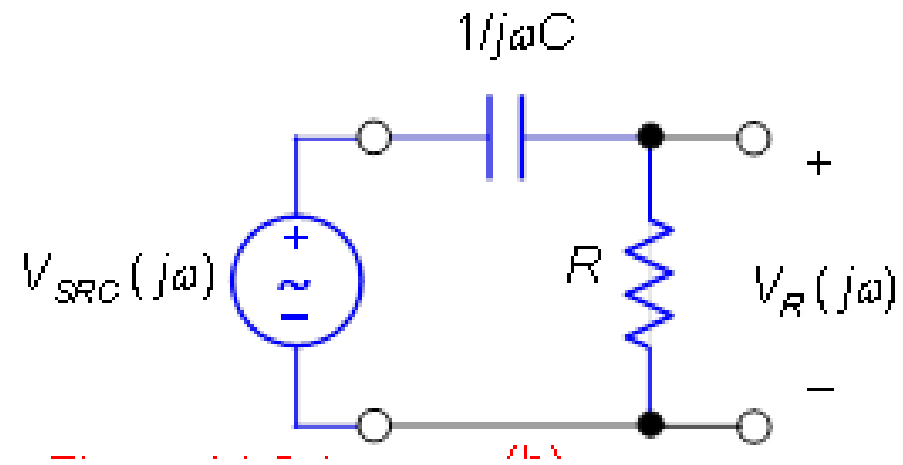- A. Lowpass
- B. Highpass
- C. Bandpass
- D. Bandstop


$$H_R(j\omega) = \frac{V_R(j\omega)}{V_{SRC}(j\omega)}$$

$R = 1 \text{ k}\Omega$, $C = 2 \text{ mF}$. The half power angular cut-off frequency ω_c is



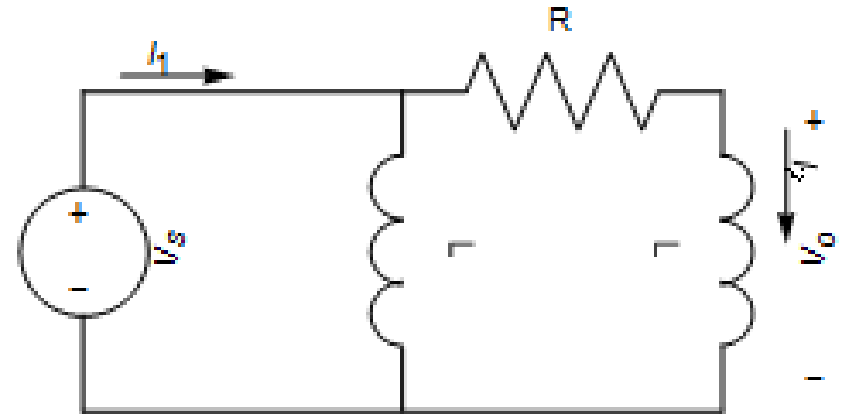
- A. 2 rad/s
- B. 1 rad/s
- C. 0.5 rad/s
- D. 20 rad/s
- E. 5 rad/s

$H(j\omega) = V_o/V_s$, $R = 1 \text{ k}\Omega$, $L = 0.5 \text{ mH}$. The half power angular cut-off frequency ω_c is



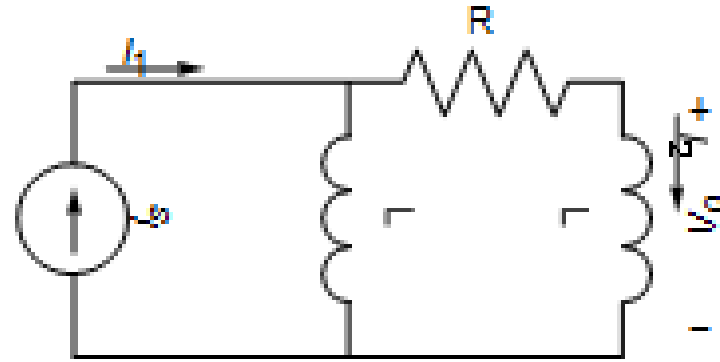- A. 1000 rad/s
- B. 1 Mrad/s
- C. 0.5 mrad/s
- D. 2 Mrad/s
- E. 5 krad/s

$H(j\omega) = I_2/I_s$, $R = 1 \text{ k}\Omega$,
 $L = 0.5 \text{ mH}$. The half
power angular cut-off
frequency ω_c is



- A. 1000 rad/s
- B. 1 Mrad/s
- C. 0.5 mrad/s
- D. 2 Mrad/s
- E. 5 krad/s