

EECE 290, Problem solving

Session 7

Review quiz 1

Summary opamps

- Analysis with ideal opamps:
 - $v_p - v_n = 0$,
 - $i_p = i_n = 0$
 - $V_{CC}^- \leq v_o \leq V_{CC}^+$
 - Implies negative feedback.


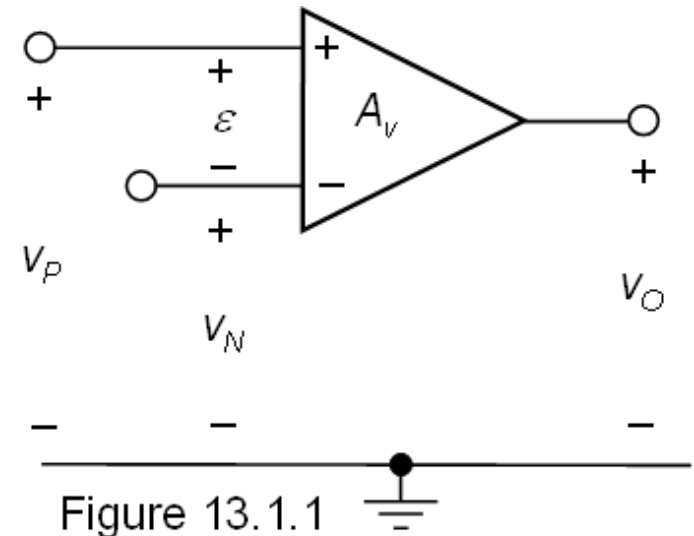








Figure 13.1.1

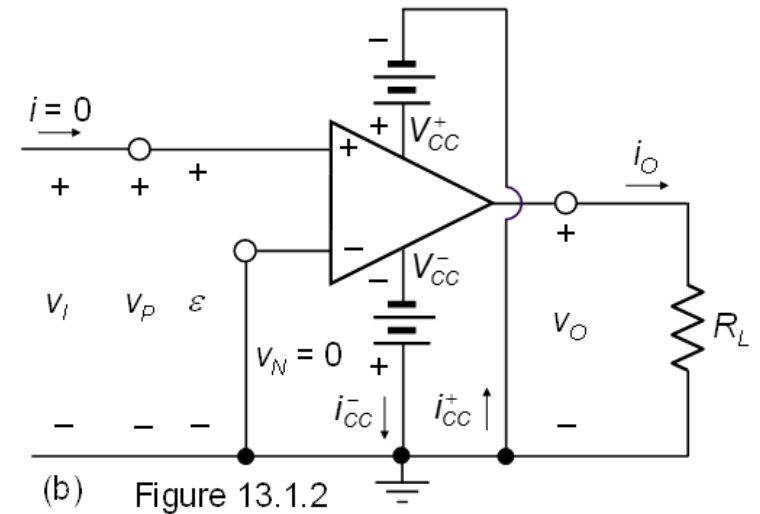

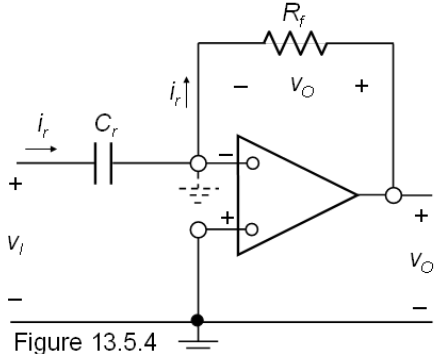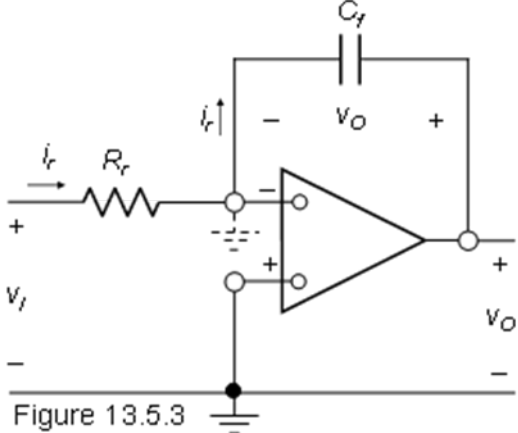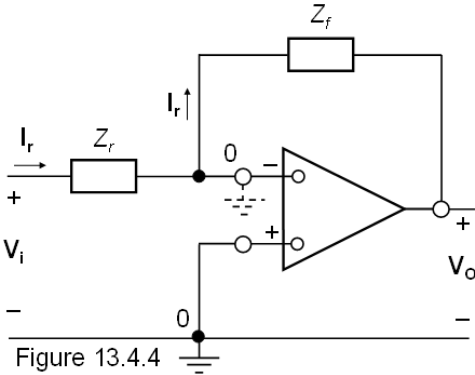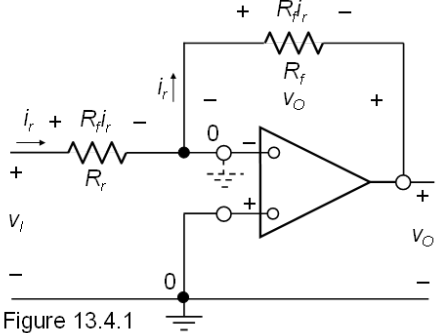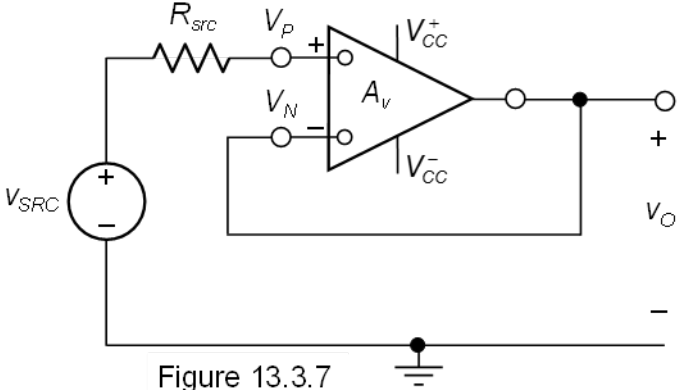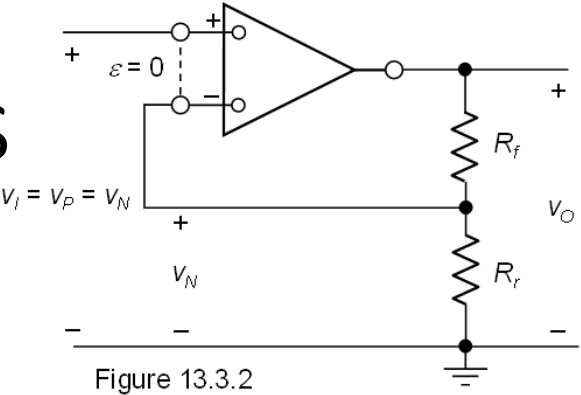(b) Figure 13.1.2


Basic configurations

- Non-inverting:
- Unity-gain:
- Inverting:
- Perfect integrator:
- Perfect differentiator:




Basic configurations cont'd

- Adder:

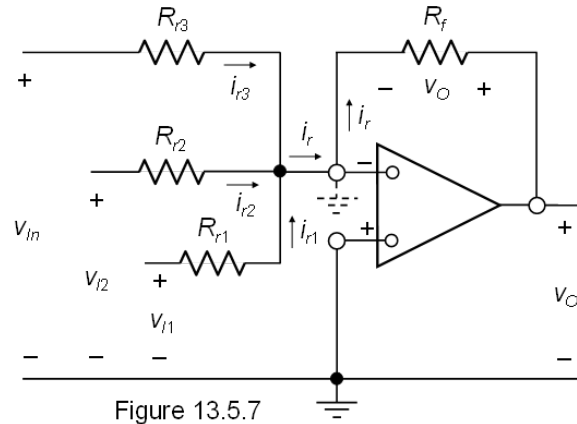

- Difference amplifier:

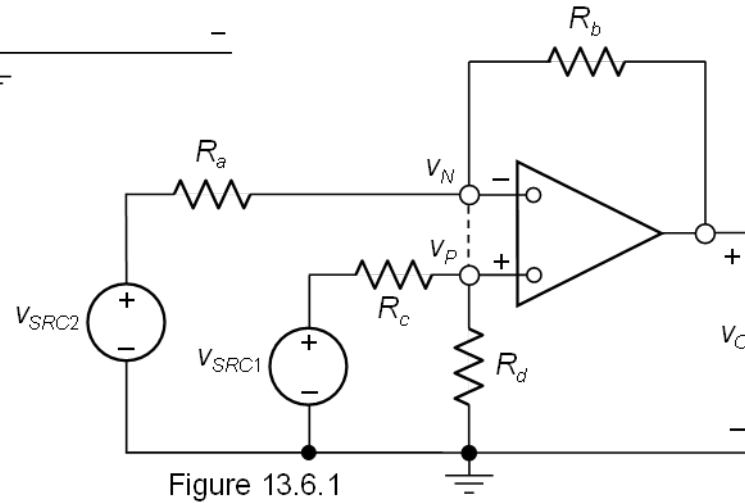

$$V_O = ?$$

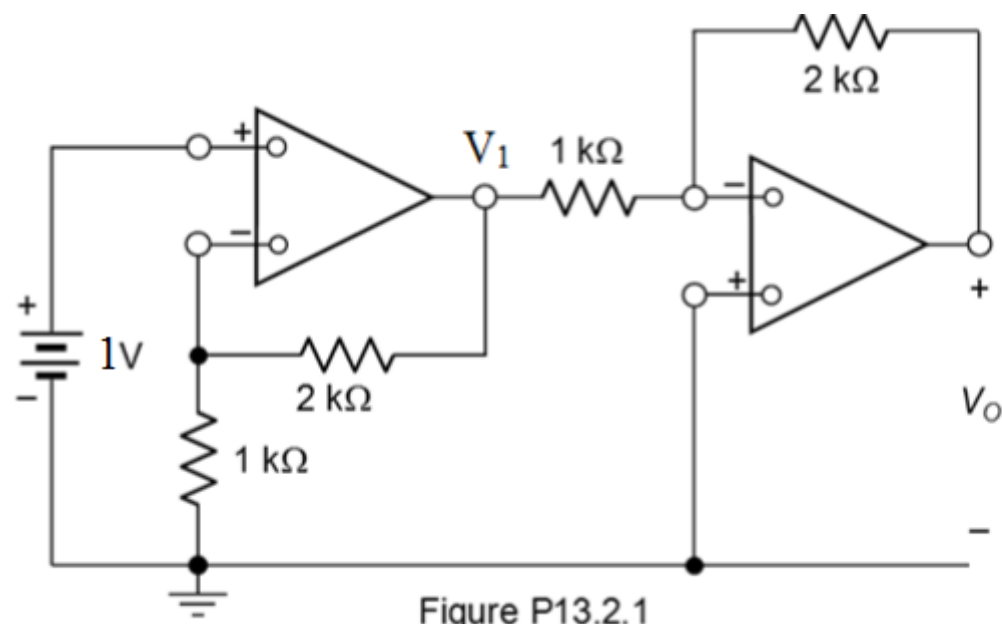


Figure P13.2.1

- A. 12 V
- B. -12 V
- C. 2 V
- D. -2 V
- E. 6 V
- F. -6 V

Complex power


using rms values: $S = VI^* = P + jQ = Z |I|^2 = (R + jX) |I|^2 = Y^* |V|^2 = (G - jB) |V|^2$

$$|S| = |V| |I| = |Z| |I|^2 = |Y| |V|^2$$

L: $S = jQ = jX |I|^2 = j\omega L |I|^2 = j |V| |I|$

C: $S = jQ = -jB |V|^2 = -j\omega C |V|^2 = -j |V| |I|$

R: $S = P = R |I|^2 = G |V|^2 = |V| |I|$

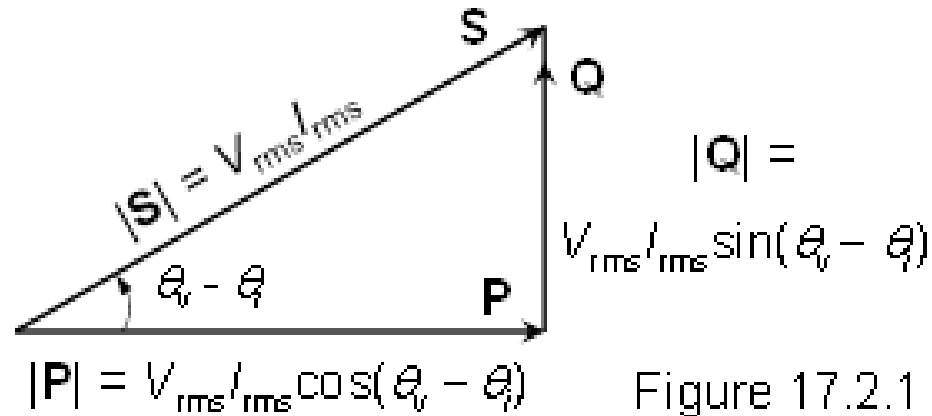

power factor: $\cos(\theta_v - \theta_i)$ lagging or leading (current with respect to voltage)

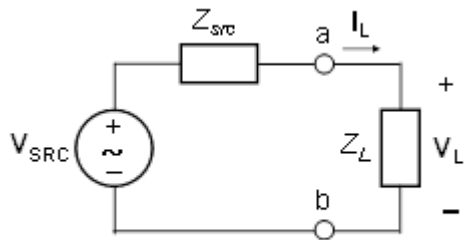


Figure 17.4.7

Maximum power transfer: $Z_L = Z_{src}^*$

using rms values: $S = VI^* = P + jQ = Z |I|^2 = (R + jX) |I|^2 = Y^* |V|^2 = (G - jB) |V|^2$

A current source of $0.1 \text{ A}_{\text{rms}}$, a capacitance of $-j2 \Omega$ and an inductance of $j4 \Omega$ are connected in series, what is the value of S ?

- A. $j20 \text{ mVA}$
- B. $-j20 \text{ mVA}$
- C. $-j2 \text{ mVA}$
- D. $j2 \text{ mVA}$

Step function: $u(t) = \begin{cases} 0 & t < 0 \\ 1 & t > 0 \end{cases}$

Impulse (Dirac, delta) function: $\begin{cases} \delta(t) = 0 & t \neq 0 \\ \int_{-\infty}^{\infty} \delta(t) dt = 1 \end{cases}$

$u(t) = \int_{-\infty}^t \delta(\tau) d\tau$, $\delta(t) = du(t)/dt$



Properties:

If t is time in s, then $\delta(t)$ has dimension of s^{-1} !

Sifting property: $\int_a^b f(t) \delta(t - t_0) dt = \begin{cases} f(t_0) & a < t_0 < b \\ 0 & \text{elsewhere} \end{cases}$

Even symmetry: $\delta(-t) = \delta(t)$

Scaling: $\delta(at) = \frac{1}{|a|} \delta(t)$

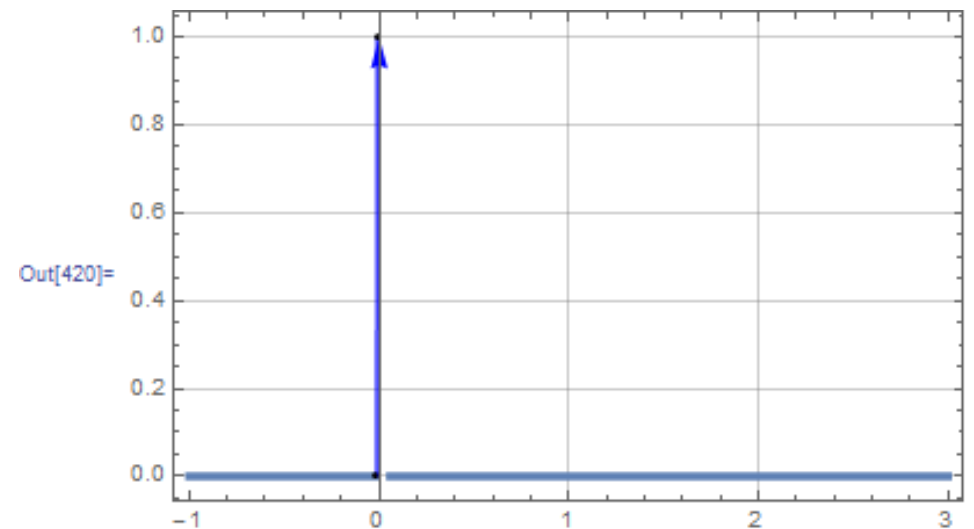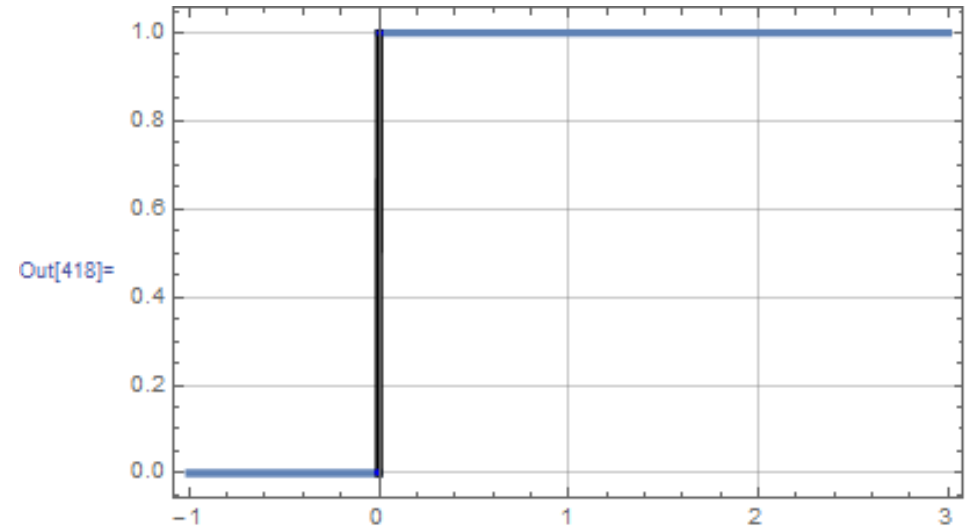

Laplace Transform

- Complex domain: $s = \sigma + j\omega$; e^{st}

$$\mathcal{L}\{f(t)\} = F(s) = \int_0^{\infty} f(t) e^{-st} dt$$

$$\mathcal{L}^{-1}\{F(s)\} = f(t) = \frac{1}{2\pi j} \int_{\sigma-j\infty}^{\sigma+j\infty} F(s) e^{st} ds$$


$$\mathcal{L}\{\delta(t)\} = 1;$$

$$\mathcal{L}\{u(t)\} = 1/s;$$


$$\mathcal{L}\{e^{-at}\} = 1/(s+a)$$

$$\lim_{t \rightarrow 0^+} f(t) = \lim_{s \rightarrow \infty} sF(s)$$
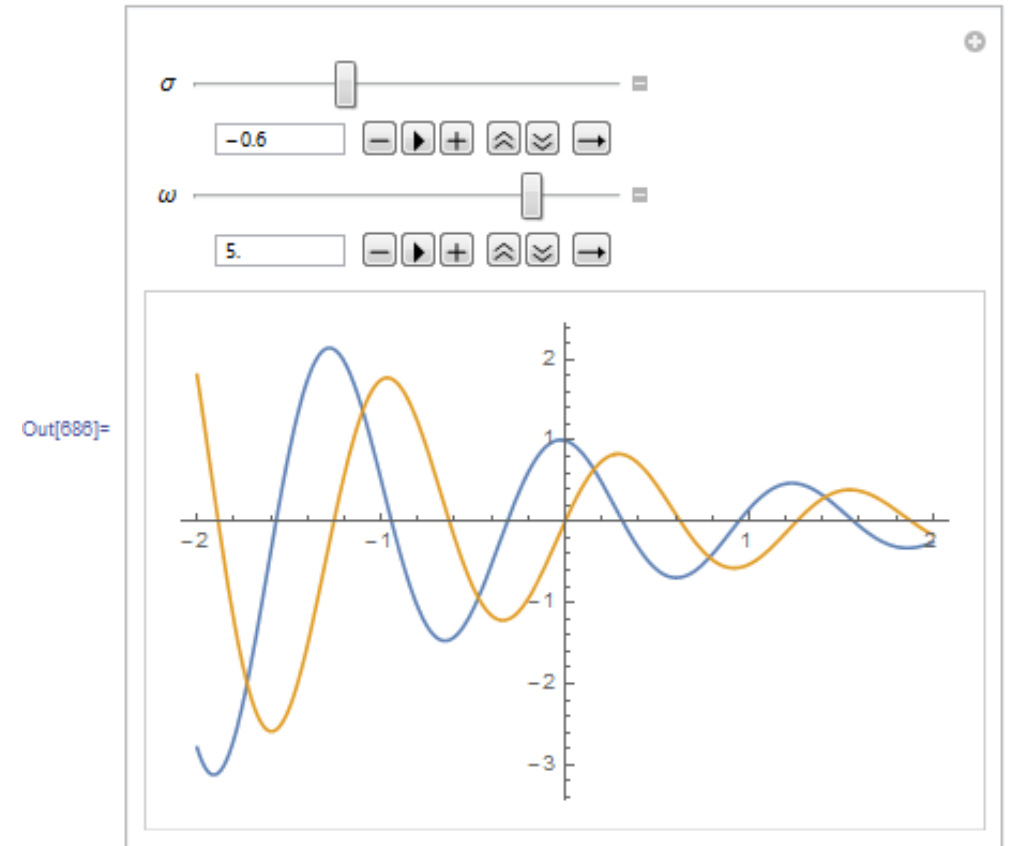
$$\lim_{t \rightarrow \infty} f(t) = \lim_{s \rightarrow 0} sF(s)$$



TYPE	$f(t) (t > 0^-)$	$F(s)$
Impulse	$\delta(t)$	1
Step	$u(t)$	$\frac{1}{s}$
Ramp	$t u(t)$	$\frac{1}{s^2}$
Exponential	$e^{-at} u(t)$	$\frac{1}{s+a}$
Sine	$\sin\omega t u(t)$	$\frac{\omega}{s^2 + \omega^2}$
Cosine	$\cos\omega t u(t)$	$\frac{s}{s^2 + \omega^2}$
Damped Ramp	$t e^{-at} u(t)$	$\frac{1}{(s+a)^2}$
Damped Sine	$(\sin\omega t)e^{-at} u(t)$	$\frac{\omega}{(s+a)^2 + \omega^2}$
Damped Cosine	$(\cos\omega t)e^{-at} u(t)$	$\frac{s+a}{(s+a)^2 + \omega^2}$

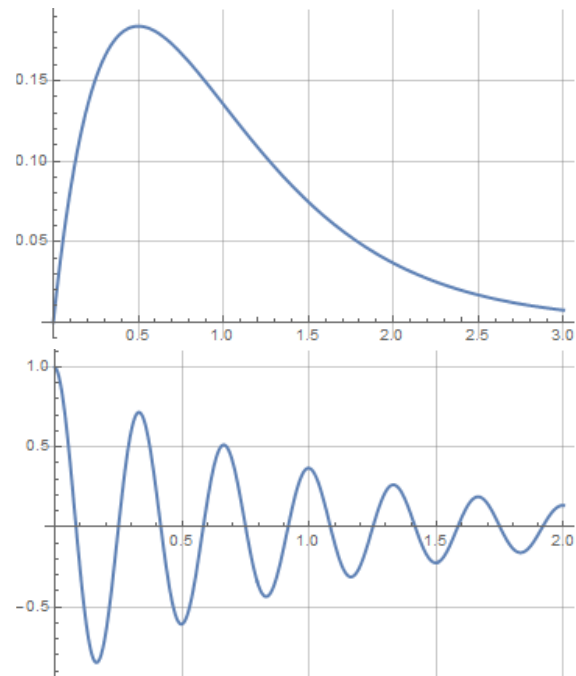

OPERATIONAL TRANSFORM

Operation	$f(t)$	$F(s)$
Multiplication by a constant	$Kf(t)$	$KF(s)$
Addition/subtraction	$f_1(t) + f_2(t) - f_3(t) + \dots$	$F_1(s) + F_2(s) - F_3(s) + \dots$
First derivative (time)	$\frac{df(t)}{dt}$	$sF(s) - f(0^-)$
Second derivative (time)	$\frac{d^2f(t)}{dt^2}$	$s^2F(s) - sf(0^-) - \frac{df(0^-)}{dt}$
n th derivative (time)	$\frac{d^n f(t)}{dt^n}$	$s^n F(s) - s^{n-1}f(0^-) - s^{n-2}\frac{df(0^-)}{dt} - s^{n-3}\frac{df^2(0^-)}{dt^2} - \dots - \frac{d^{n-1}f(0^-)}{dt^{n-1}}$
Time integral	$\int_0^t f(x) dx$	$\frac{F(s)}{s}$
Translation in time	$f(t-a)u(t-a), a > 0$	$e^{-as}F(s)$
Translation in frequency	$e^{-at}f(t)$	$F(s+a)$
Scale changing	$f(at), a > 0$	$\frac{1}{a}F\left(\frac{s}{a}\right)$
First derivative (s)	$tf(t)$	$\frac{dF(s)}{ds}$
n th derivative (s)	$t^n f(t)$	$(-1)^n \frac{d^n F(s)}{ds^n}$
s integral	$\frac{f(t)}{t}$	$\int_s^\infty F(u) du$

$$\mathcal{L}\{\delta(t)\} = 1$$

$$\mathcal{L}\{u(t)\} = \frac{1}{s}$$

$$\mathcal{L}\{e^{-at} u(t)\} = \frac{1}{s+a}$$

$$\mathcal{L}\{f(t-a)\} = e^{-as} F\{s\}$$

$$\mathcal{L}\{(t-1) u(t-1)\} = ?$$

A. e^{-s}/s^2

B. e^{-s}/s


C. $e^{-s}/(s+1)$

D. $1/(s-2)$



E. $1/s^2$

F. e^{-s}

LT for circuits

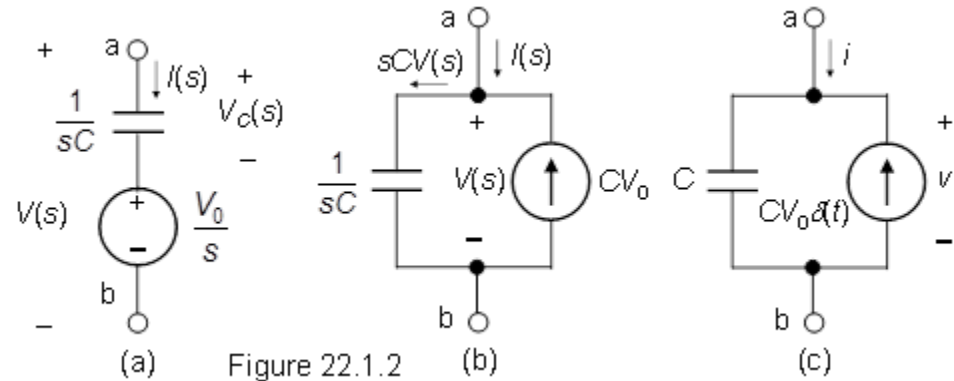


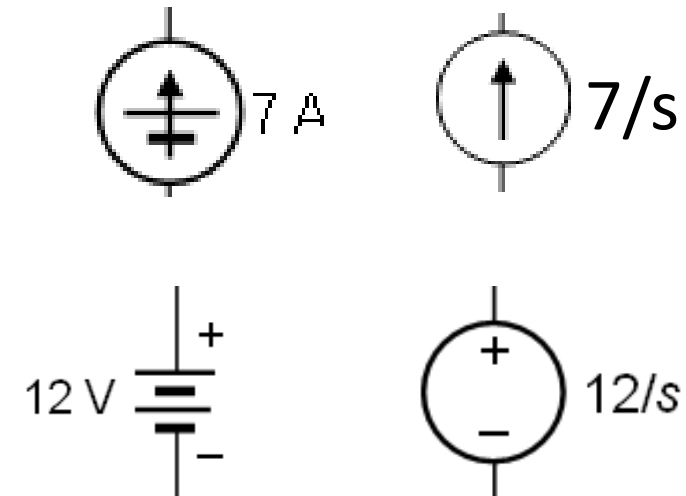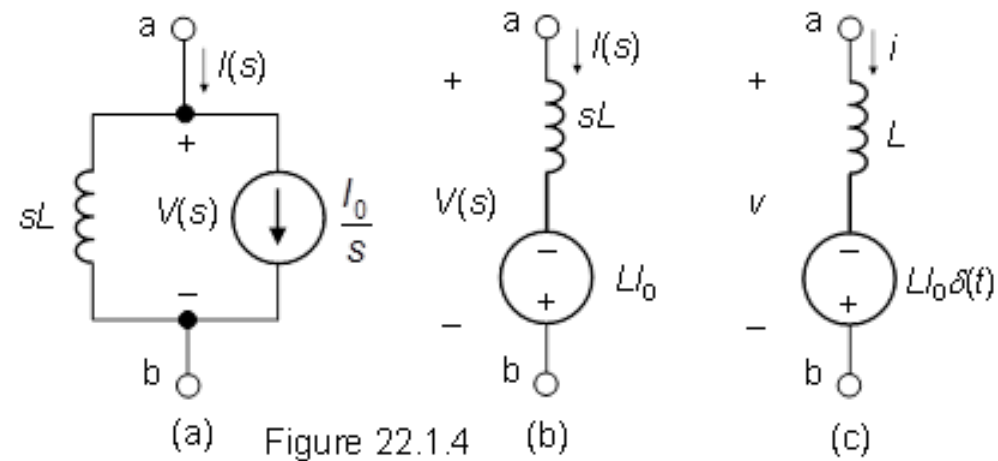- Convert circuit with initial conditions to s-domain.
- Apply circuit analysis.
- Apply ILT to result (in s domain) to get expression in time domain.





An inductance of 2 H has an initial current of 4 A. In the s-domain circuit this is modeled by a voltage source

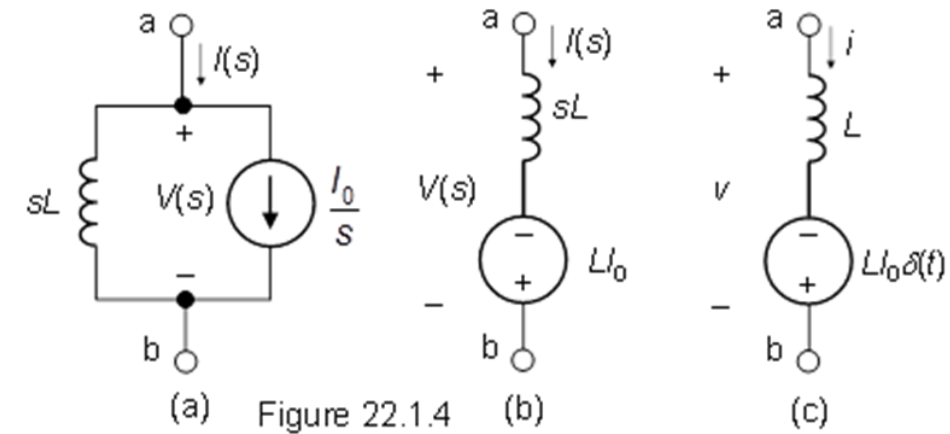- A. of $4/s$ in parallel
- B. of $4/s$ in series
- C. of $2/s$ in parallel
- D. of $2/s$ in series
- E. of 8 in parallel
- F. of 8 in series





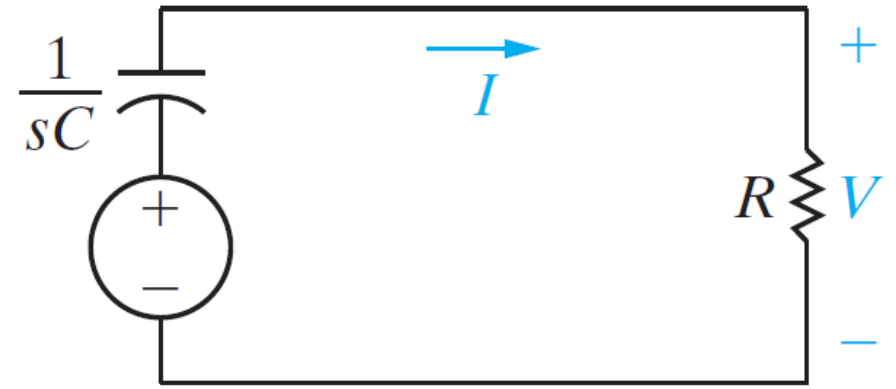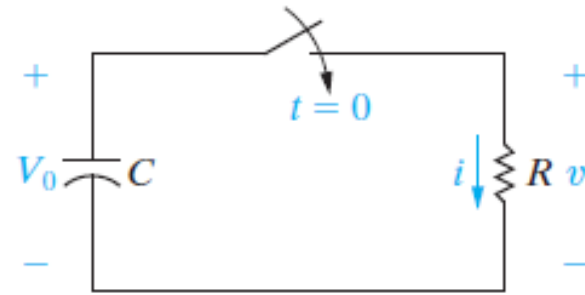$C=0.5\text{F}$. Right before switching $V_0=8\text{V}$. The value of the voltage source should be



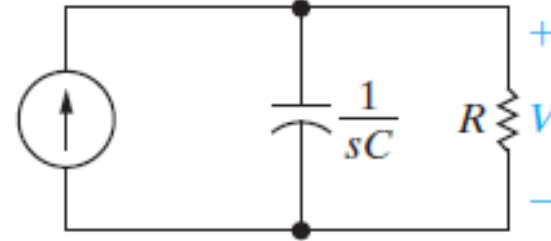
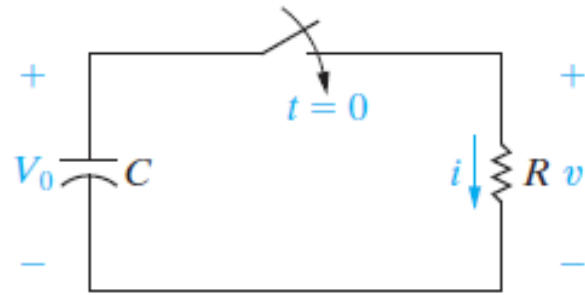
- A. $8/s$
- B. 8
- C. 4
- D. $4/s$
- E. -8
- F. -4

$C=0.5\text{F}$. Right before switching $V_0=8\text{V}$. The value of the current source should be



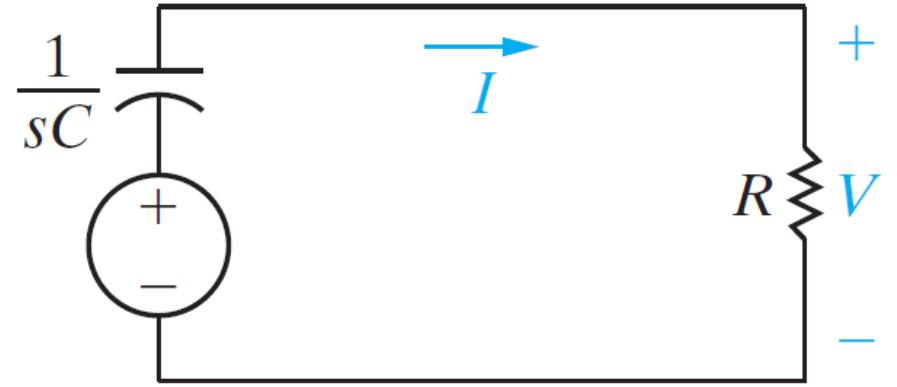
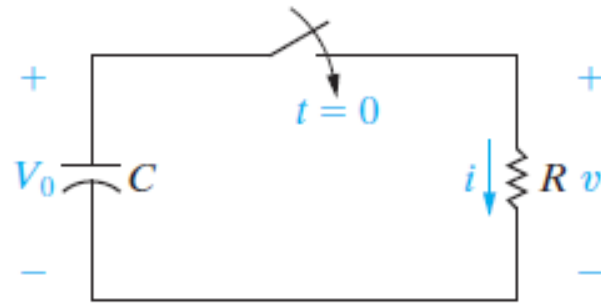
- A. $8/s$
- B. 8
- C. 4
- D. $4/s$
- E. -8
- F. -4

$C=0.5\text{F}$, $R=4\Omega$. Right before switching
 $V_0=8\text{V}$. $I(s)=$



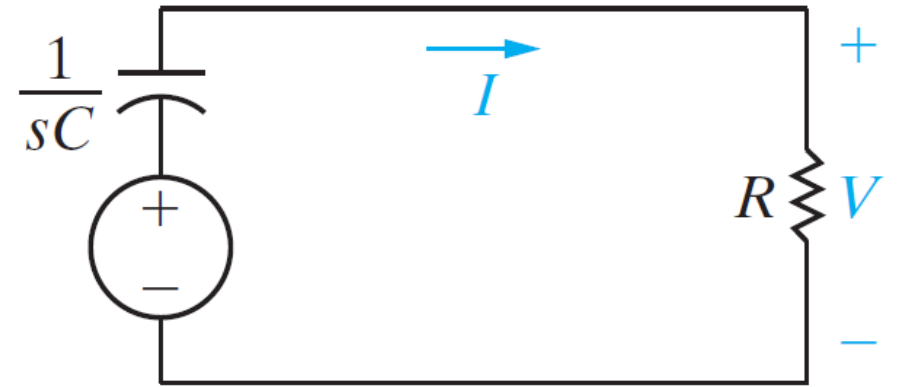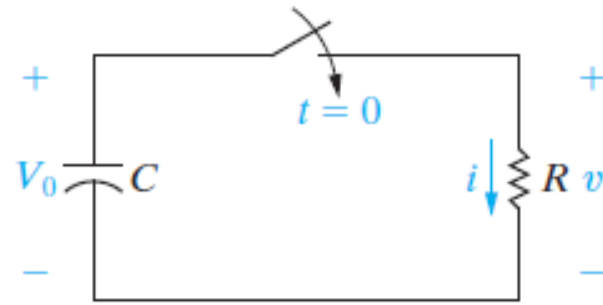- A. 2
- B. $2/s$
- C. $2/(s+2)$
- D. $2/(s+1/2)$
- E. $4/(s+1/2)$
- F. $8/(s+2)$

$C=0.5\text{F}$, $R=4\Omega$. Right before switching $V_0=8\text{V}$. $i(t)=$



- A. $4e^{-t/2}$
- B. $2e^{-t/2}$
- C. $2e^{-2t}$
- D. $4e^{-2t}$

P13.2.20 Determine V_o in Figure P13.2.20.

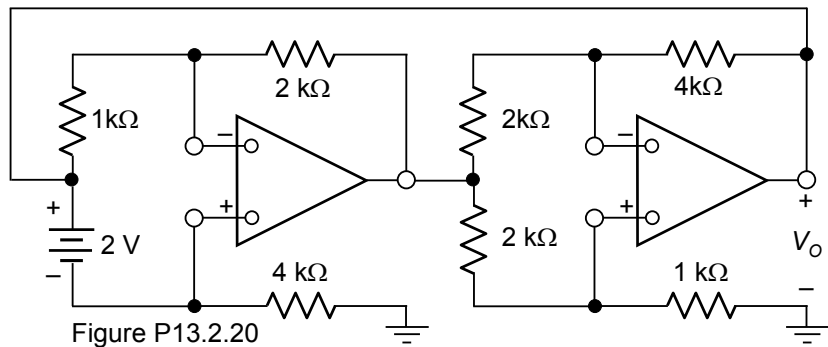


Figure P13.2.20

P17.1.27 Determine the complex power delivered by \mathbf{V}_{SRC1} and \mathbf{V}_{SRC2} in Figure P17.1.27 given that L_1 absorbs 4 kW at a power factor of 0.6 lagging, L_2 absorbs 3 kW at a power factor of 0.6 leading, and the complex power absorbed by L_3 is $12 + j5$ kVA. Assume that $\mathbf{V}_{\text{SRC1}} = 400\angle 0^\circ$ V rms and $\mathbf{V}_{\text{SRC2}} = 400\angle 90^\circ$ V rms.


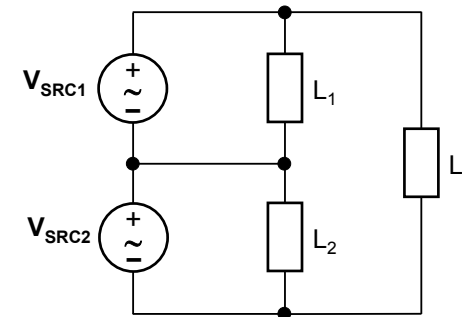


Figure P17.1.27

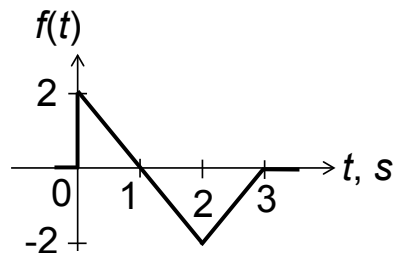P12.2.9 Determine the LT of the derivative of $f(t)$ in Figure P21.2.9.



Determine the ILT of $F(s) = \frac{8s^2 + 4s + 6}{(2s + 3)(s + 4)}$

P22.2.5 Both switches in Figure P22.2.5 are opened at $t = 0$ after being closed for a long time. Determine $i_o(t)$.

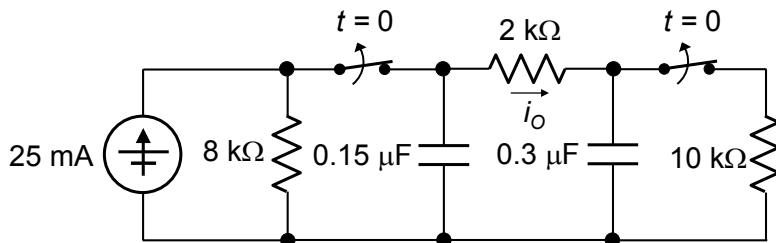


Figure P22.2.5

Ans. 3 V.

Ans. \mathbf{V}_{SRC1} delivers $12.5 + j1.83$ kVA, and \mathbf{V}_{SRC2} delivers $6.5 + j4.5$ kVA.

Ans. $2\left(1 - \frac{1}{s}\right) + \frac{2e^{-2s}}{s}(2 - e^{-s})$.

Ans. $4\delta(t) + (3.6e^{-1.5t} - 23.6e^{-4t})u(t)$.

Ans. $10e^{-5t}$ mA, t is in ms.