

Complex power


using rms values: $S = VI^* = P + jQ = Z |I|^2 = (R + jX) |I|^2 = Y^* |V|^2 = (G - jB) |V|^2$

$$|S| = |V| |I| = |Z| |I|^2 = |Y| |V|^2$$

L: $S = jQ = jX |I|^2 = j\omega L |I|^2$

C: $S = jQ = -jB |V|^2 = -j\omega C |V|^2$

R: $S = P = R |I|^2 = G |V|^2$

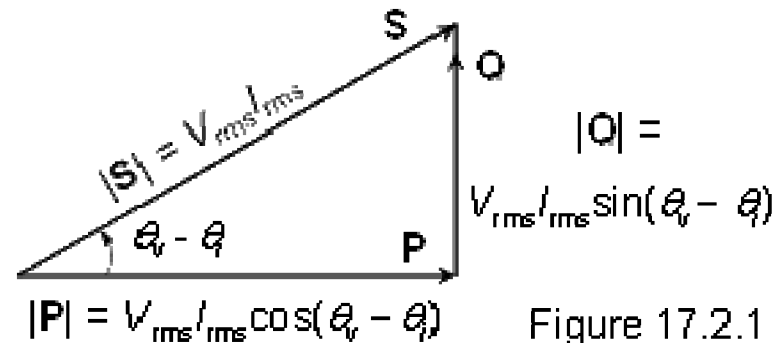

power factor: $\cos(\theta_v - \theta_i)$ lagging or leading (current with respect to voltage)

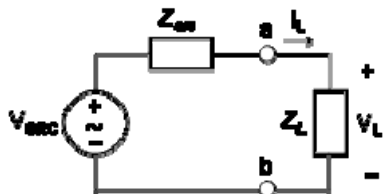


Figure 17.4.7

Maximum power transfer: $Z_L = Z_{src}^*$