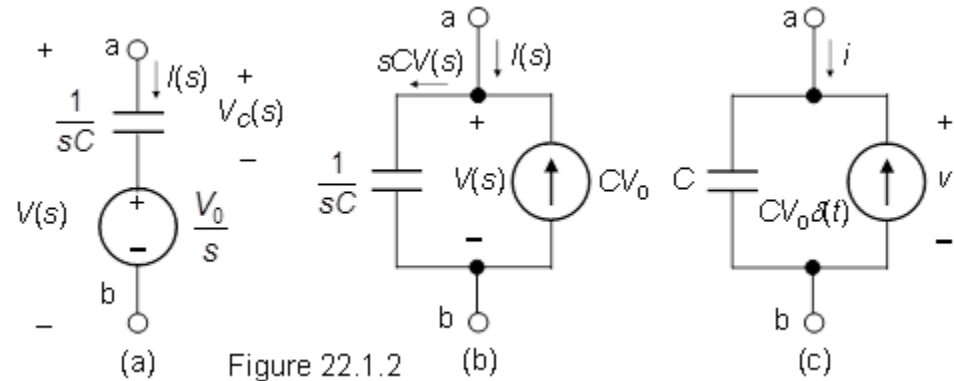




# EECE 290, Problem solving

Session 6
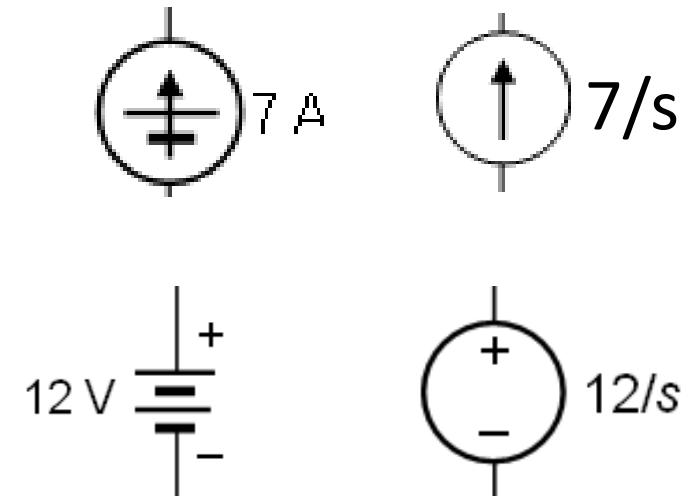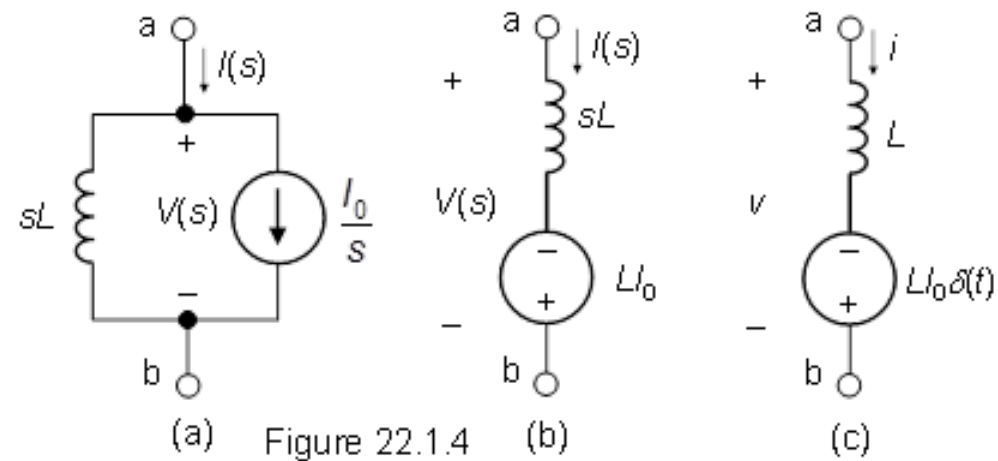
# LT for circuits




- Convert circuit with initial conditions to s-domain.
- Apply circuit analysis.
- Apply ILT to result (in s domain) to get expression in time domain.




A capacitance of .5 F has a initial voltage of 4 V. In the s-domain circuit this is modeled by a current source

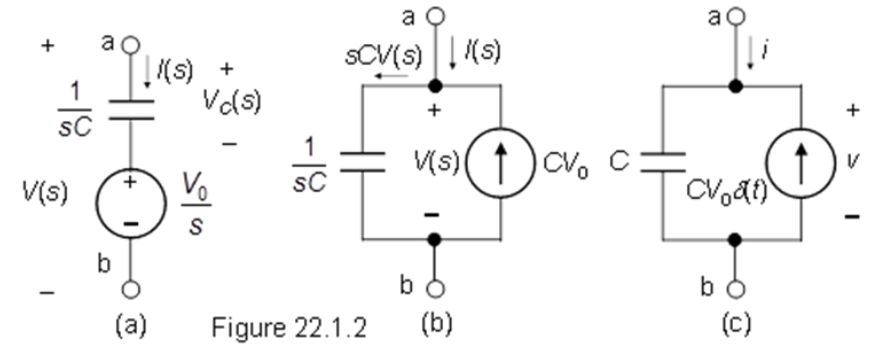- A. of  $4/s$  in parallel
- B. of  $4/s$  in series
- C. of  $8/s$  in parallel
- D. of  $8/s$  in series
- E. of 2 in series
- F. of 2 in parallel




An inductance of 2 H has an initial current of 4 A. In the s-domain circuit this is modeled by a current source

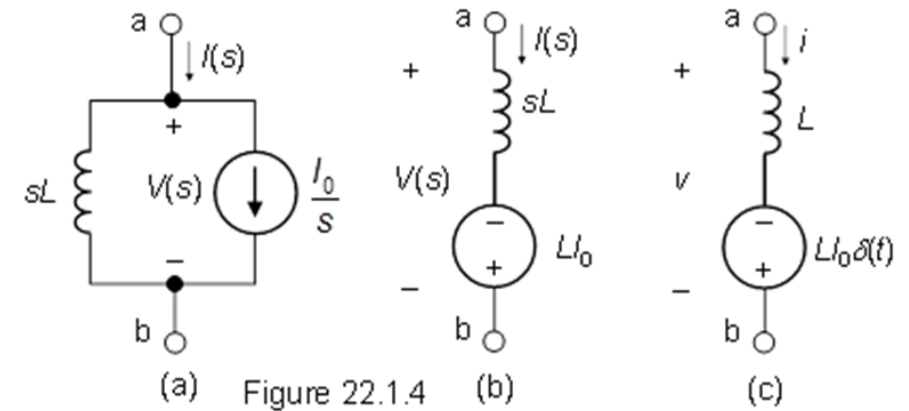- A. of  $4/s$  in parallel
- B. of  $4/s$  in series
- C. of  $2/s$  in parallel
- D. of  $2/s$  in series
- E. of 8 in series
- F. of 8 in parallel



An inductance of 2 H has an initial current of 4 A. In the s-domain circuit this is modeled by a voltage source

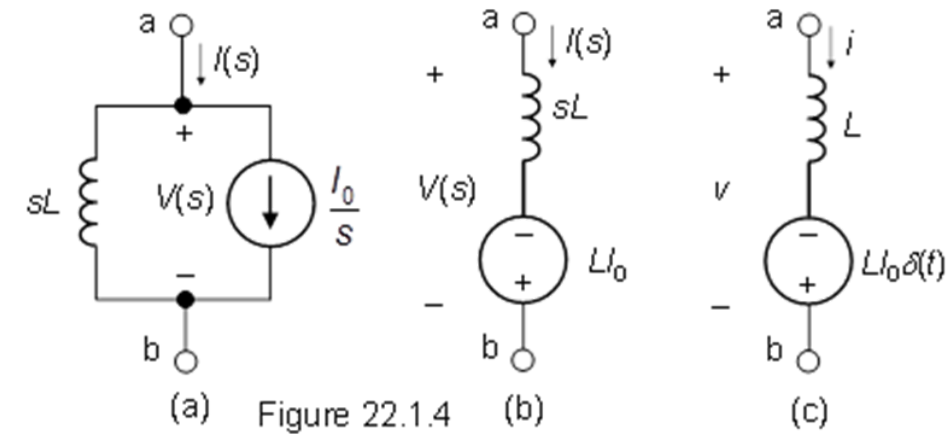- A. of  $4/s$  in parallel
- B. of  $4/s$  in series
- C. of  $2/s$  in parallel
- D. of  $2/s$  in series
- 😊 E. of 8 in series
- F. of 8 in parallel




# Transfer functions

- Ratio of output quantity (V or I) to input quantity (V or I source) in s-domain:  $H(s)$
- If input is  $G(s)$ , then output is  $F(s)=H(s)G(s)$  (multiplication)
- ILT of  $H(s)$  is impulse response  $h(t)$ .
- If the input is  $g(t)$ , then the output is  $f(t)=h(t)*g(t)$  (convolution).


$$I_L(s)/I_S(s) = ?$$

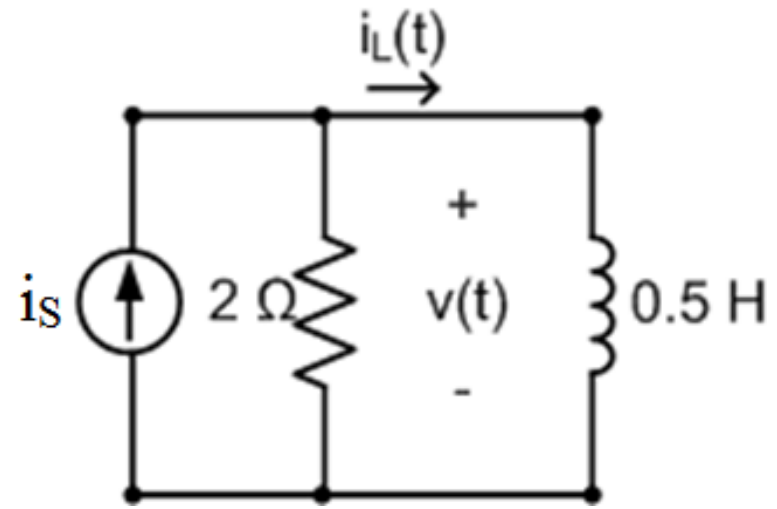- A.  $1/(s+4)$
- B.  $2/(s+4)$
- C. 12
- D. 6
- E.  $4/(s+4)$



$$I_L(s)/I_S(s)=4/(s+4)$$
$$i_S(t)=2\delta(t), i_L(t)= ?$$

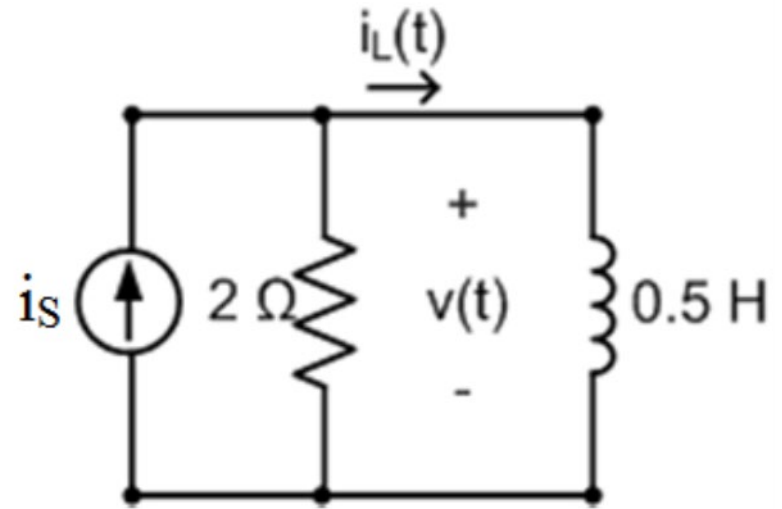
- A. 12 A
- B. 6 A
- C.  $8 e^{-4t}$  A
- D.  $e^{-4t}$  A
- E.  $4 e^{-4t}$  A






$$V(s)/I_S(s) = ?$$

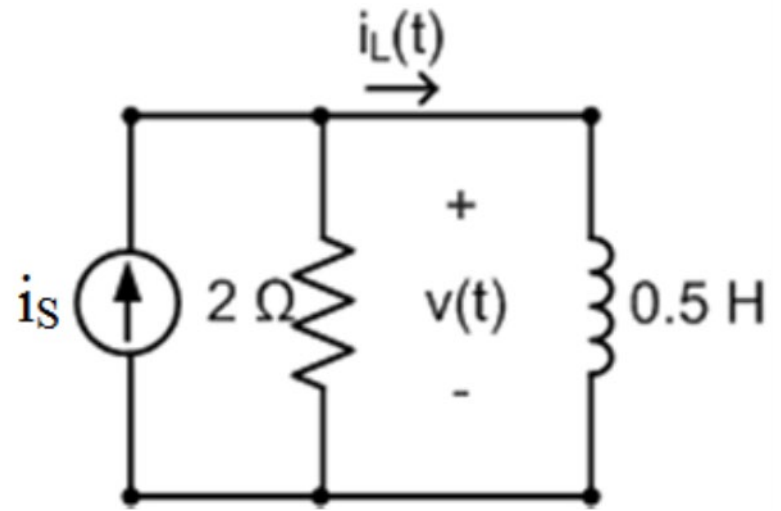- A.  $-24/(s+4)$
- B. 4
- C.  $2s/(s+4)$
- D. 6
- E.  $s/(s+4)$








$$V(s)/I_S(s) = 2s/(s+4)$$
$$i_S(t) = 2\delta(t), v(t) = ?$$

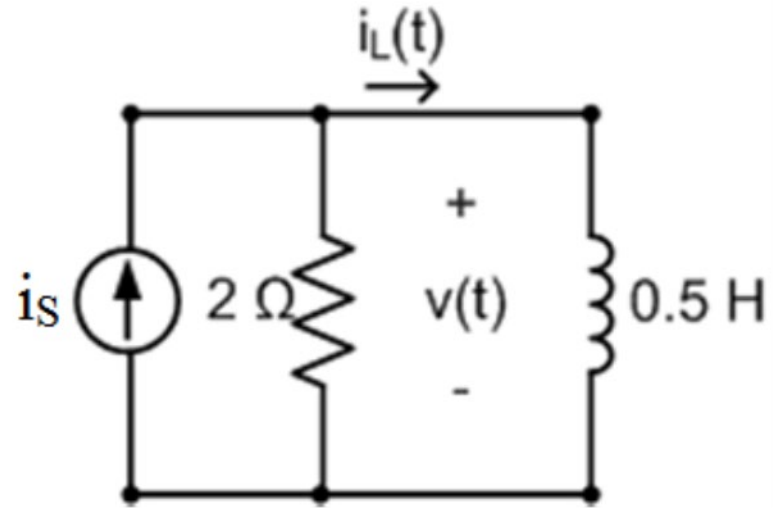- A.  $2\delta(t) - 8e^{-4t} \text{ V}$
- B.  $6 \text{ V}$
- C.  $\delta(t) - e^{-4t} \text{ V}$
- D.  $8e^{-4t} \text{ V}$
- E.  $4\delta(t) - 16e^{-4t} \text{ V}$


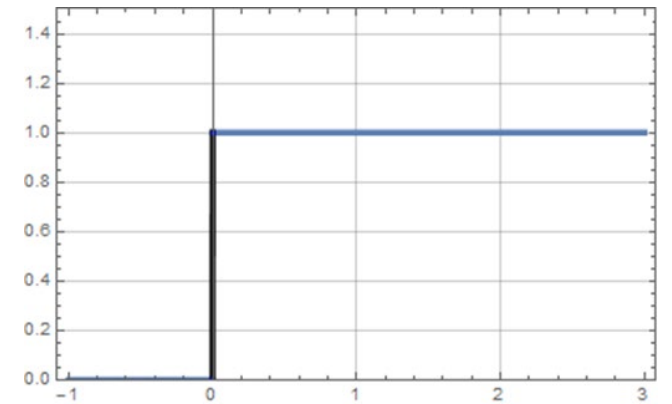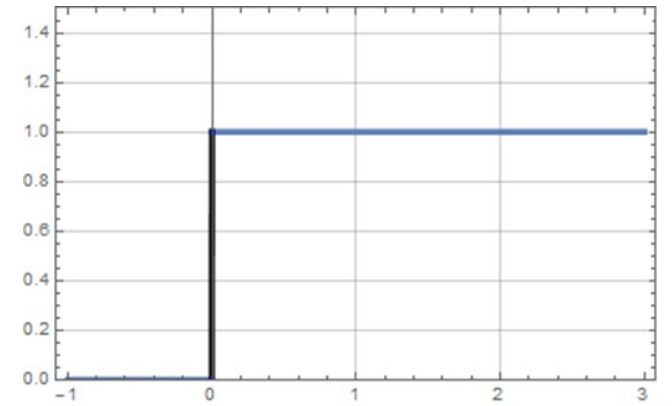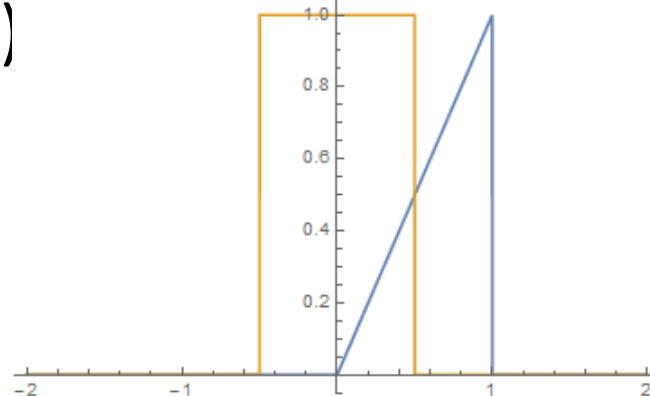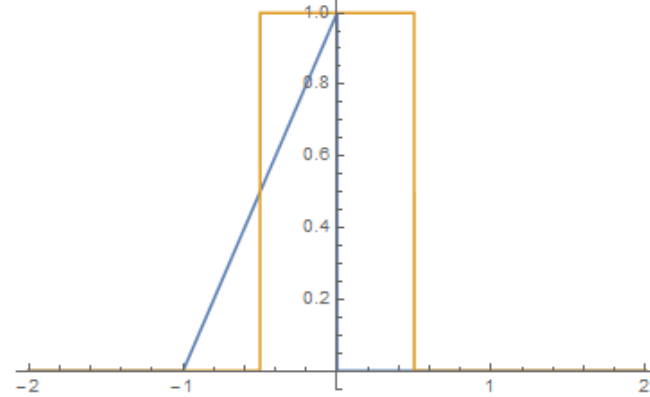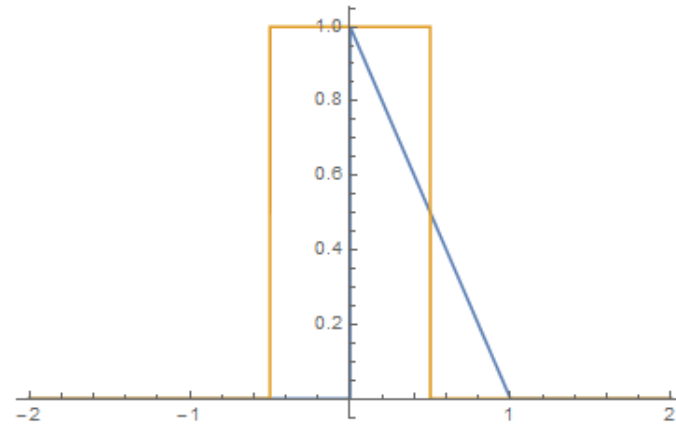
# Convolution

- Given  $g(t)$  and  $h(t)$
- $f = g * h = \int_{-\infty}^{\infty} g(\lambda) h(t - \lambda) d\lambda$
- Properties
  - Commutative
  - Associative
  - Distributive
- (Staircase: use polynomials)



$$u(t) * t u(t) = ?$$

A. -1


B. 0

C. 1


D.  $t$

E.  $t^2$


F.  $\frac{1}{2} t^2$

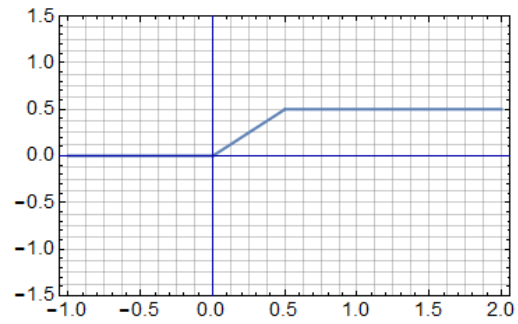

$$u(t)^*$$

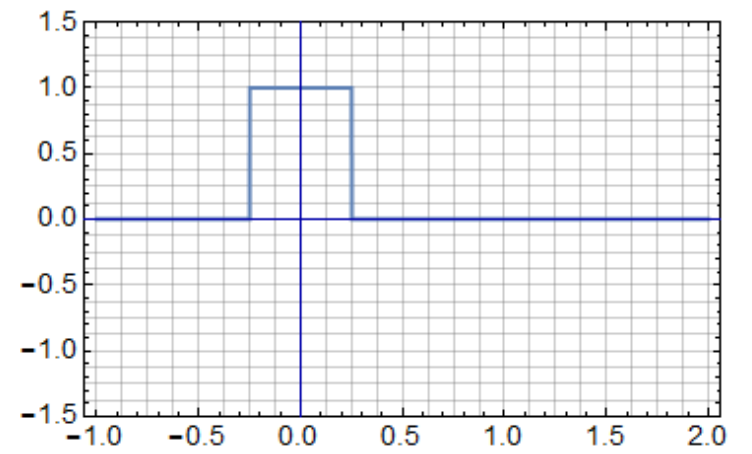








A.

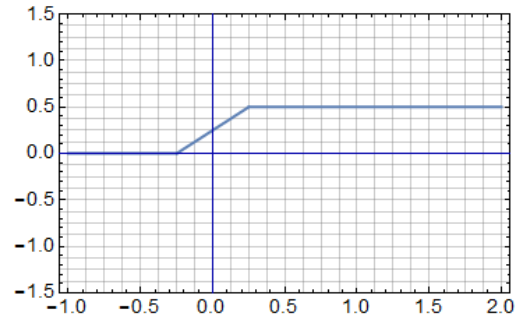






B.

C.

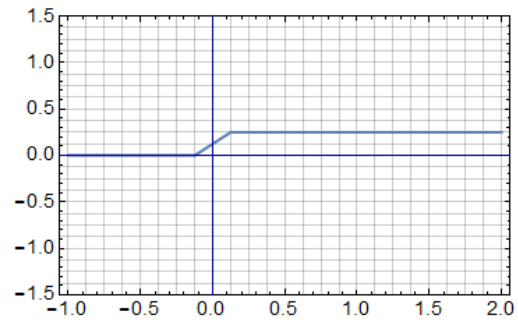

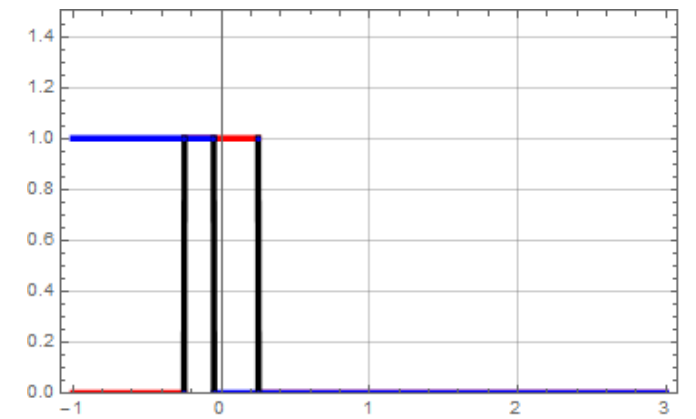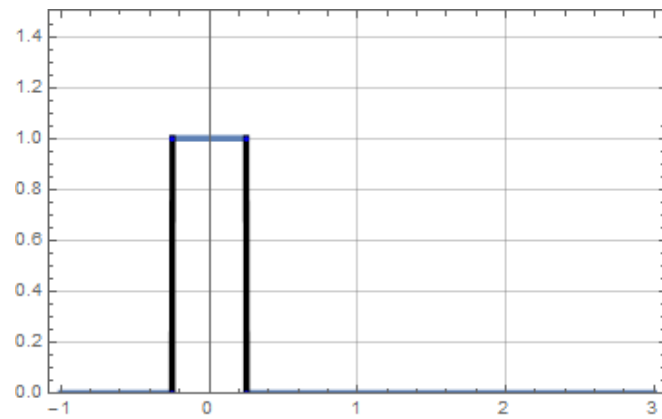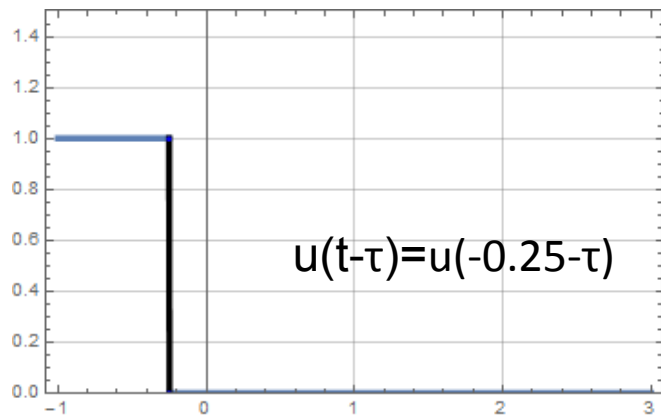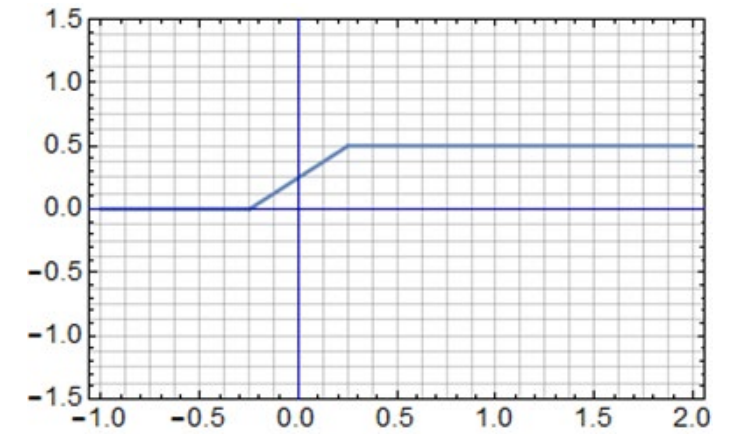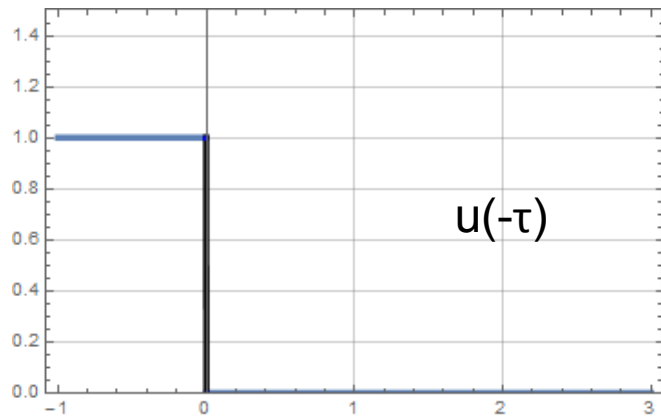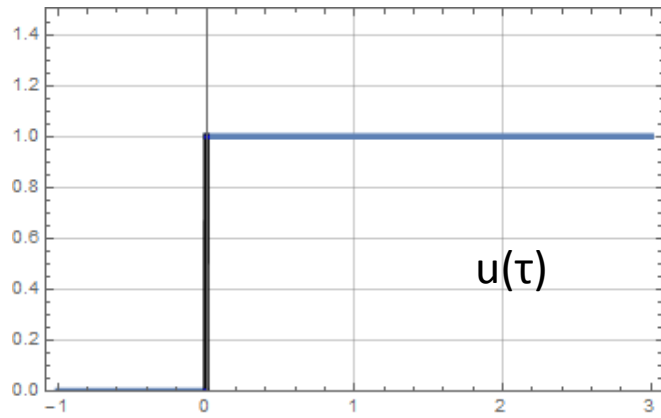

# Convolve

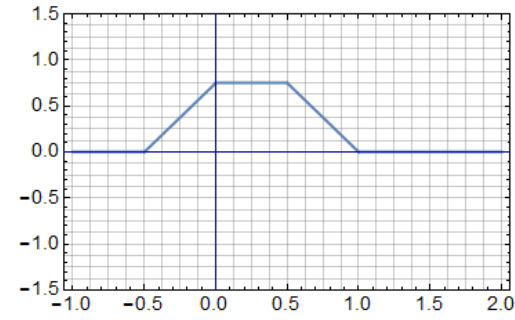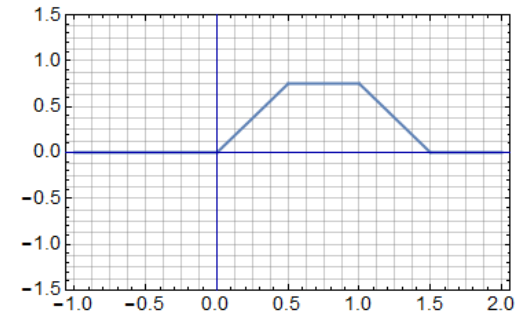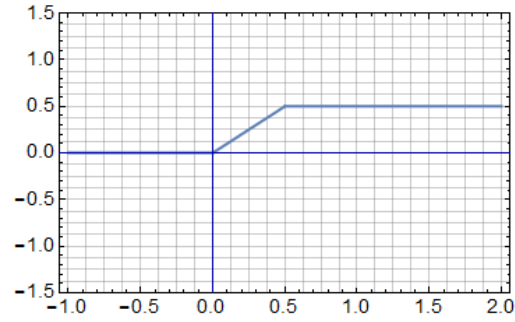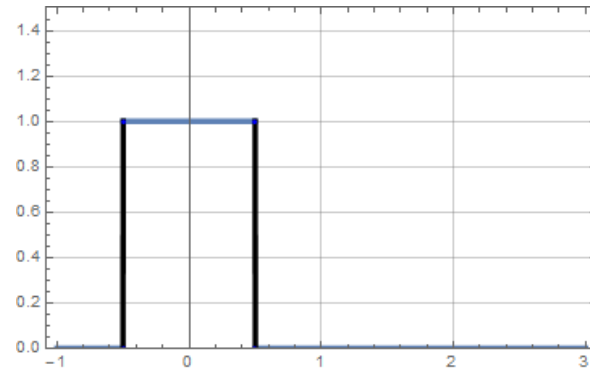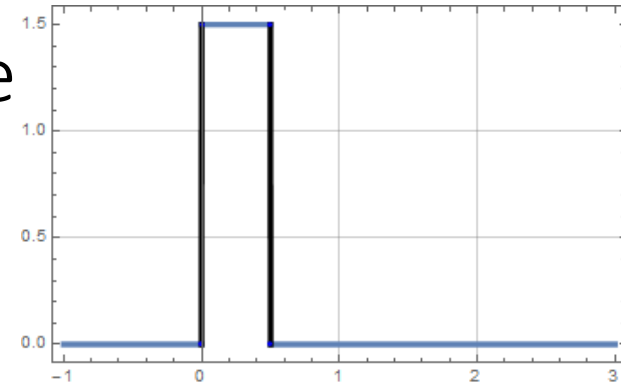






A.

B.

C.

# Convolve


A.  
B.  
C.

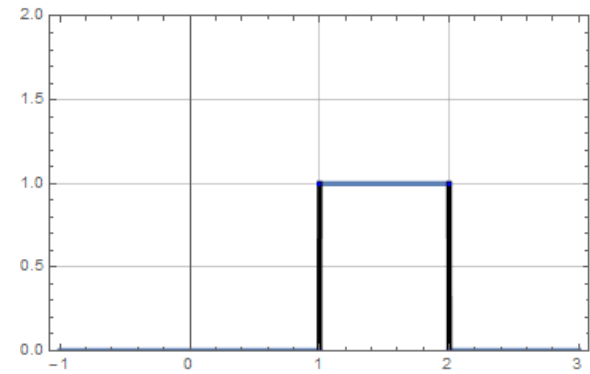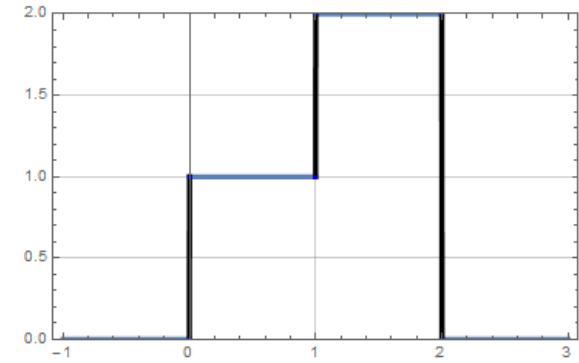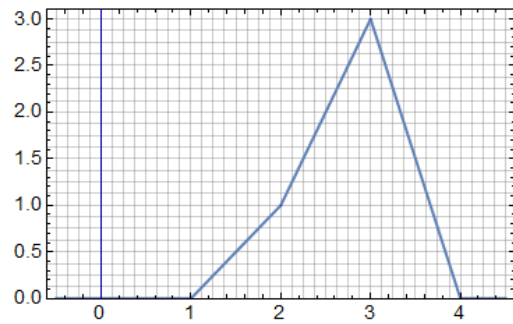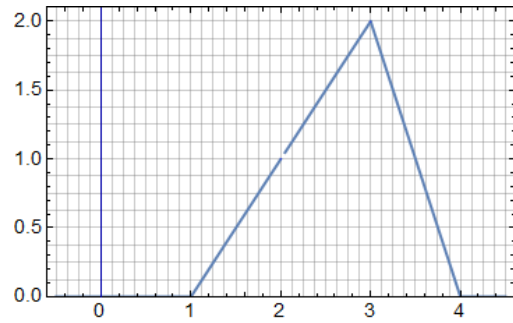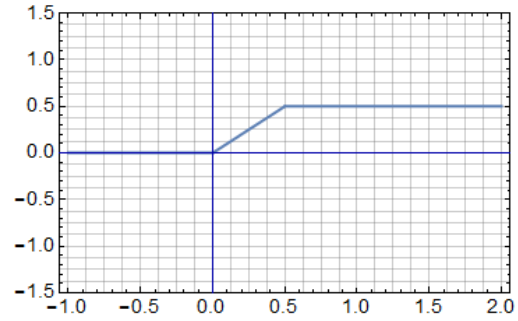



What is the extent in the time domain of the convolution?

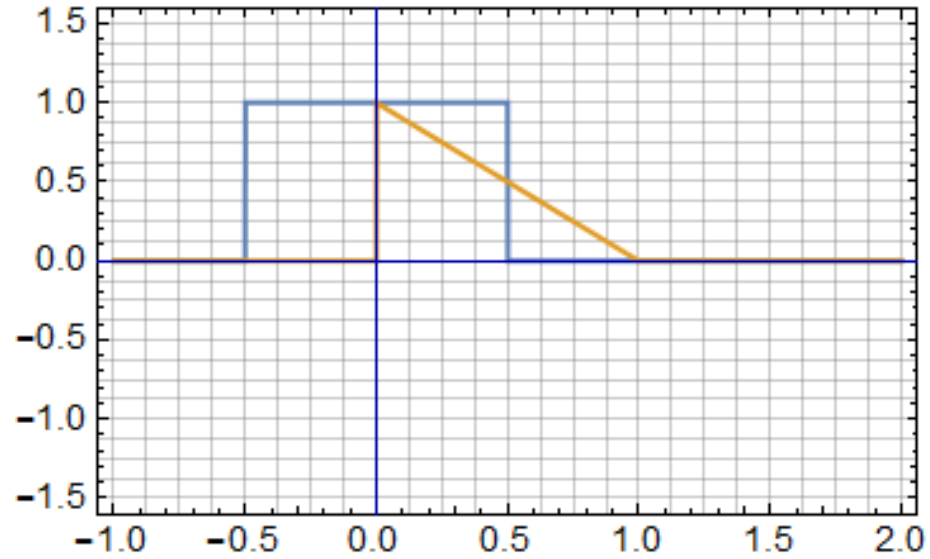- A. 0.5
- B. 1
- C. 1.5
- D. 2
- E. 2.5
- F. 3



$f(t)$  is the convolution of the functions shown. What is the value of  $f(3)$ ?

- A. 0.5
- B. 1
- C. 1.5
- D. 2
- E. 2.5
- F. 3

