


EECE 290, Problem solving

Session 4

using rms values: $S = VI^* = P + jQ = Z |I|^2 = (R + jX) |I|^2 = Y^* |V|^2 = (G - jB) |V|^2$

For a capacitance,

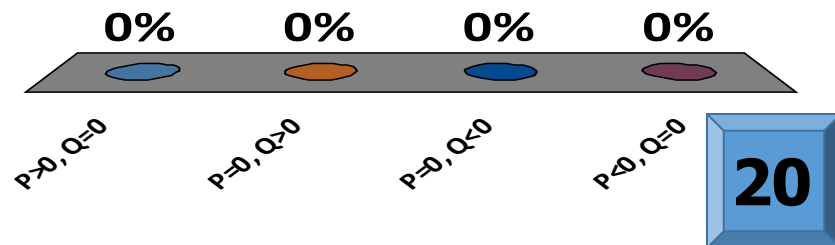
- A. $P > 0, Q = 0$
- B. $P = 0, Q > 0$
- C. $P = 0, Q < 0$
- D. $P < 0, Q = 0$



using rms values: $S = VI^* = P + jQ = Z |I|^2 = (R + jX) |I|^2 = Y^* |V|^2 = (G - jB) |V|^2$

$$|S| = 50 \text{ kVA}, P = 40 \text{ kW}, |Q| = ?$$

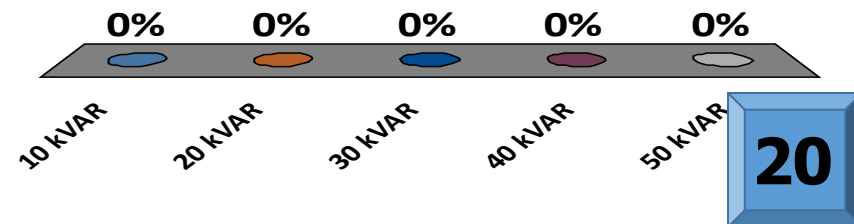
- A. 10 kVAR
- B. 20 kVAR
- C. 30 kVAR
- D. 40 kVAR
- E. 50 kVAR



using rms values: $S = VI^* = P + jQ = Z |I|^2 = (R + jX) |I|^2 = Y^* |V|^2 = (G - jB) |V|^2$

Over a 1 mF capacitance the rms voltage is 4 V with $\omega = 100$ rad/s, what is the value of Q?

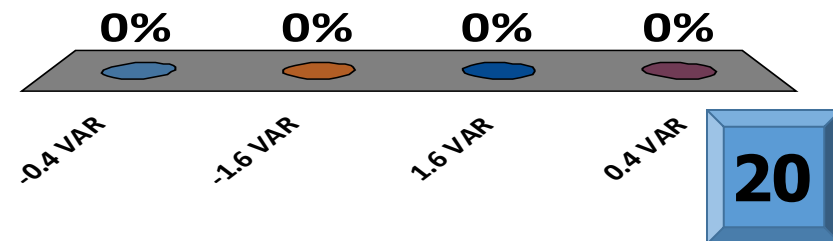
- A. -0.4 VAR
- B. -1.6 VAR
- C. 1.6 VAR
- D. 0.4 VAR



using rms values: $S = VI^* = P + jQ = Z |I|^2 = (R + jX) |I|^2 = Y^* |V|^2 = (G - jB) |V|^2$

A load absorbs 1-j kVA. In order to get pf=1, we must?

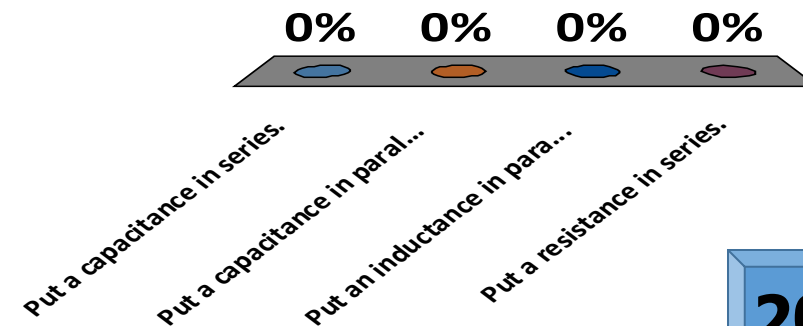
- A. Put a capacitance in series.
- B. Put a capacitance in parallel.
- C. Put an inductance in parallel or series
- D. Put a resistance in series.




using rms values: $S = VI^* = P + jQ = Z |I|^2 = (R + jX) |I|^2 = Y^* |V|^2 = (G - jB) |V|^2$

A current source of $0.1 \text{ A}_{\text{rms}}$, a capacitance of $-j4 \Omega$ and an inductance of $j2 \Omega$ are connected in series, what is the value of S ?

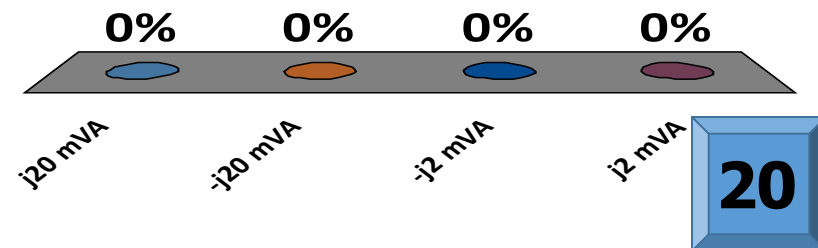- A. $j20 \text{ mVA}$
- B. $-j20 \text{ mVA}$
- C. $-j2 \text{ mVA}$
- D. $j2 \text{ mVA}$



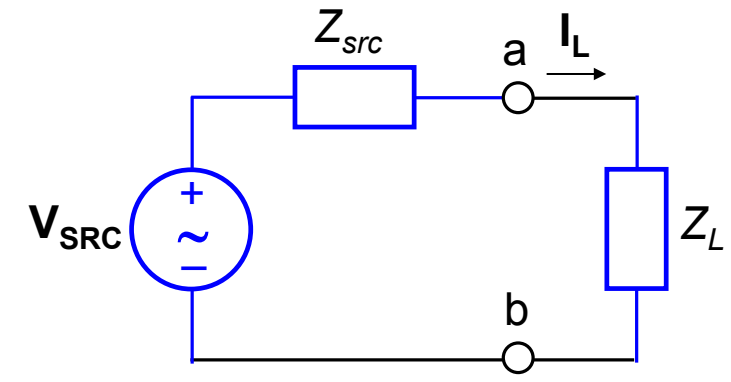$Z_{src} = 2 + j2\Omega$, for maximum power transfer, $Z_L = ?$




- A. $2 + j2\Omega$
- B. $2 - j2\Omega$
- C. $-2 + j2\Omega$
- D. $-2 - j2\Omega$

0%	0%	0%	0%
2+j2Ω	2-j2Ω	-2+j2Ω	-2-j2Ω


20


$Z_{src} = 2 + j2\Omega$, Z_L has the value for maximum power transfer, how much power is transferred?

V_{src} is the amplitude.

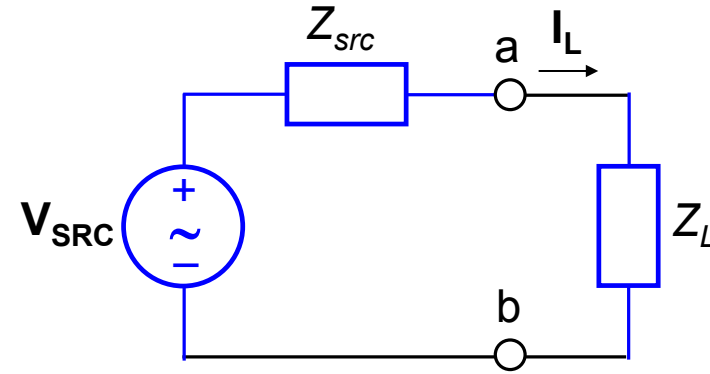

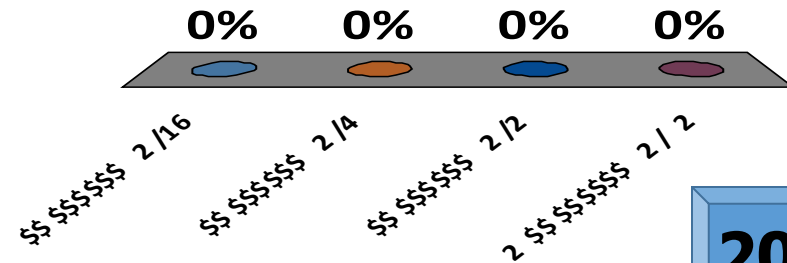- A. $V_{src}^2 / 16$
- B. $V_{src}^2 / 4$
- C. $V_{src}^2 / 2$
- D. $2V_{src}^2 / \sqrt{2}$



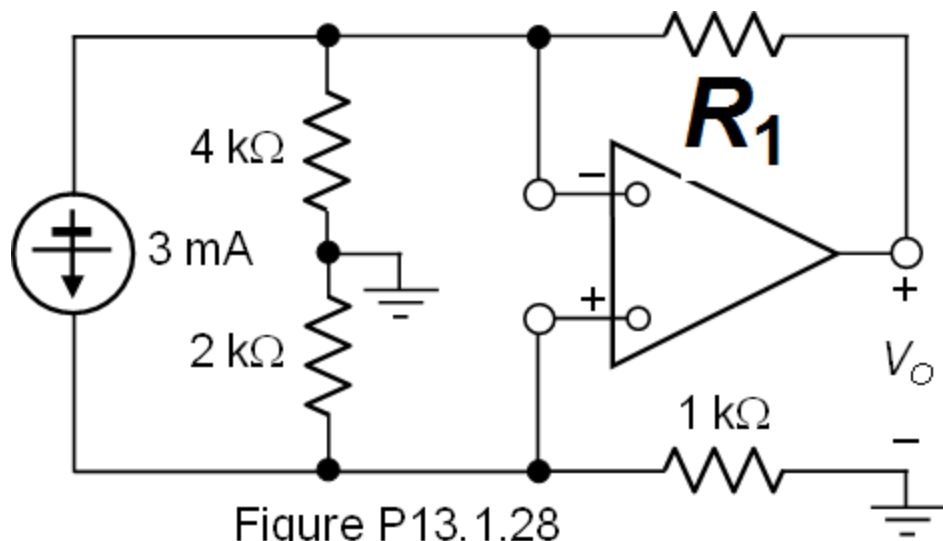

P13.2.19 Determine V_o in Figure P13.2.19.

