

American University of Beirut

Department of Electrical and Computer Engineering

EECE 310 Electronics

Final Exam - Closed Book

2 hours (120 minutes)

December 18, 2015

*ALL QUESTIONS ARE GRADED EQUALLY
PENALTY IS 5 TO 1*

NAME ID number


signature here

SIGN: I HAVE NEITHER GIVEN NOR RECEIVED AID ON THIS EXAM

- ❖
- ❖
- ❖ There are 8 pages and 25 problems
- ❖
- ❖
- ❖ Unless otherwise specified, assume that:

- $V_T = 25 \text{ mV}$
- $|V_{BE(\text{ACTIVE})}| = 0.7 \text{ V}$
- $|V_{BE(\text{SAT})}| = 0.7 \text{ V}$
- $|V_{CE(\text{SAT})}| = 0.2 \text{ V}$
- $|V_{CE(\text{EDGE OF SAT})}| = 0.3 \text{ V}$
-
- All capacitors are very large
-
- *Base-width modulation (Early effect) and channel-length modulation effects are negligible*

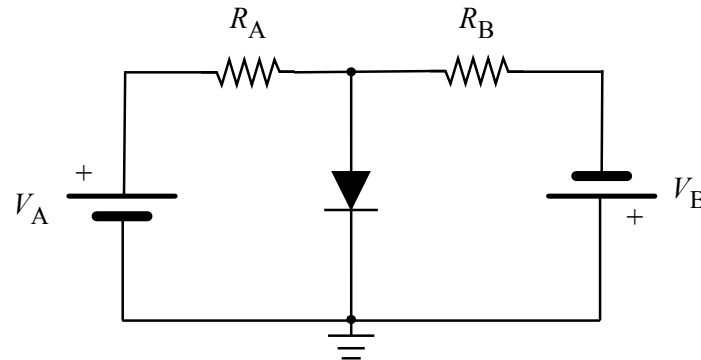1. In the circuit shown below, the diode is ideal. At what value of V_A (in V) does the diode start to conduct? Assume that $R_A = 22 \text{ k}\Omega$, $V_B = 16 \text{ V}$, and $R_B = 10 \text{ k}\Omega$.




- a) 35.2 b) 30.8 c) 26.4 d) 39.6 e) 44.0

2. Find the current in R_A (in mA) when $V_A = 10 \text{ V}$.

- a) 0.750 b) 0.813 c) 0.875 d) 0.938 e) 0.688

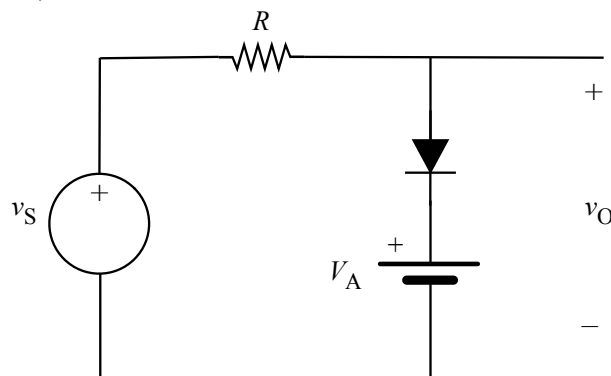3. In the circuit shown below, the diode drops 0.7 V when conducting, and is considered an open-circuit when OFF. Find the maximum diode current (in mA) if v_S is a square wave that varies between $+20 \text{ V}$ (for 50% of the time) and -20 V (for the other 50% of the time). Assume $V_A = 8 \text{ V}$ and $R = 2.2 \text{ k}\Omega$.



- a) 2.86 b) 5.14 c) 4.23 d) 3.77 e) 3.32


4. In the previous problem, find the average value of the output voltage v_O (in V).

- a) -3.65 b) -3.15 c) -5.65 d) -4.65 e) -4.15

5. A series connection of 10 identical PN junction diodes in the same polarity, also connected in series with a battery such that all diodes are forward biased, results in a forward current of 1 mA when the battery voltage is 7 V , and 6 mA when the battery voltage is 7.5 V . Find the value of n for the diodes.

- a) 1.820 b) 1.116 c) 1.243 d) 1.443 e) 1.028

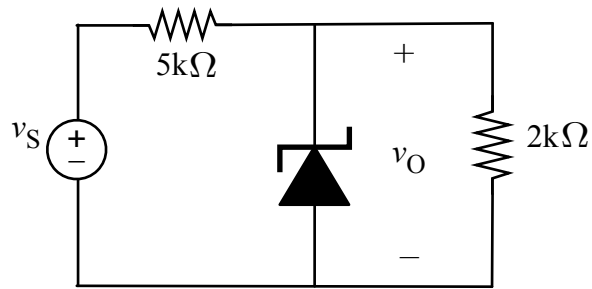6. Consider the Zener diode in the circuit shown below. The diode has $V_{Z0} = 12.0 \text{ V}$, $r_Z = 100 \Omega$, and $I_{ZK} = 5 \text{ mA}$. Find the output voltage v_O (in V) when v_S is 35.0 V?



- a) 10.0 b) 11.0 c) 11.5 d) 11.7 e) 11.9

7. A logic inverter has $NM_L = NM_H = 0.5 \text{ V}$, $V_{OL} = 0.4 \text{ V}$, and $V_{OH} = 3.5 \text{ V}$. Find the value of V_{IL} for this inverter (in V).

- a) 0.9 b) 1.0 c) 0.7 d) 0.8 e) 0.6

The drain current of an enhancement NMOS is measured at several values of V_{GS} and V_{DS} , as shown in the table below. For this MOSFET: $k'_n \frac{W}{L} = 1 \text{ mA/V}^2$, $V_t = 1 \text{ V}$, and $\lambda \neq 0$. Answer the following 2 questions.

$V_{GS} [\text{V}]$	$V_{DS} [\text{V}]$	$I_D [\text{mA}]$
3	3	2.06
3	8	I_{D1}
3	0.2	I_{D2}


8. Find the value of I_{D1} (in mA).

- a) 2.48 b) 2.16 c) 2.24 d) 2.32 e) 2.40

9. Find the value of I_{D2} (in mA).

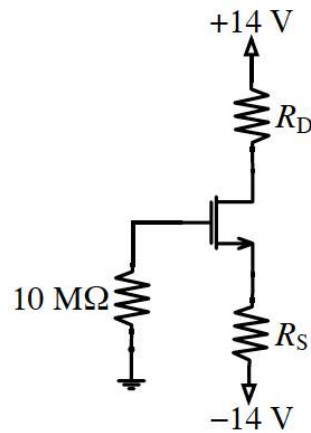- a) 0.38 b) 0.72 c) 1.02 d) 1.28 e) 1.5

The enhancement NMOS in the circuit shown below has $k'_n \frac{W}{L} = 2 \text{ mA/V}^2$, $V_t = 1 \text{ V}$, and $\lambda = 0$. $R_D = 6 \text{ k}\Omega$ and the MOSFET operates at the *boundary* between the triode and saturation regions. Answer the following 2 questions.




10. Find the value of the drain current I_D (in mA).
 a) 2.5 b) 7.5 c) 5 d) 3.75 e) 3

11. Find the value of R_S (in kΩ).
 a) 3.76 b) 4.57 c) 1.37 d) 2.15 e) 2.95

12. The enhancement PMOS in the circuit shown has $k'_p \frac{W}{L} = 2 \text{ mA/V}^2$, $V_t = -1.5 \text{ V}$, and $\lambda = 0$. Find V_{DS} (in V) if $R_D = R_S$, and the MOSFET is biased such that $V_{GS} = -3.5 \text{ V}$.


a) -15 b) -16 c) -17 d) -19 e) -18

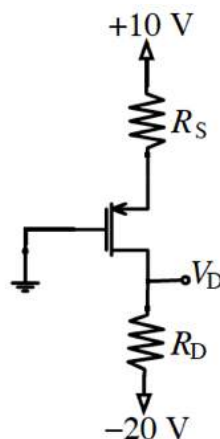


13. A voltage amplifier has an *open-circuit* voltage gain of 100 V/V , an output resistance of 100Ω , and a power gain of $150 \times 10^6 \text{ W/W}$ when a 100Ω load is connected across the output terminals. Find the input resistance (in MΩ).

a) 6 b) 5 c) 2 d) 3 e) 4

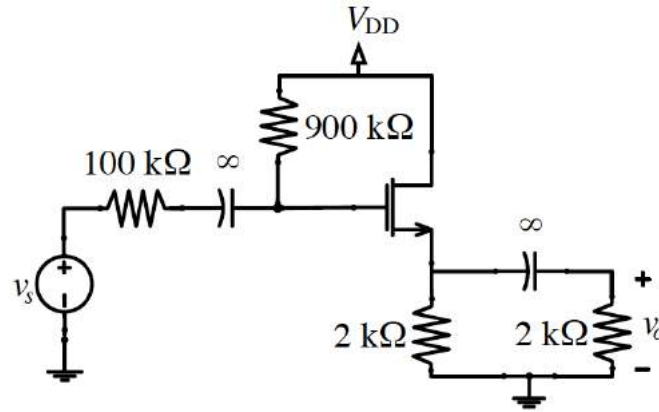14. The enhancement NMOS in the circuit shown below is biased in the saturation region such that the gate to source overdrive voltage V_{OV} is 0.5 V and the drain current $I_D = 1$ mA. If v_s is a 60 mV peak-to-peak sinusoid, find the peak-to-peak variation of v_o (in mV). Assume that $\lambda = 0$.
- a) 36.0 b) 43.2 c) 50.4 d) 21.6 e) 28.8



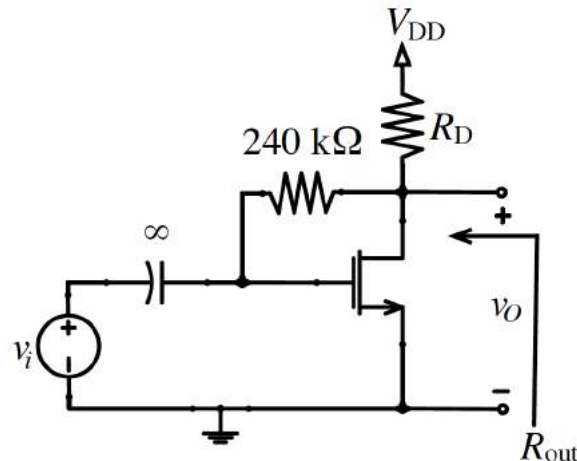
The enhancement NMOS in the circuit shown below has an early voltage $V_A = 75$ V; it is biased in the saturation region such that $I_D = 1$ mA and $V_{DS} = 5$ V. v_i is a signal voltage. Answer the following 2 questions.



15. If $R_{out} = 10$ kΩ, find the value of R_D (in kΩ).
- a) 25.71 b) 9.23 c) 12 d) 18.26 e) 21.82
16. If $R_D = 20$ kΩ and the MOSFET transconductance $g_m = 1.2$ mA/V, find the small-signal voltage gain v_o/v_i (in V/V); v_o is the signal component of the total output voltage v_o .
- a) -23.94 b) -17.94 c) -20.94 d) -26.94 e) -14.94


17. The *npn* transistor in the circuit shown below has $\beta = 99$. Find the value of V_{CE} (in V) if $R_C = 6 \text{ k}\Omega$.

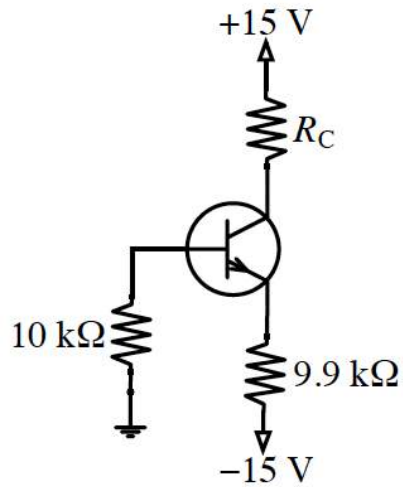- a) 10.18 b) 8.76 c) 7.35 d) 5.93 e) 4.52




18. The *npn* transistor in the circuit shown below is biased such that $V_{CE} = 4.7 \text{ V}$. Find the value of β .

- a) 74 b) 59 c) 119 d) 99 e) 149

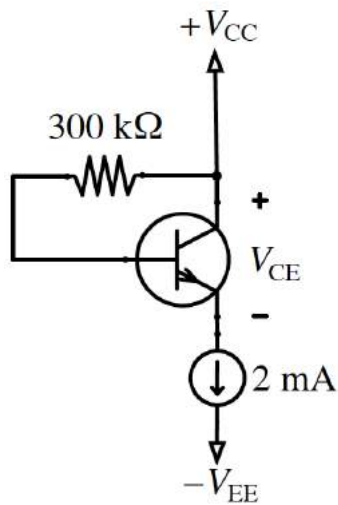


19. The *pn*p transistor in the circuit shown below has $\beta = 49$. Find the value of I_E (in mA) if $R_E = 3 \text{ k}\Omega$.

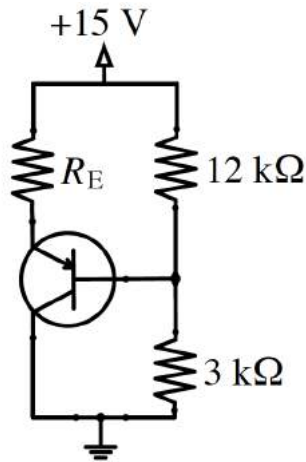- a) 1.12 b) 10.78 c) 5.52 d) 3.71 e) 2.79



20. The *npn* transistor in the circuit shown below has $\beta = 119$. Find the value of I_B (in μA) so that the transistor operates at the *Edge of Saturation*.

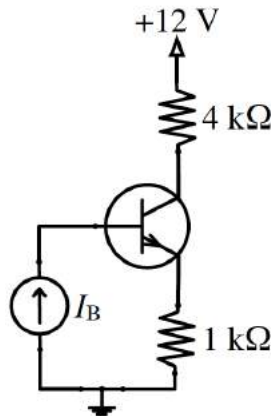
- a) 29.55 b) 19.63 c) 59.69 d) 47.56 e) 39.53



21. An *npn* transistor has $\beta = 49$; it is biased in the active mode so that its small-signal T-model has $r_e = 10 \Omega$. Find the value of the DC current in the collector (in mA).

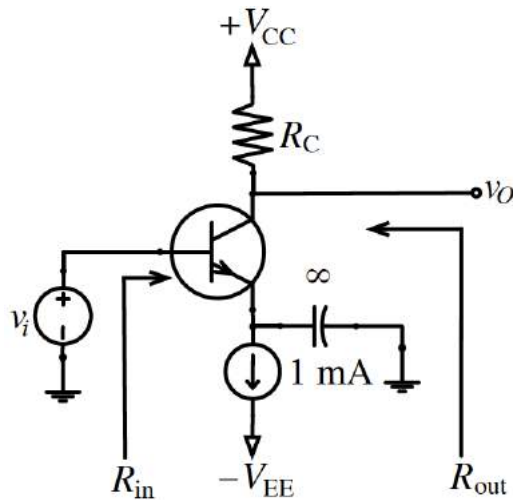
- a) 6.13 b) 2.45 c) 3.06 d) 4.90 e) 1.63

The *npn* transistor in the circuit shown below is biased in the active region; v_i is a pure signal voltage with zero DC component. The small-signal voltage gain $v_o/v_i = -43.56$ V/V, where v_o is the signal component of the total output voltage v_O . Answer the following 2 questions.



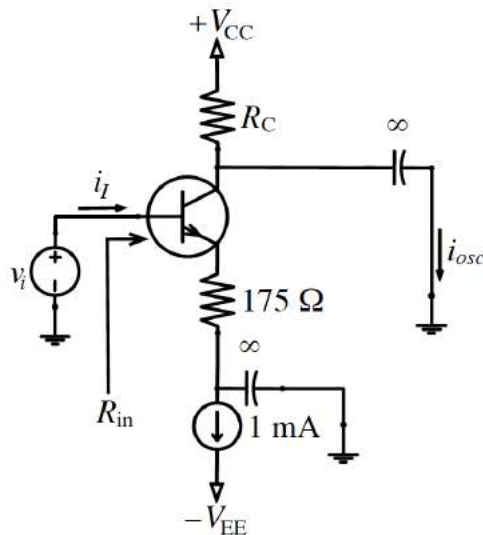22. Find the value of β if $R_{in} = 1.25$ k Ω .
 a) 69 b) 79 c) 89 d) 49 e) 59
23. Find the value of R_{out} (in k Ω) if $\beta = 99$.
 a) 1.1 b) 1.2 c) 1.3 d) 1.4 e) 1.5

The *npn* transistor in the circuit shown below is biased in the active region; v_i is a pure signal voltage with zero DC component. The input resistance of the amplifier $R_{in} = 16.2$ k Ω . Answer the following 2 questions.



24. Find the small-signal short-circuit current gain i_{osc}/i_i (in A/A), where i_i is the signal component of the total input current i_i .
 a) -140 b) -80 c) -100 d) -120 e) -60
25. Find the peak value of v_i (in mV) that results in a signal voltage v_{be} having a peak value of 1 mV.
 a) 20 b) 8 c) 12 d) 16 e) 24